

Principles of Magnetics and Transformers

ELEC2005 Electrical and Electronic Systems - Week 10

Dr. Leonardo Callegaro

School of Engineering
Faculty of Science and Engineering



MACQUARIE
University

Table of Contents

- 1 Basic magnetic relations
- 2 Magnetic circuits
- 3 Transformer modelling
- 4 Transformer in AC circuits

1 Basic magnetic relations


2 Magnetic circuits

3 Transformer modelling

4 Transformer in AC circuits

Right hand thumb rule

H = magnetic field intensity

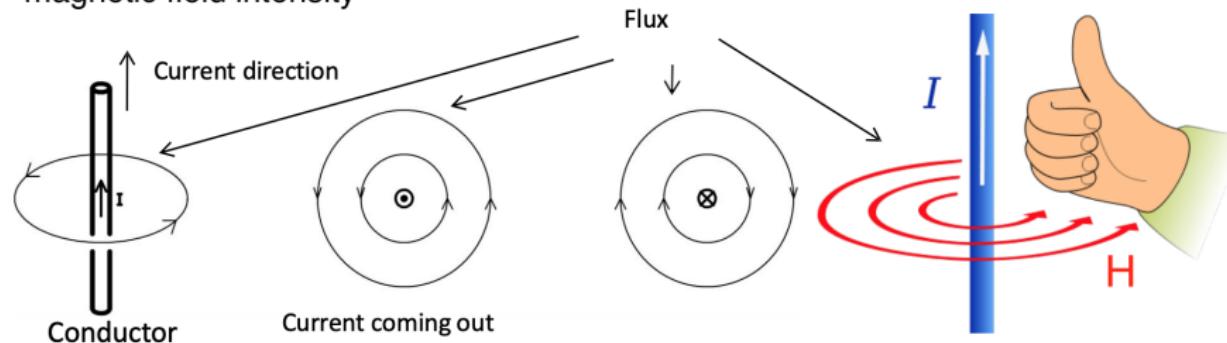


Source: <http://en.wikipedia.org/wiki/File:Manoderecha.svg>

If a conductor is held with the right hand with the thumb indicating the current direction, then the fingertips will indicate the direction of the magnetic field intensity H


Also consult: www.khanacademy.org (click here)

Right-hand thumb rule (cont'd.)

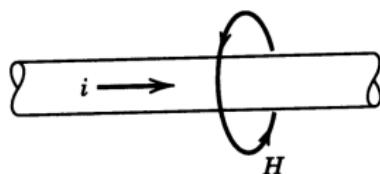Direction of \mathbf{H} around wire (a) and inside magnetic core (b) depends on the current direction and the way the coil is wound




(a)

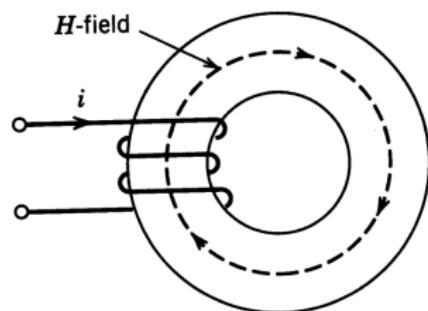


(b)

Basic magnetic relations

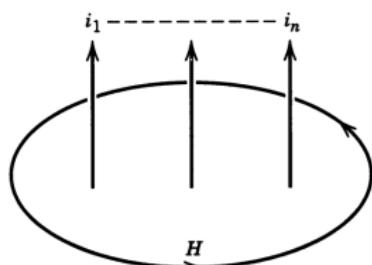- Ampere's law: since a current produces a magnetic field, the line integral of magnetic field intensity \mathbf{H} equals total enclosed current



(a)

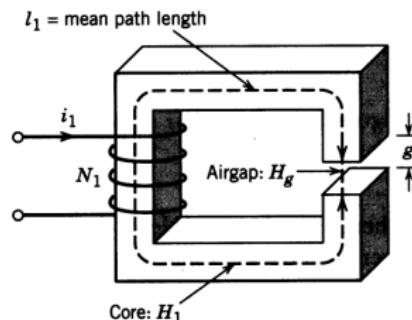

(b)



$$\underbrace{\oint \mathbf{H} \cdot d\ell}_{\text{line integral of } \mathbf{H}} = \sum i \quad \sum_k H_k \ell_k = \sum_m N_m i_m$$

$$\underbrace{H_1 \ell_1 + H_g \ell_g}_{\mathcal{F} \text{ Magneto Motive Force (MMF)}} = N_1 i_1$$

\mathcal{F} Magneto Motive Force (MMF)

Basic magnetic relations (cont'd 1)

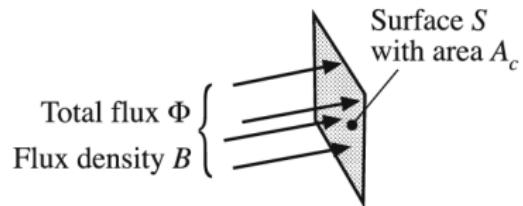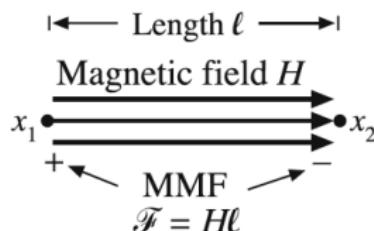Magnetic field intensity \mathbf{H} , field density \mathbf{B} , flux Φ




- Flux density (aka magnetic induction) or \mathbf{B} -field:

$$\mathbf{B} = \mu \mathbf{H} = \mu_0 \mu_r \mathbf{H}$$

μ magnetic permeability (material)

μ_0 air permeability

μ_r relative permeability

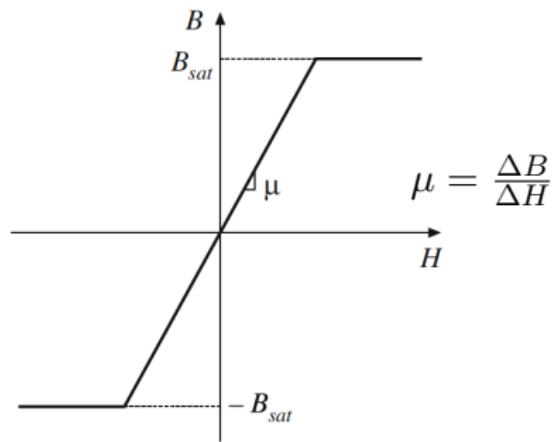


Basic magnetic relationships (cont'd 2)

Magnetic field intensity \mathbf{H} , field density \mathbf{B} , flux Φ

- Flux Φ , is the amount of \mathbf{B} passing through area A_c
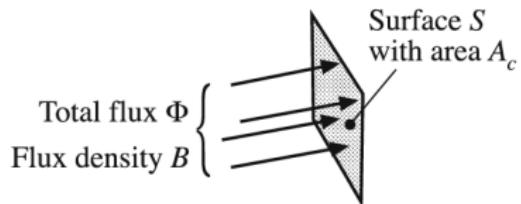
$$\Phi = \iint_{A_c} \mathbf{B} \cdot d\mathbf{A}$$




- Faraday's law: $v(t)$ induced by change in flux $\Phi(t)$

- in one turn:

$$v_{\text{turn}}(t) = \frac{d\Phi}{dt}$$

- in n -turns:

$$v(t) = n \frac{d\Phi}{dt}$$

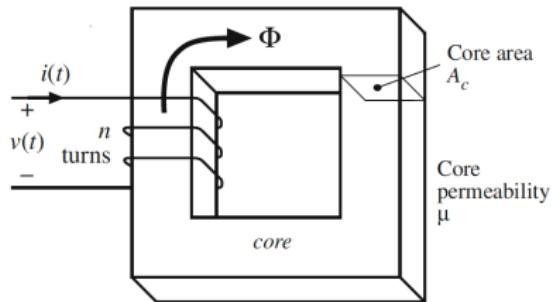

Basic magnetic relationships (cont'd 3)


Inductance definition

$$v(t) = n \frac{d\Phi}{dt} = n A_c \frac{dB}{dt} = n A_c \mu \frac{dH}{dt}$$


$$= \frac{n^2 A_c \mu}{\ell_m} \frac{di}{dt} = L \frac{di}{dt}$$

$\text{v}(t) = L \frac{di(t)}{dt}$
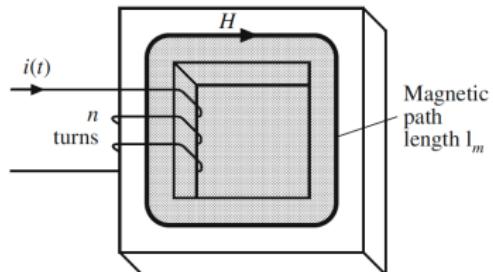
$$n i = H \ell_m \rightarrow H = \frac{n i}{\ell_m}$$



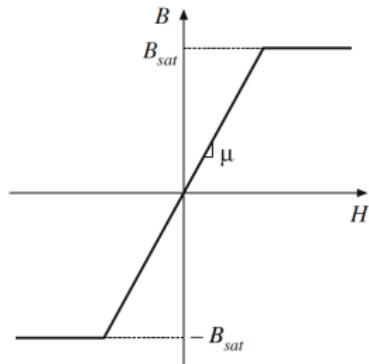- Inductance, L , depends on
 - ▶ number of turns: n
 - ▶ geometry: A_c, ℓ_m
 - ▶ material: μ
- if the core is saturated $\frac{dB}{dt} = 0$,
hence $v(t) = 0$ (inductance
behaves like a *short circuit*)



Basic magnetic relations (cont'd 4)

Inductance definition


We have derived: $v = L \frac{di}{dt}$ where L is a constant

$$\int v dt = \int L \frac{di}{dt} dt \rightarrow \int v dt = L i$$


$$v = n \frac{d\Phi}{dt} \rightarrow \int v dt = n\Phi = \lambda$$

Inductance definition

$$\lambda = L i$$

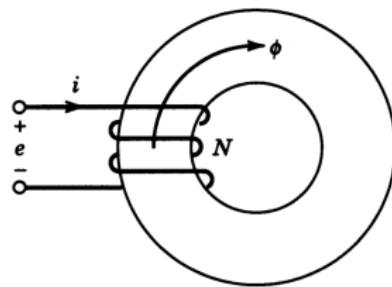

(a)

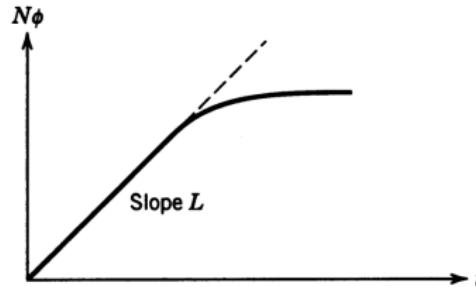

(b)

Figure 3-17 Self-inductance L .

Basic magnetic relations (cont'd 5)

Magnetic energy stored

- Magnetic energy stored in an inductor, in J (joules)

$$W = \frac{1}{2} Li^2$$

- is energy stored due to magnetic field inside a material (μ is a material-dependent constant)

$$W = \frac{1}{2} \frac{B^2}{\mu} Volume$$

- magnetic energy density, in J/m^3

$$w = \frac{1}{2} \frac{B^2}{\mu}$$

Magnetic units (International System)

$$\mu_0, \mu \left[\frac{N}{A} \right]$$

Quantity	MKS
Core material equation	$B = \mu_0 \mu_r H$
B	Tesla
H	Ampere/meter
Φ	Weber



1 Basic magnetic relations

2 Magnetic circuits

3 Transformer modelling

4 Transformer in AC circuits

Magnetic circuits

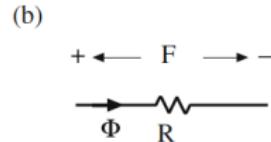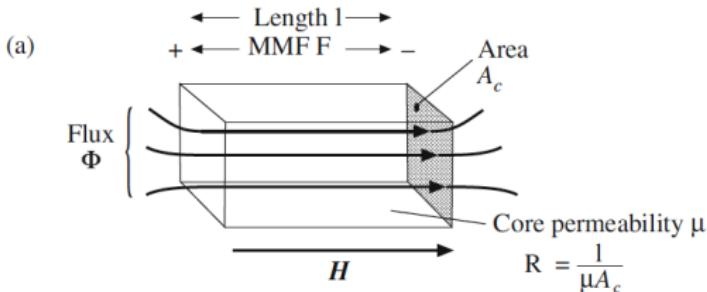

$$(\text{Magneto-motive force}) \mathcal{F} = \mathcal{R} \Phi \leftrightarrow (\text{Electro-motive force}) V = R i$$

$$\mathcal{F} = H \ell$$

$$H = \frac{B}{\mu}$$

$$B = \frac{\Phi}{A_c}$$

$$\mathcal{F} = \mathcal{R} \Phi = \frac{\ell}{\mu A_c} \Phi$$

Remember



The concept of magnetic reluctance, \mathcal{R} , is similar to the electric resistance, R

elec. $R = \mathcal{S} \cdot \frac{l}{A_c} = \frac{1}{\mu} \frac{l}{A_c}$ magn. Rel $= \frac{l}{\mu A_c}$

Magnetic circuits (cont.'d)

Kirchhoff's current law, for magnetic circuits, in a node:

$$\sum_{\text{Node}} \Phi_k = 0$$

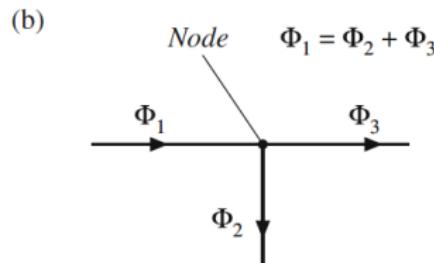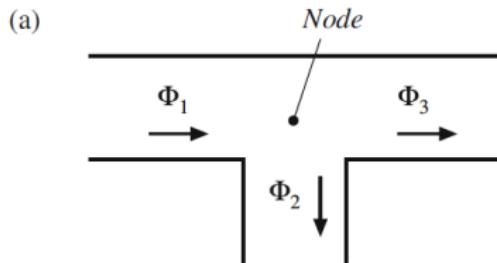


Kirchhoff's voltage law, for magnetic circuits

$$H_m \ell_m + H_g \ell_g = n i$$



$$\mathcal{F}_m + \mathcal{F}_g = n i$$

$$(\mathcal{R}_m + \mathcal{R}_g) \Phi = n i$$
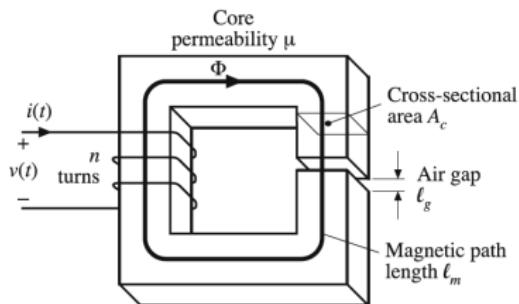
$$\sum_{\text{loop}} \mathcal{R} \Phi = \sum_{\text{loop}} n i$$



Magnetic circuits (cont.'d 2)

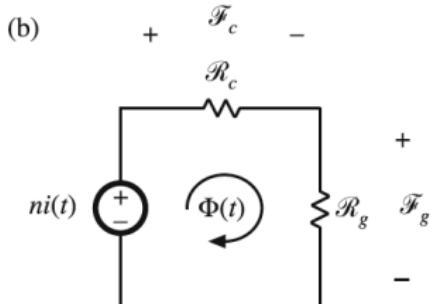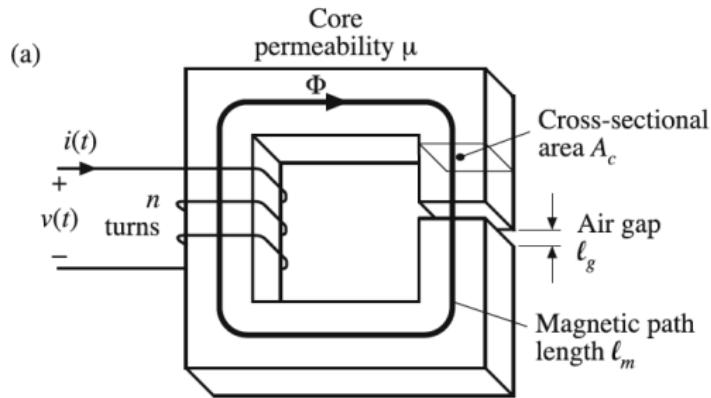

$$\mathcal{R}_c = \frac{\ell_m}{\mu A_c}$$


$$\mathcal{R}_g = \frac{\ell_g}{\mu_0 A_c}$$

$$\sum_{\text{loop}} \mathcal{R} \Phi = \sum_{\text{loop}} n i$$

$$(\mathcal{R}_c + \mathcal{R}_g) \Phi = n i$$

Magnetic circuits (cont.'d 3)

Inductance and magnetic core reluctance

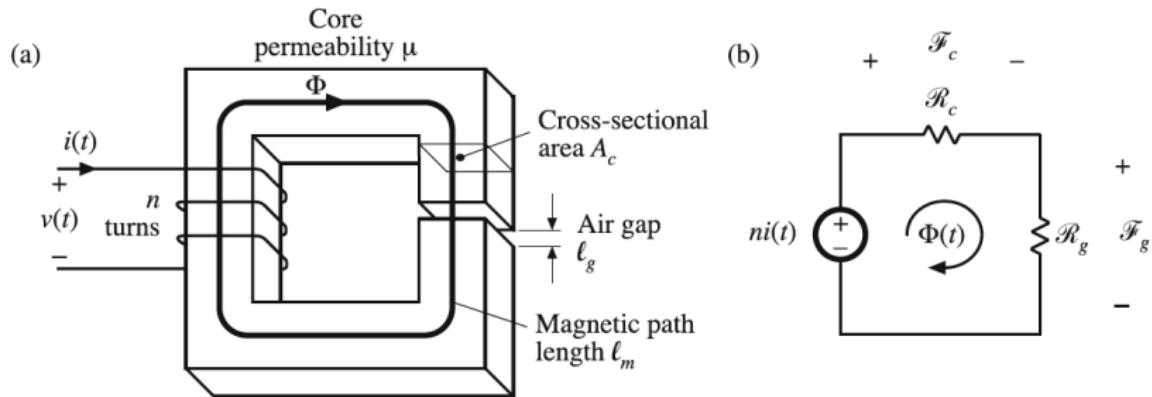

We can determine the inductance using the magnetic circuit relations

$$(\mathcal{R}_c + \mathcal{R}_g) \Phi = n i(t)$$

$$v(t) = n \frac{d\Phi(t)}{dt}$$

$$v(t) = L \frac{di(t)}{dt}$$

$$v(t) = \left(\frac{n^2}{\mathcal{R}_c + \mathcal{R}_g} \right) \frac{di(t)}{dt}$$

Electrical and magnetic circuits analogies

Table 3-3 Magnetic–Electrical Circuit Equation Analogy

Magnetic	Electrical (dc)
$\frac{Ni}{\phi} = \mathcal{R} = \frac{l}{\mu A}$	Ohm's law: $\frac{v}{i} = R = \frac{l}{A/\rho}$
$\phi \sum_k \mathcal{R}_k = \sum_m N_m i_m$	Kirchhoff's voltage law: $i \sum_k R_k = \sum_m v_m$
$\sum \phi_k = 0$	Kirchhoff's current law: $\sum_k i_k = 0$

Source: Mohan, Undeland, Robbins (2002) *Power Electronics: Converters, Applications, and Design*, 3rd Edition, Chapter 3



1 Basic magnetic relations

2 Magnetic circuits

3 Transformer modelling

4 Transformer in AC circuits

Transformer modelling

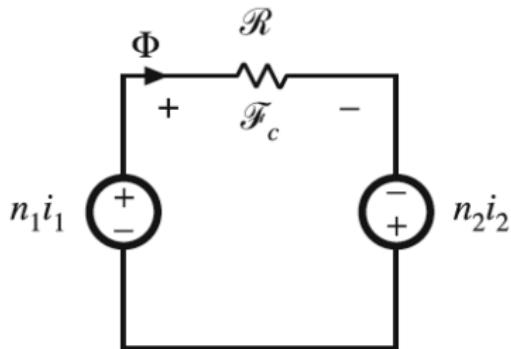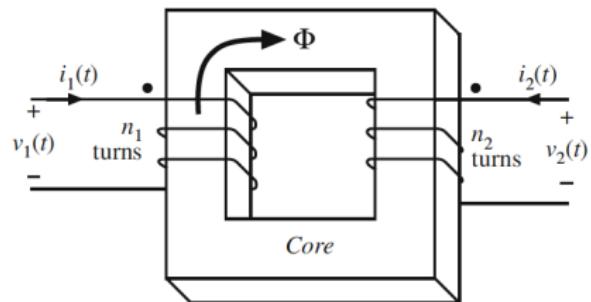

$$\sum_{\text{loop}} \mathcal{R} \Phi = \sum_{\text{loop}} n i$$

$$\begin{aligned}\mathcal{R} \Phi &= n_1 i_1 + n_2 i_2 \\ 0 &= n_1 i_1 + n_2 i_2\end{aligned}$$



$$H_m \ell_m = n_1 i_1 + n_2 i_2$$

(ideal transformer $\mathcal{R} = 0$)

dot (\bullet) convention (on transformer windings):

- (1) current entering the \bullet produces flux in the direction shown (right hand thumb rule)
- (2) current entering/leaving the \bullet in one winding, induces +ve/-ve voltage at the \bullet of the other winding


Ideal transformer $\mathcal{R} = 0$

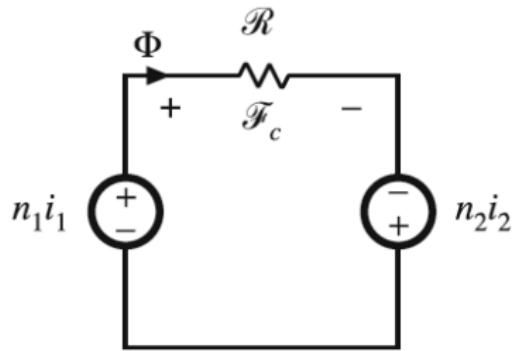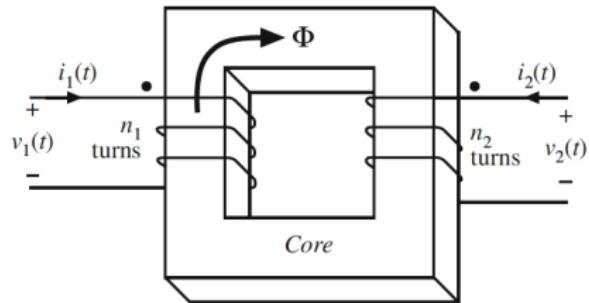



$$0 = n_1 i_1 + n_2 i_2$$

Faraday's law:
$$\begin{cases} v_1 = n_1 \frac{d\Phi}{dt} \\ v_2 = n_2 \frac{d\Phi}{dt} \end{cases}$$
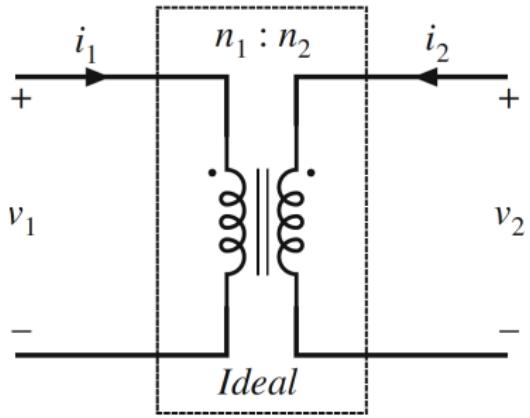
$$\frac{d\Phi}{dt} = \frac{v_1}{n_1} = \frac{v_2}{n_2} \rightarrow \boxed{\frac{v_1}{v_2} = \frac{n_1}{n_2}}$$



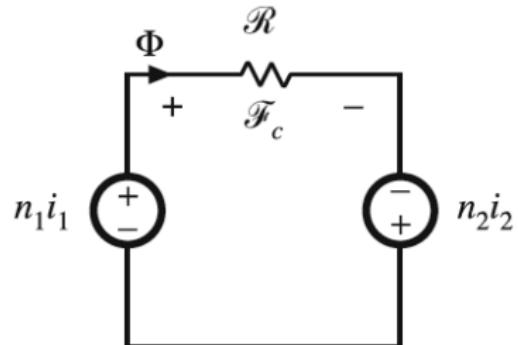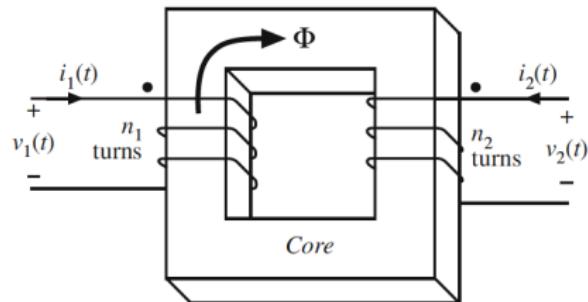Actual transformer $\mathcal{R} > 0$, magnetizing inductance L_M




$$\mathcal{R}\Phi = n_1 i_1 + n_2 i_2$$

$$\Phi = \frac{n_1 i_1 + n_2 i_2}{\mathcal{R}}$$

Faraday's law:
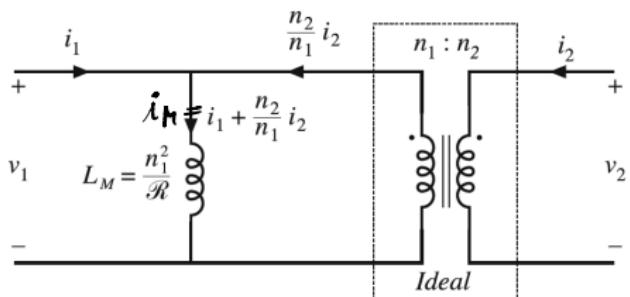
$$v_1 = n_1 \frac{d\Phi}{dt} = \underbrace{\frac{n_1^2}{\mathcal{R}}}_{L_M} \frac{d}{dt} \left(\underbrace{i_1 + \frac{n_2}{n_1} i_2}_{i_M} \right)$$



Actual transformer (cont'd)

- dc input voltage



$$v_1 = V_{\text{dc}} = \text{constant}$$

$$v_1 = \underbrace{\frac{n_1^2}{\mathcal{R}}}_{L_M} \frac{d}{dt} \underbrace{\left(i_1 + \frac{n_2}{n_1} i_2 \right)}_{i_M}$$

$$\frac{d}{dt} \underbrace{\left(i_1 + \frac{n_2}{n_1} i_2 \right)}_{i_M} = \text{constant}$$

i_M grows at constant rate, i.e.
the primary sees a short-circuit!


- Secondary disconnected ($i_2 = 0$)

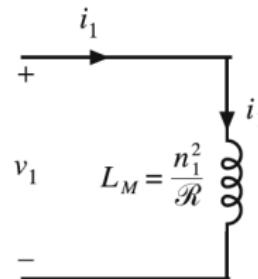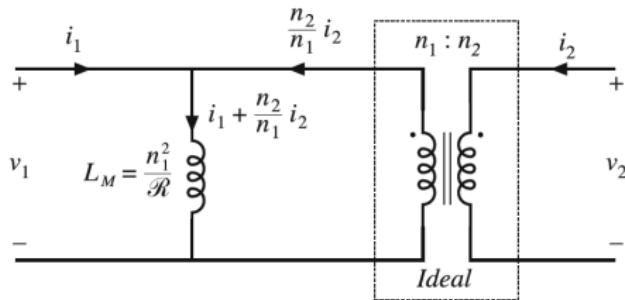

Actual transformer (cont'd 2)

key takeaways:

- transformer changes voltage (and current) level between two circuits
- ideal transformer ($\mathcal{R} = 0$): $n_1 i_1 + n_2 i_2 = 0$
- actual transformer ($\mathcal{R} > 0$): $n_1 i_1 + n_2 i_2 = \mathcal{R} \Phi \rightarrow \mathcal{R} \Phi = n_1 i_M$
 - ▶ $n_1 i_M$ is the magneto motive force establishing flux Φ in the core
 - ▶ $n_1 i_M$ is the amount by which $n_1 i_1 + n_2 i_2 \neq 0$
- alternative way to represent the actual transformer, based on
 $n_1 i_1 + n_2 i_2 = n_1 i_M \rightarrow n_1 (i_1 - i_M) + n_2 i_2 = 0$

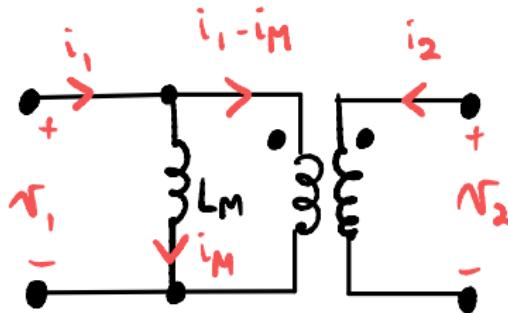

- often, it is posed: $i_1 - i_M = i'_1$


1 Basic magnetic relations

2 Magnetic circuits

3 Transformer modelling

4 Transformer in AC circuits

Ideal transformer in AC circuits

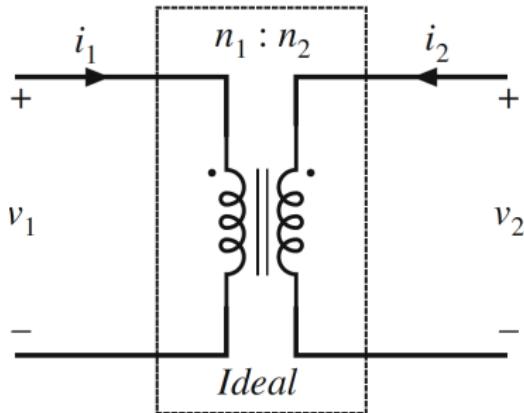


$$\bar{V}_1 = n_1 \frac{d\bar{\Phi}}{dt} = j \omega n_1 \bar{\Phi}$$

$$\bar{V}_2 = n_2 \frac{d\bar{\Phi}}{dt} = j \omega n_2 \bar{\Phi}$$


$$\boxed{\frac{\bar{V}_1}{\bar{V}_2} = \frac{n_1}{n_2}} \quad \frac{n_1}{n_2} = a_t: \text{turns ratio}$$

Ideal transformer in AC circuits (cont'd 1)

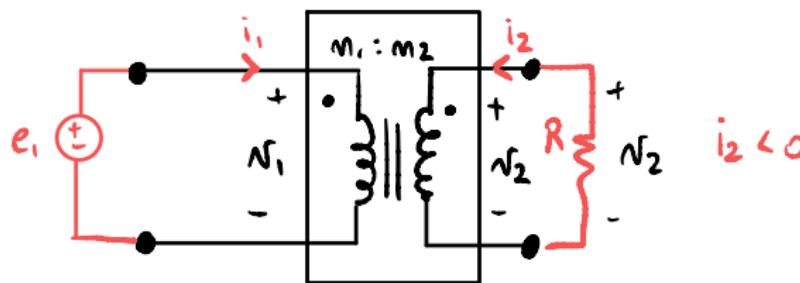Assuming power flow from left to right (from voltage source to R-load), then secondary current is +ve if the convention is as per the bottom figure



$$n_1 i_1 + n_2 i_2 = 0$$

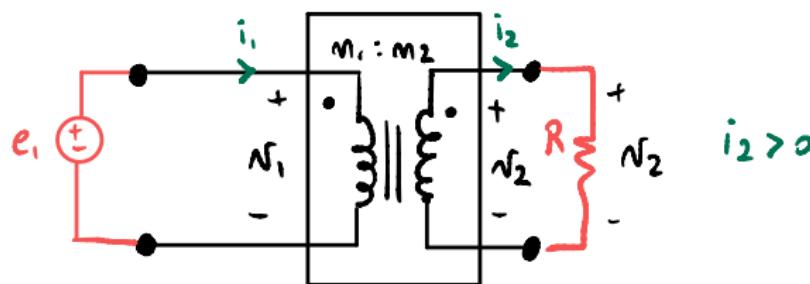


$$n_1 i_1 + n_2 (-i_2) = 0$$

$$n_1 i_1 - n_2 i_2 = 0$$

dot convention → since i_1 enters primary •, the voltage induced in the secondary, v_2 , is +ve at the •

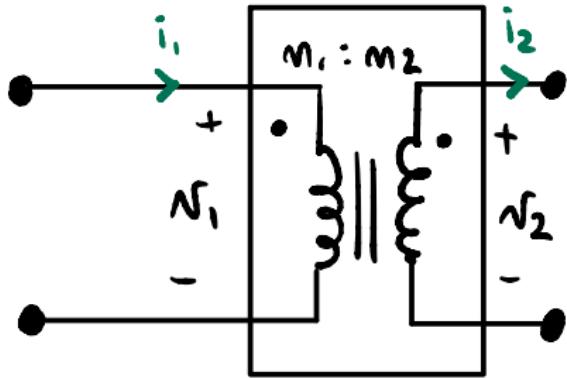Ideal transformer in AC circuits (cont'd 2)



- Complex power entering winding 1 equals the complex power leaving winding 2:

$$\bar{S}_1 = \bar{S}_2$$

$$\bar{V}_1 \bar{I}_1^* = \bar{V}_2 \bar{I}_2^*$$

$$\bar{S}_1 = \bar{V}_1 \bar{I}_1^* = a_t \bar{V}_2 \frac{\bar{I}_2^*}{a_t} = \bar{S}_2$$

$$V = n \frac{d\Phi}{dt} \rightarrow \boxed{\frac{\bar{V}_1}{\bar{V}_2} = \frac{n_1}{n_2} = a_t}$$


- impedance $Z_2 = \frac{\bar{V}_2}{\bar{I}_2}$ seen from winding 1

$$n_1 \bar{I}_1 = n_2 \bar{I}_2 \rightarrow \boxed{\frac{\bar{I}_1}{\bar{I}_2} = \frac{n_2}{n_1} = \frac{1}{a_t}}$$

$$Z_2' = \frac{\bar{V}_1}{\bar{I}_1} = \frac{a_t \bar{V}_2}{\bar{I}_2/a_t} = a_t^2 Z_2$$



Practical transformer in AC circuits

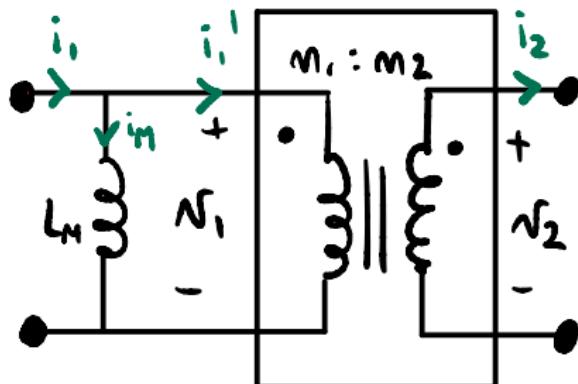Magnetic core reluctance $\mathcal{R} > 0$




$$\bar{V} = n \frac{d\bar{\Phi}}{dt} \rightarrow \frac{\bar{V}_1}{\bar{V}_2} = \frac{n_1}{n_2} = a_t$$
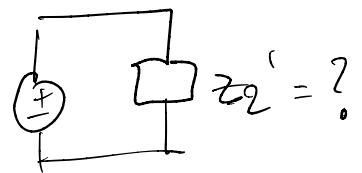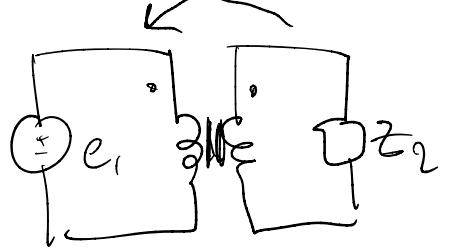
$$n_1 \bar{I}'_1 = n_2 \bar{I}_2 \rightarrow \frac{\bar{I}'_1}{\bar{I}_2} = \frac{n_2}{n_1} = \frac{1}{a_t}$$




Practical transformer in AC circuits (cont'd 1)

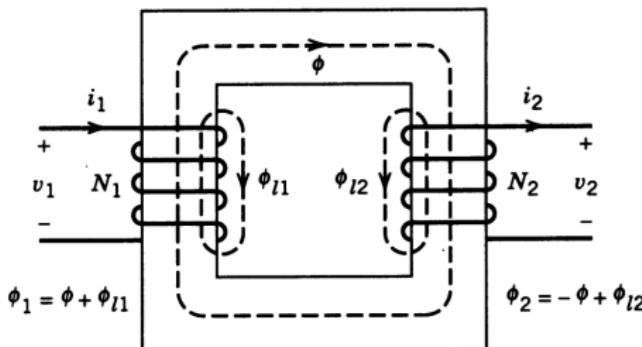Magnetic core reluctance $\mathcal{R} > 0$, and windings leak some flux outside the core




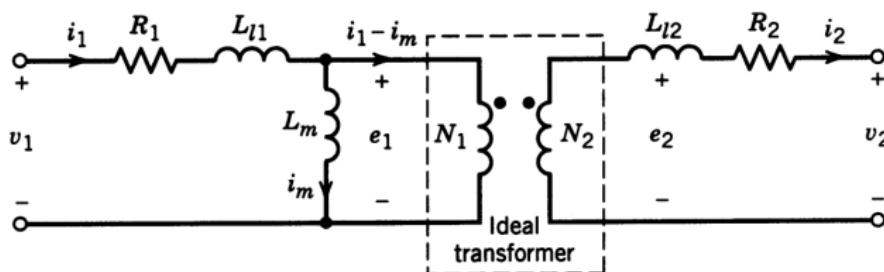- Flux is “leaked” outside the core by each winding Φ_{l1}, Φ_{l2}
- these leaked flux is modelled by leakage inductance L_{l1}, L_{l2}
- R_1 and R_2 represent windings' copper (ohmic) losses




Practical transformer in AC circuits (cont'd 2)

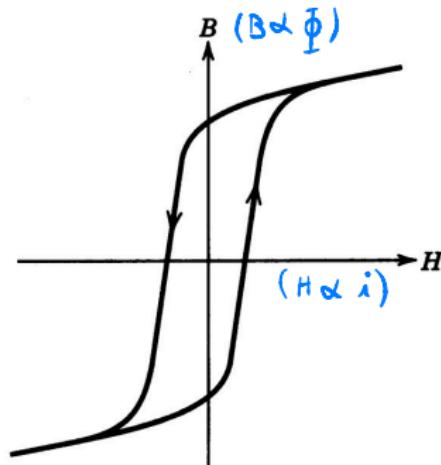Magnetic core reluctance $\mathcal{R} > 0$, windings leak some flux outside the core, and core dissipates active power (hysteresis and other losses)



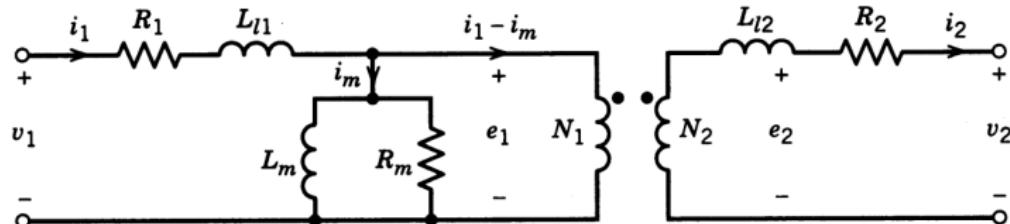- due to hysteresis of the B-H curve, energy is dissipated inside the core to create the magnetizing flux
- this energy loss in the magnetization process is represented by an additional shunt resistance R_m in parallel with L_m



Readings

From *Mohan (2011), Power Electronics - A First Course*

- Chapter 7: Magnetic Circuit Concepts Fundamentals (MQ library [link](#))
 - ▶ 7.1: Ampere-Turns and Flux
 - ▶ 7.2: Inductance L
 - ▶ 7.3: Faraday's Law: Induced Voltage in a Coil Due to Time-Rate of Change of Flux Linkage
 - ▶ 7.5: Transformers

From *Glover (2017), Power System Analysis & Design*

- Chapter 3: Power Transformers (MQ library [link](#))
 - ▶ 3.1: The Ideal Transformer
 - ★ Example 3.1: Ideal, single-phase two windings transformer
 - ▶ 3.2: Equivalent Circuits for Practical Transformers
 - ★ Example 3.2 (optional): Transformer short-circuit and open-circuit tests

References


- ① Ned Mohan, Tore M. Undeland, William P. Robbins (2002), *Power Electronics: Converters, Applications, and Design*, 3rd Edition, Wiley
- ② Erickson, R. W., Maksimovic, D. (2020), *Fundamentals of Power Electronics*, Springer International Publishing

Example 3.1 p. 99 (Glover 2017)

- 1φ transformer (ideal)

$$S = 20 \text{ kVA}$$
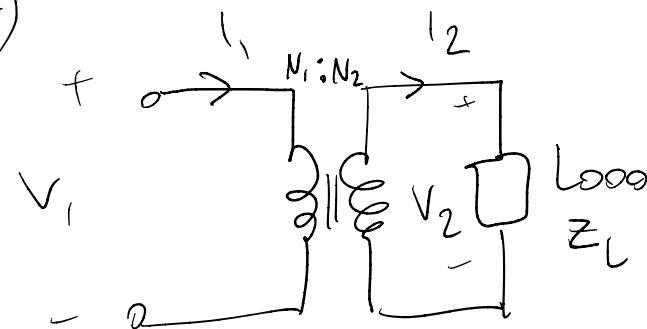
$$\left. \begin{array}{l} V_1 = 480 \text{ V} \\ V_2 = 120 \text{ V} \\ f = 60 \text{ Hz} \end{array} \right\} \begin{array}{l} \text{rated} \\ \text{values} \end{array}$$



$$\bar{V}_2 = 118 e^{j0^\circ} \text{ V}$$

- Load

$$S_L = 15 \text{ kVA}$$

$$\cos \phi = 0.8 \text{ (lagging)}$$

$$V_2 = 118 \text{ V} \quad (\text{assume } \bar{V}_2 = 118 e^{j0^\circ} \text{ V})$$

a) $V_1 = ?$

b) $Z_L = ?$

c) $Z'_L = ?$ (Z_L seen by the primary windings)

d) P, Q supplied by the transformer

$$a) \frac{V_1}{V_2} = \frac{480 \text{ V}}{120 \text{ V}} = \alpha_t = \frac{N_1}{N_2} = 4$$


if $V_2 = 118 \text{ V}$ then $V_1 = \frac{N_1}{N_2} V_2 = 4 \cdot 118 = 472 \text{ V}$

b) $Z_L = ?$ $\cos \phi = 0.8$ lagging

$$|S_2| = |V_2| \cdot |I_2^*|$$

$$S_2 = V_2 \cdot I_2$$

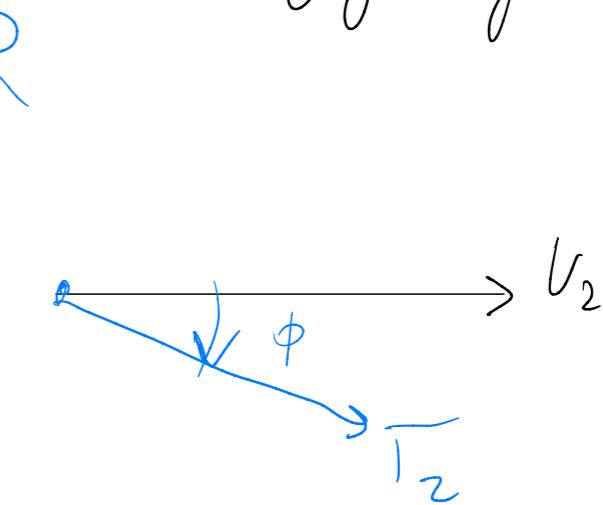
$$I_2 = \frac{S_2}{V_2} = \frac{15 \text{ kVA}}{118 \text{ V}} = 127.12 \text{ A} \quad \phi = \cos^{-1}(0.8)$$




$$\bar{I}_2 = 127.12 e^{-j\phi} = 127.12 e^{-j36.87^\circ} \text{ A}$$

$$Z_L = \frac{\bar{V}_2}{\bar{I}_2} = \frac{118}{127.12 e^{j36.87^\circ}} = 0.928 e^{+j36.87^\circ} \Omega$$


(c) load impedance seen at the primary

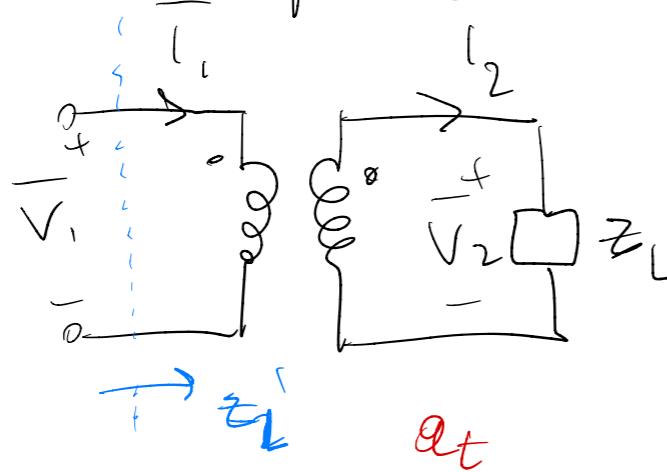
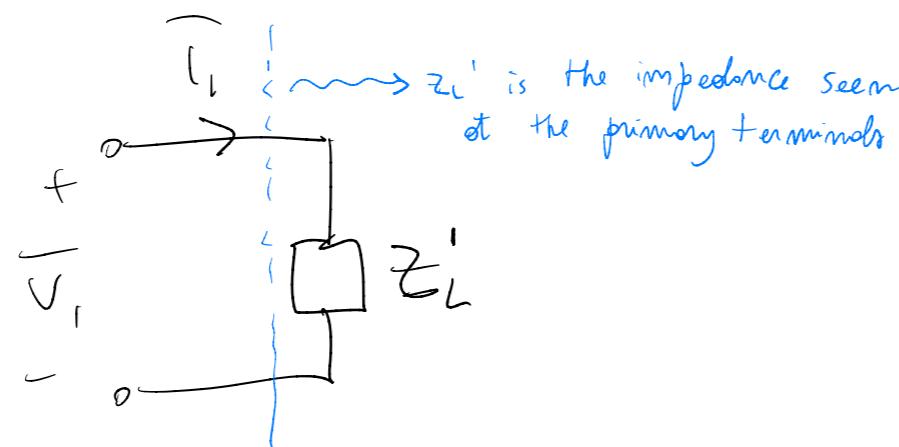
$$\begin{aligned} z_L' &= \frac{\bar{V}_1}{\bar{I}_1} = \frac{\frac{N_1}{N_2} \bar{V}_2}{\frac{N_2}{N_1} \bar{I}_2} = (\alpha_t)^2 \frac{\bar{V}_2}{\bar{I}_2} = (\alpha_t)^2 Z_L \\ &= (4)^2 \cdot 0.928 e^{+j36.87^\circ} = 14.8528 e^{+j36.87^\circ} \Omega \end{aligned}$$



(d) P and Q supplied by the ferries my

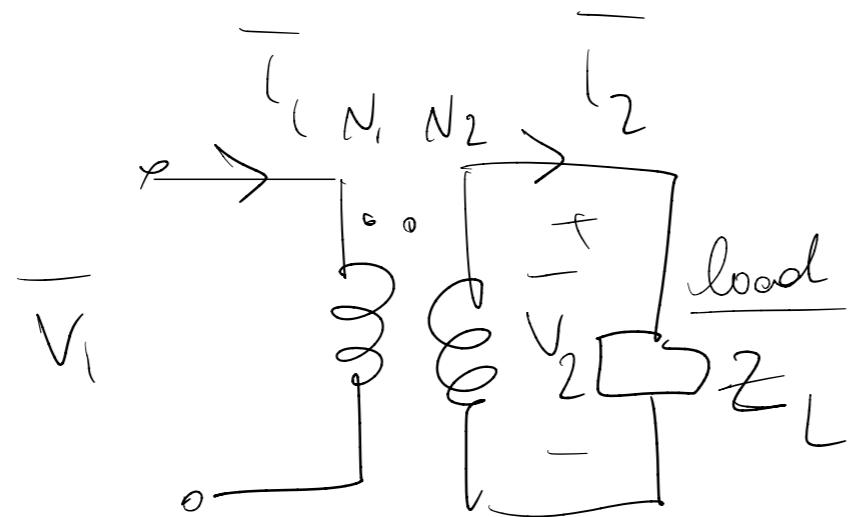


load

$$S_L = 15 \text{ kVA}$$

$$\cos \phi = 0.8 \text{ (lapping)}$$

ATM

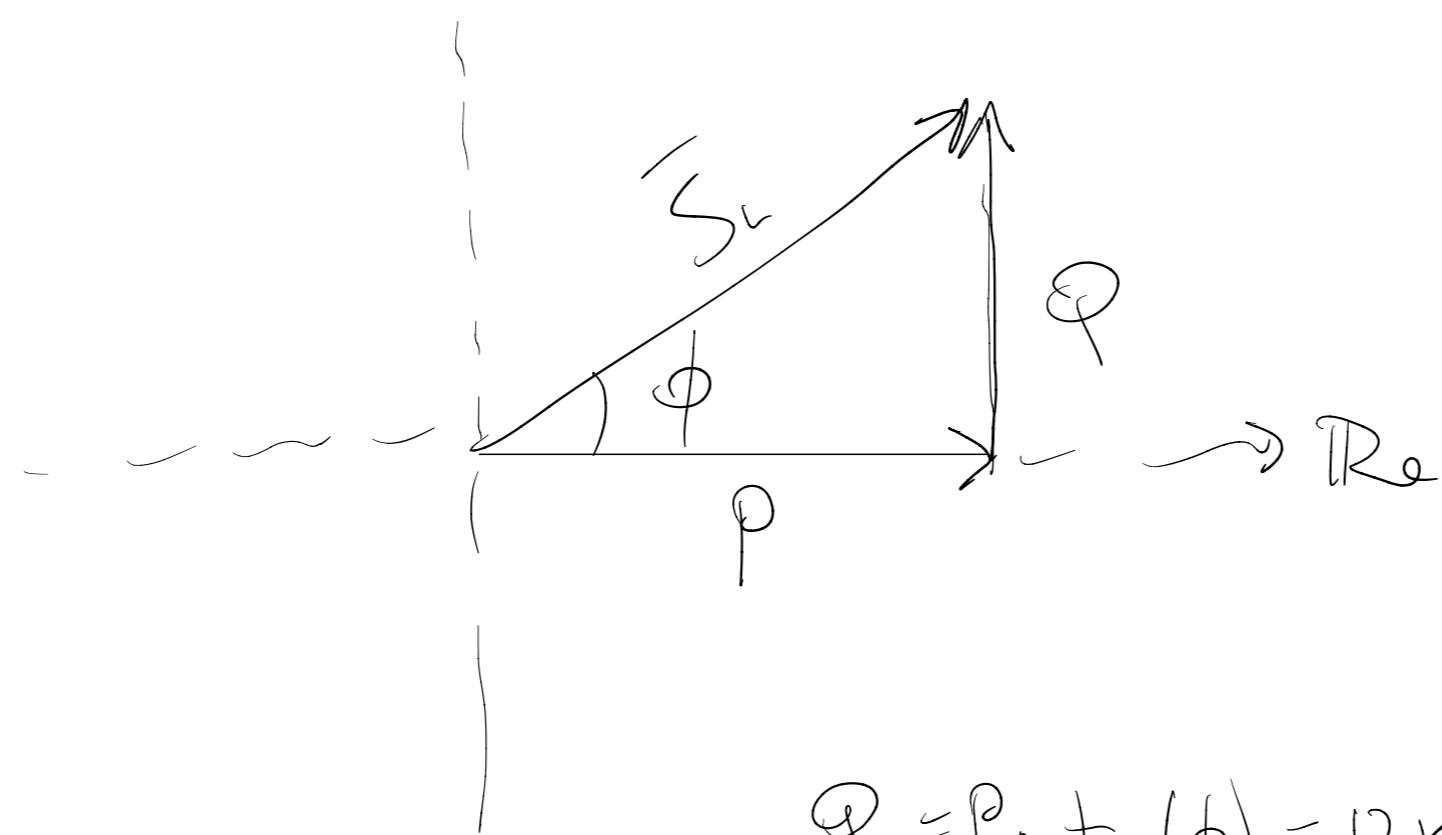


$$\begin{aligned} P &= S_L \cdot \cos \phi \\ &= 15 \text{ kVA} \cdot 0.8 \end{aligned}$$

$$= 12 \text{ kW}$$

$$\frac{Q}{P} = +j \phi$$

$$Q = P \cdot +j \phi = 12 \text{ kW} \cdot +j (\cos(0.8)) = 9 \text{ kVAr}$$
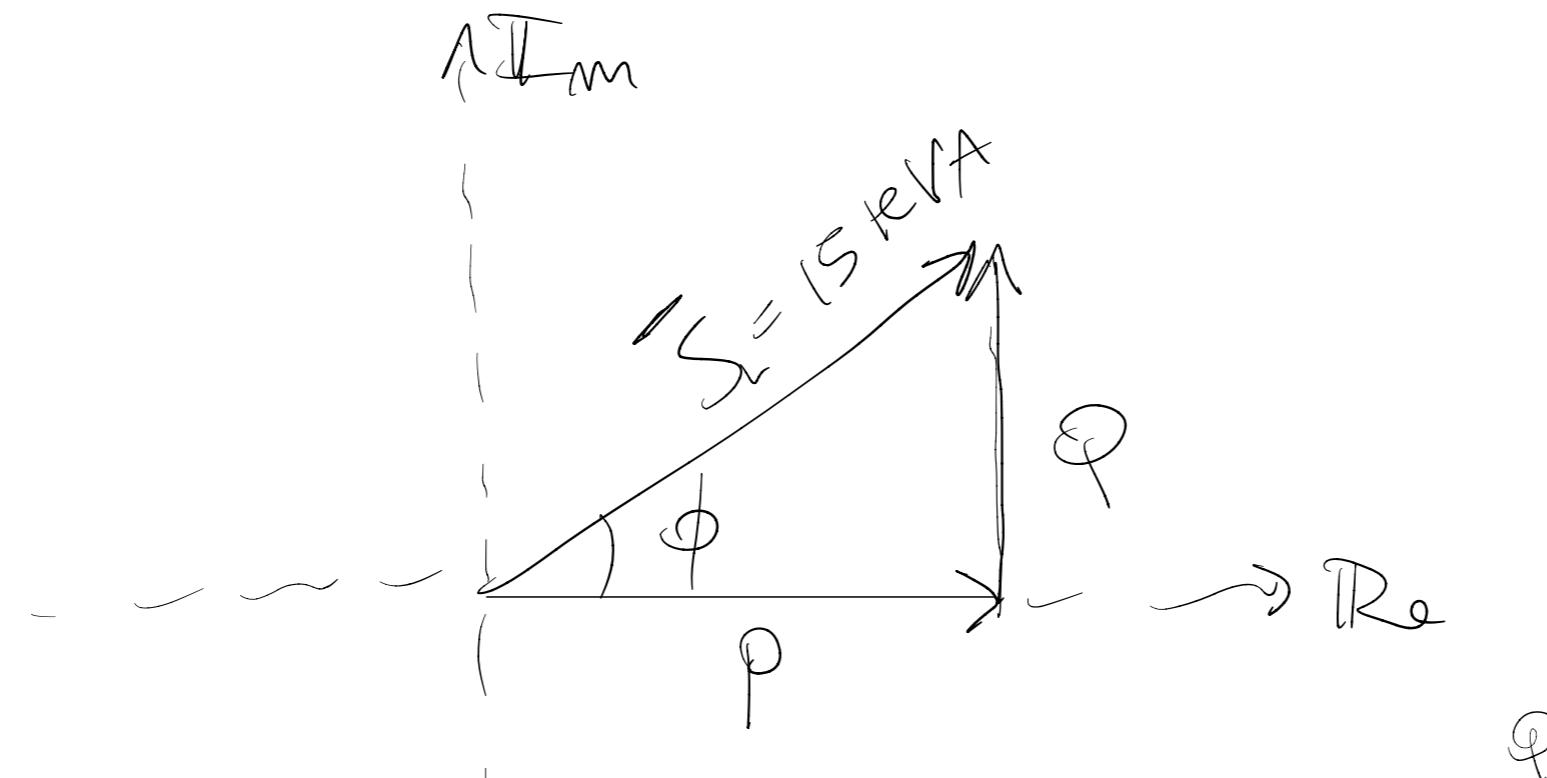
$$S_L = 12 \text{ kW} + j 9 \text{ kVAr} = \bar{S}_1$$



Alternative way to calculate
P, and Q using the complex power:

$$\begin{aligned}
 \bar{S}_L &= S_L e^{j\phi} = 15 \text{ kVA} e^{j \cos^{-1}(0.8)} \\
 &= 15 \text{ kVA} (\cos(36.87^\circ) + j \sin(36.87^\circ)) \\
 &= 12 \text{ kW} + j 9 \text{ kVAr}
 \end{aligned}$$

