




# ELEC2005

# Electrical and Electronic Systems

DIODES

DAVID PAYNE

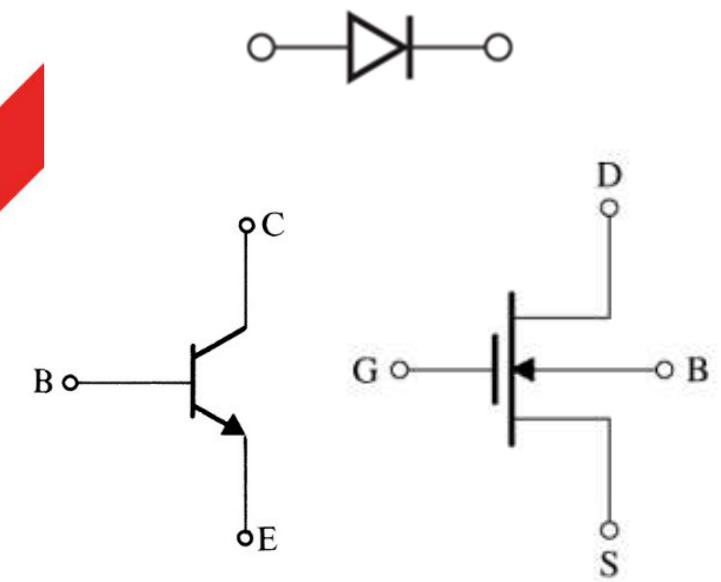

# Goals of this lecture

---



- Understand what nonlinearity means
- Understand how we can use nonlinearity
- Be familiar with Diodes and their non-linear characteristics
- Analyse basic diode circuits
- Be able to use models for analysing diode circuits
- Understand diode applications: rectifiers and wave-shaping circuits
- Small signal analysis

# Intro to Nonlinear Devices




MACQUARIE  
University
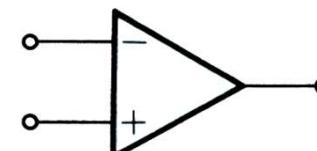
## WHAT IS A NONLINEAR DEVICE/CIRCUIT?

---


- Many systems/subsystems involve complex nonlinear circuits with multiple nonlinear devices
- Four of the most common nonlinear devices are shown here, diodes and transistors and the circuits constructed with them are the focus of part 1 of this unit
- For each of these, the relationship between their output and input characteristics is not linear




Opamp



Diode

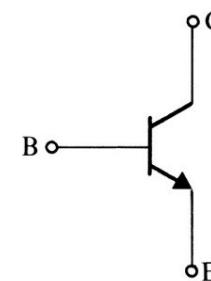

Bipolar Junction  
Transistor

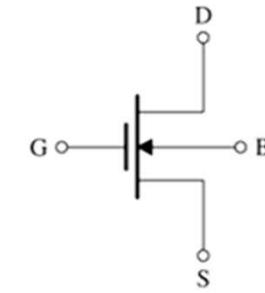

Field Effect  
Transistor

# Intro to Nonlinear Devices





MACQUARIE  
University
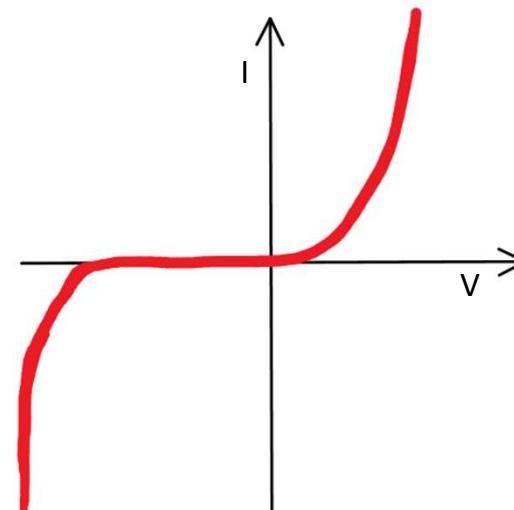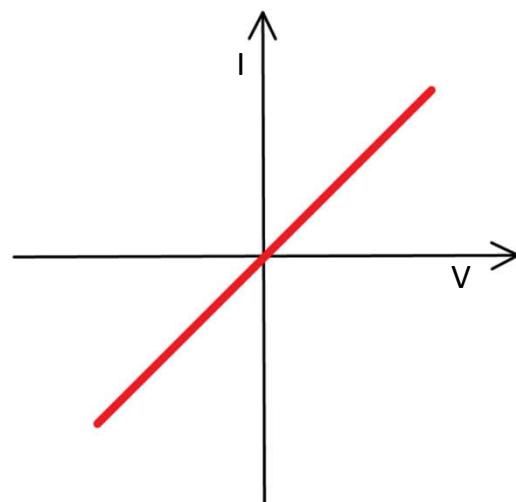
## WHAT IS A NONLINEAR DEVICE/CIRCUIT?

---

- Devices such as *ideal* resistors, capacitors and inductors have a output characteristics that are a linear function of input.
- Diodes and transistors have a more complex relationship between input and output
  - Though they have regions of linearity







# Lecture 2

- 1. Diode Fundamentals & Models**
- 2. Diode Circuits & Applications**
- 3. Small Signal Analysis**
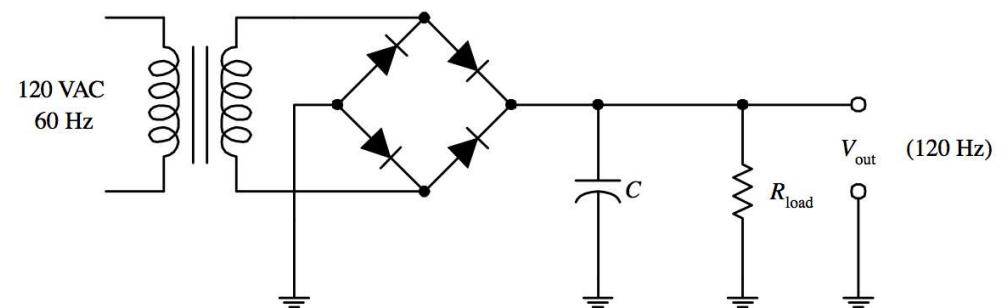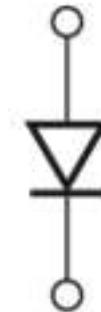
# Diodes: What is a diode?

- An two terminal device with non-linear IV characteristics
- Exhibits asymmetric conductance - primarily conducts current in one direction
- Fabricated using a semiconductor with a p-n junction (more on this later)
- They have many applications, including:
  - ❖ Power conversion
  - ❖ Over-voltage protection
  - ❖ Detectors
  - ❖ Signal Generation




# A little bit of history....

---

- Originally known as rectifiers and were developed as radio receiver detectors in the early 1900s (vacuum-tubes and semiconductors versions simultaneously developed)
- The Thermionic diode (Vacuum tube) effect was first discovered as far back as 1873, by Frederick Guthrie
- The effect was first discovered in a semiconductor in 1874 by Ferdinand Braun
- The term diode was first coined in 1919, from it's Greek roots, it means two (di) paths (ode)



Frederick Guthrie

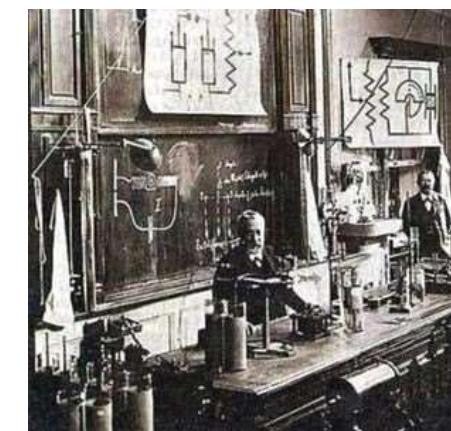


Ferdinand Braun
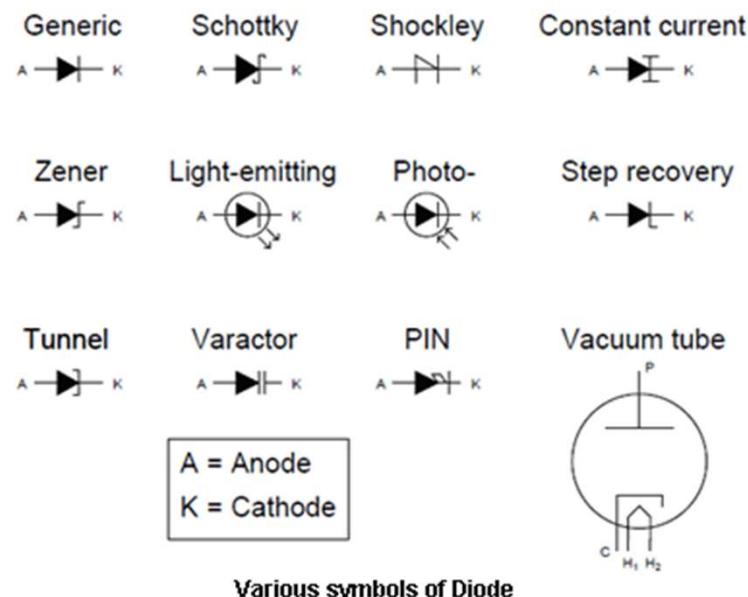
# Types of diode




- Nowadays, a huge variety of diode technology has been developed, they are widely used!




Not all are based on p-n junctions!
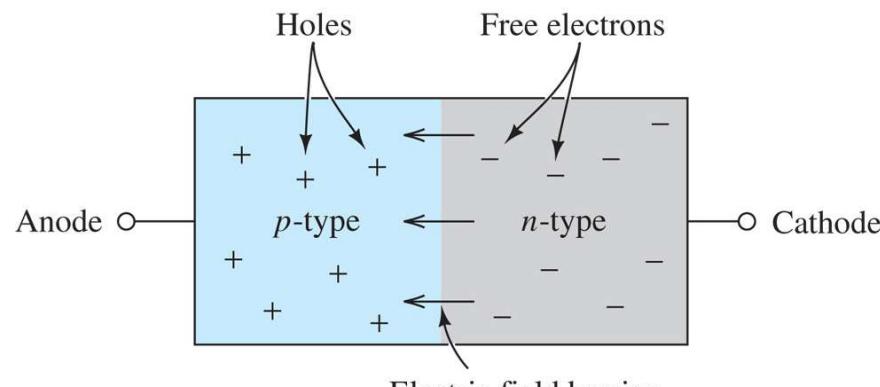
# The PN Junction

- Modern diodes are typically based on p-n junctions fabricated using semiconductors (commonly silicon)
- These junctions conduct current asymmetrically



(c) Simplified physical structure

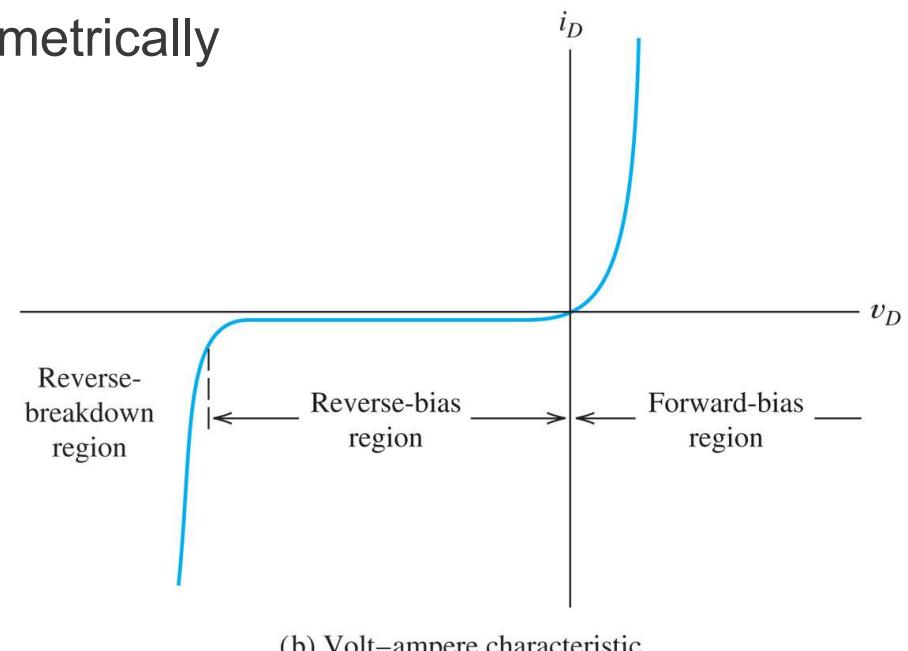


(b) Volt–ampere characteristic

# Junction Diode Characteristics



MACQUARIE  
University

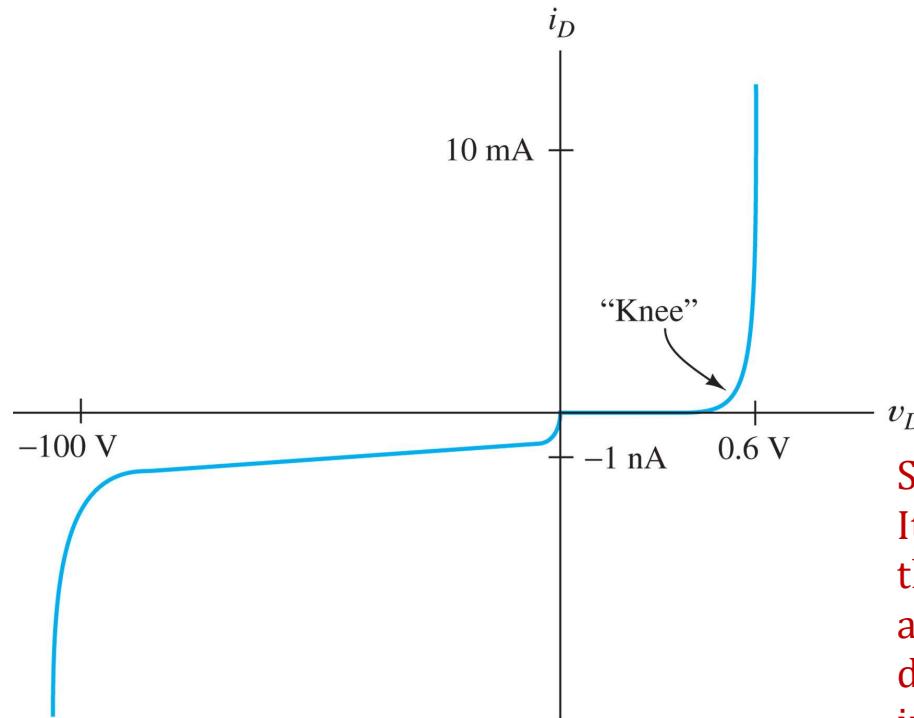

Approximate Shockley Equation  
(for forward bias more than several tenths of a volt)

$$i_D \cong I_s \exp\left(\frac{v_D}{nV_T}\right)$$

Much easier to use

Shockley Equation  
(for forward bias)

$$i_D = I_s (e^{v_D/nV_T} - 1)$$

$$i_D = I_s \left[ \exp\left(\frac{v_D}{nV_T}\right) - 1 \right]$$

Saturation current.  
Its value depends on  
the area of the diode  
and the temperature,  
doubling for each 5°  
increase for silicon  
diodes.

$\sim 10^{-14} \text{ A}$  at 300 K

Emission  
coefficient  
(ideality factor)

$$1 < n < 2 \\ n \approx 1$$

Thermal voltage.  
 $V_T = kT/q \approx$   
**26 mV at 300 K**

Temperature in K  
(273 + temp in °C)

$k = 1.38 \times 10^{-23}$  joules/kelvin Boltzmann's constant



$q = 1.60 \times 10^{-19}$  coulomb magnitude of charge of an electron
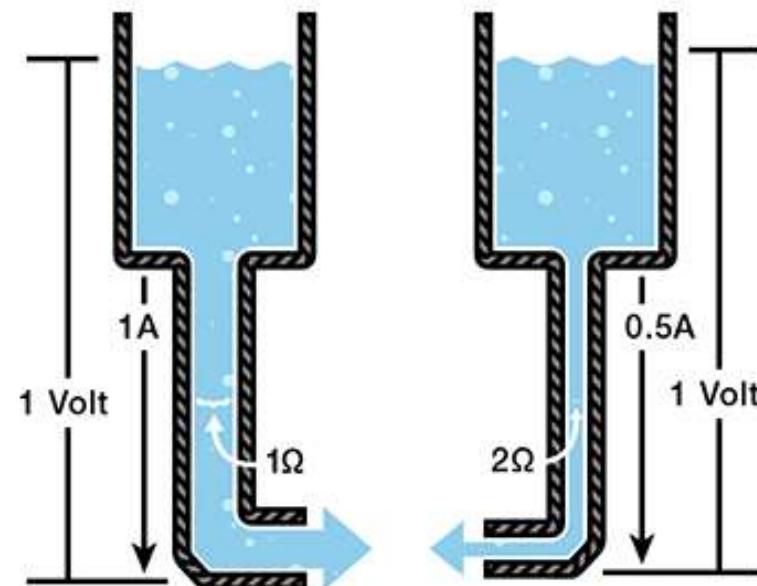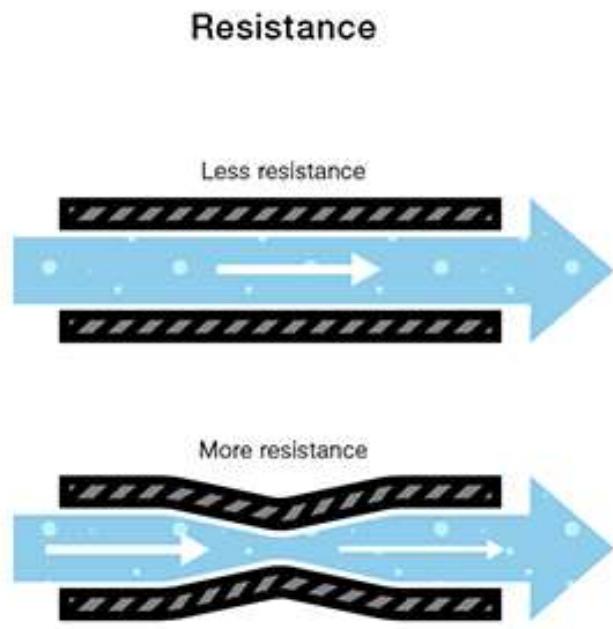
# The Pipe Analogy



MACQUARIE  
University

- In the pipe analogy (AKA hydraulic analogy):
- Electric potential is equivalent to pressure. i.e. voltage is equivalent to the difference in pressure between two points
- Current is equivalent to flow rate, and charge is equivalent to quantity of water



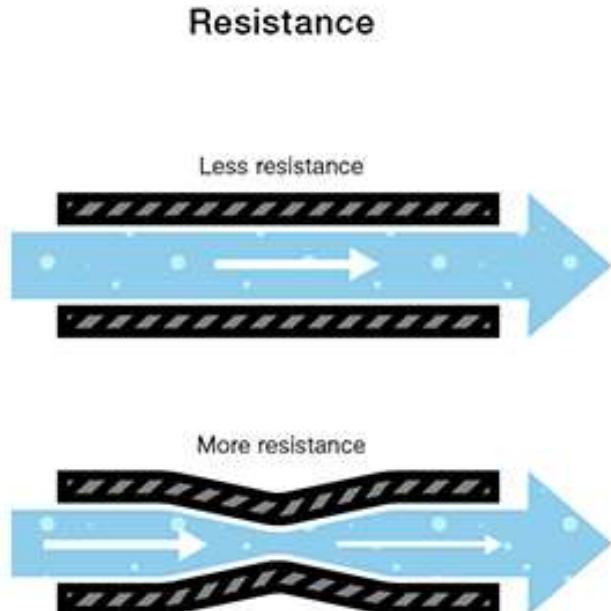
# The Pipe Analogy



MACQUARIE  
University

- In the pipe analogy (AKA hydraulic analogy):
- Electric potential is equivalent to pressure. i.e. voltage is equivalent to the difference in pressure between two points
- Current is equivalent to flow rate, and charge is equivalent to quantity of water



What would the hydraulic equivalent to a diode be?

- A narrow pipe
- A T-Junction
- A valve
- A pump

Start the presentation to see live content. For screen share software, share the entire screen. Get help at [polliev.com/app](http://polliev.com/app)

Go to [PollEv.com/davidpayne187](http://PollEv.com/davidpayne187) on your mobile or laptop to vote

# The Pipe Analogy




MACQUARIE  
University

Element	Circuit Analogy	Pipe Analogy	Flow Equation
Node	Junction	●	Junction
Path	Wire	—	Rigid Pipe
Resistance	Resistor	—■—	Aperture
Compliance	Capacitor	—  —	Diaphram
Inertance	Inductor	—○○○—	Heavy Paddle
Switch	Switch	—\—	Gate Valve
Valve	Diode	—►—	Check Valve
Pressure Source	Voltage Source	—  +—	Pump
Flow Source	Current Source	—○—	$F = F$

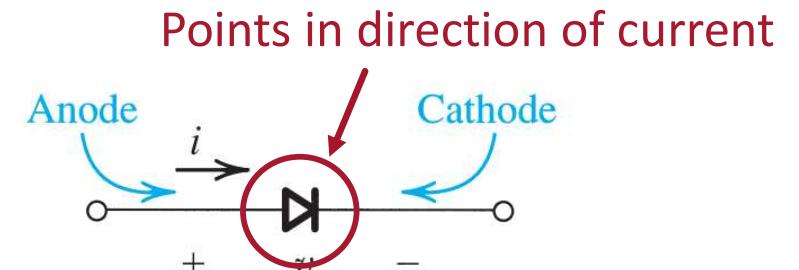
# The Ideal Diode



- If a negative voltage is applied (reverse bias), no current flows – open circuit
- If a positive current is applied (forward bias), there is no voltage drop – short circuit




i-v characteristic

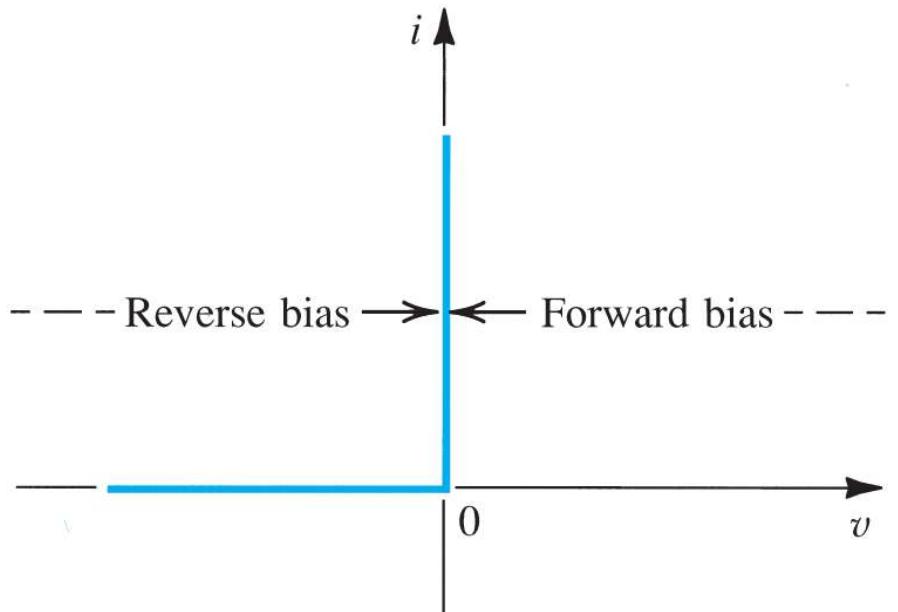


## Equivalent Circuits

### Reverse Direction

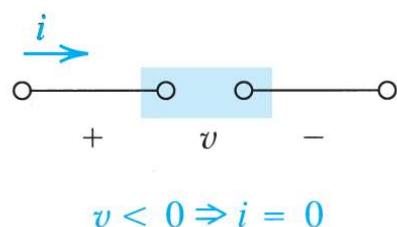

### Forward Direction

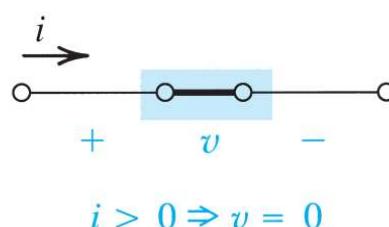

# Analysis by Assumed States

---



In a circuit with a number of diodes:


- Assume a state for each diode (ON or OFF).
- $n$  diodes will require  $2^n$  possible combinations.
- Calculate currents of ON diodes and voltages of OFF diodes.
- Check to see if the calculations are consistent with the assumptions.
- If yes, the assumption works. If not, return to step 1 and make a new assumption.
- Making a table for your assumptions helps!
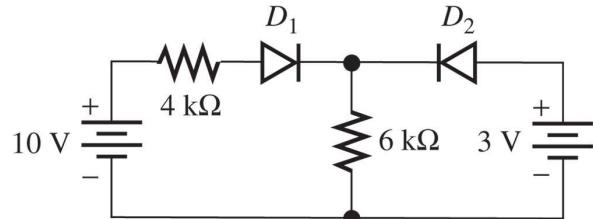
# Example Exercise



MACQUARIE  
University


See *Hambley Example 10.5* for more details



(a) Circuit diagram


Use the ideal diode model to solve the circuit.

Assume  $D_1$  off and  $D_2$  on:

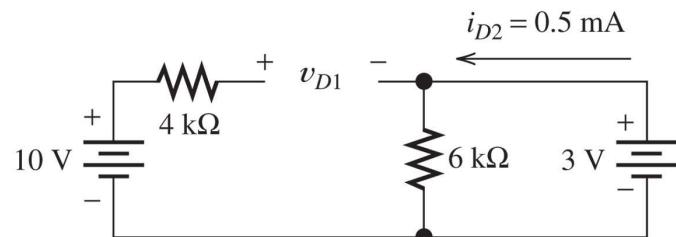

(b) Equivalent circuit assuming  $D_1$  off and  $D_2$  on  
(since  $v_{D1} = +7 \text{ V}$ , this assumption is not correct)

Assume  $D_1$  on and  $D_2$  off:

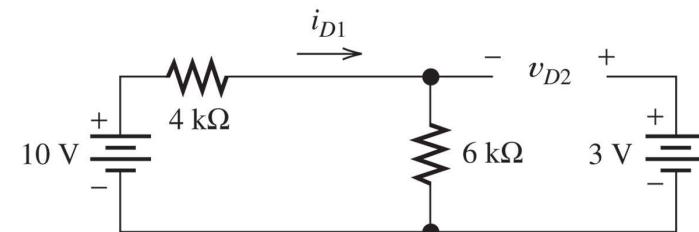



(c) Equivalent circuit assuming  $D_1$  on and  $D_2$  off  
(this is the correct assumption since  $i_{D1}$  turns out  
to be a positive value and  $v_{D2}$  turns out negative)

What about the other two states?

# Class Exercise




MACQUARIE  
University

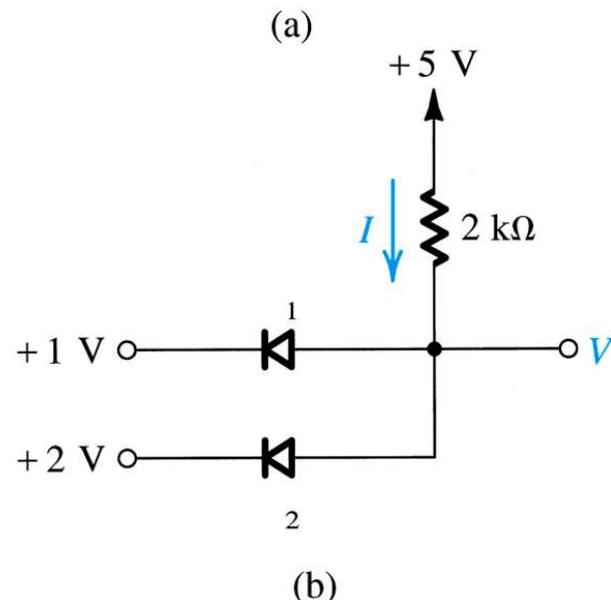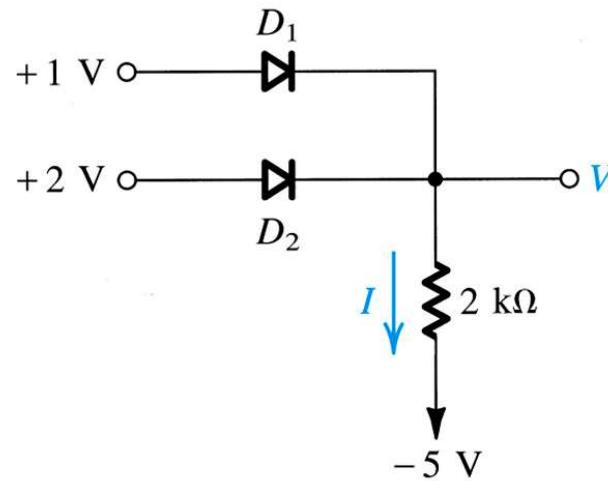

Use the ideal diode model to solve each circuit.

What are the diode states?

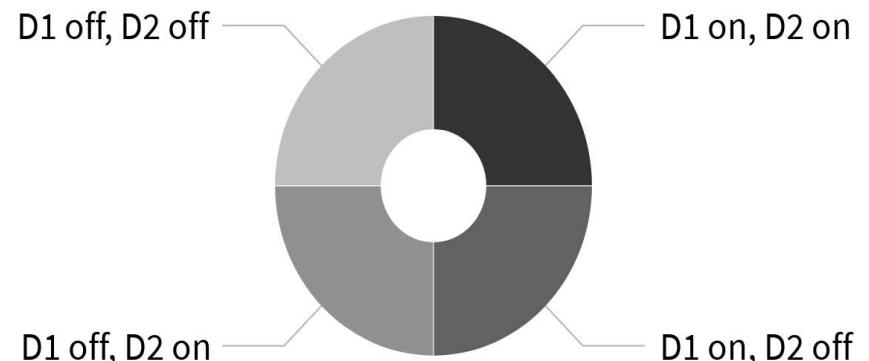D1 on, D2 on    D1 on, D2 off    D1 off, D2 on    D1 off, D2 off



Poll Everywhere Start the presentation to see live content. Still no live content? Install the app or get help at PollEv.com/app


Go to **PollEv.com/davidpayne187**  
on your mobile or laptop to vote

# Class Exercise



MACQUARIE  
University

## IDEAL MODEL

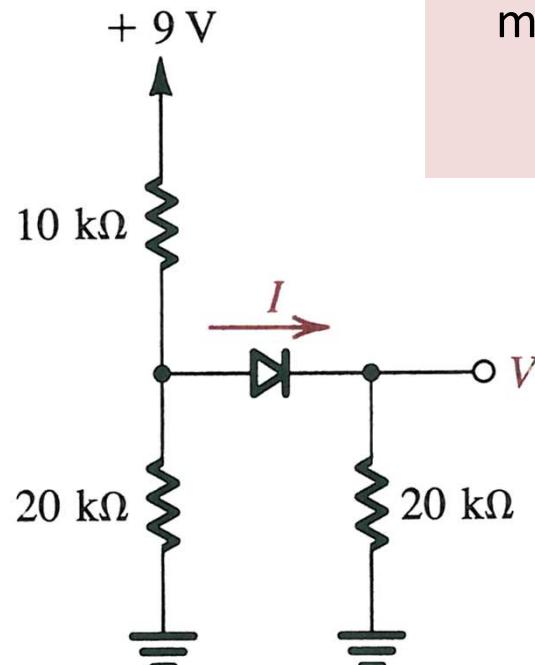


(a)

Use the ideal diode model to solve the circuit.

Hint: use Thévenin equivalents

Go to **PollEv.com/davidpayne187** on your mobile or laptop to vote

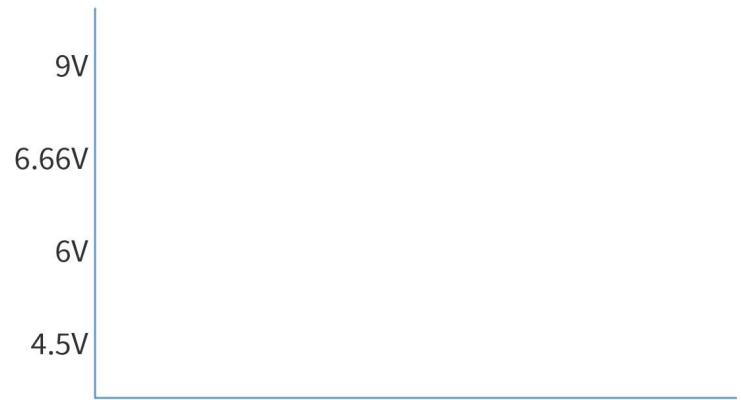What is the voltage value at the output  $V$ ?



Start the presentation to see live content. For screen share software, share the entire screen. Get help at [pollev.com/app](http://pollev.com/app)


Timer Bar  
(1 min)



# Class Exercise

## IDEAL MODEL

---

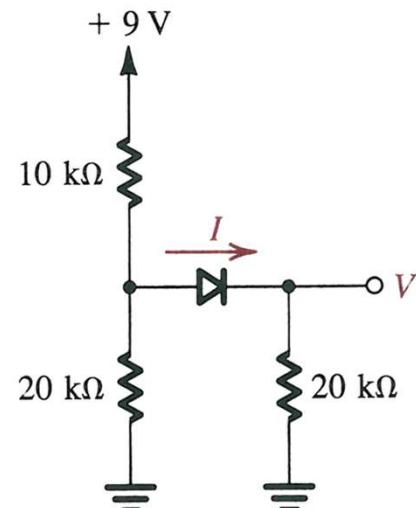

(a)


# Non-ideal Diodes




MACQUARIE  
University

In practice diode behaviour is typically more complex

Ideal Characteristics

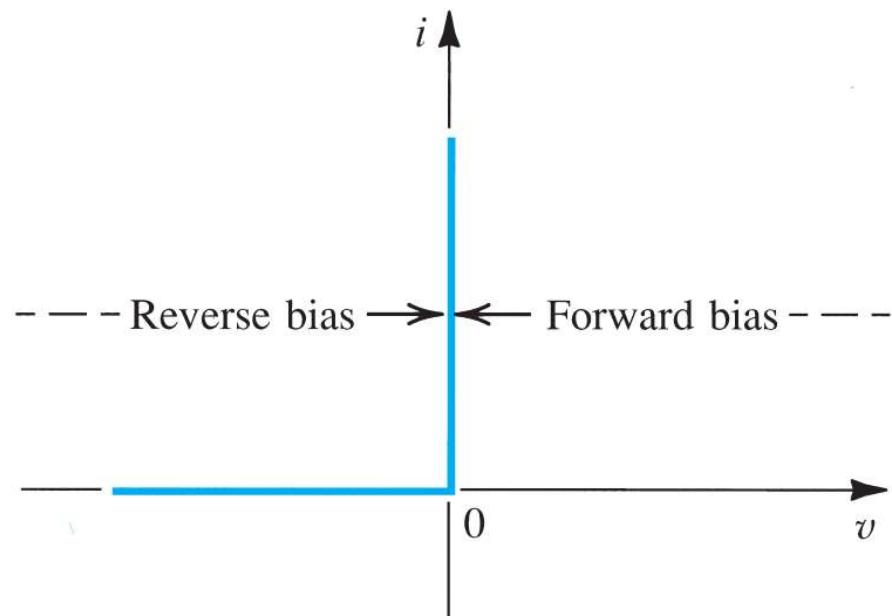

Realistic Characteristics

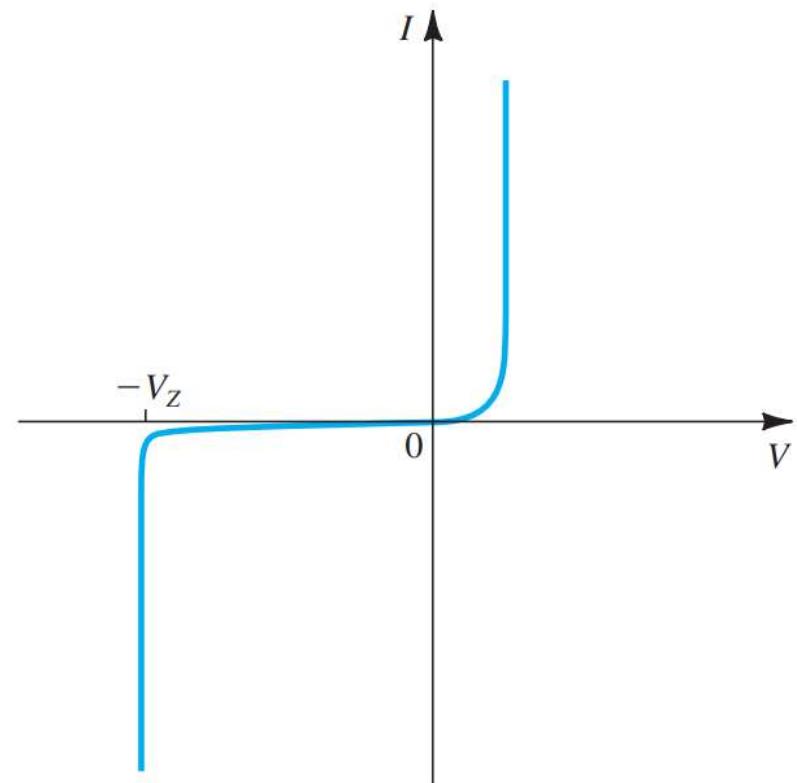

We can improve our model to  
approximate this!


# Accounting for turn on voltage



MACQUARIE  
University
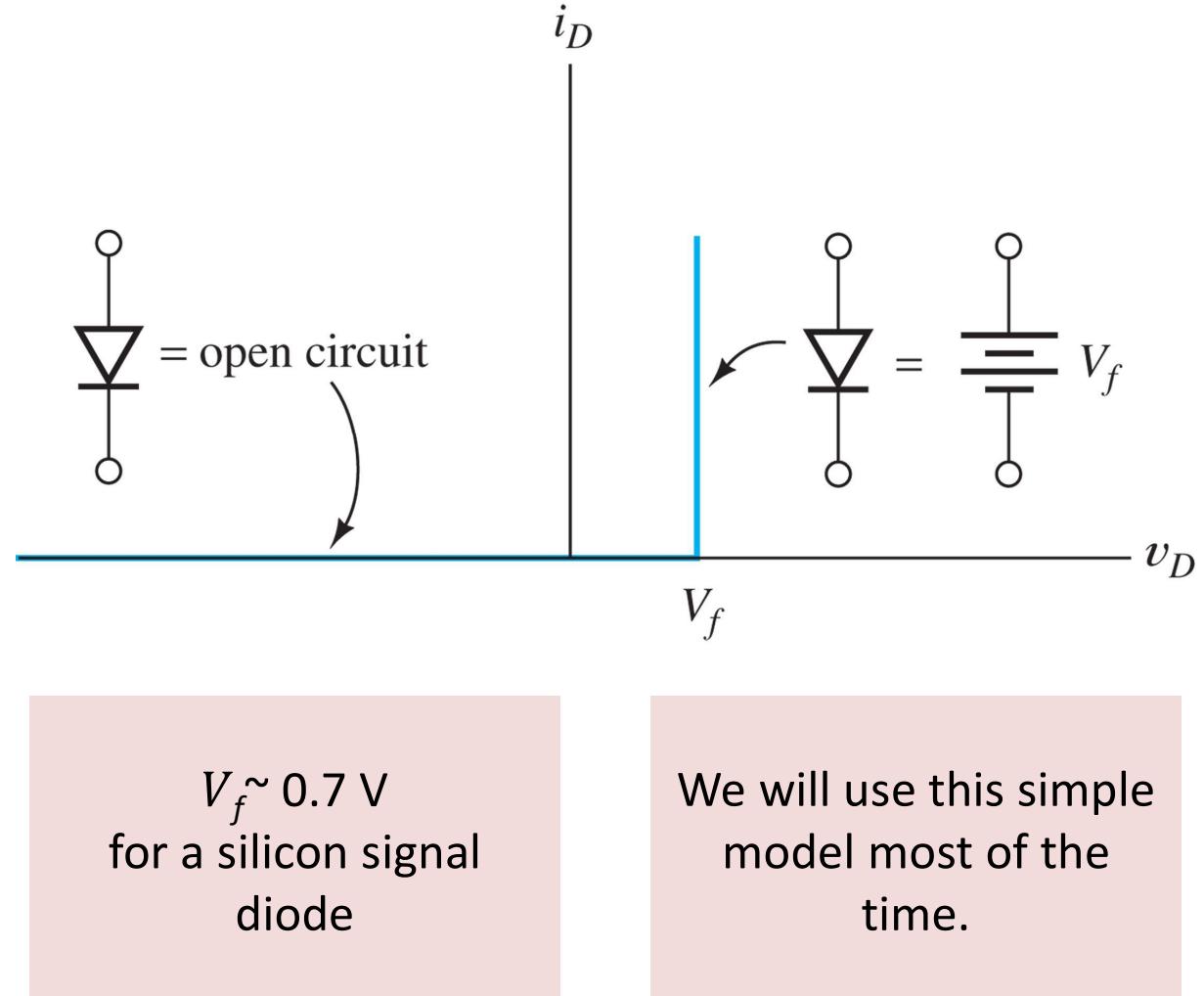
## CONSTANT VOLTAGE DROP MODEL

- A basic model that accounts for the forward turn on voltage of the diode
- Does not account for the slope, or reverse breakdown





# Example
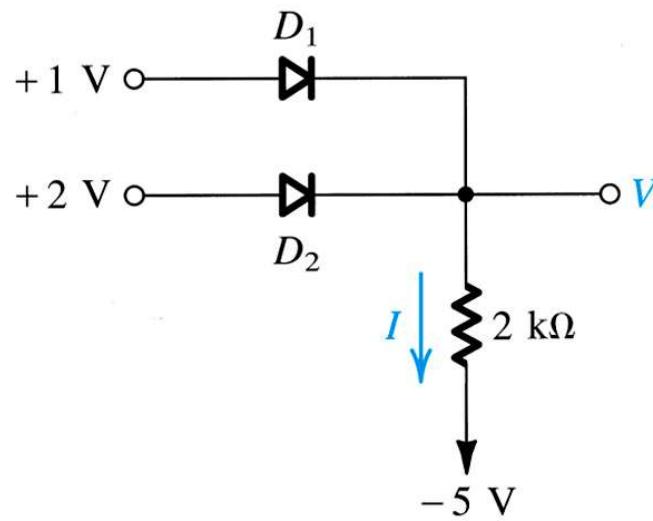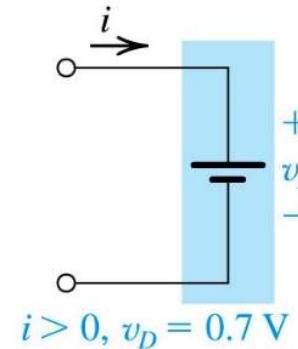
## CONSTANT VOLTAGE DROP MODEL




MACQUARIE  
University

Use the 0.7V drop  
diode model to solve  
each circuit.



(a)

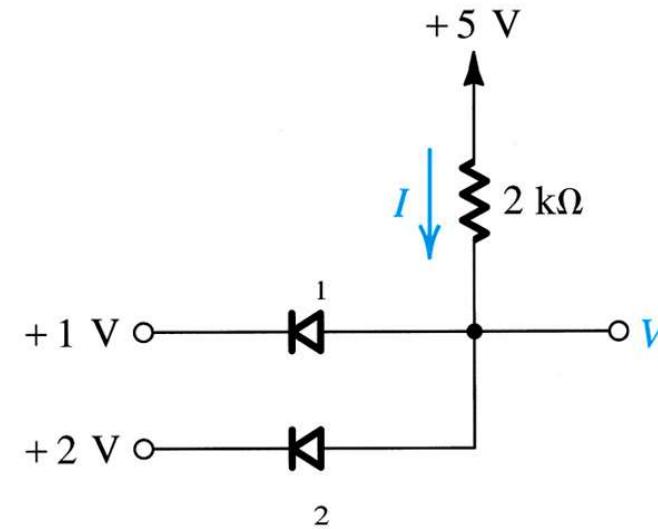


(b)

# Class Exercise

## CONSTANT VOLTAGE DROP MODEL



MACQUARIE  
University

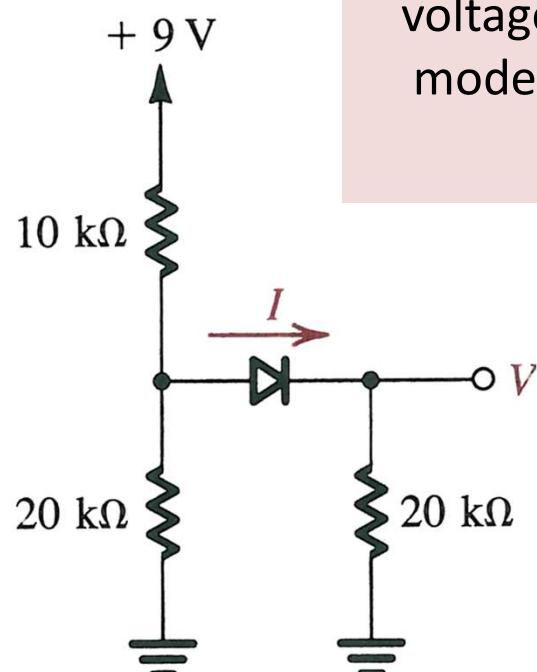

(a)

Use the constant voltage drop (0.7 V) model to solve the circuit.

Go to [PollEv.com/davidpayne187](https://PollEv.com/davidpayne187) on your mobile or laptop to vote

What is the voltage value at the output  $V$  (using 0.7 drop model)?

- 3.6V
- 4V
- 6V
- 4.5V

Start the presentation to see live content. For screen share software, share the entire screen. Get help at [polliev.com/app](https://polliev.com/app)

Timer Bar  
(1 min)




# Class Exercise

## CONSTANT VOLTAGE DROP MODEL



MACQUARIE  
University

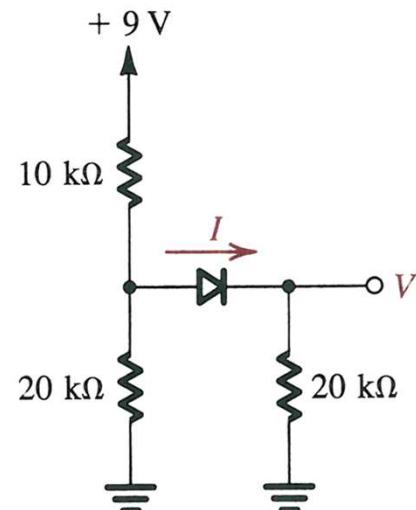

(a)

# What about the slope?


## A SIMPLE LINEAR MODEL




MACQUARIE  
University

In practice diode behaviour is typically more complex

Is this enough for  
modelling a diode?

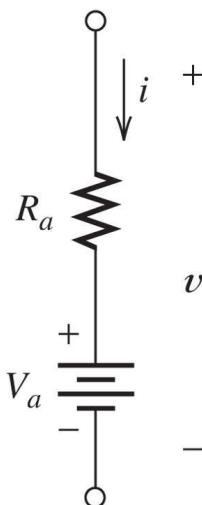

(a) Circuit diagram

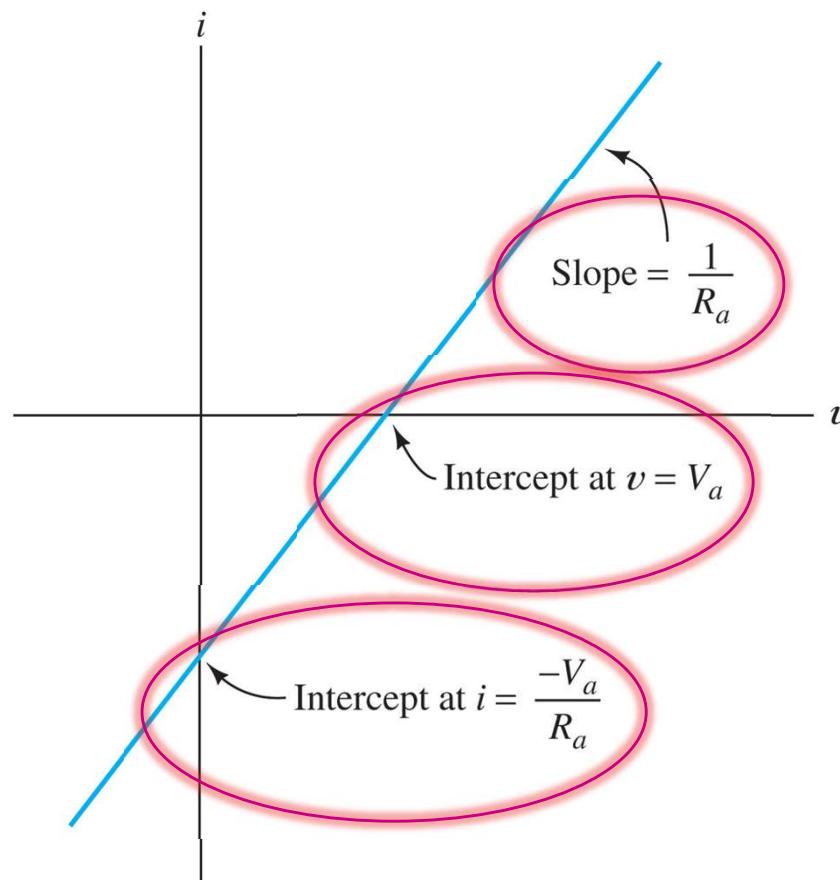

(b) Volt–ampere characteristic


What is the  
mathematical  
equation for this  
model?

# An Improved Model

A NONLINEAR BUT PIECE-WISE LINEAR MODEL



MACQUARIE  
University

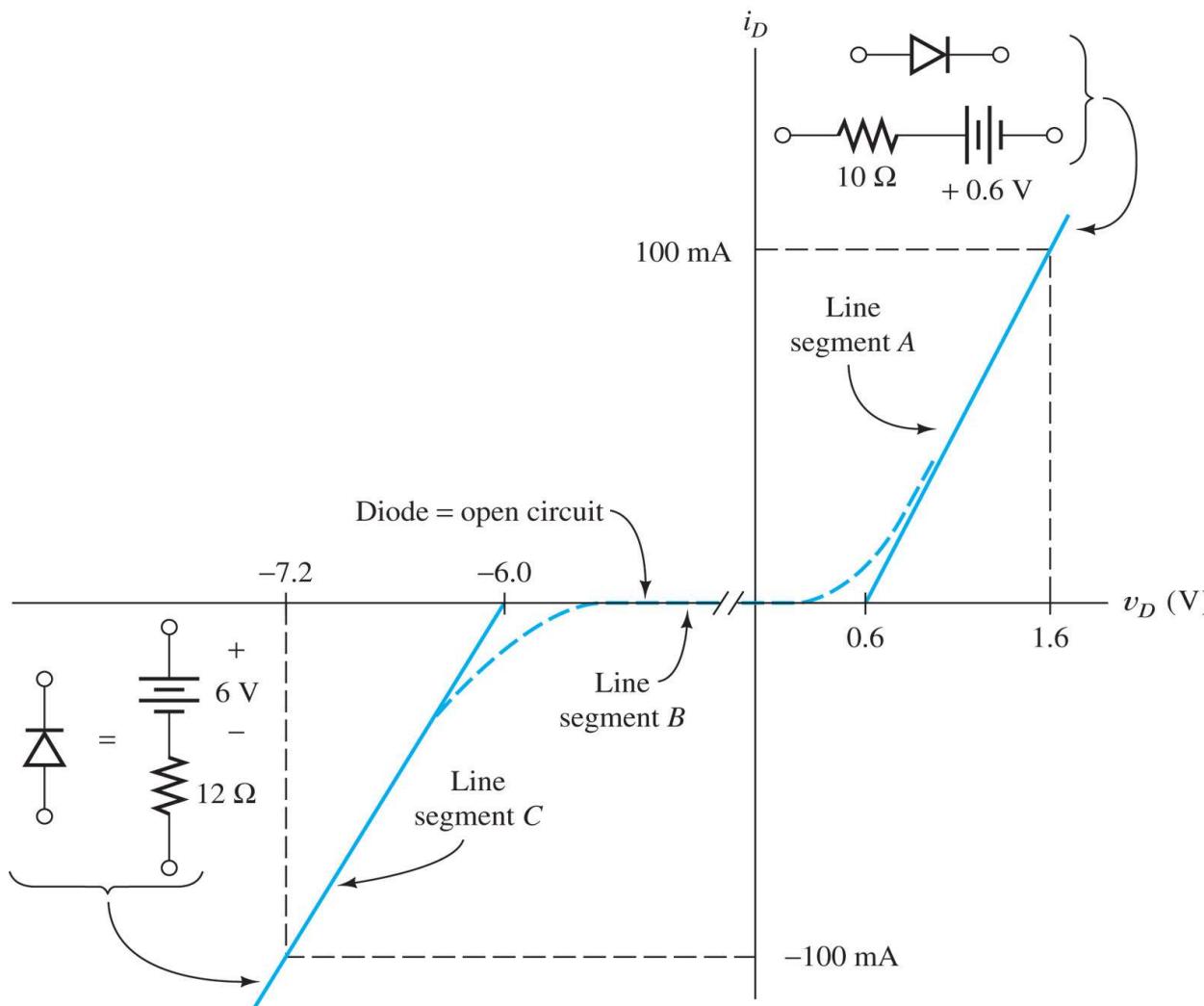


This is the graphical model.  
Good for load-line analysis.

What is the mathematical model?

# The Shockley Equation



MACQUARIE  
University

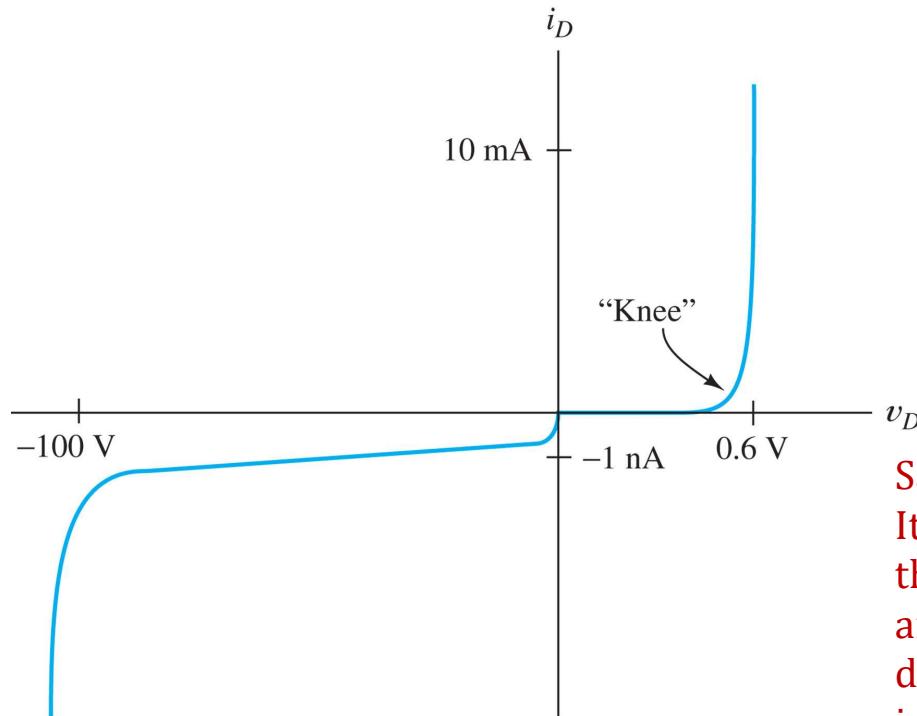

Approximate Shockley Equation  
(for forward bias more than several tenths of a volt)

$$i_D \cong I_s \exp\left(\frac{v_D}{nV_T}\right)$$

Much easier to use

Shockley Equation  
(for forward bias)

$$i_D = I_s (e^{v_D/nV_T} - 1)$$

$$i_D = I_s \left[ \exp\left(\frac{v_D}{nV_T}\right) - 1 \right]$$

Saturation current.  
Its value depends on  
the area of the diode  
and the temperature,  
doubling for each 5°  
increase for silicon  
diodes.

~ $10^{-14}$  A at 300 K

Emission  
coefficient  
(ideality factor)

$$1 < n < 2$$

$$n \approx 1$$

Thermal voltage.  
 $V_T = kT/q \approx$   
26 mV at 300 K

Temperature in K  
(273 + temp in °C)

$k = 1.38 \times 10^{-23}$  joules/kelvin Boltzmann's constant

$q = 1.60 \times 10^{-19}$  coulomb magnitude of charge of an electron


# Diode Analysis
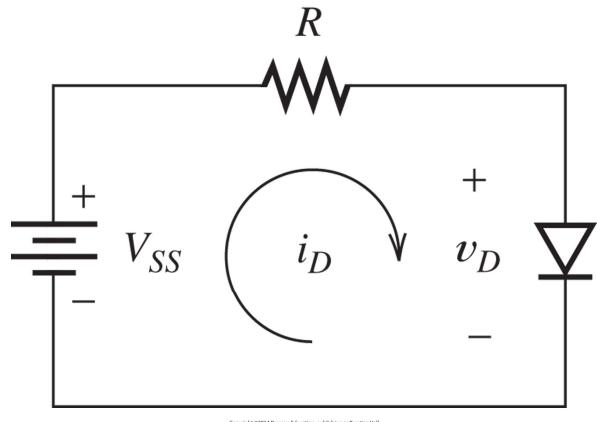
## USING THE SHOCKLEY EQUATION



MACQUARIE  
University

- We want to find the diode voltage and current (operating point)




We know the diode I-V equation:


$$i_D = I_s \left[ \exp\left(\frac{v_D}{nV_T}\right) - 1 \right] \quad (1)$$

or:  $i_D \cong I_s \exp\left(\frac{v_D}{nV_T}\right)$

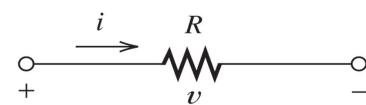There is no straightforward way to solve these two equations analytically



We know the resistor I-V equation

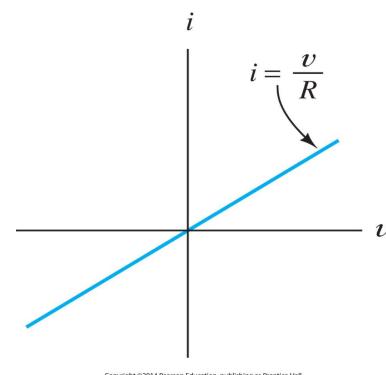

We know Kirchhoff's voltage law:

$$V_{ss} = Ri_D + v_D \quad (2)$$

Graphical method called load-line analysis can be used.



# Load Line Analysis



MACQUARIE  
University
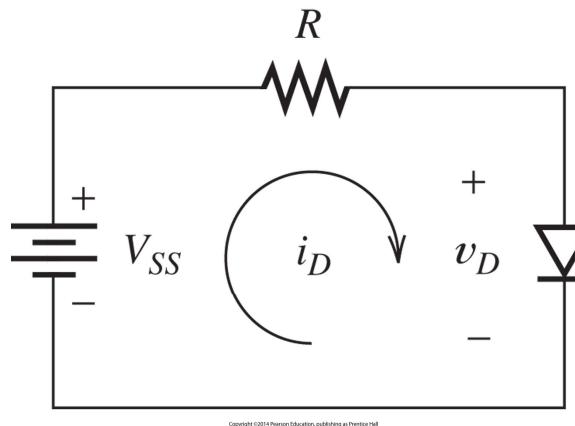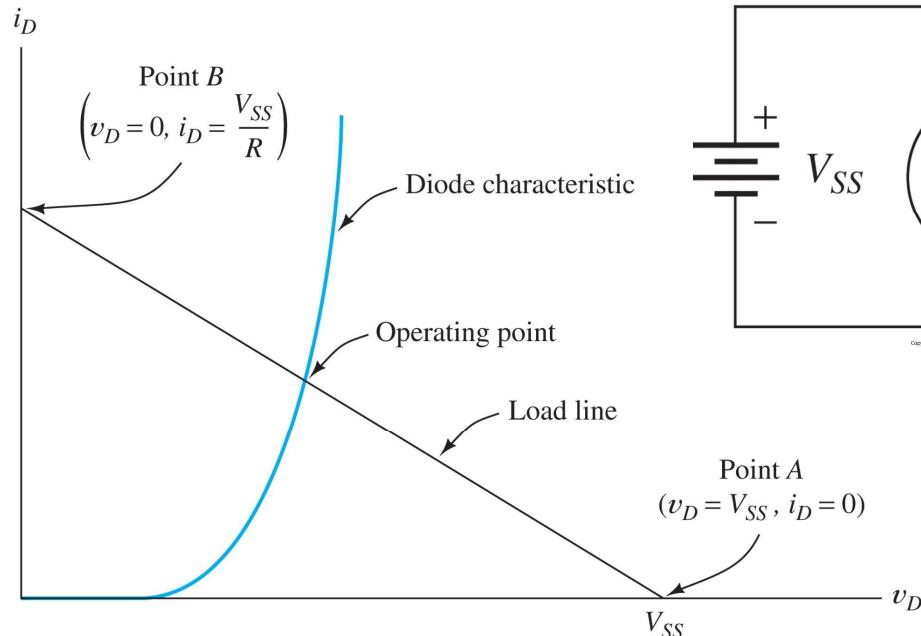
## EXAMPLE PROBLEM

See Hambley Exercise 10.1 for more details



We know the diode I-V equation:

$$i_D = I_s \left[ \exp\left(\frac{v_D}{nV_T}\right) - 1 \right] \quad (1)$$

or:  $i_D \cong I_s \exp\left(\frac{v_D}{nV_T}\right)$

We know Kirchhoff's voltage law:

$$V_{SS} = R i_D + v_D \quad (2)$$

$$i_D = \frac{V_{SS} - v_D}{R}$$

What else do we need to find the operating point?

$$V_{SS} = 2 \text{ V}$$

$$R = 1 \text{ k}\Omega$$

$$V_{DQ} \cong 0.7 \text{ V} \quad I_{DQ} \cong 1.3 \text{ mA}$$

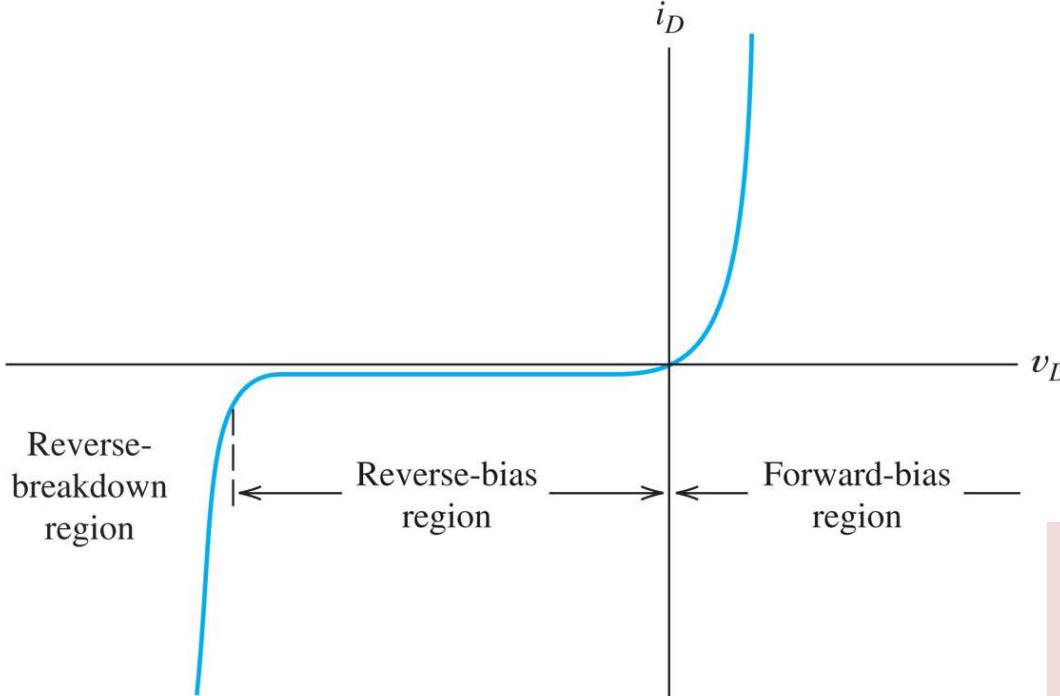
# The Zener Diode




MACQUARIE  
University



Diodes that are designed to work at the reverse breakdown region are Zener diodes.



(b) Volt–ampere characteristic

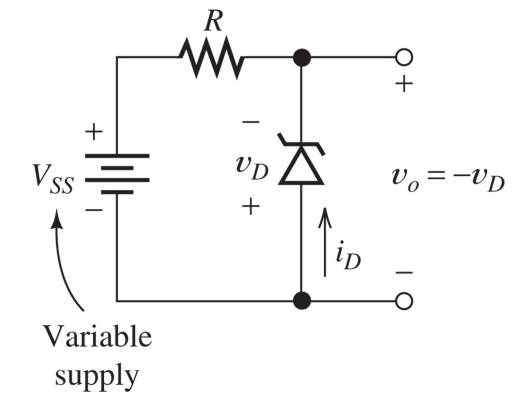

Commonly used for  
voltage regulator  
circuits – constant  
output from variable  
supply


# Zener Diode Voltage Regulator



MACQUARIE  
University
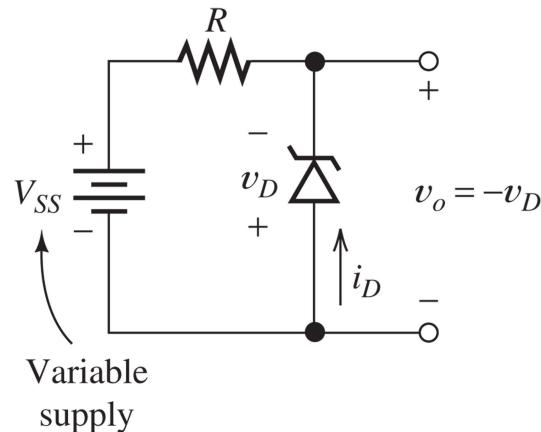
## LOAD-LINE ANALYSIS IN THE REVERSE BREAKDOWN REGION

See Hambley Exercise 10.3 for more details




5V change in the supply voltage results in only a 0.5V change in the regulated output voltage.

Actual Zener diodes can do much better than this

$V_{SS} = 15 \text{ V}$  and  $20 \text{ V}$

$R = 1 \text{ k}\Omega$

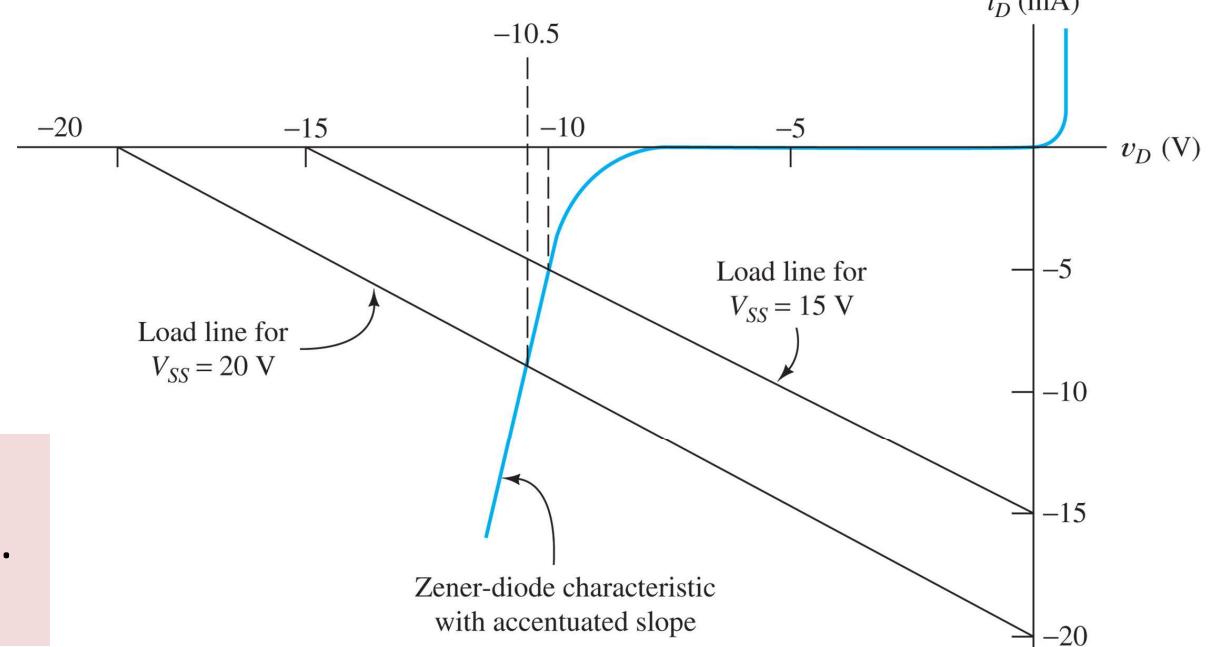
Notice the slope of the load line did not change.  
Why?



# L-L Analysis of complex circuits




MACQUARIE  
University

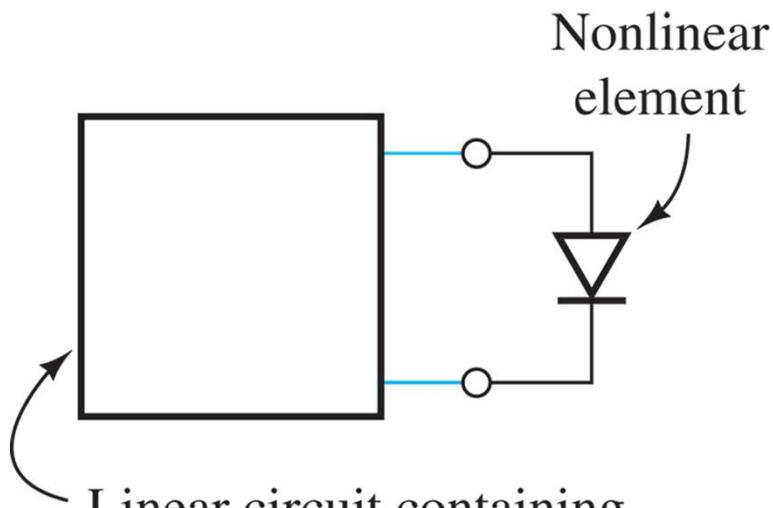

Linear circuit containing  
voltage sources, current  
sources, and resistors

(a) Original circuit

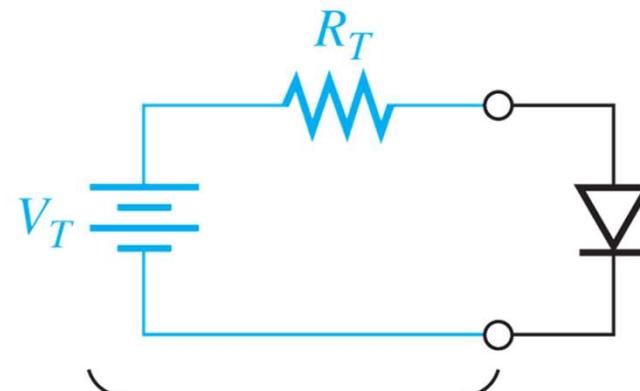

Thévenin  
equivalent  
circuit


(b) Simplified circuit
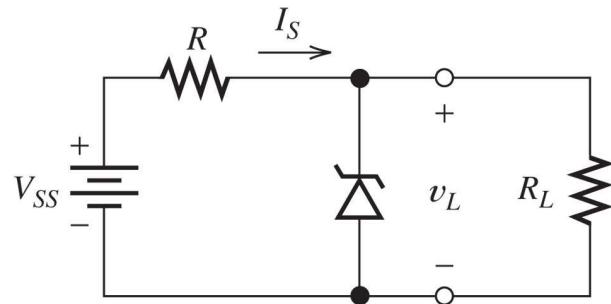
# Example




MACQUARIE  
University


See Hambley Exercise 10.4 for more details



(a) Regulator circuit with load

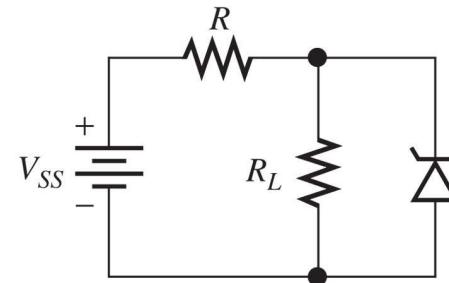

(b) Circuit of (a) redrawn

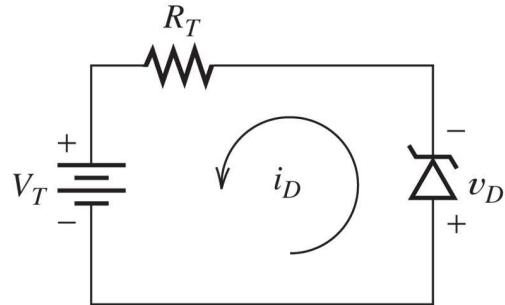


(c) Circuit with linear portion  
replaced by Thévenin equivalent

$$V_{SS} = 24 \text{ V}$$

$$R = 1.2 \text{ k}\Omega$$

$$R_L = 6 \text{ k}\Omega$$

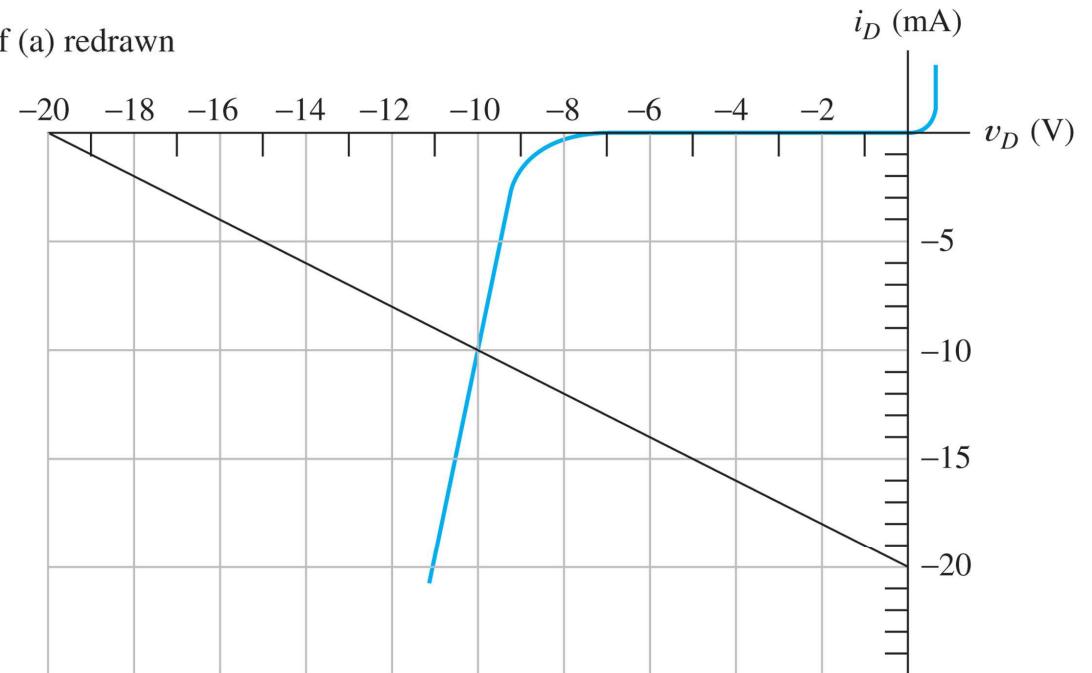Find the load  
voltage and  
source current





# Lecture 2

1. Diode Fundamentals & Models
2. **Diode Circuits & Applications**
3. Small Signal Analysis


# Logic Gates

## LOGIC GATES WITH DIODES



MACQUARIE  
University

What kind of logic gate is this?

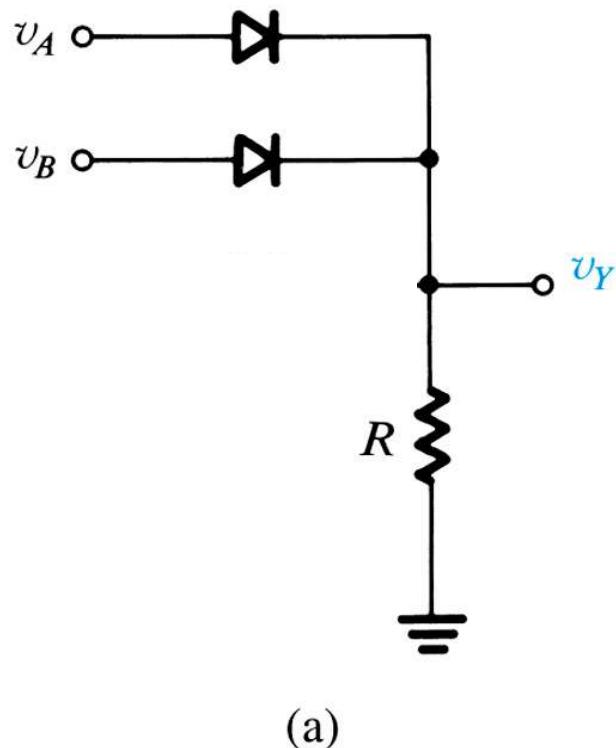

Assuming ideal diodes

$v_A$ (V)	$v_B$ (V)	$v_Y$ (V)
5	0	
0	5	
5	5	
0	0	


# Logic Gates

## LOGIC GATES WITH DIODES




MACQUARIE  
University

What kind of logic gate is this?

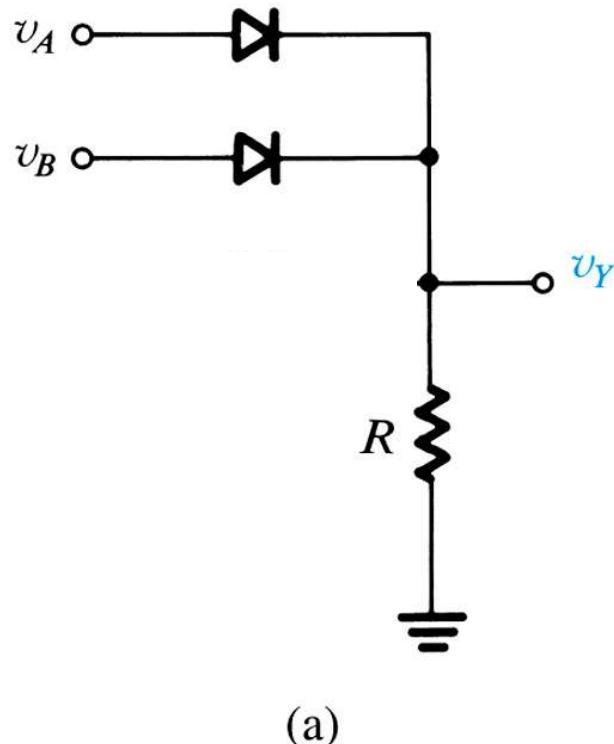

What logic gate is this?

AND    OR    NOT    XOR

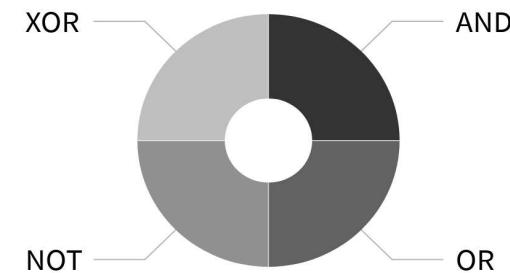

Off Everywhere Start the presentation to see live content. Still no live content? Install the app or get help at [PoliEv.com/app](https://PoliEv.com/app)

Assuming ideal diodes

$v_A$ (V)	$v_B$ (V)	$v_Y$ (V)
5	0	
0	5	
5	5	
0	0	


# Logic Gates

## LOGIC GATES WITH DIODES



MACQUARIE  
University

What kind of gate is this?

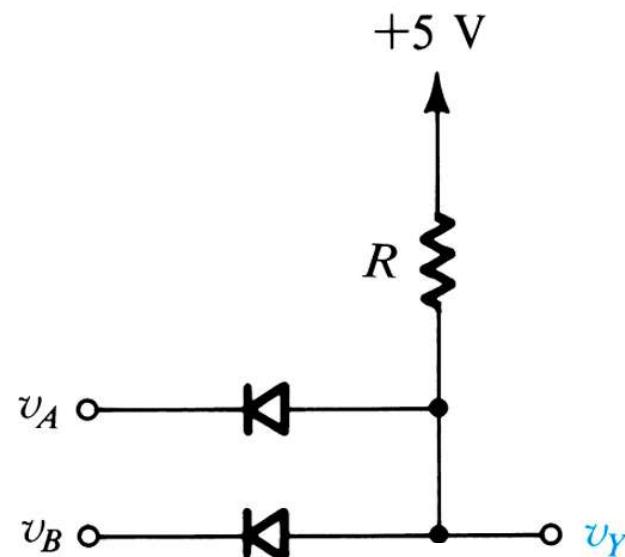

(b)

Assuming ideal diodes

$v_A$ (V)	$v_B$ (V)	$v_Y$ (V)
5	0	
0	5	
5	5	
0	0	


# Logic Gates

## LOGIC GATES WITH DIODES



MACQUARIE  
University


What kind of gate is this?

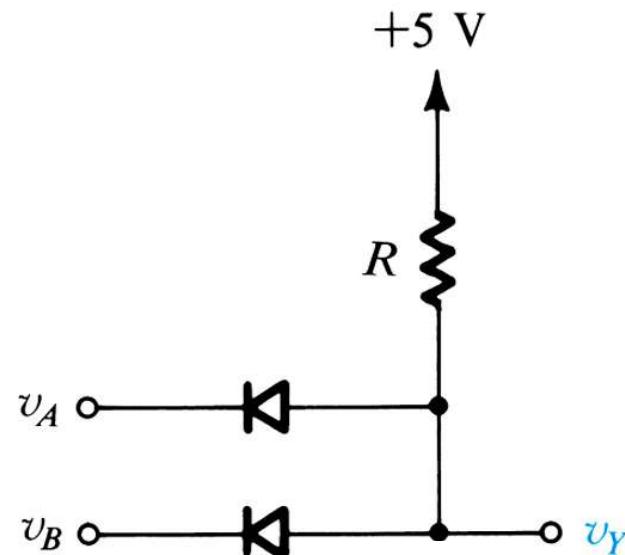

(b)

What logic function can this circuit implement?

AND    OR    NOT    XOR

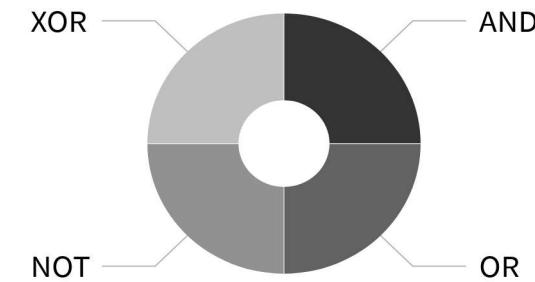

Poll Everywhere Start the presentation to see live content. Still no live content? Install the app or get help at [PollEv.com/app](https://PollEv.com/app)

Assuming ideal diodes

$v_A$ (V)	$v_B$ (V)	$v_Y$ (V)
5	0	
0	5	
5	5	
0	0	


# Rectifier Circuits




MACQUARIE  
University

## HALF-WAVE RECTIFIER


- Used to convert AC power to DC power

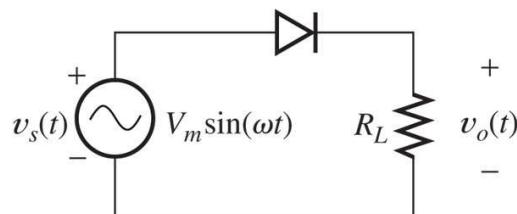

(a) Circuit diagram

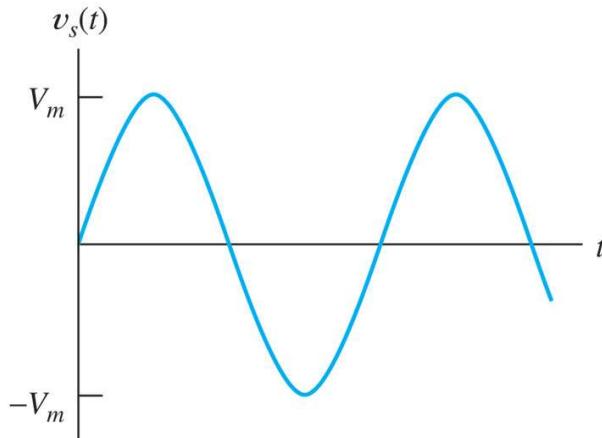


(b) Source voltage versus time

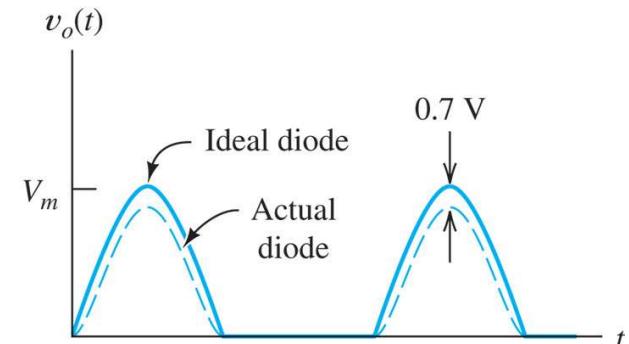

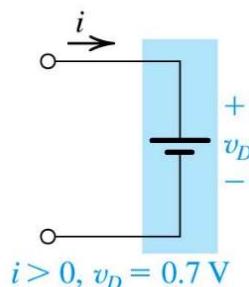(c) Load voltage versus time

Copyright ©2014 Pearson Education, publishing as Prentice Hall



We can use the 0.7V drop model or ideal diode model without losing much accuracy because voltage levels  $\gg 0.7\text{V}$


# Rectifier Circuits



MACQUARIE  
University
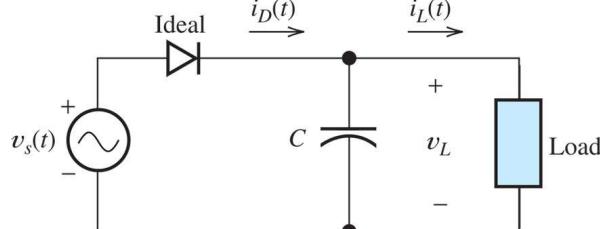
## HALF-WAVE RECTIFIER – WITH SMOOTHING

- We can add a capacitor to smoothen the output




(a) Circuit diagram

Average load  
current

$$C \cong \frac{I_L T}{V_r}$$

Period of the ac voltage

Ripple voltage

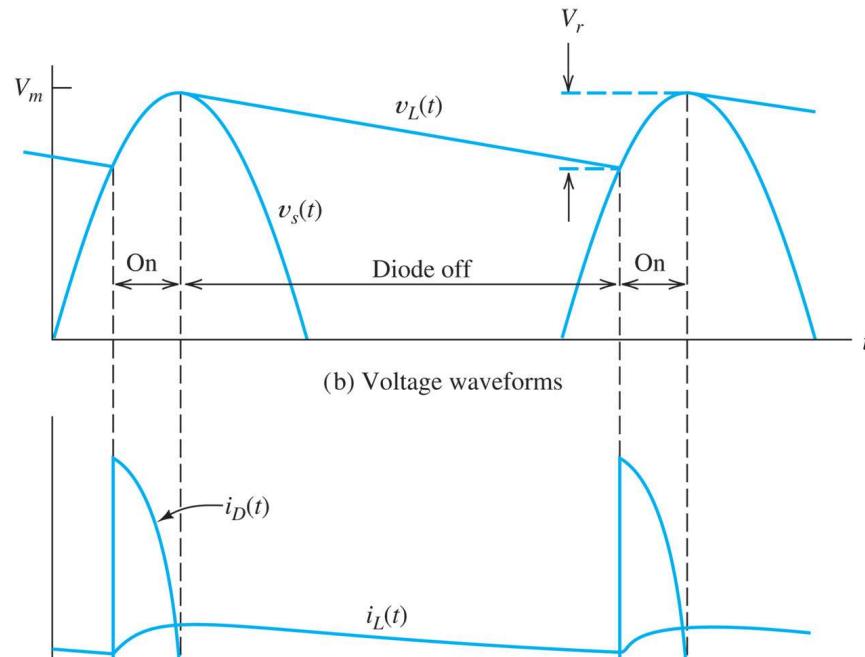

(b) Voltage waveforms

(c) Current waveforms

Chose diode to withstand  
Peak Inverse Voltage

$$\text{PIV} \cong 2V_m$$

PIV needs to be less  
than the breakdown  
voltage of the diode.


# Rectifier Circuits




MACQUARIE  
University
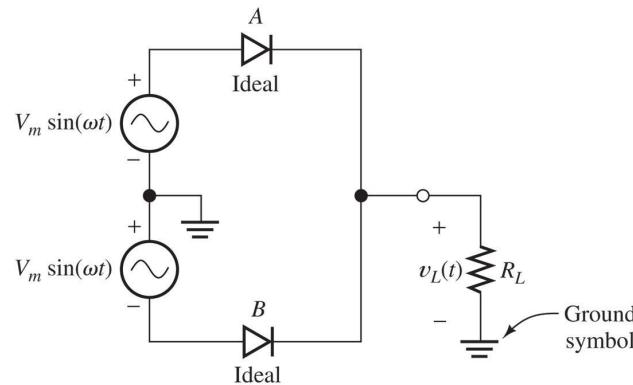
## FULL-WAVE RECTIFIER


A transformer can provide this (out-of-phase ac voltages) →



(a) Circuit diagram

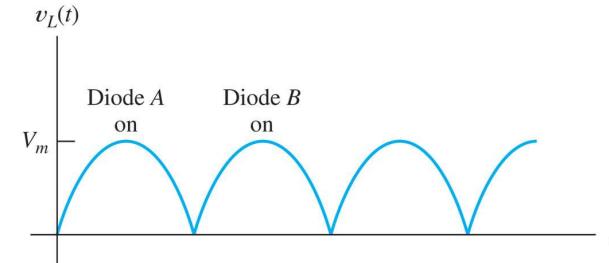

(b)

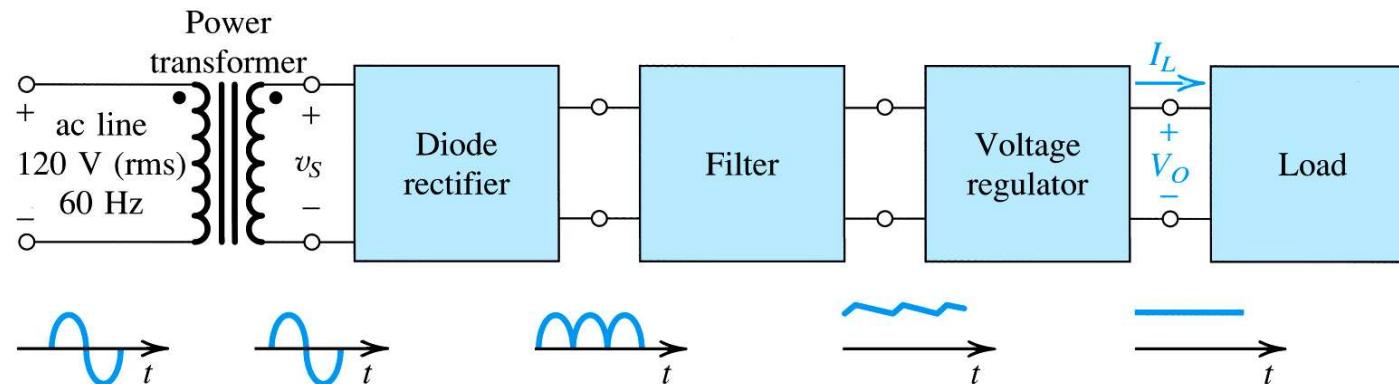

Block diagram of a dc power supply.


# Rectifier Circuits



MACQUARIE  
University

## DIODE-BRIDGE FULL-WAVE RECTIFIER

**Figure 10.28**

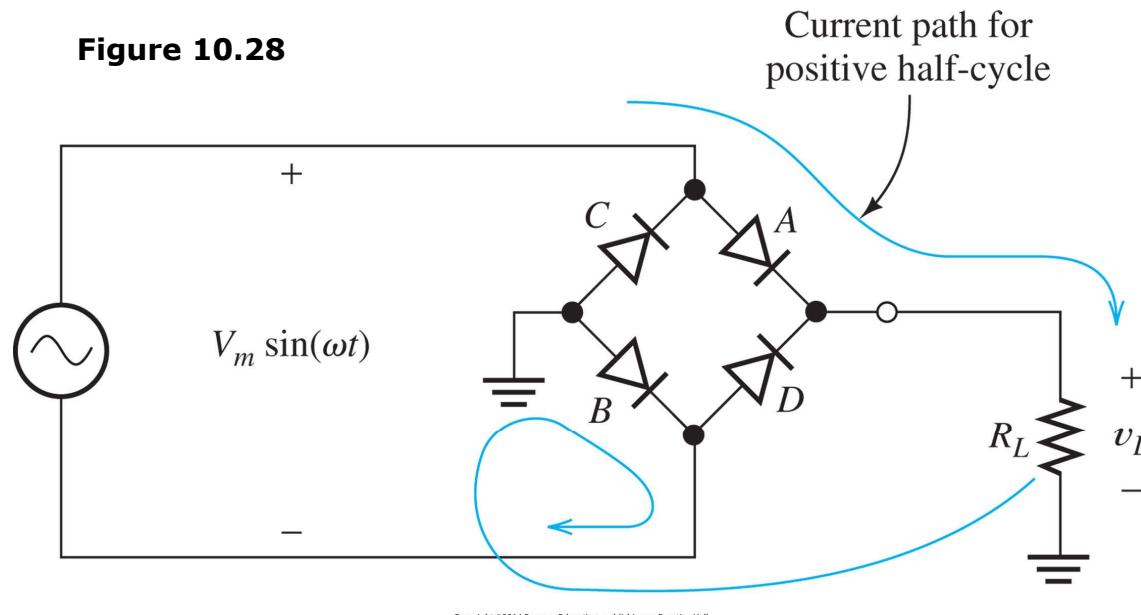



Copyright ©2014 Pearson Education, publishing as Prentice Hall

# Rectifier Circuits



MACQUARIE  
University

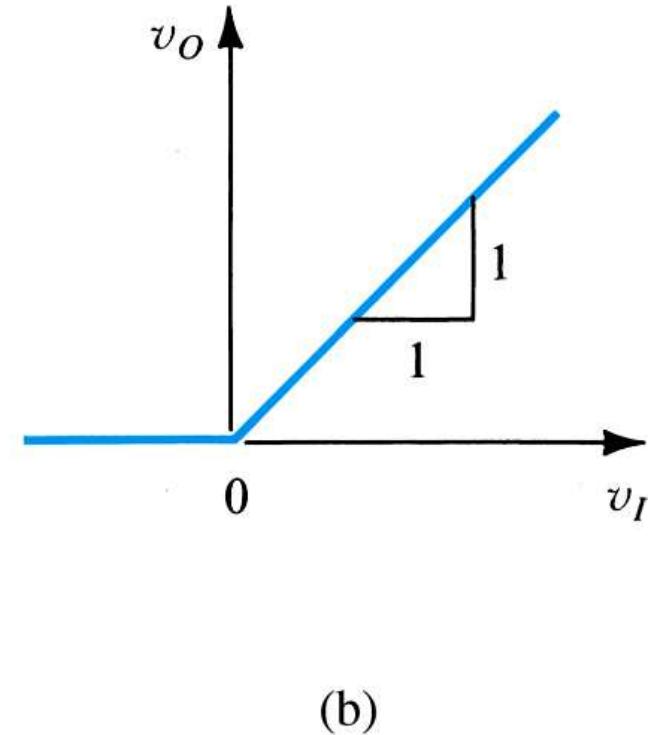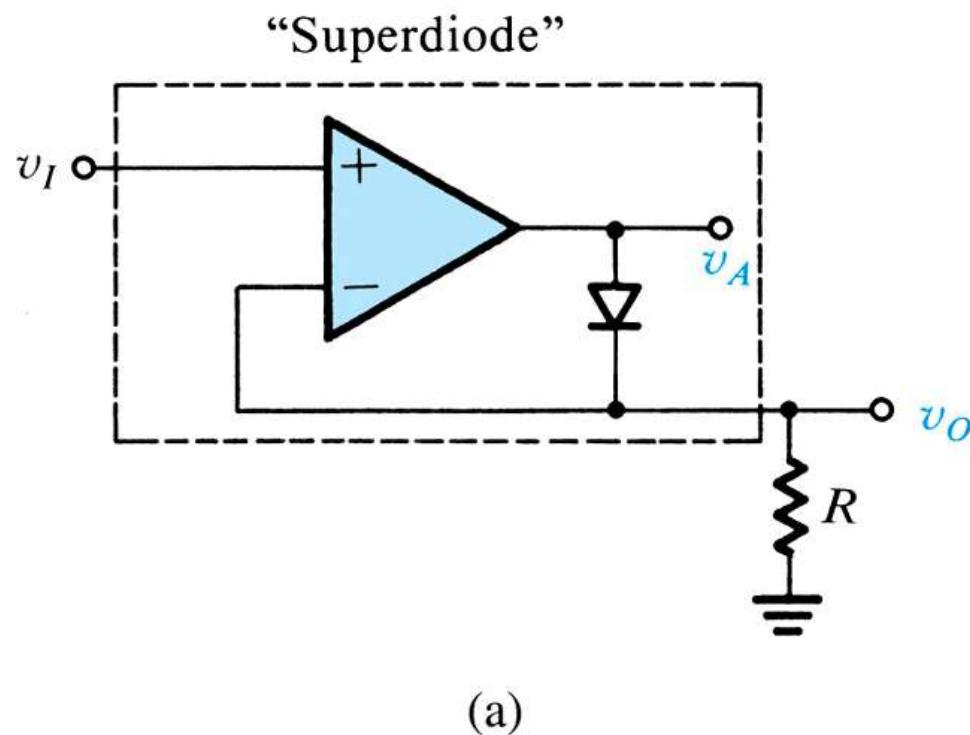
## PRECISION RECTIFIER – THE “SUPERDIODE”



# Voltage Regulator



MACQUARIE  
University

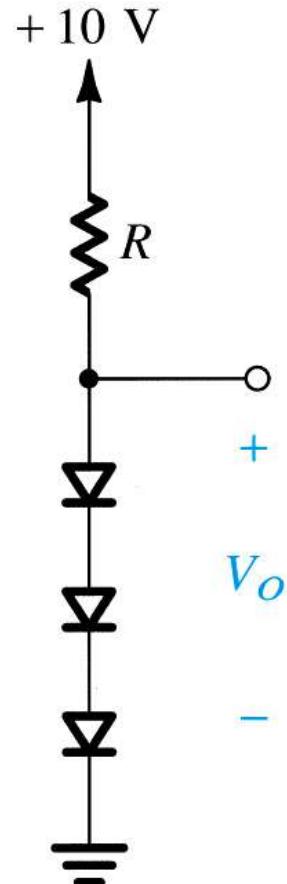

Using Si diodes (0.7V constant  
Voltage drop)

$$V_O \simeq 2.1 \text{ V}$$


# Wave Shaping Circuits




MACQUARIE  
University

## LIMITING CIRCUITS

---

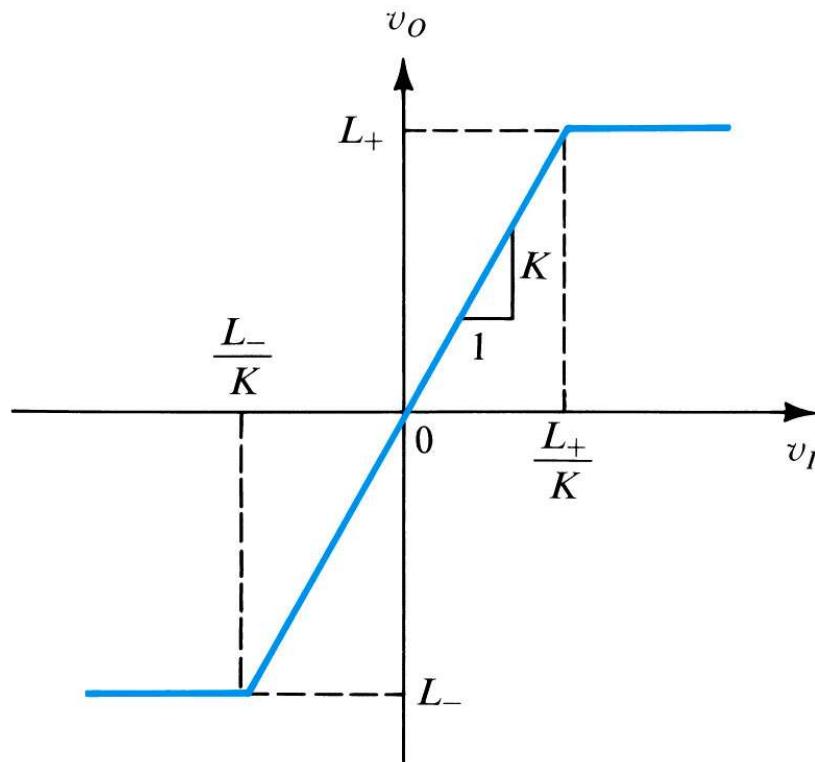

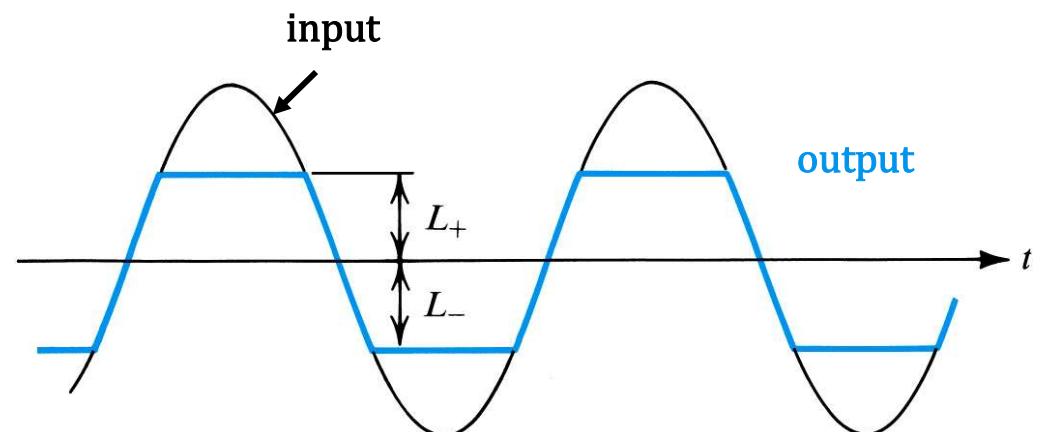Voltage transfer characteristic  
of a limiting circuit (a “limiter”)




Example: “clipped” output

# Wave Shaping Circuits

## CLIPPER CIRCUITS





MACQUARIE  
University

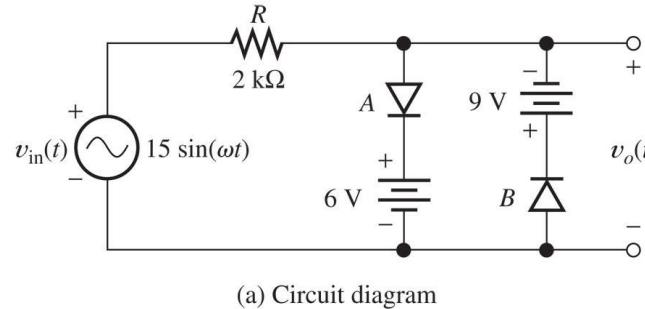

Ideal  
diodes.

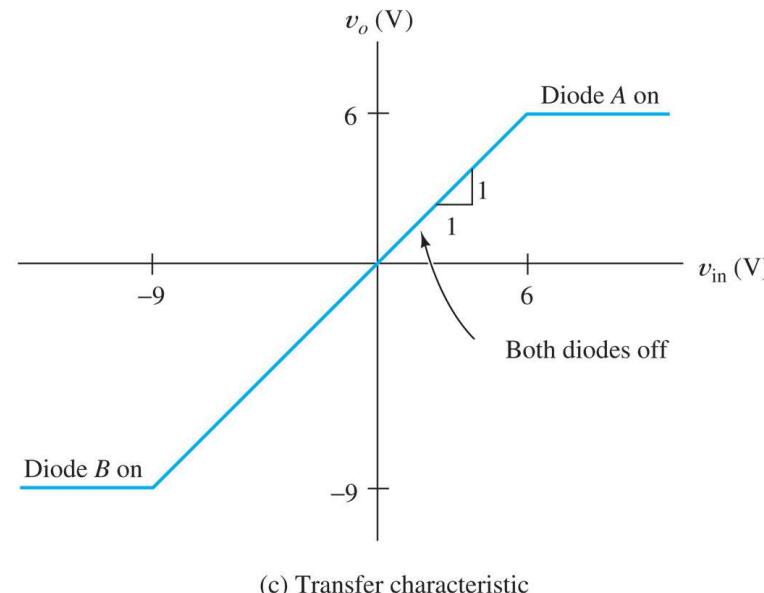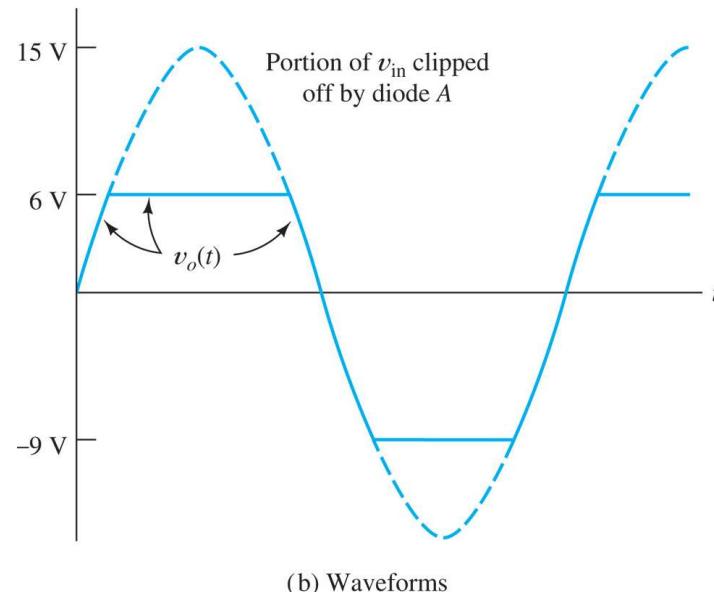You need to  
practice drawing  
these by hand!




Voltage transfer characteristic !

# Wave Shaping Circuits


## LIMITING CIRCUITS WITH DIODES



MACQUARIE  
University

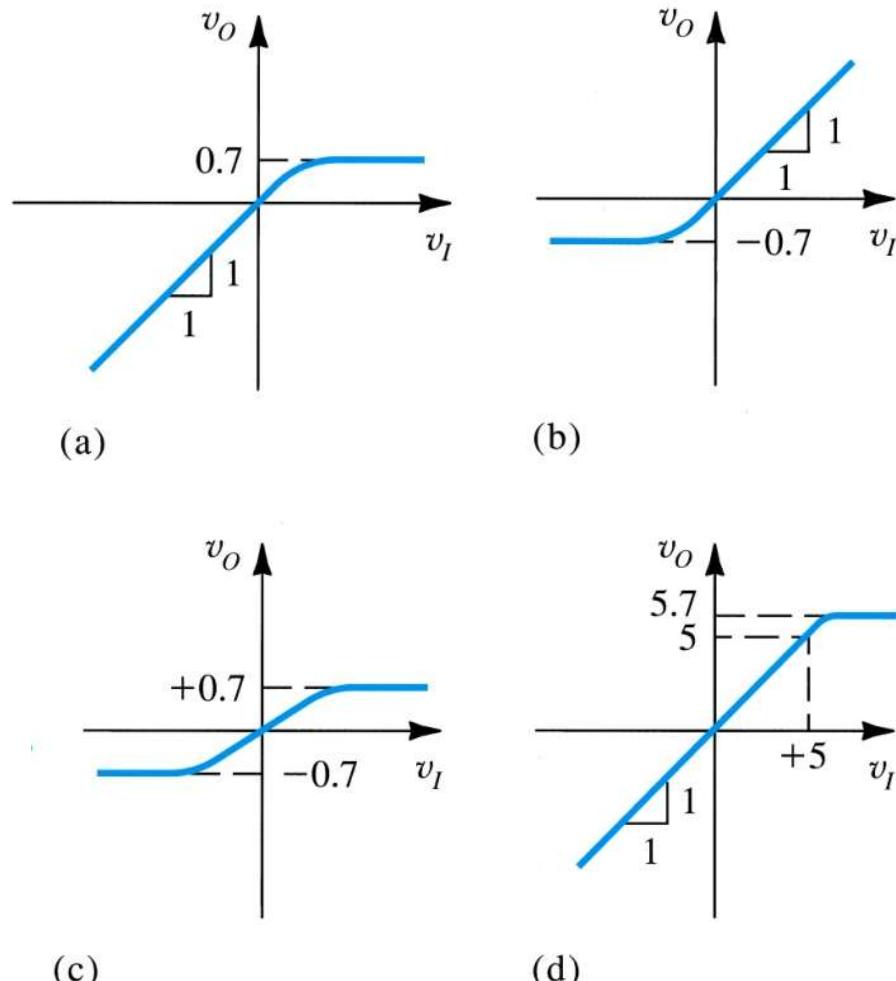

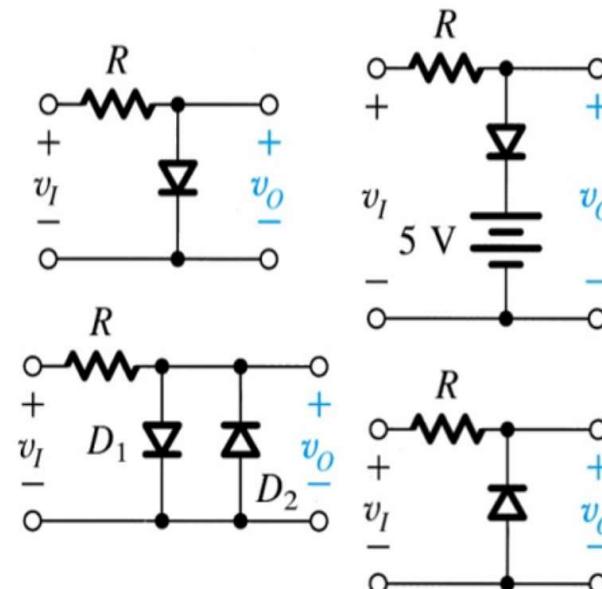Which circuit will give the shown transfer characteristic?



Poll Everywhere

Start the presentation to see live content. Still no live content? Install the app or get help at [PollEv.com/app](https://PollEv.com/app)



# Lecture 2

1. Diode Fundamentals & Models
2. Diode Circuits & Applications
3. **Small Signal Analysis**


# Diode Analysis – Small Signals



MACQUARIE  
University
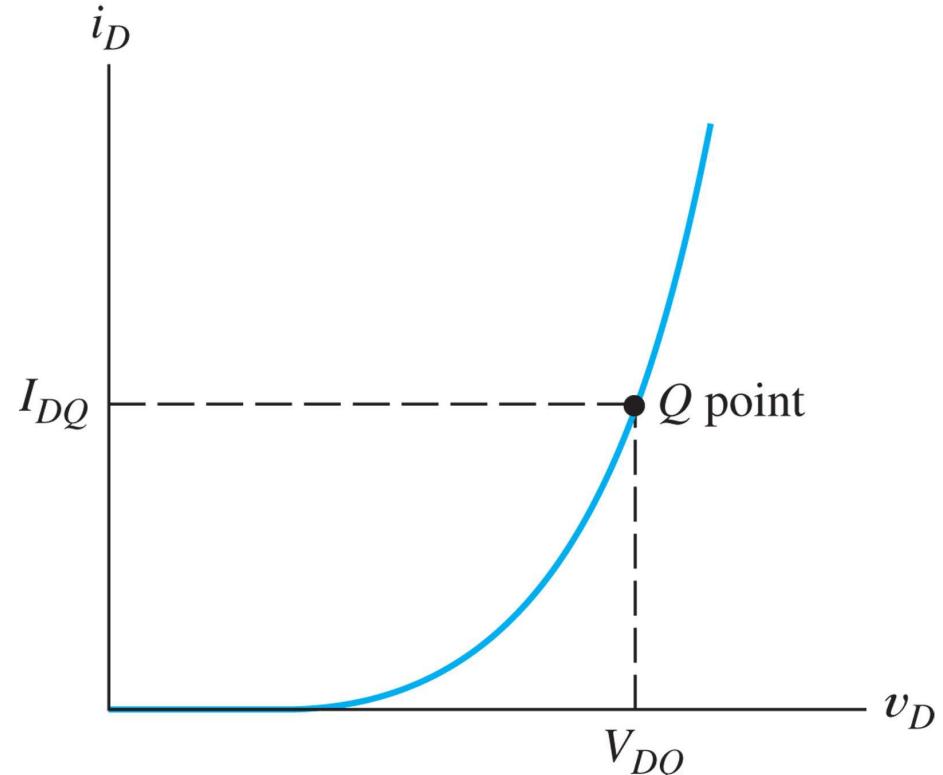
## STEADY STATE AC ANALYSIS

- So far we analysed the diode circuits in the time domain
- We calculated and plotted instantaneous voltages and currents
- We applied dc voltages (or currents) to the diodes and found the operating points (Q point)
- Q stands for quiescent (i.e. quiet or no- signal point)




If the Q point is known (using the nonlinear diode characteristic), the linear ac analysis method can be applied to find the response to small (ac) signals.

# Diode Analysis – Small Signals



MACQUARIE  
University

## CURRENT AND VOLTAGE NOTATION

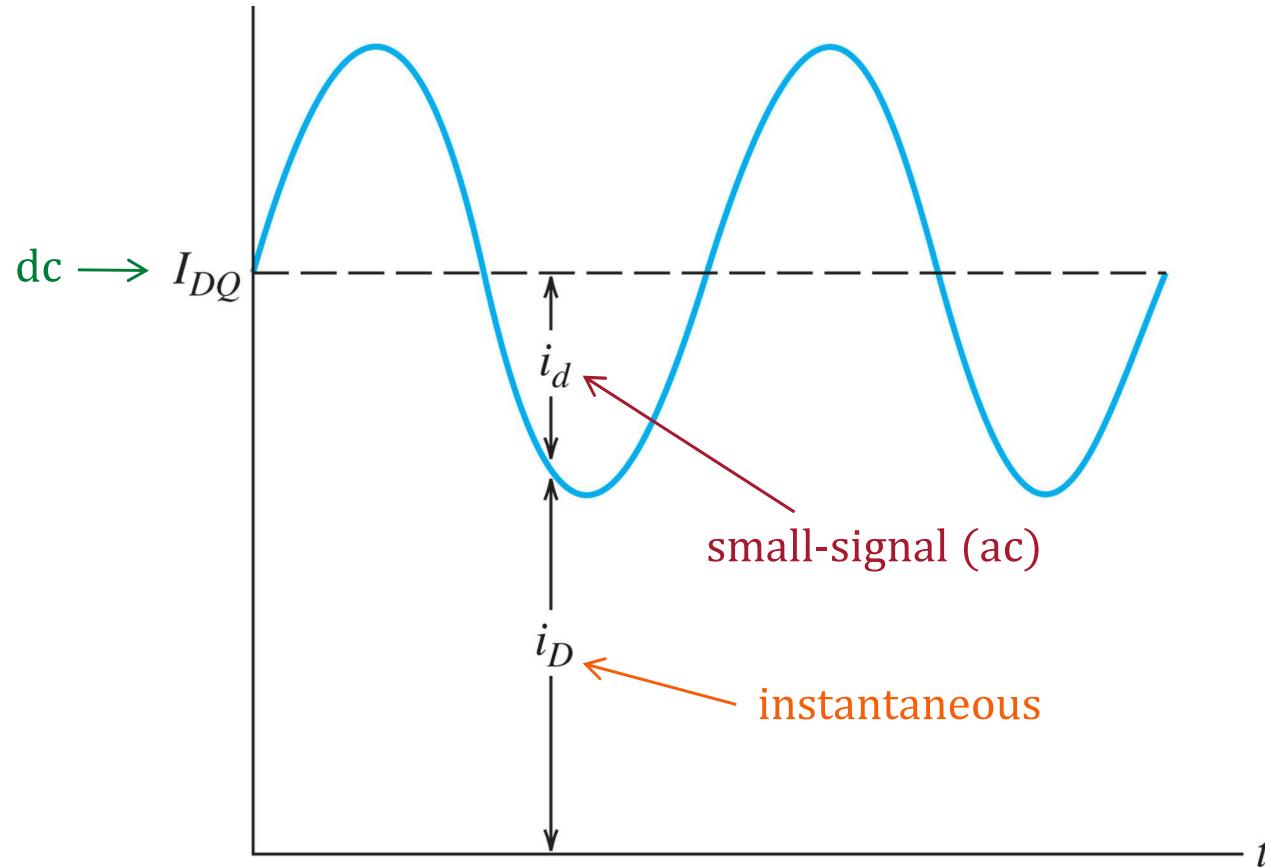

$$i_D(t) = I_{DQ} + i_d(t)$$


$$i_d(t) = I_d \cos(2\pi ft - 90^\circ)$$

# Diode Analysis – Small Signals



MACQUARIE  
University

## SMALL SIGNAL DIODE MODEL

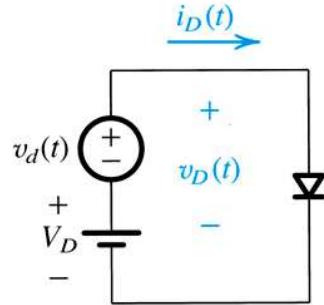

dc      small-signal (ac)

$$v_D(t) = V_D + v_d(t)$$

$$i_D(t) = I_D + i_d(t)$$

The exponential diode characteristic in the forward region:

$$i_D = I_S e^{v_D/nV_T} = I_S e^{(V_D+v_d)/nV_T} = I_S e^{V_D/nV_T} e^{v_d/nV_T}$$

$$i_D = I_D e^{v_d/nV_T}$$


$$\underbrace{I_S e^{V_D/nV_T}}_{I_D}$$

Taylor series approximation:  $e^x \cong 1+x$ , with  $x \ll 1$

$$\text{if } \frac{v_d}{nV_T} \ll 1 \rightarrow i_D \cong I_D \left( 1 + \frac{v_d}{nV_T} \right) = I_D + \frac{I_D}{nV_T} v_d = I_D + i_d$$

$$\text{So ..... } i_d = \frac{I_D}{nV_T} v_d$$
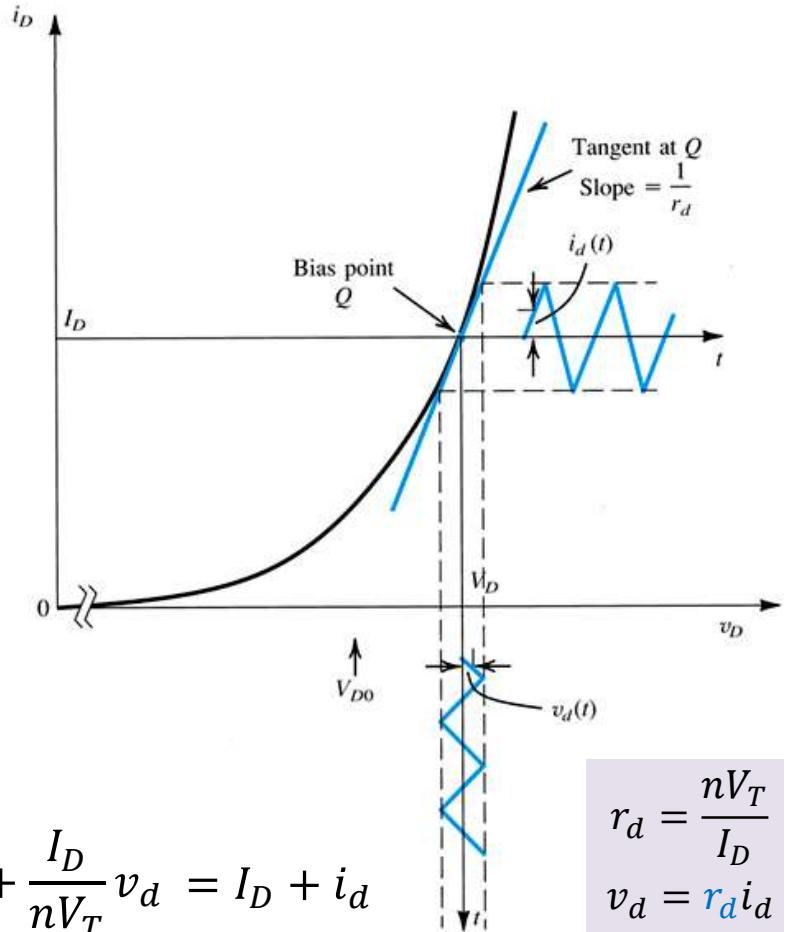
$$i_d = \frac{v_d}{r_d} \quad \text{Linear!}$$



$$r_d = \frac{nV_T}{I_D}$$

$$v_d = r_d i_d$$

$\uparrow$   
dynamic  
resistance

# Diode Analysis – Small Signals



MACQUARIE  
University

## EXAMPLE 1

---

Calculate the **dynamic resistance** of a junction diode having  $n = 1$  at a temperature of 300 K for  $I_{DQ} = 0.1 \text{ mA}$   $1 \text{ mA}$   $10 \text{ mA}$

Does the dynamic resistance increase or decrease as the current increases?

Increases



Decreases




# Diode Analysis – Small Signals




MACQUARIE  
University
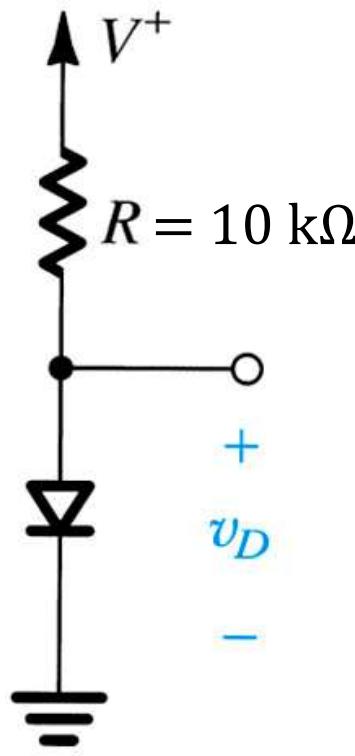
## EXAMPLE 2 – VOLTAGE REGULATOR


The power supply of the circuit below has a dc value of +10V and a ripple of 1V. Calculate the dc voltage of the diode and its variation caused by the power supply ripple. Assume the diode to have 0.7V drop at 1 mA current and  $n = 1$ .



**Step 1: find the DC operating point**

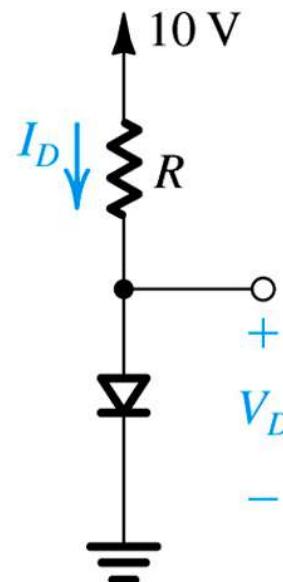

**Step 2: calculate  $r_d$**

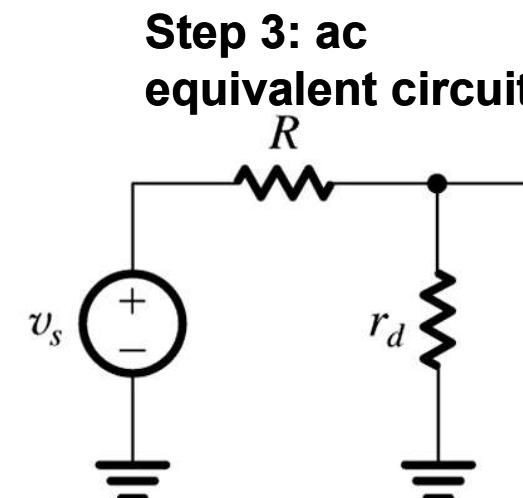

# Preparation for Lab 1



## LTSPICE AND ANALOG DISCOVERY 2

---

### Preparation before the lab:

- The worksheet has been available for several days now
- Do at least the pre-lab section before coming to the timetabled support session
- Record your worksheet answers in a digital logbook and upload individual answers to the iLearn submission before 11:55pm on Tuesday