




MACQUARIE
University

ELEC2005

Electrical and Electronic Systems

DIODES

DAVID PAYNE

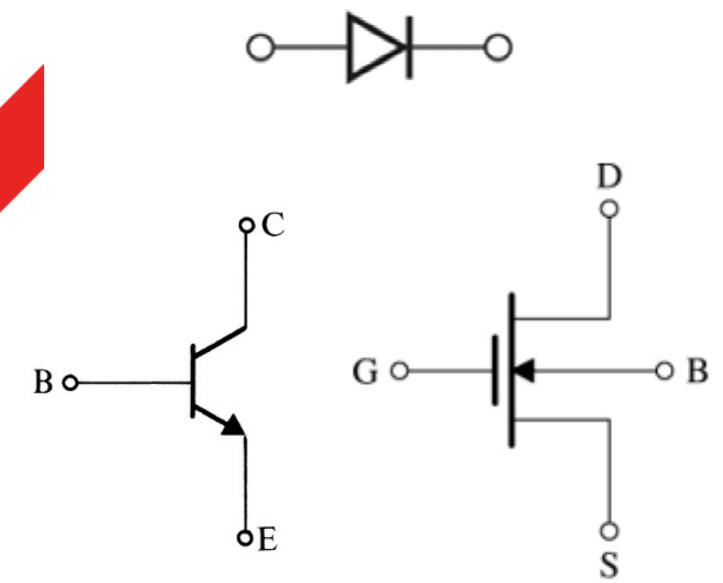

Goals of this lecture




- Understand what nonlinearity means
- Understand how we can use nonlinearity
- Be familiar with Diodes and their non-linear characteristics
- Analyse basic diode circuits
- Be able to use models for analysing diode circuits
- Understand diode applications: rectifiers and wave-shaping circuits
- Small signal analysis

Intro to Nonlinear Devices


WHAT IS A NONLINEAR DEVICE/CIRCUIT?

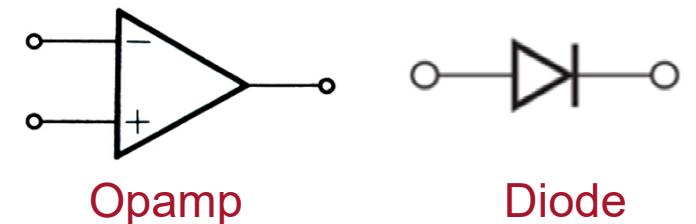- Many systems/subsystems involve complex nonlinear circuits with multiple nonlinear devices
- Four of the most common nonlinear devices are shown here, diodes and transistors and the circuits constructed with them are the focus of part 1 of this unit
- For each of these, the relationship between their output and input characteristics is not linear



Opamp

Diode

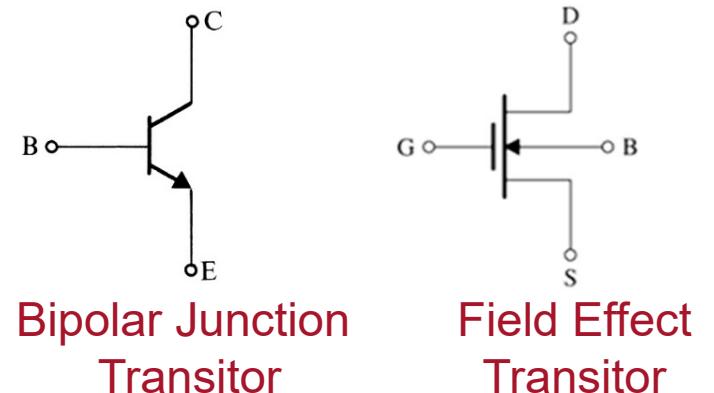



Bipolar Junction
Transistor

Field Effect
Transistor

Intro to Nonlinear Devices

WHAT IS A NONLINEAR DEVICE/CIRCUIT?

- Devices such as *ideal* resistors, capacitors and inductors have a output characteristics that are a linear function of input.
- Diodes and transistors have a more complex relationship between input and output
 - Though they have regions of linearity

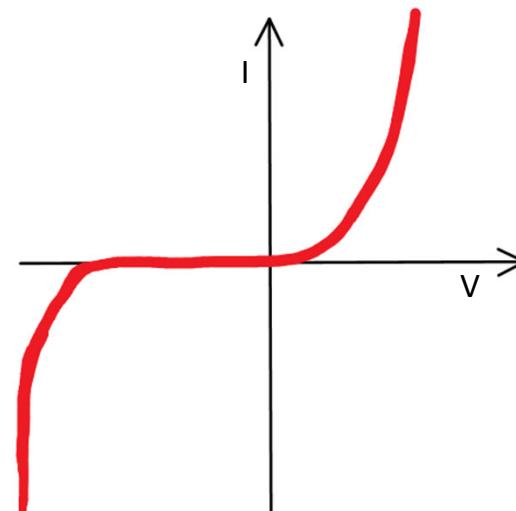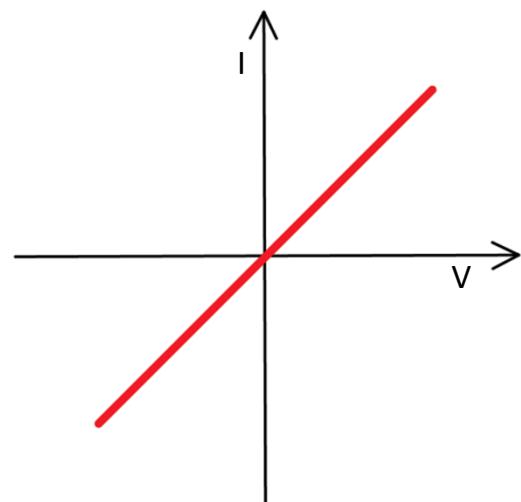




Lecture 2

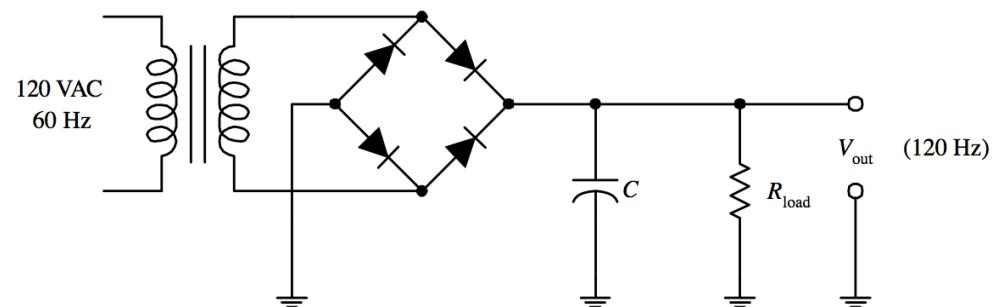1. Diode Fundamentals & Models
2. Diode Circuits & Applications
3. Small Signal Analysis

Diodes: What is a diode?

- An two terminal device with non-linear IV characteristics
- Exhibits asymmetric conductance - primarily conducts current in one direction
- Fabricated using a semiconductor with a p-n junction (more on this later)
- They have many applications, including:
 - ❖ Power conversion
 - ❖ Over-voltage protection
 - ❖ Detectors
 - ❖ Signal Generation




A little bit of history....

- Originally known as rectifiers and were developed as radio receiver detectors in the early 1900s (vacuum-tubes and semiconductors versions simultaneously developed)
- The Thermionic diode (Vacuum tube) effect was first discovered as far back as 1873, by Frederick Guthrie
- The effect was first discovered in a semiconductor in 1874 by Ferdinand Braun
- The term diode was first coined in 1919, from it's Greek roots, it means two (di) paths (ode)



Frederick Guthrie

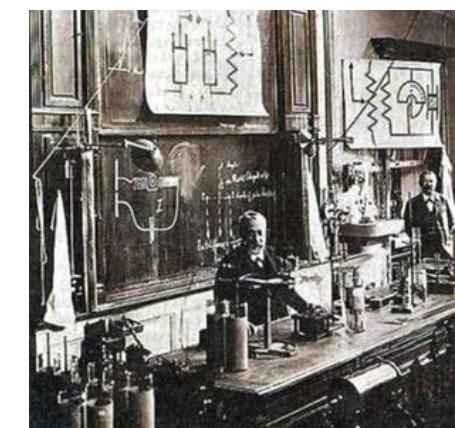


Ferdinand Braun

Types of diode




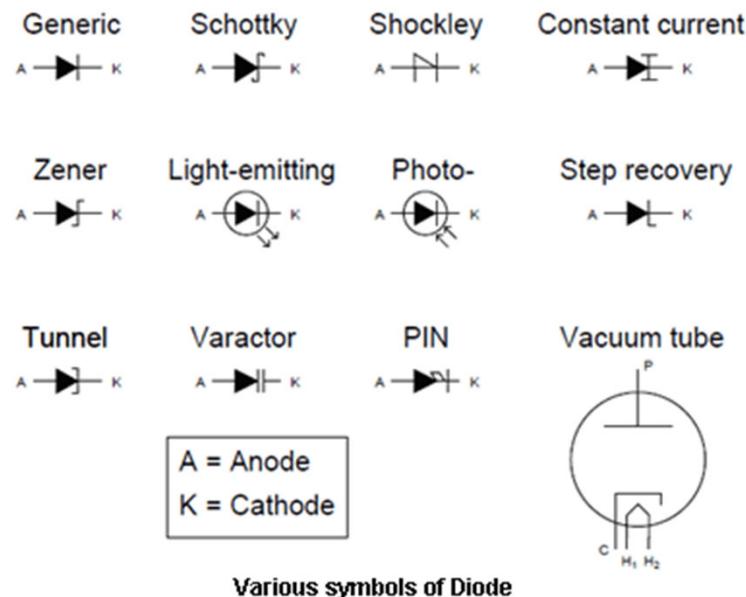
- Nowadays, a huge variety of diode technology has been developed, they are widely used!



Not all are based on p-n junctions!

The PN Junction

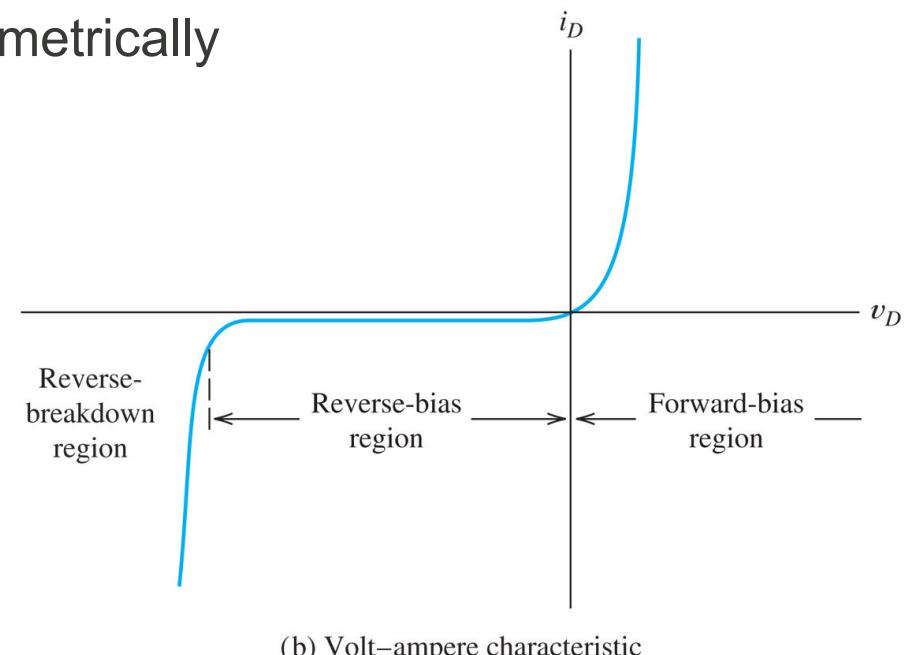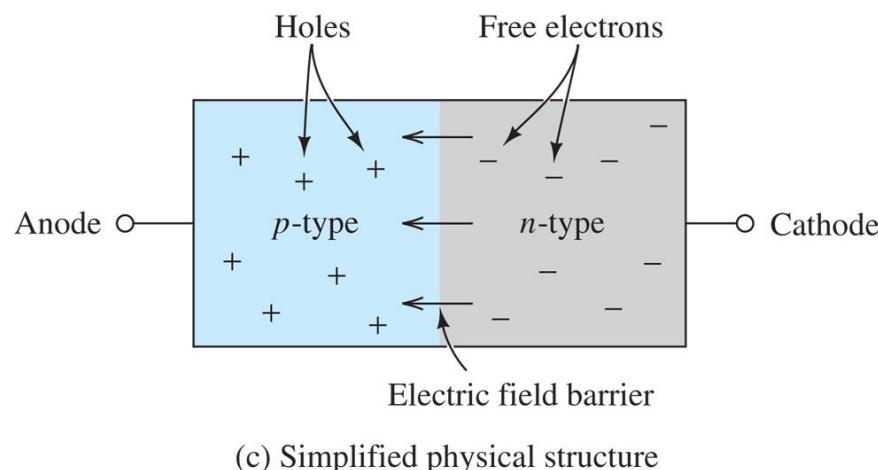
- Modern diodes are typically based on p-n junctions fabricated using semiconductors (commonly silicon)
- These junctions conduct current asymmetrically



Junction Diode Characteristics



MACQUARIE
University

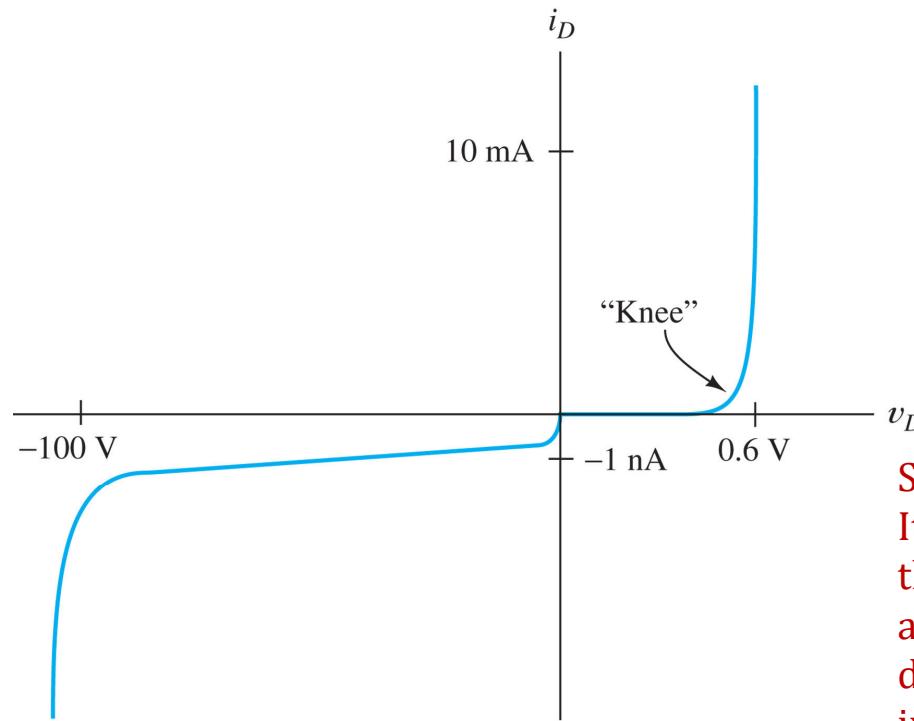

Approximate Shockley Equation
(for forward bias more than several tenths of a volt)

$$i_D \cong I_s \exp\left(\frac{v_D}{nV_T}\right)$$

Much easier to use

Shockley Equation
(for forward bias)

$$i_D = I_s (e^{v_D/nV_T} - 1)$$

$$i_D = I_s \left[\exp\left(\frac{v_D}{nV_T}\right) - 1 \right]$$

Saturation current.
Its value depends on
the area of the diode
and the temperature,
doubling for each 5°
increase for silicon
diodes.

$$\sim 10^{-14} \text{ A at } 300 \text{ K}$$

Emission
coefficient
(ideality factor)

$$1 < n < 2 \\ n \approx 1$$

Thermal voltage.
 $V_T = kT/q \cong$
25 mV at 300 K



Temperature in K
(273 + temp in °C)

$$k = 1.38 \times 10^{-23} \text{ joules/kelvin Boltzmann's constant}$$

$$q = 1.60 \times 10^{-19} \text{ coulomb magnitude of charge of an electron}$$


The Pipe Analogy

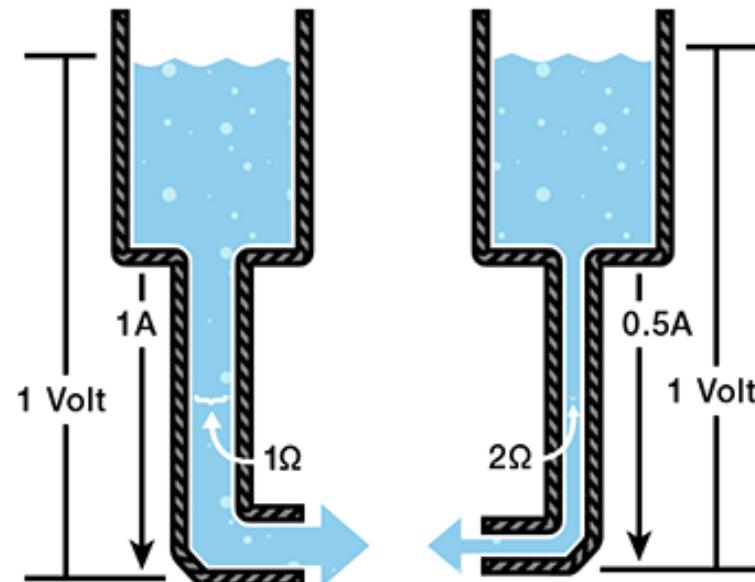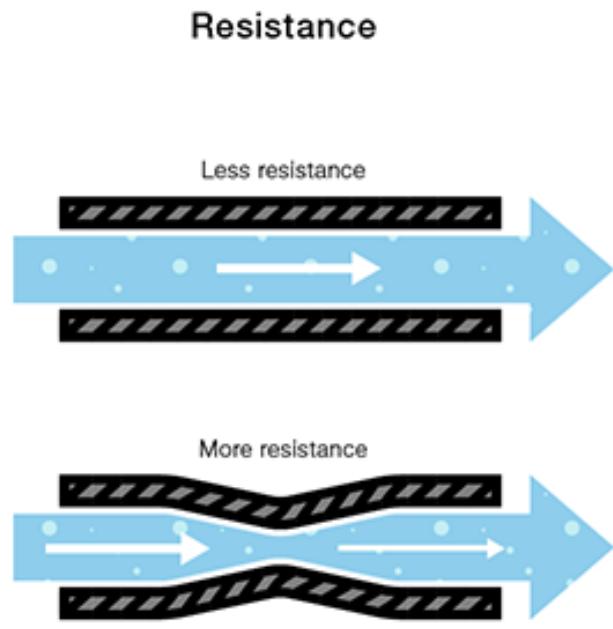- In the pipe analogy (AKA hydraulic analogy):
- Electric potential is equivalent to pressure. i.e. voltage is equivalent to the difference in pressure between two points
- Current is equivalent to flow rate, and charge is equivalent to quantity of water



The Pipe Analogy

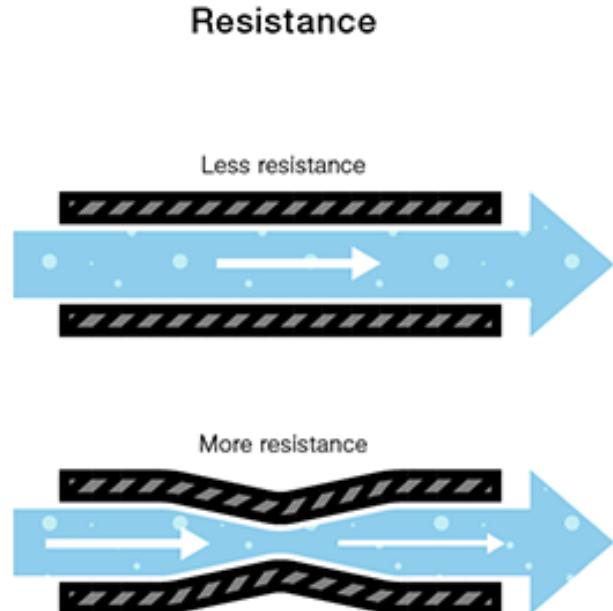- In the pipe analogy (AKA hydraulic analogy):
- Electric potential is equivalent to pressure. i.e. voltage is equivalent to the difference in pressure between two points
- Current is equivalent to flow rate, and charge is equivalent to quantity of water



What would the hydraulic equivalent to a diode be?

A narrow pipe

A T-Junction

A valve

A pump

Start the presentation to see live content. For screen share software, share the entire screen. Get help at pollev.com/app

Go to PollEv.com/davidpayne187 on your mobile or laptop to vote

The Pipe Analogy




Element	Circuit Analogy		Pipe Analogy		Flow Equation
Node	Junction	●	Junction		Total Flow = 0
Path	Wire	—	Rigid Pipe		Solve Directly
Resistance	Resistor	—■—	Aperture		$F = P/R$
Compliance	Capacitor	— —	Diaphragm		$F(t) = C \frac{dP(t)}{dt}$
Inertance	Inductor	—m—	Heavy Paddle		$F = \frac{1}{L} \int_{t_0}^t P dt + F(t_0)$
Switch	Switch	—\—	Gate Valve		Solve Directly
Valve	Diode	—>—	Check Valve		Solve Directly
Pressure Source	Voltage Source	— +—	Pump		Solve Directly
Flow Source	Current Source	—○→—			$F = F$


The Ideal Diode



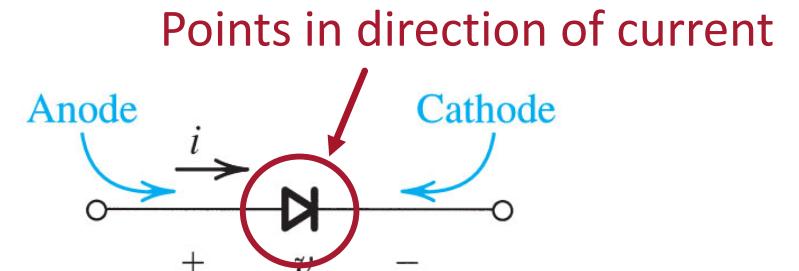- If a negative voltage is applied (reverse bias), no current flows – open circuit
- If a positive current is applied (forward bias), there is no voltage drop – short circuit




i-v characteristic

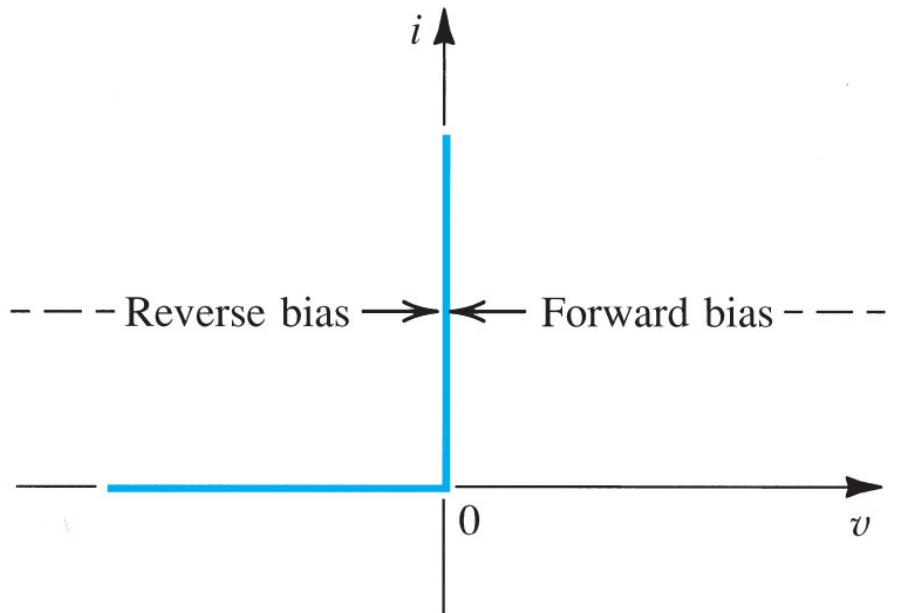


Equivalent Circuits

Reverse Direction

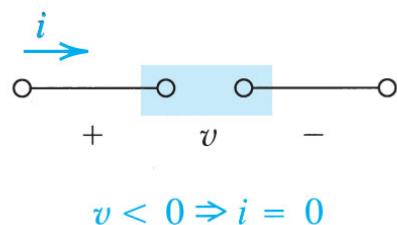

Forward Direction

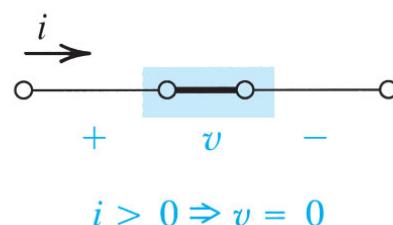

Analysis by Assumed States




In a circuit with a number of diodes:

- Assume a state for each diode (ON or OFF).
- n diodes will require 2^n possible combinations.
- Calculate currents of ON diodes and voltages of OFF diodes.
- Check to see if the calculations are consistent with the assumptions.
- If yes, the assumption works. If not, return to step 1 and make a new assumption.
- Making a table for your assumptions helps!

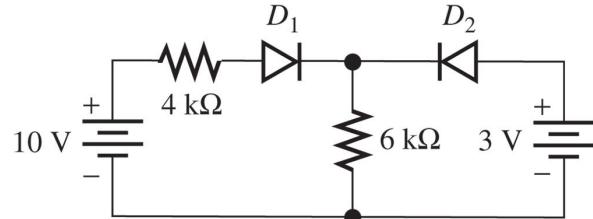Example Exercise


See *Hambley Example 10.5* for more details



(a) Circuit diagram


Use the ideal diode model to solve the circuit.

Assume D1 off and D2 on:

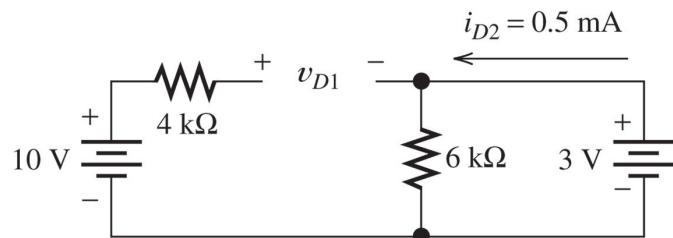

(b) Equivalent circuit assuming D_1 off and D_2 on
(since $v_{D1} = +7$ V, this assumption is not correct)

Assume D1 on and D2 off:

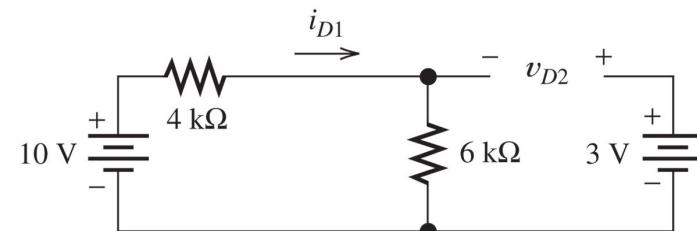



(c) Equivalent circuit assuming D_1 on and D_2 off
(this is the correct assumption since i_{D1} turns out to be a positive value and v_{D2} turns out negative)

What about the other two states?

Class Exercise




MACQUARIE
University

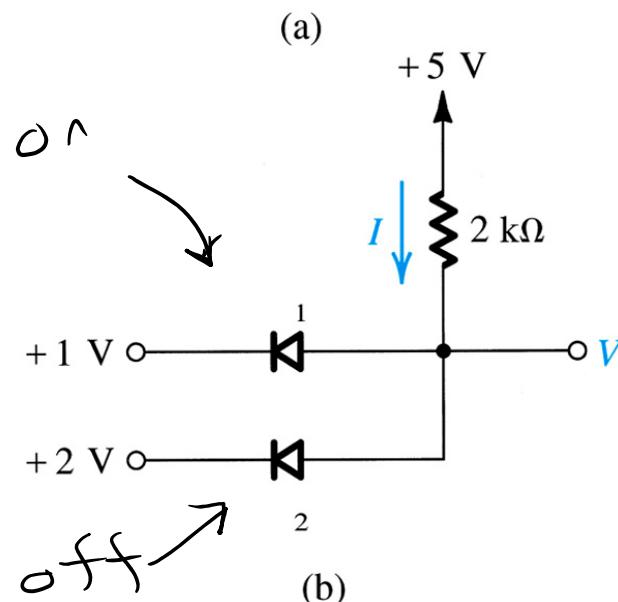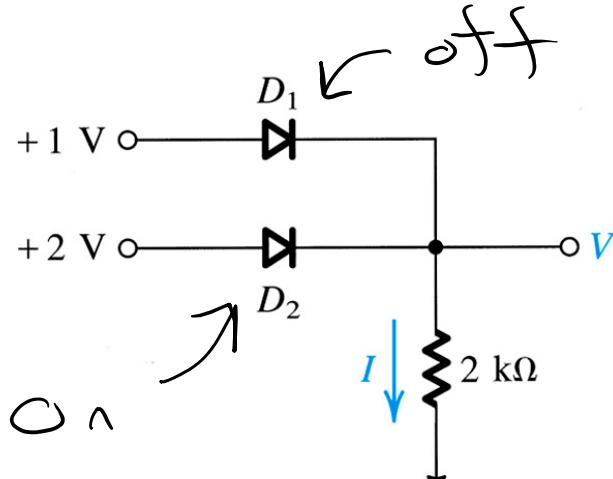

Use the ideal diode model to solve each circuit.

What are the diode states?

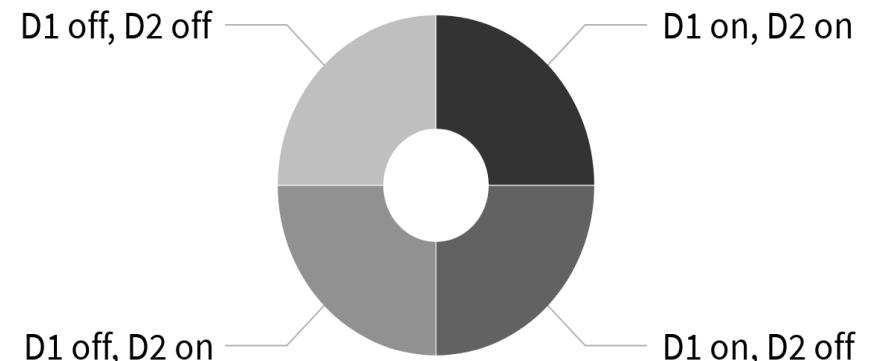D1 on, D2 on D1 on, D2 off D1 off, D2 on D1 off, D2 off



Poll Everywhere Start the presentation to see live content. Still no live content? Install the app or get help at PollEv.com/app


Go to PollEv.com/davidpayne187
on your mobile or laptop to vote

Class Exercise



MACQUARIE
University

IDEAL MODEL

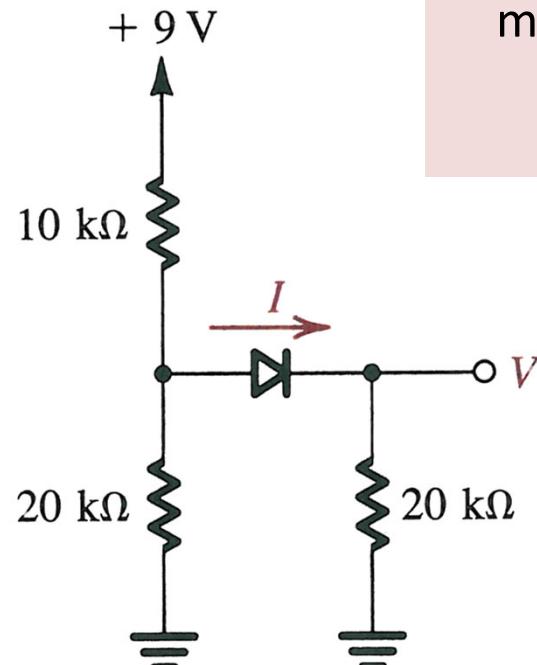

(a)

Use the ideal diode model to solve the circuit.

Hint: use Thévenin equivalents

Go to **PollEv.com/davidpayne187** on your mobile or laptop to vote

What is the voltage value at the output V ?



Start the presentation to see live content. For screen share software, share the entire screen. Get help at pollev.com/app

Timer Bar
(1 min) :




Class Exercise




MACQUARIE
University

IDEAL MODEL

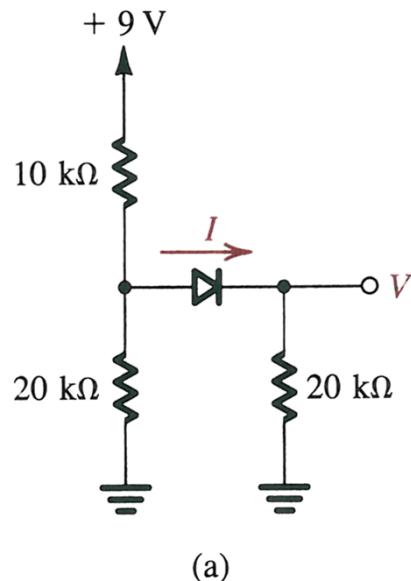

① Redraw with Thevenin..

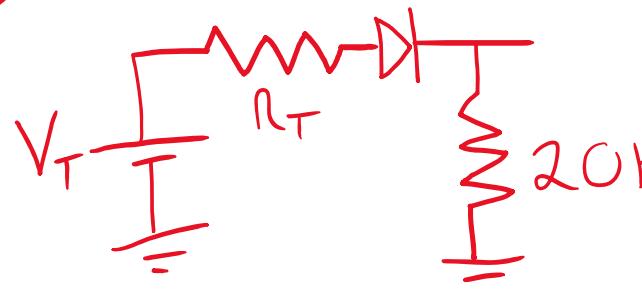

$$R_T = 10 \parallel 20 = \frac{10 \times 20}{30} = 6.66\text{k}$$

$$V_T = \frac{20}{30} V_{in} = 6\text{V}$$

② Calculate I

$$I = \frac{6\text{V}}{6.66\text{k} + 20\text{k}} = 0.225\text{mA}$$


③ Find V

$$V = \frac{20\text{k}}{20\text{k} + 6.66\text{k}} \times 6 = 4.5\text{V}$$


Non-ideal Diodes

In practice diode behaviour is typically more complex

Ideal Characteristics

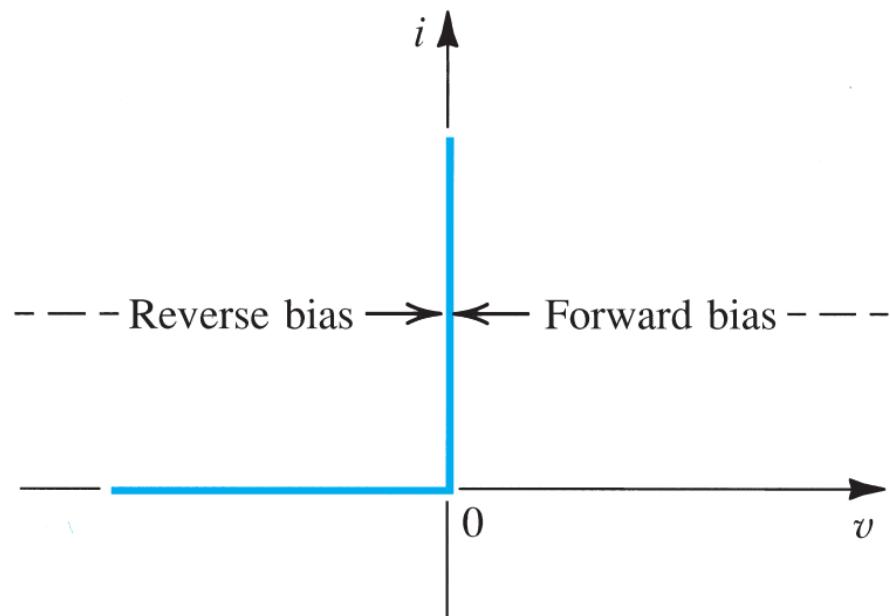

Realistic Characteristics

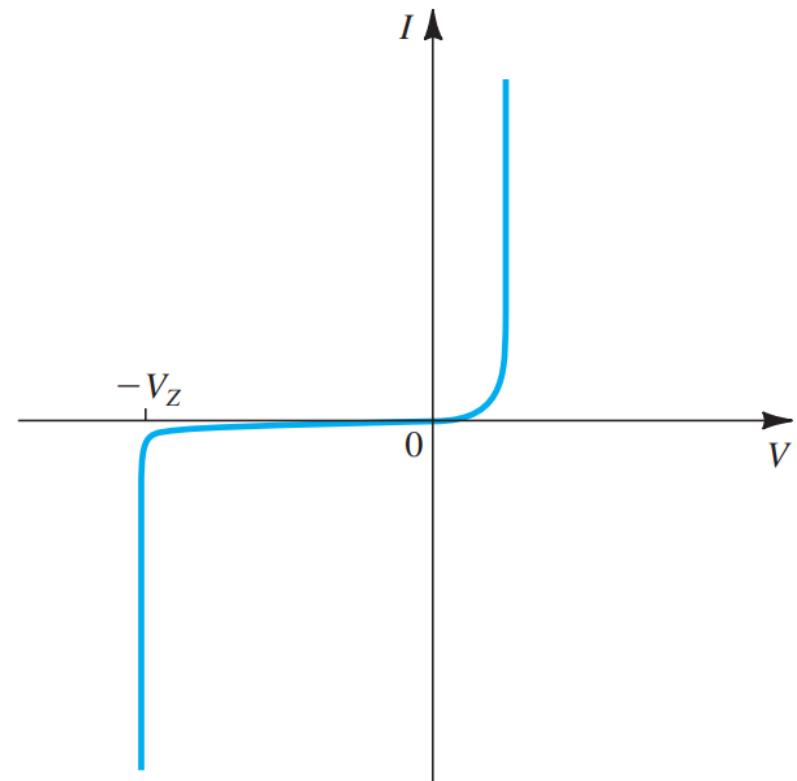


We can improve our model to approximate this!

Accounting for turn on voltage

CONSTANT VOLTAGE DROP MODEL

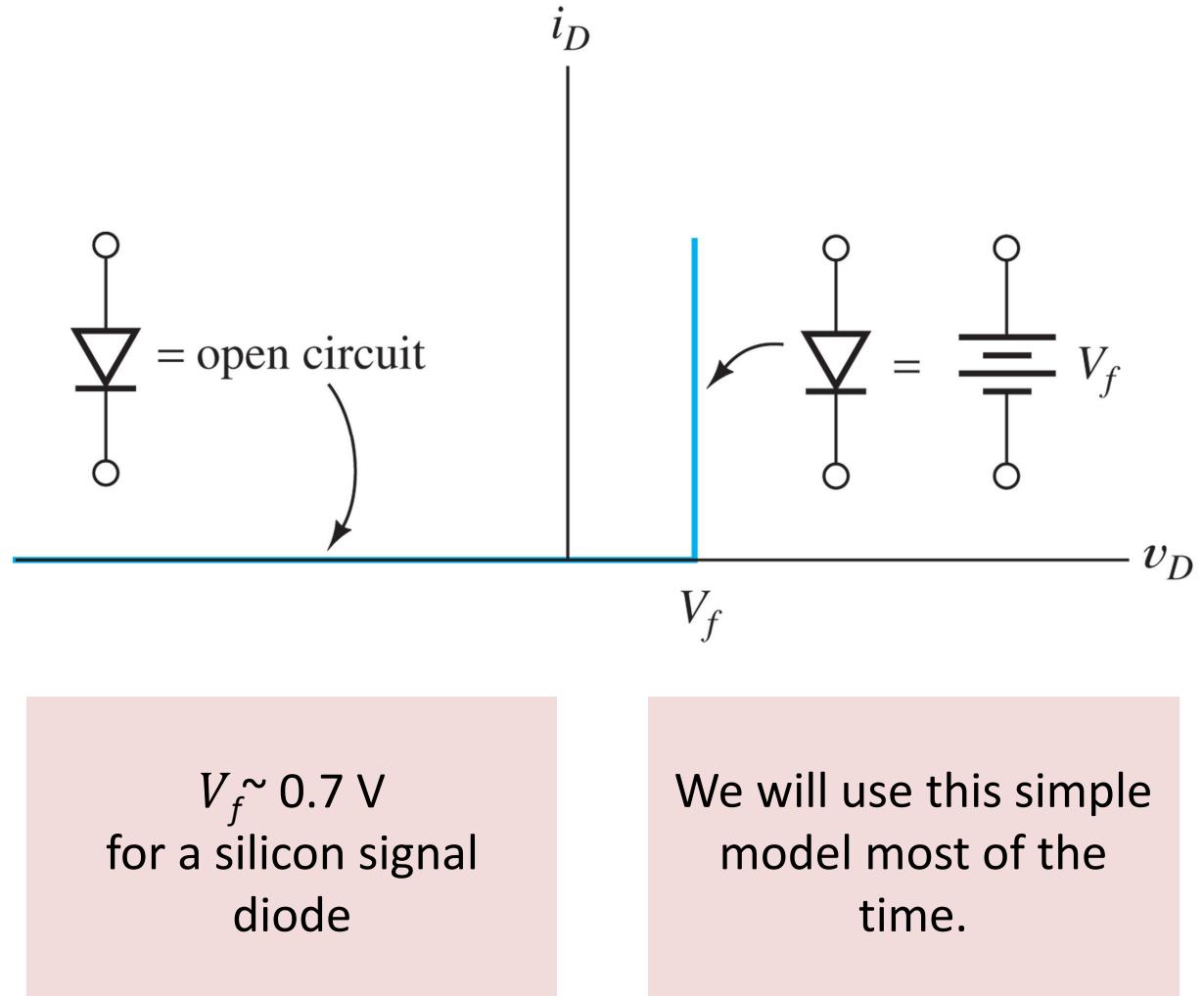- A basic model that accounts for the forward turn on voltage of the diode
- Does not account for the slope, or reverse breakdown





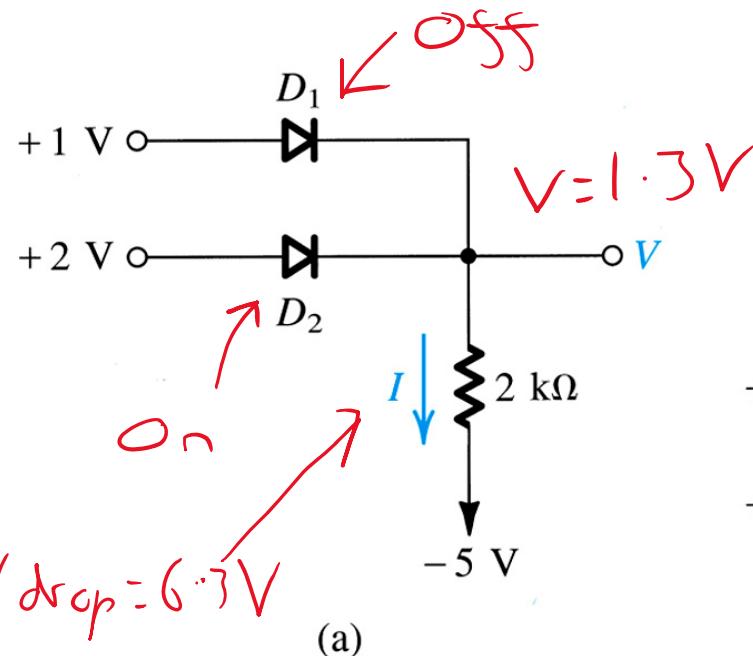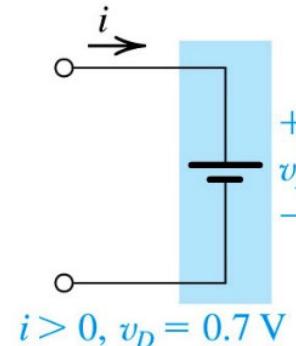Example


CONSTANT VOLTAGE DROP MODEL



Use the 0.7V drop diode model to solve each circuit.


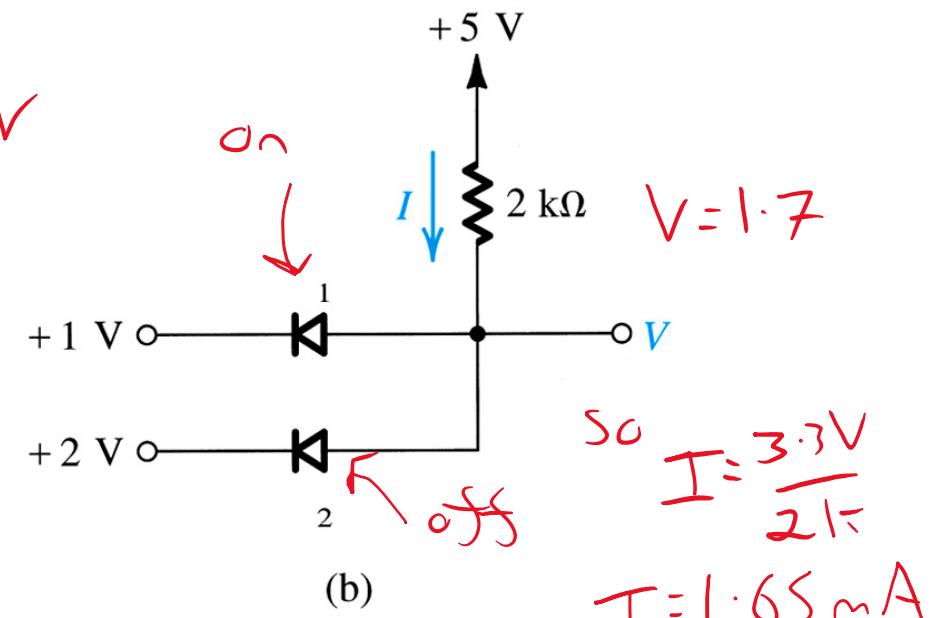
$$I = \frac{6.3 \text{ V}}{2 \text{ k}\Omega} = 3.15 \text{ mA}$$




Class Exercise

CONSTANT VOLTAGE DROP MODEL



MACQUARIE
University

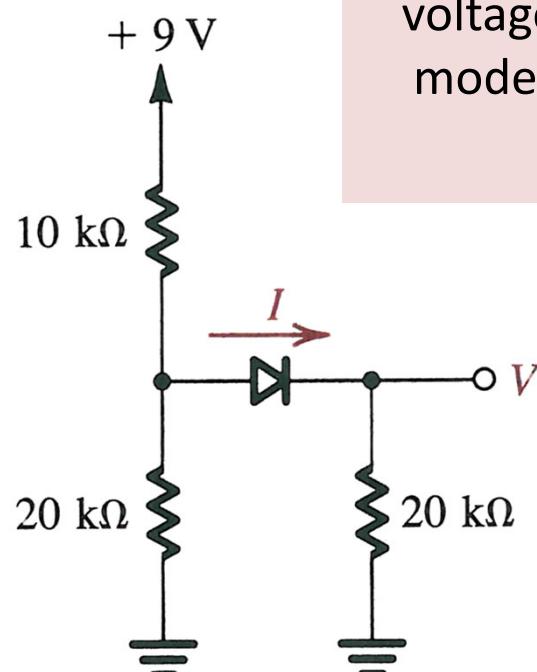

(a)

Use the constant voltage drop (0.7 V) model to solve the circuit.

Go to PollEv.com/davidpayne187 on your mobile or laptop to vote

What is the voltage value at the output V (using 0.7 drop model)?

- 3.6V
- 4V
- 6V
- 4.5V

Start the presentation to see live content. For screen share software, share the entire screen. Get help at polliev.com/app

Timer Bar
(1 min) :




Class Exercise




MACQUARIE
University

CONSTANT VOLTAGE DROP MODEL

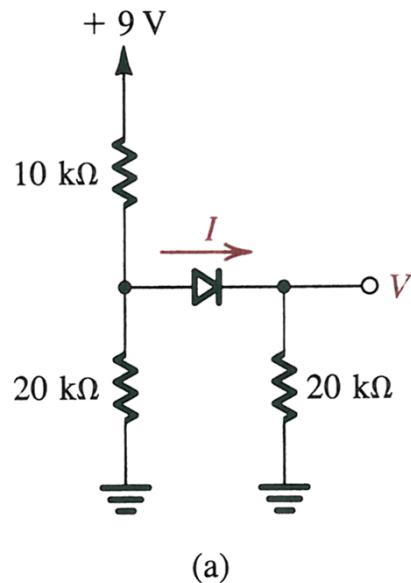

① Redraw with Thevenin..

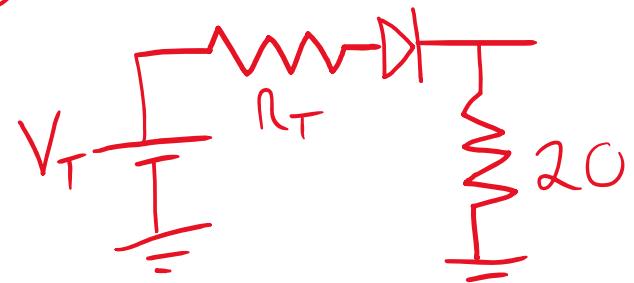

$$R_T = 10//20 = \frac{10 \times 20}{30} = 6.66\text{k}$$

$$V_T = \frac{20}{30} V_{in} = 6\text{V}$$

② Calculate I

$$I = \frac{6 - 0.7}{20\text{k} + 6.66\text{k}} = 0.199\text{ mA}$$

③ Find V


$$V = I \times R_L = 20\text{k} \times 0.199\text{ mA} = 3.98\text{ V}$$

What about the slope?


A SIMPLE LINEAR MODEL

In practice diode behaviour is typically more complex

Is this enough for
modelling a diode?

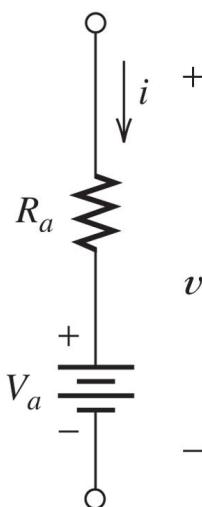

(a) Circuit diagram

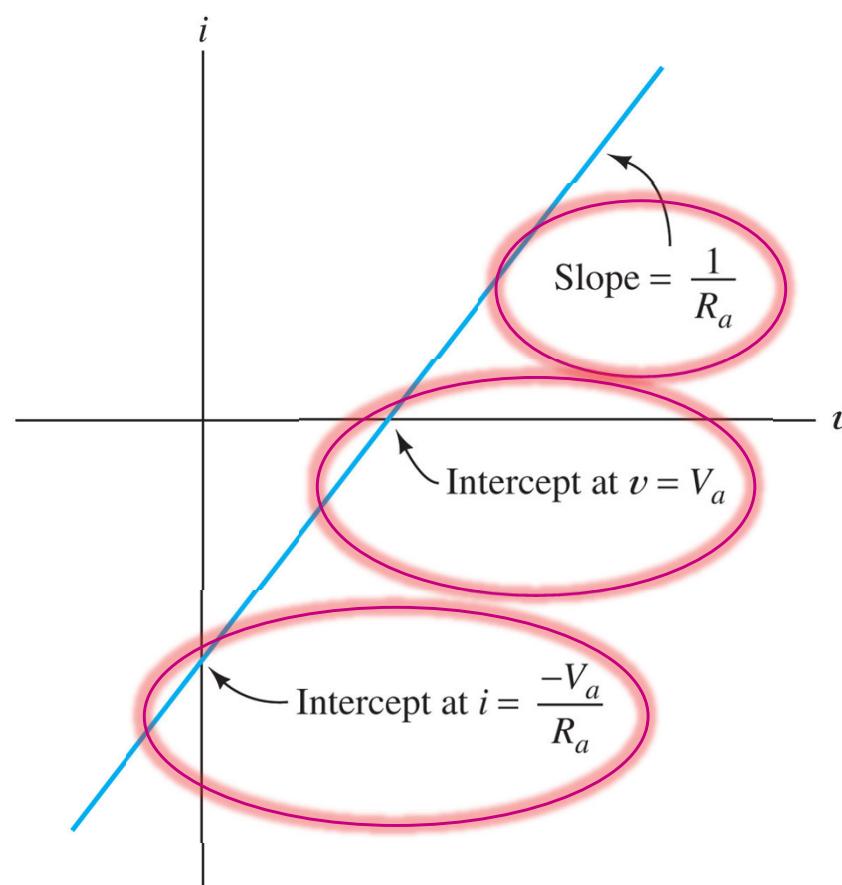

(b) Volt–ampere characteristic


What is the
mathematical
equation for this
model?

An Improved Model

A NONLINEAR BUT PIECE-WISE LINEAR MODEL



MACQUARIE
University

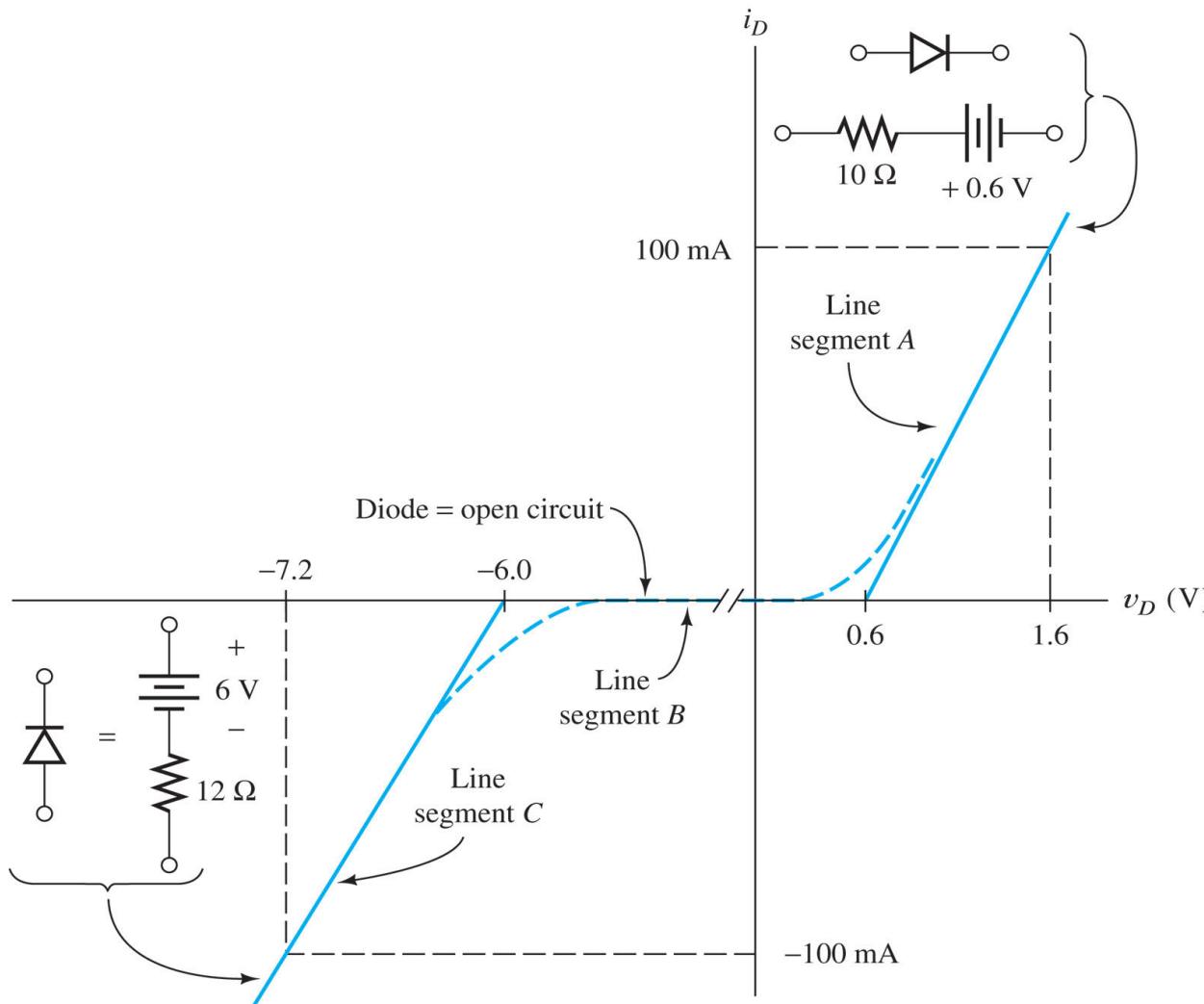


This is the graphical model.
Good for load-line analysis.

What is the mathematical model?

The Shockley Equation



MACQUARIE
University

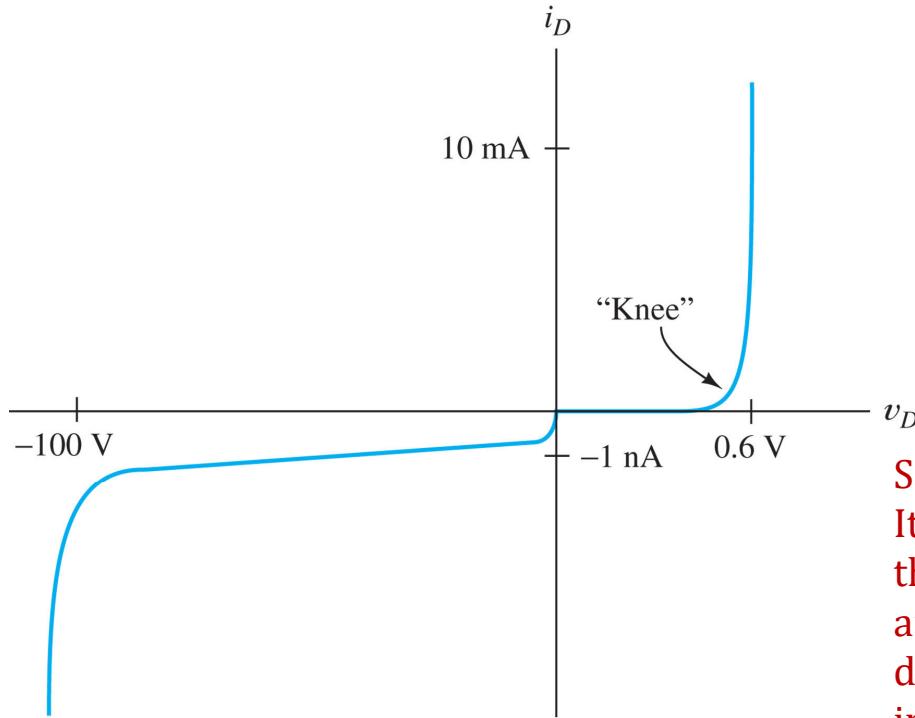

Approximate Shockley Equation
(for forward bias more than several tenths of a volt)

$$i_D \approx I_s \exp\left(\frac{v_D}{nV_T}\right)$$

Much easier to use

Shockley Equation
(for forward bias)

$$i_D = I_s (e^{v_D/nV_T} - 1)$$

$$i_D = I_s \left[\exp\left(\frac{v_D}{nV_T}\right) - 1 \right]$$

Saturation current.
Its value depends on
the area of the diode
and the temperature,
doubling for each 5°
increase for silicon
diodes.

$$\sim 10^{-14} \text{ A at } 300 \text{ K}$$

Emission
coefficient
(ideality factor)

$$1 < n < 2 \\ n \approx 1$$

Thermal voltage.
 $V_T = kT/q \approx$
25 mV at 300 K

Temperature in K
(273 + temp in °C)

$$k = 1.38 \times 10^{-23} \text{ joules/kelvin Boltzmann's constant}$$

$$q = 1.60 \times 10^{-19} \text{ coulomb magnitude of charge of an electron}$$


Diode Analysis

USING THE SHOCKLEY EQUATION



MACQUARIE
University

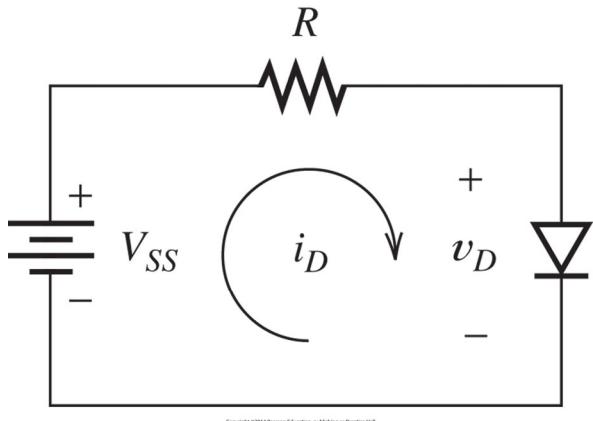- We want to find the diode voltage and current (operating point)




We know the diode I-V equation:


$$i_D = I_s \left[\exp\left(\frac{v_D}{nV_T}\right) - 1 \right] \quad (1)$$

or: $i_D \cong I_s \exp\left(\frac{v_D}{nV_T}\right)$

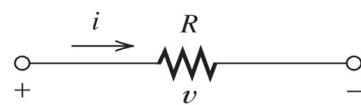There is no straightforward way to solve these two equations analytically



We know the resistor I-V equation

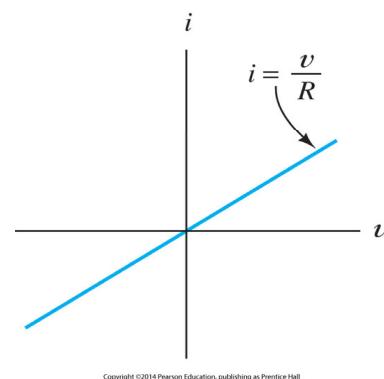

We know Kirchhoff's voltage law:

$$V_{SS} = Ri_D + v_D \quad (2)$$

Graphical method called load-line analysis can be used.



Load Line Analysis



MACQUARIE
University

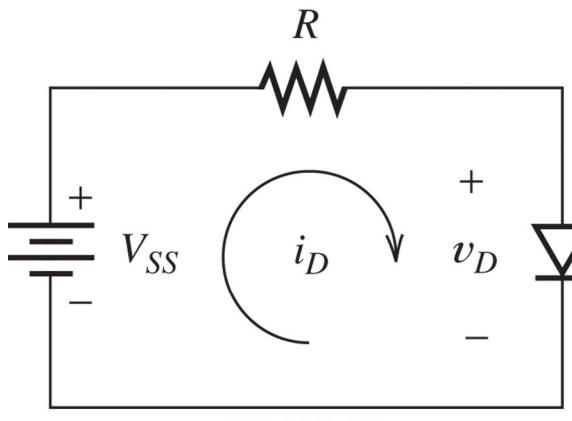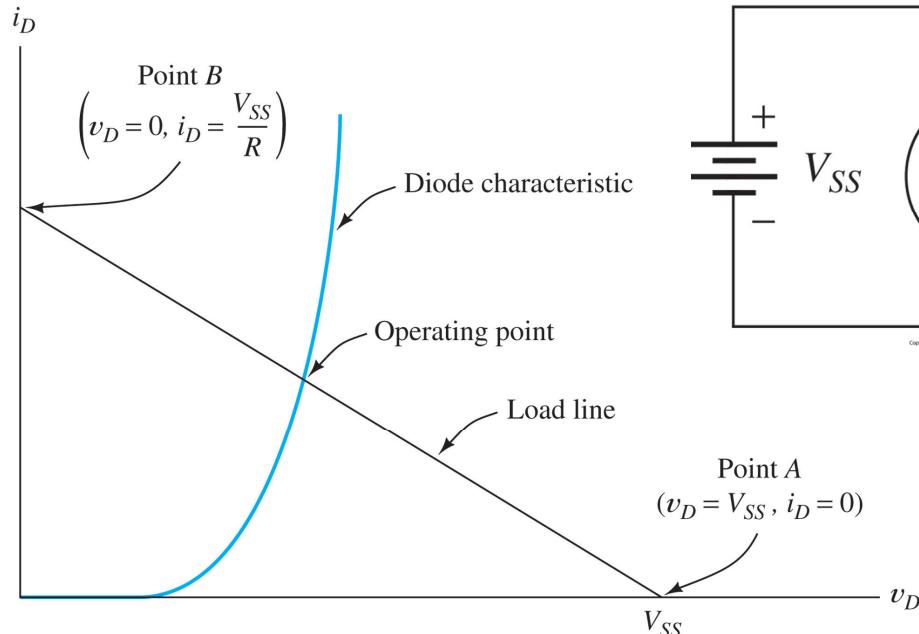EXAMPLE PROBLEM

See *Hambley* Exercise 10.1 for more details



We know the diode I-V equation:

$$i_D = I_s \left[\exp\left(\frac{v_D}{nV_T}\right) - 1 \right] \quad (1)$$

or: $i_D \cong I_s \exp\left(\frac{v_D}{nV_T}\right)$

We know Kirchhoff's voltage law:

$$V_{SS} = Ri_D + v_D \quad (2)$$

$$i_D = \frac{V_{SS} - v_D}{R}$$

What else do we need to find the operating point?

$$V_{SS} = 2 \text{ V}$$


$$R = 1 \text{ k}\Omega$$

$$V_{DQ} \cong 0.7 \text{ V} \quad I_{DQ} \cong 1.3 \text{ mA}$$


The Zener Diode



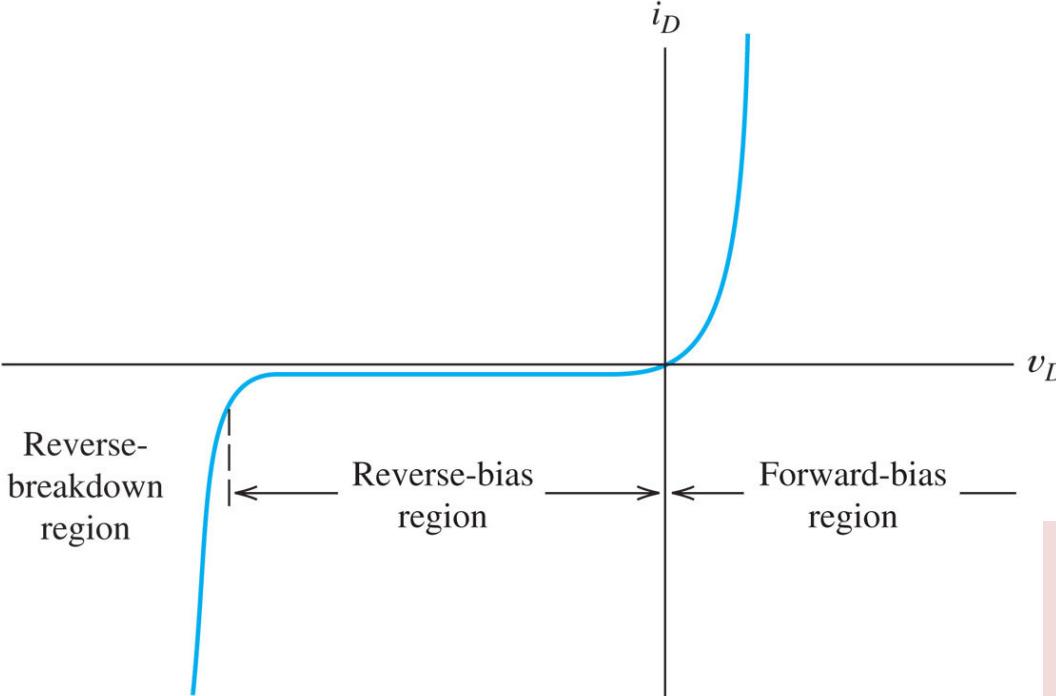Diodes that are designed to work at the reverse breakdown region are Zener diodes.



(b) Volt–ampere characteristic

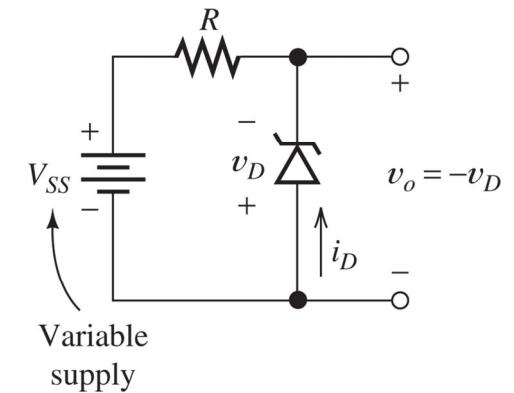


Commonly used for
voltage regulator
circuits – constant
output from variable
supply

Zener Diode Voltage Regulator

LOAD-LINE ANALYSIS IN THE REVERSE BREAKDOWN REGION

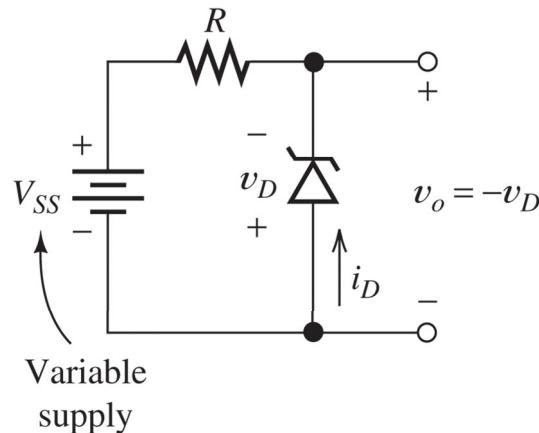See Hambley Exercise 10.3 for more details




$V_{SS} = 15 \text{ V}$ and 20 V

$R = 1 \text{ k}\Omega$


Notice the slope of the load line did not change.
Why?

5V change in the supply voltage results in only a 0.5V change in the regulated output voltage.

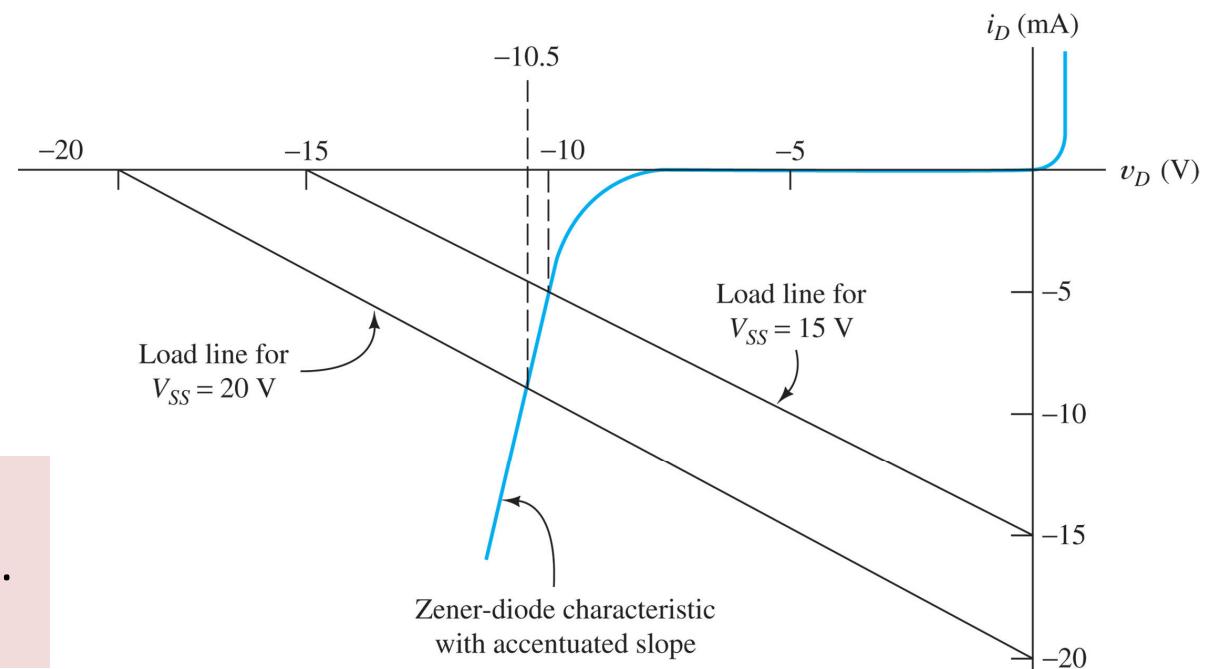Actual Zener diodes can do much better than this




L-L Analysis of complex circuits

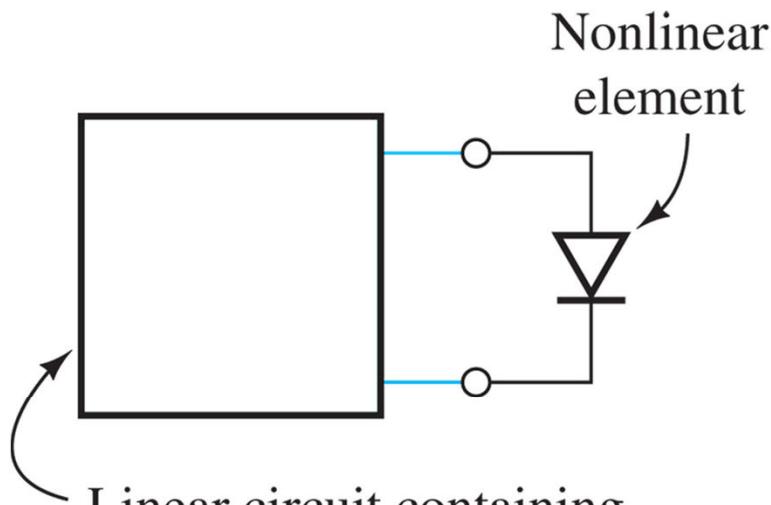

Linear circuit containing
voltage sources, current
sources, and resistors

(a) Original circuit

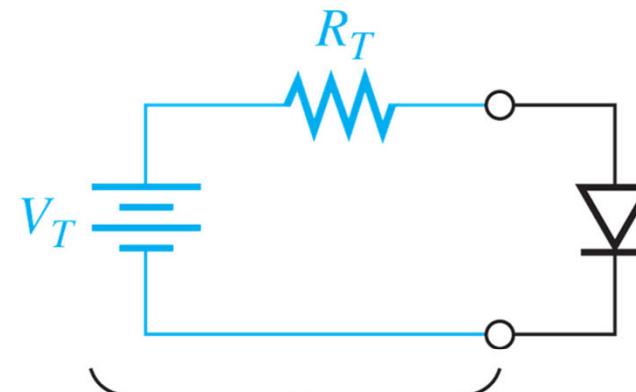


Thévenin
equivalent
circuit

(b) Simplified circuit

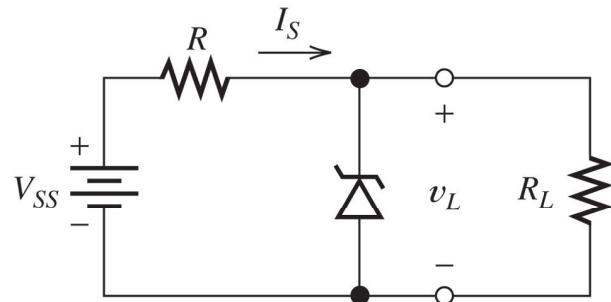
Example




See Hambley Exercise 10.4 for more details



(a) Regulator circuit with load

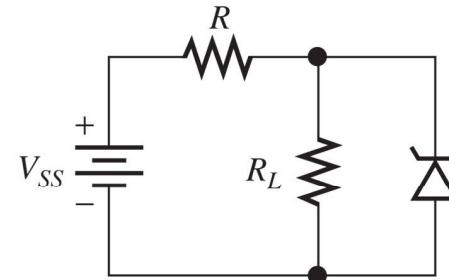

(b) Circuit of (a) redrawn

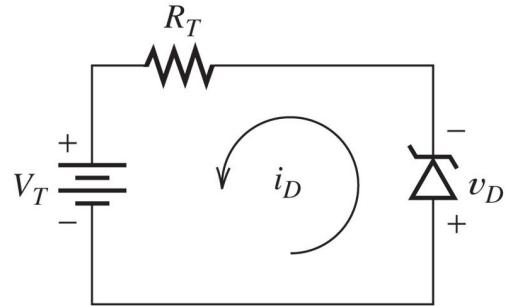


(c) Circuit with linear portion
replaced by Thévenin equivalent

$$V_{SS} = 24 \text{ V}$$

$$R = 1.2 \text{ k}\Omega$$

$$R_L = 6 \text{ k}\Omega$$

Find the load
voltage and
source current

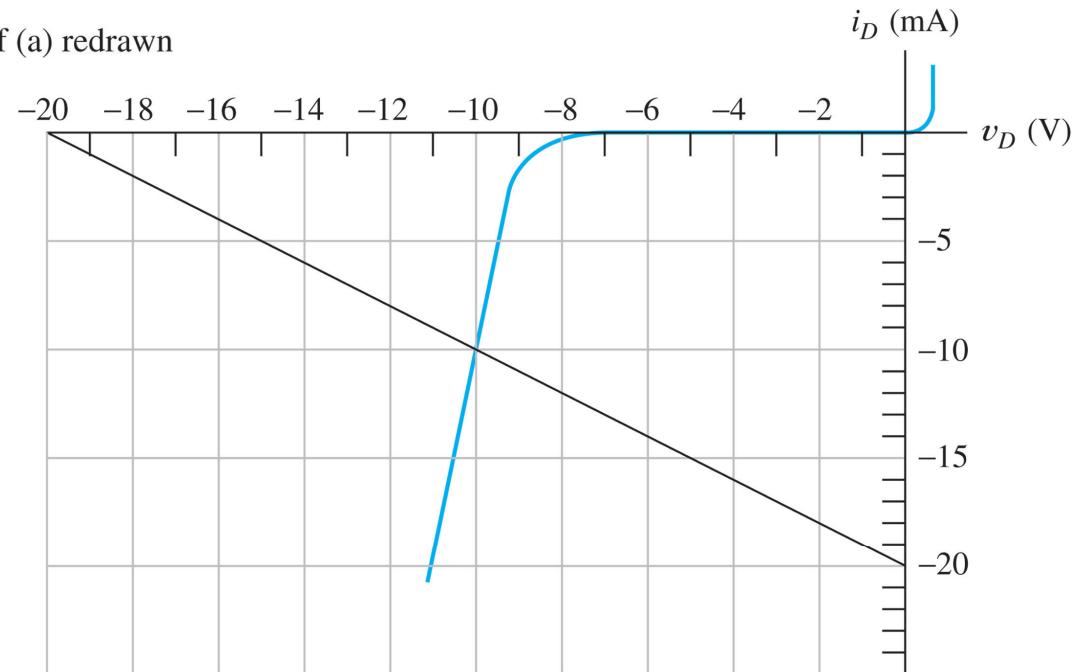



Lecture 2

1. Diode Fundamentals & Models
2. **Diode Circuits & Applications**
3. Small Signal Analysis


Logic Gates



MACQUARIE
University

LOGIC GATES WITH DIODES

What kind of logic gate is this?

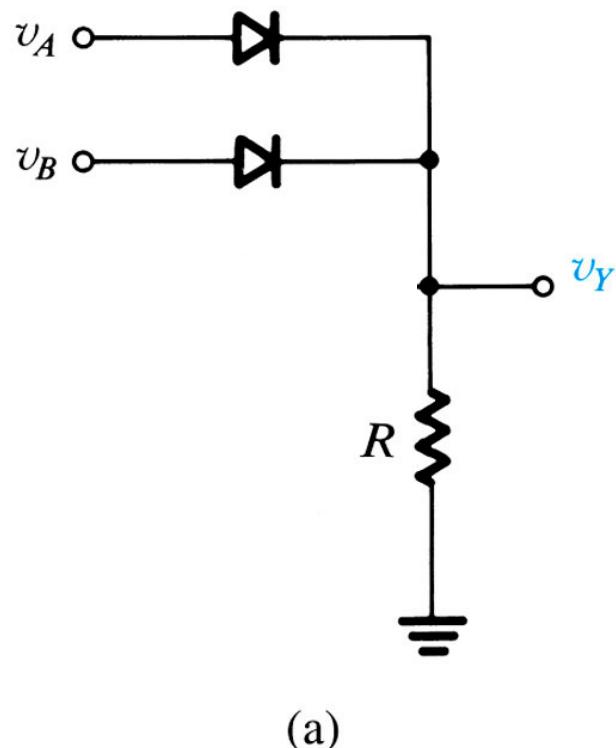

Assuming ideal diodes

v_A (V)	v_B (V)	v_Y (V)
5	0	
0	5	
5	5	
0	0	


Logic Gates



MACQUARIE
University

LOGIC GATES WITH DIODES


What kind of logic gate is this?

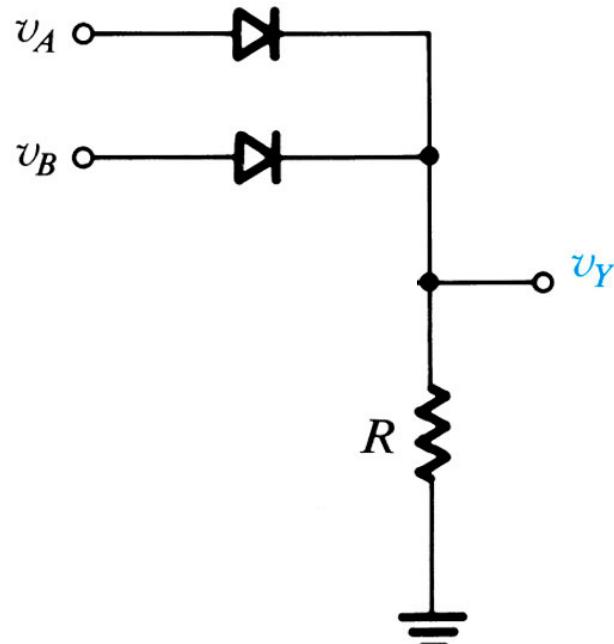

(a)

What logic gate is this?

AND OR NOT XOR

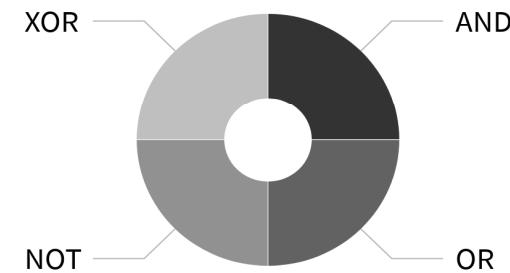

Poll Everywhere Start the presentation to see live content. Still no live content? Install the app or get help at PollEv.com/app

Assuming ideal diodes

v_A (V)	v_B (V)	v_Y (V)
5	0	
0	5	
5	5	
0	0	


Logic Gates



MACQUARIE
University

LOGIC GATES WITH DIODES
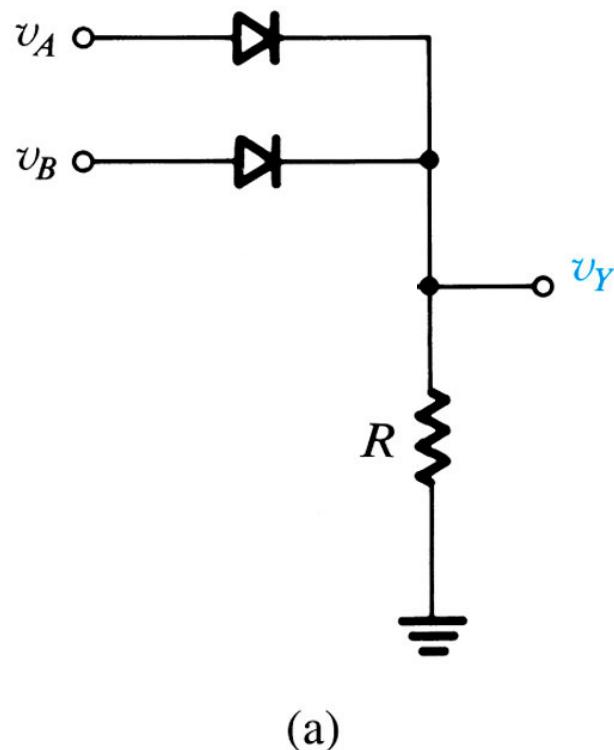
$$Y = A \text{ OR } B \\ (A+B \text{ in Boolean notation})$$



Assuming ideal diodes

v_A (V)	v_B (V)	v_Y (V)
5	0	5
0	5	5
5	5	5
0	0	0

Logic Gates




MACQUARIE
University

LOGIC GATES WITH DIODES – OR GATE

$$Y = A \text{ OR } B \text{ OR } C$$

($A+B+C$ in Boolean notation)

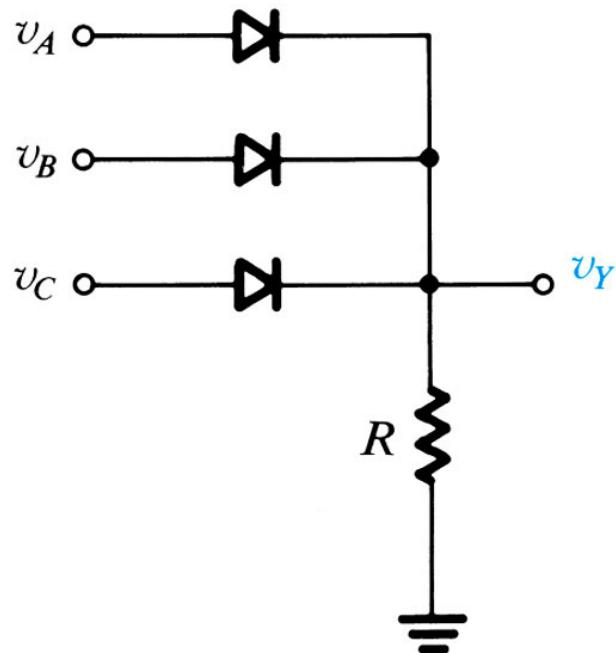

(a)


Logic Gates

LOGIC GATES WITH DIODES



MACQUARIE
University

What kind of gate is this?

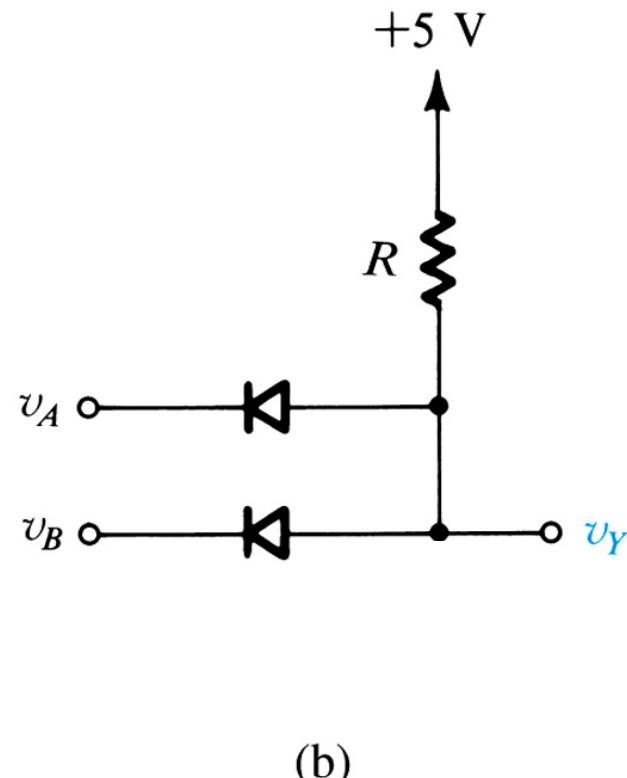

Assuming ideal diodes


v_A (V)	v_B (V)	v_Y (V)
5	0	
0	5	
5	5	
0	0	

Logic Gates

LOGIC GATES WITH DIODES




What kind of gate is this?

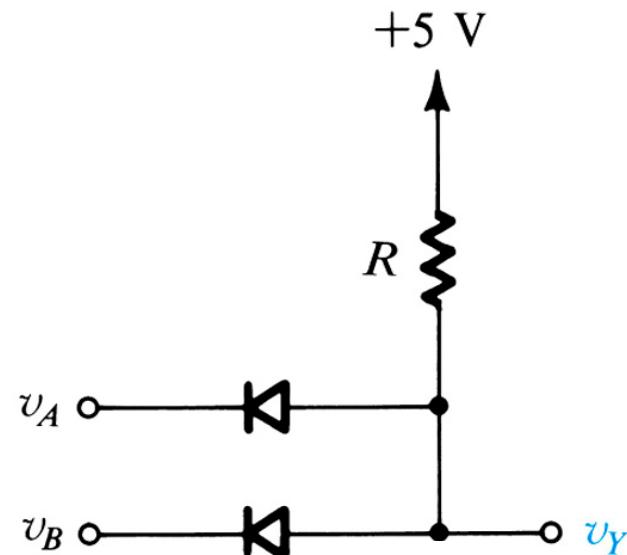

(b)

What logic function can this circuit implement?

AND OR NOT XOR

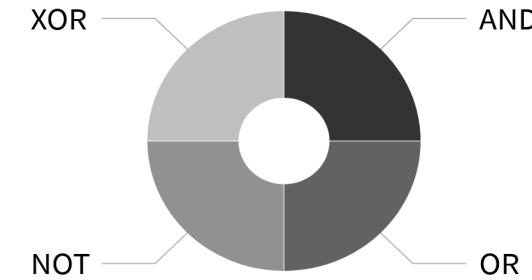

Join Everywhere Start the presentation to see live content. Still no live content? Install the app or get help at PollEv.com/app

Assuming ideal diodes

v_A (V)	v_B (V)	v_Y (V)
5	0	
0	5	
5	5	
0	0	

Logic Gates


LOGIC GATES WITH DIODES



MACQUARIE
University

$$Y = A \text{ AND } B$$

($A \cdot B$ in Boolean notation)

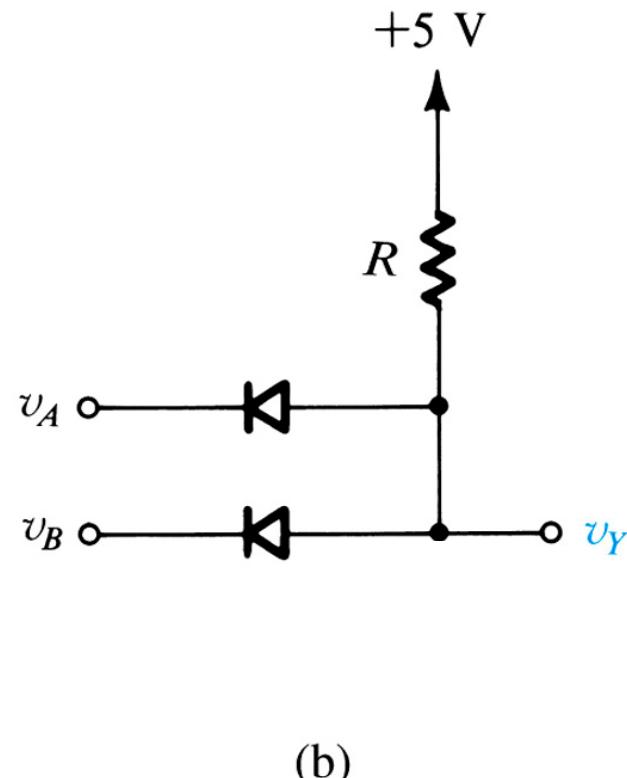

Assuming ideal diodes

v_A (V)	v_B (V)	v_Y (V)
5	0	0
0	5	0
5	5	5
0	0	0


Rectifier Circuits




MACQUARIE
University

HALF-WAVE RECTIFIER


- Used to convert AC power to DC power

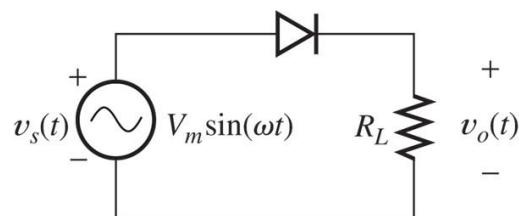

(a) Circuit diagram

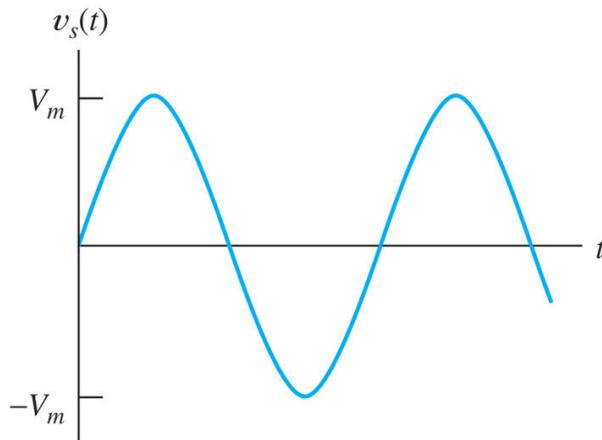


(b) Source voltage versus time

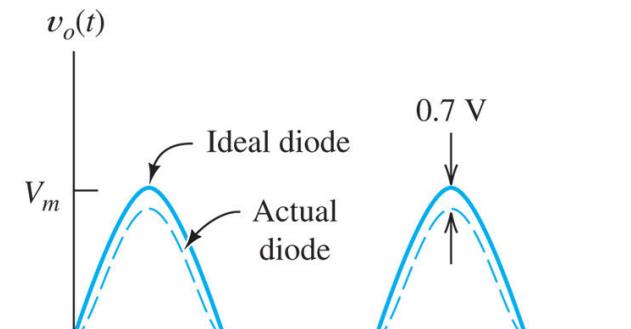

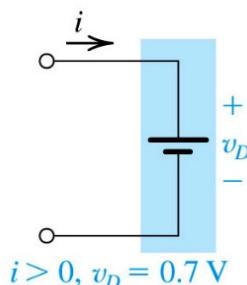(c) Load voltage versus time

Copyright ©2014 Pearson Education, publishing as Prentice Hall



We can use the 0.7V drop model or ideal diode model without losing much accuracy because voltage levels $\gg 0.7\text{V}$


Rectifier Circuits



MACQUARIE
University

HALF-WAVE RECTIFIER – WITH SMOOTHING

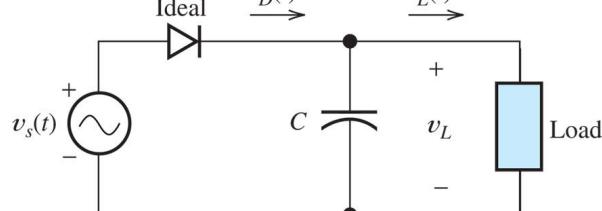- We can add a capacitor to smoothen the output




(a) Circuit diagram

Average load
current

$$C \cong \frac{I_L T}{V_r}$$

Period of the ac voltage

Ripple voltage

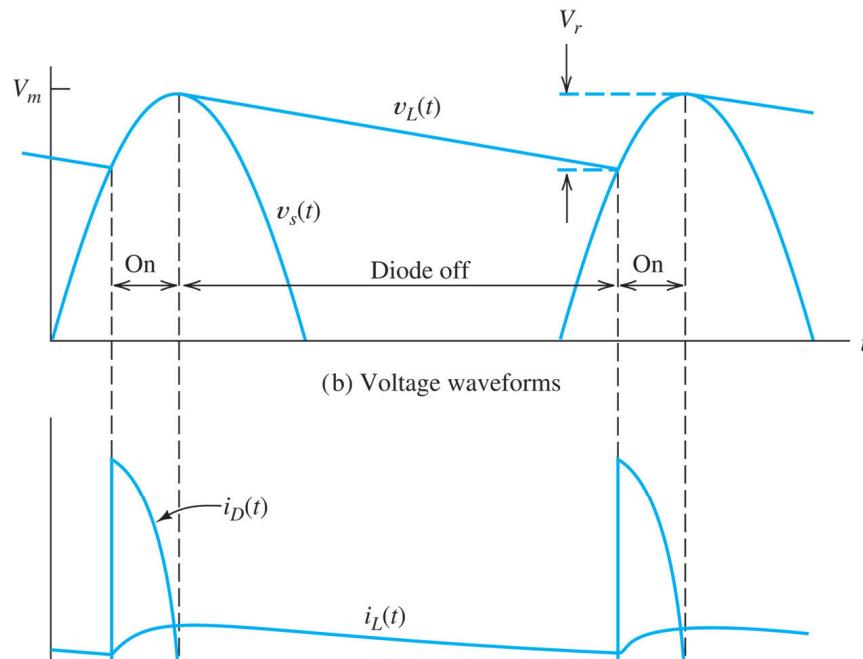

(b) Voltage waveforms

(c) Current waveforms

Choose diode to withstand
Peak Inverse Voltage

$$\text{PIV} \cong 2V_m$$

PIV needs to be less
than the breakdown
voltage of the diode.


Rectifier Circuits




MACQUARIE
University

FULL-WAVE RECTIFIER

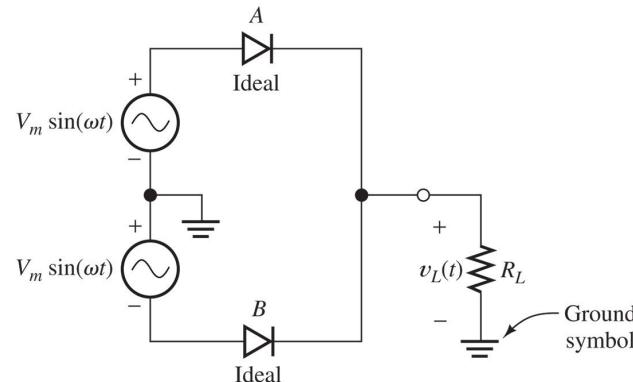
A transformer can provide this (out-of-phase ac voltages) →



(a) Circuit diagram

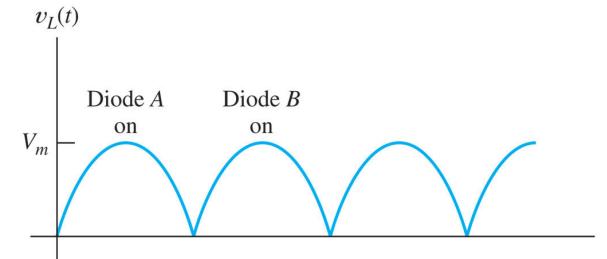

(b)

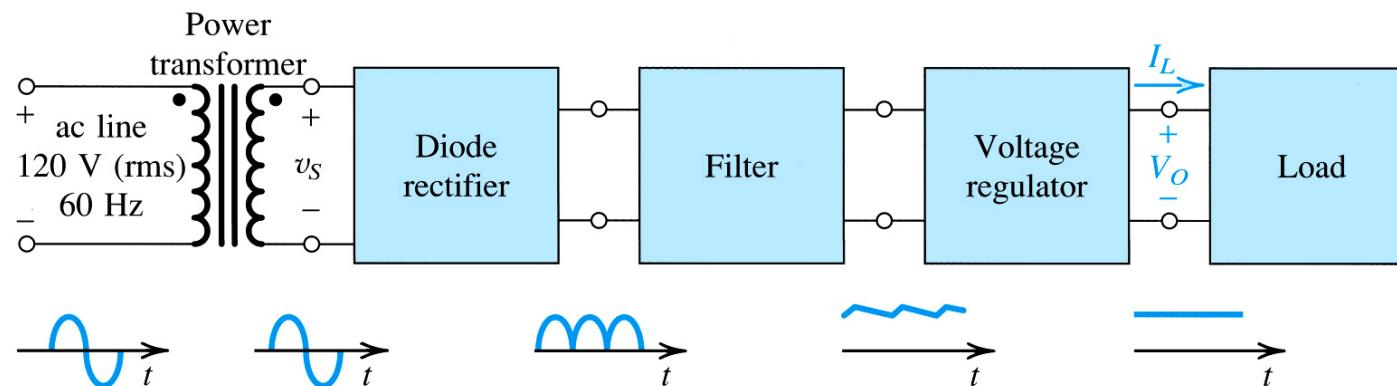

Block diagram of a dc power supply.


Rectifier Circuits



MACQUARIE
University

DIODE-BRIDGE FULL-WAVE RECTIFIER



Figure 10.28

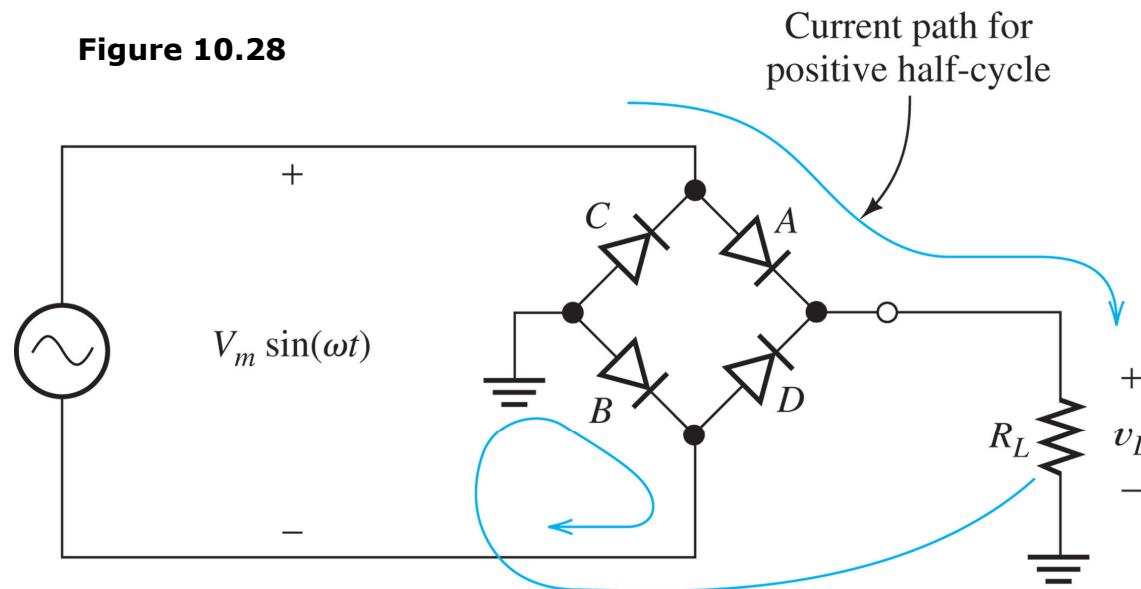


Copyright ©2014 Pearson Education, publishing as Prentice Hall

Rectifier Circuits

PRECISION RECTIFIER – THE “SUPERDIODE”

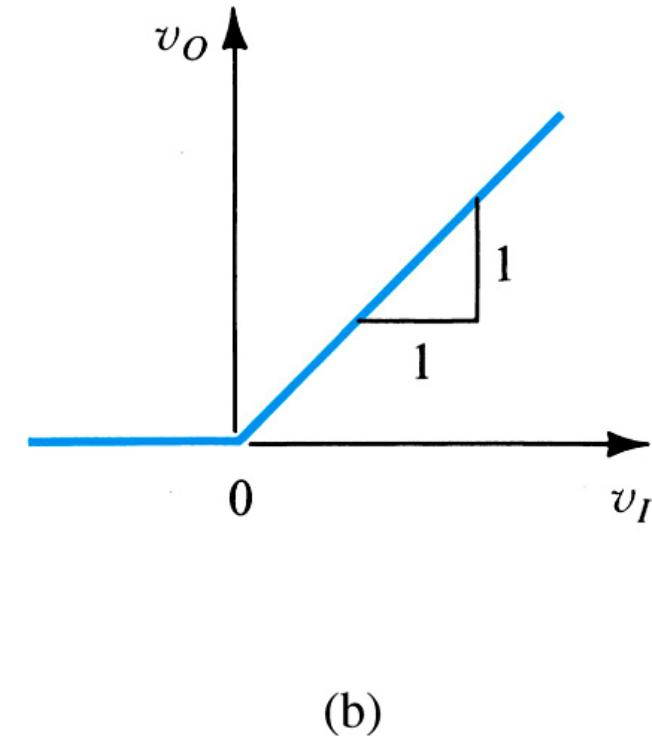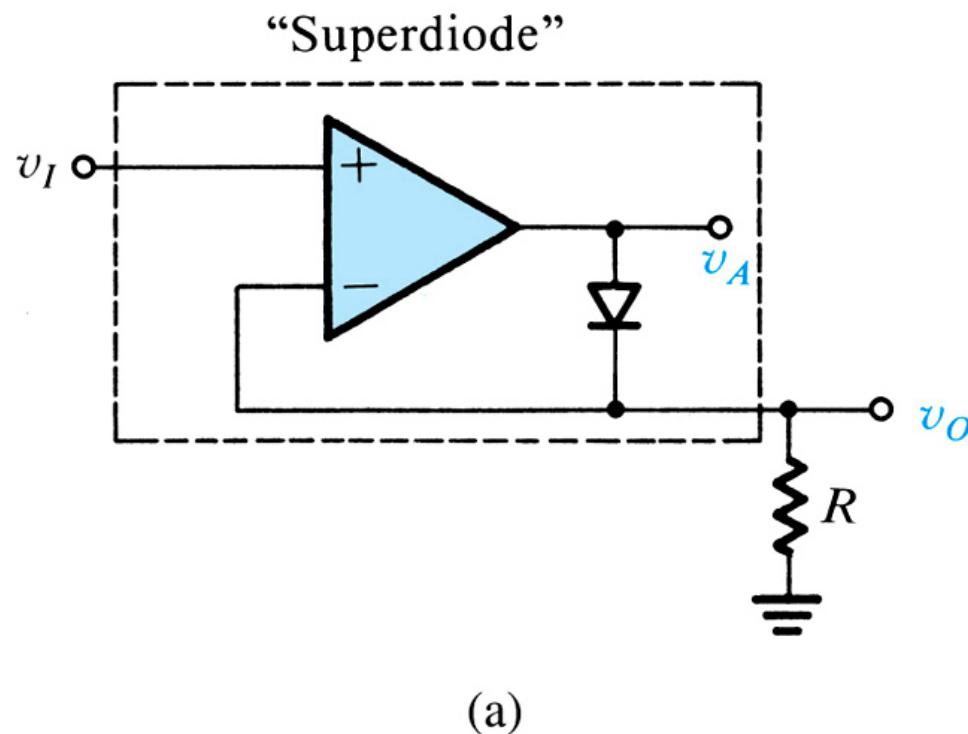

Voltage Regulator

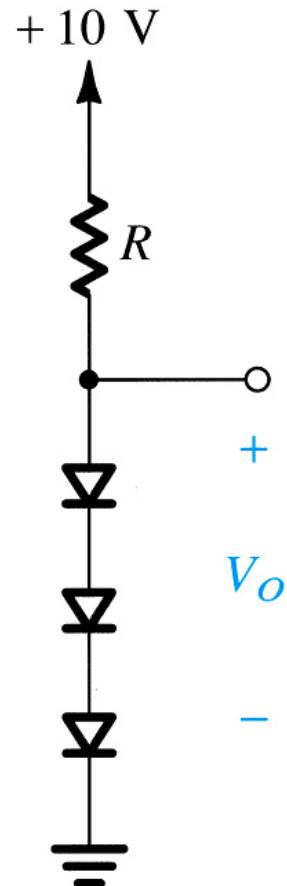

Using Si diodes (0.7V constant Voltage drop)


$$V_O \simeq 2.1 \text{ V}$$

Wave Shaping Circuits




MACQUARIE
University

LIMITING CIRCUITS

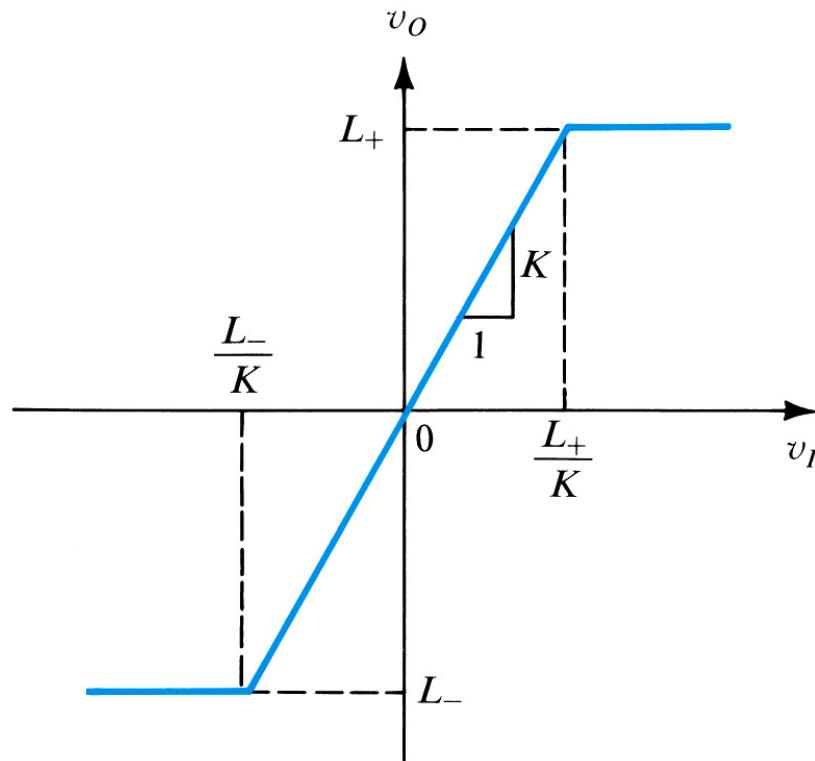

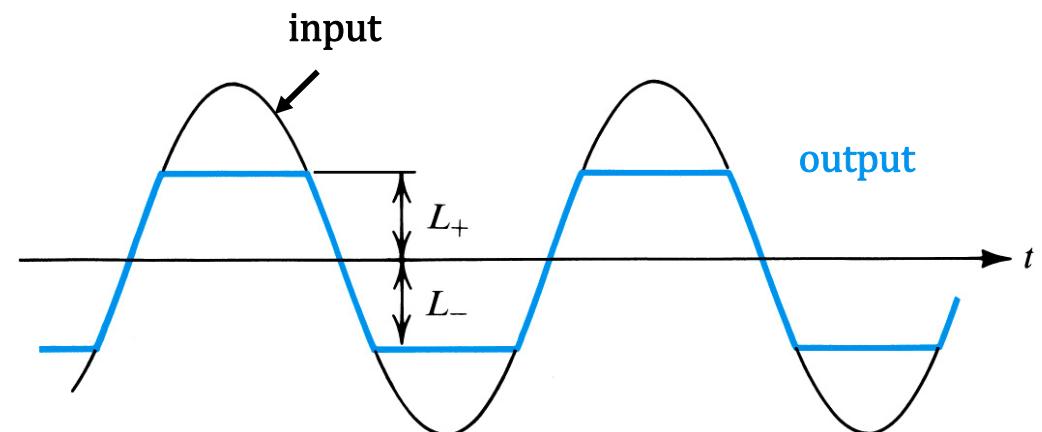Voltage transfer characteristic
of a limiting circuit (a “limiter”)




Example: “clipped” output

Wave Shaping Circuits

CLIPPER CIRCUITS




MACQUARIE
University

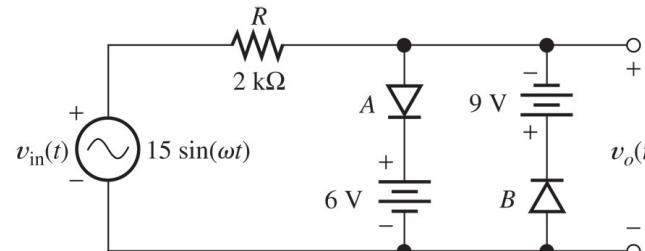

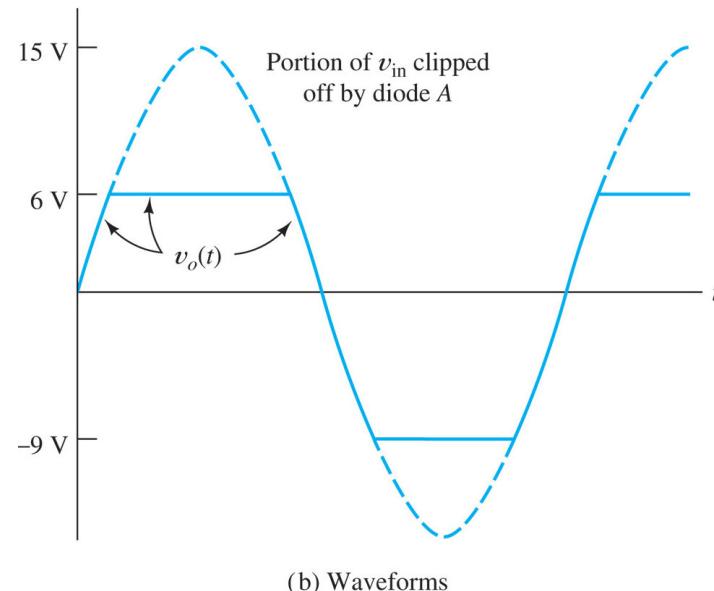
(a) Circuit diagram

Ideal
diodes.

You need to
practice drawing
these by hand!



(b) Waveforms

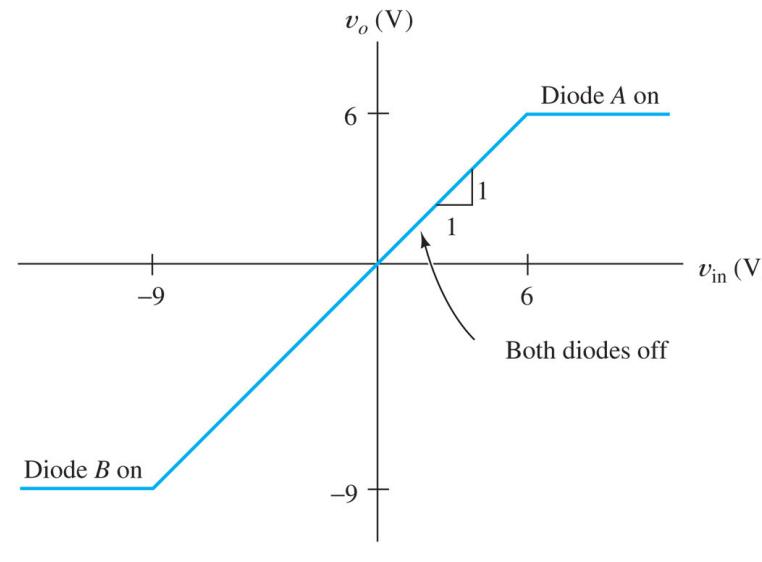

(c) Transfer characteristic





Voltage transfer characteristic !

Wave Shaping Circuits







MACQUARIE
University

LIMITING CIRCUITS WITH DIODES

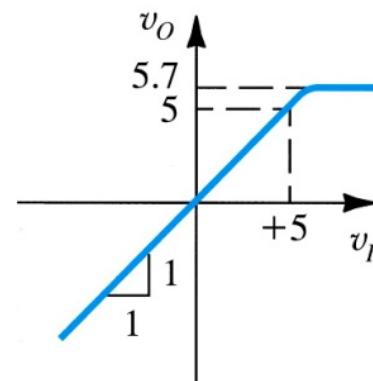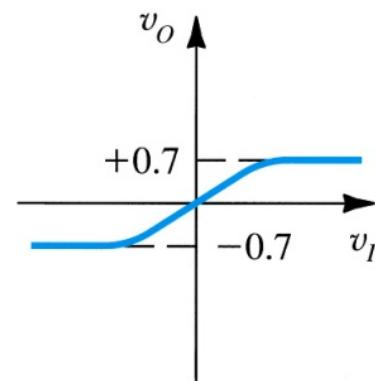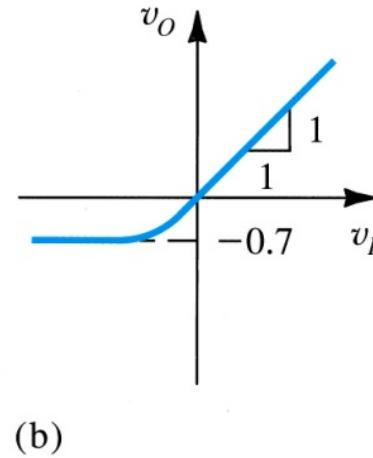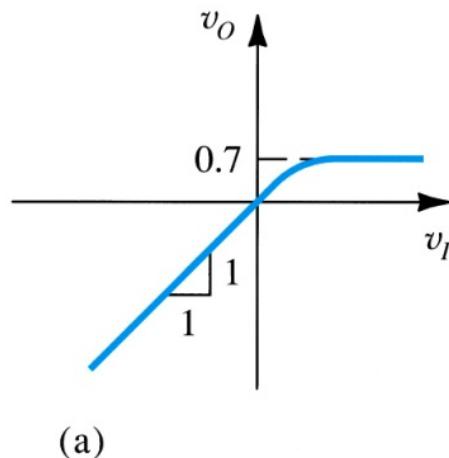

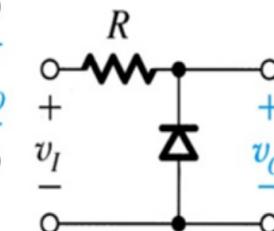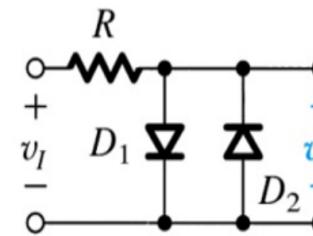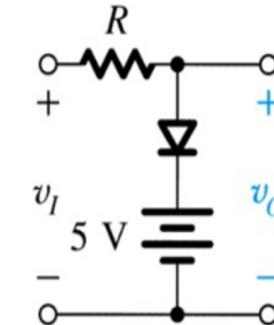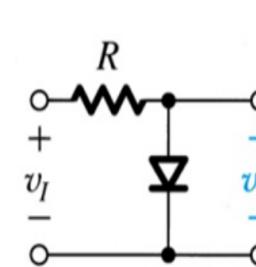Which circuit will give the shown transfer characteristic?



Poll Everywhere

Start the presentation to see live content. Still no live content? Install the app or get help at PollEv.com/app

Answers:
Top-left = a
Top right = d
Bottom left = c
Bottom right = b




Lecture 2

1. Diode Fundamentals & Models
2. Diode Circuits & Applications
3. **Small Signal Analysis**

Diode Analysis – Small Signals

STEADY STATE AC ANALYSIS

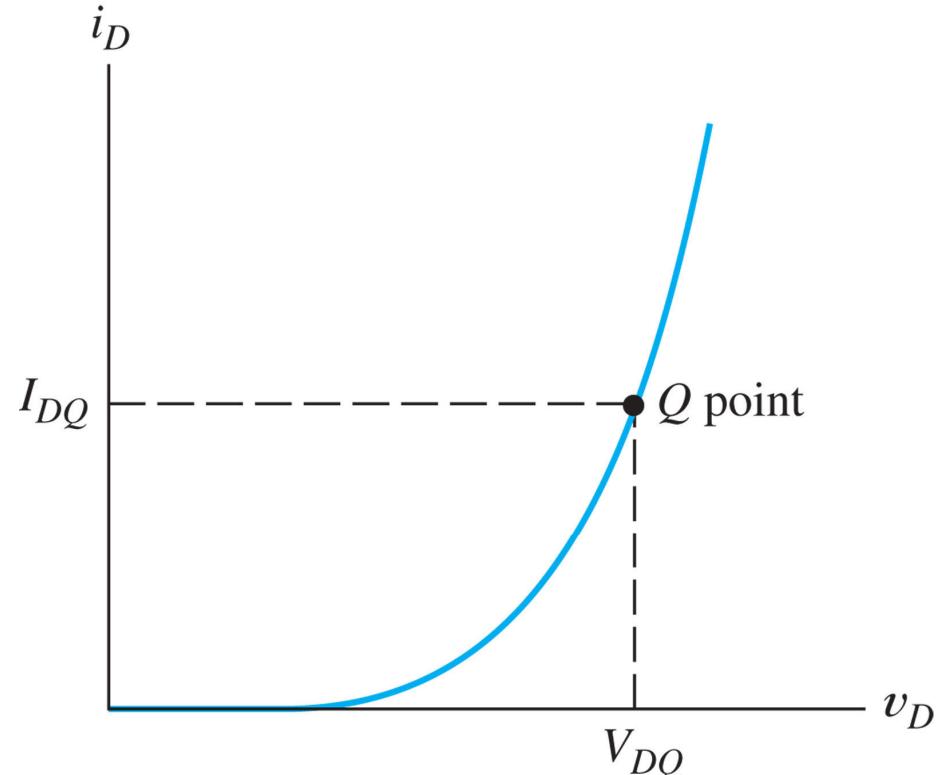- So far we analysed the diode circuits in the time domain
- We calculated and plotted instantaneous voltages and currents
- We applied dc voltages (or currents) to the diodes and found the operating points (Q point)
- Q stands for quiescent (i.e. quiet or no- signal point)




If the Q point is known (using the nonlinear diode characteristic), the linear ac analysis method can be applied to find the response to small (ac) signals.

Diode Analysis – Small Signals



MACQUARIE
University

CURRENT AND VOLTAGE NOTATION

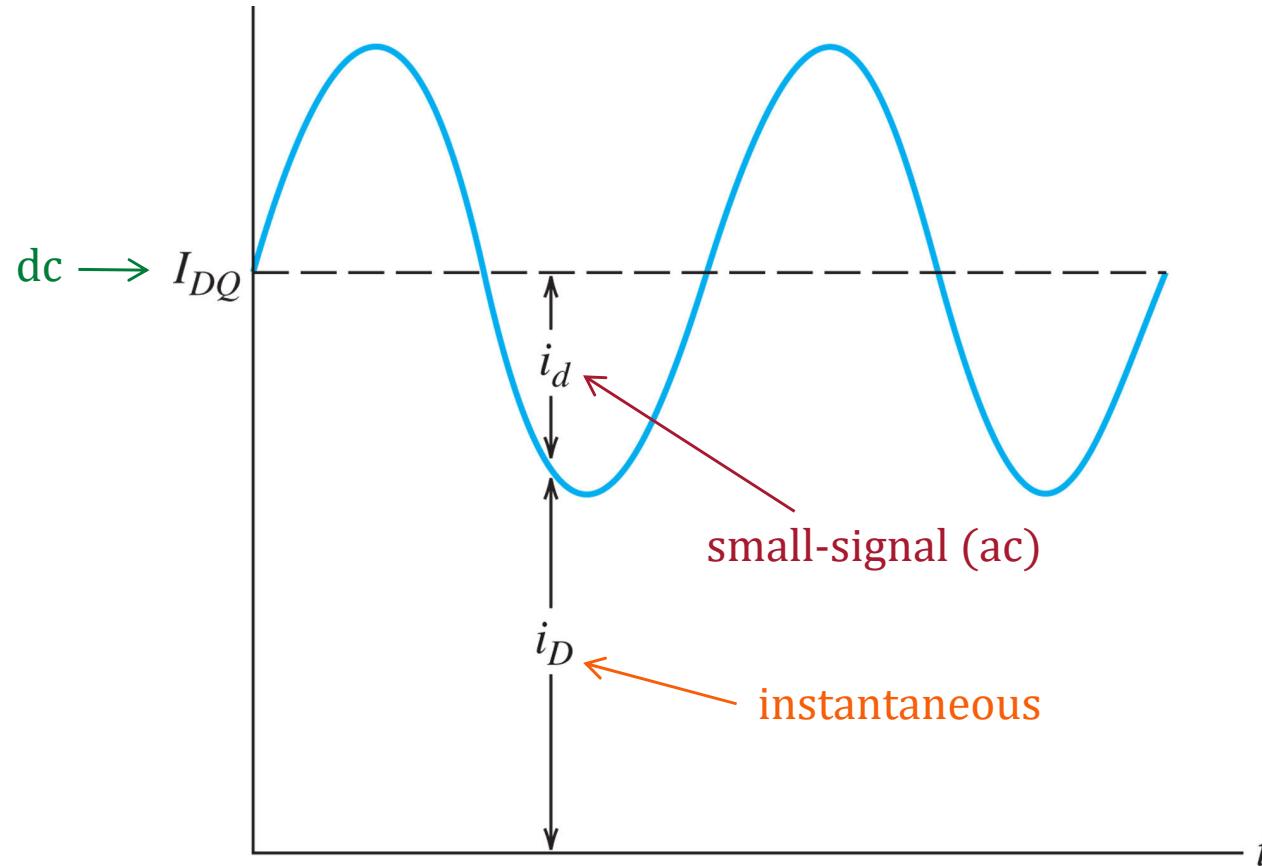

$$i_D(t) = I_{DQ} + i_d(t)$$


$$i_d(t) = I_d \cos(2\pi ft - 90^\circ)$$

Diode Analysis – Small Signals



MACQUARIE
University

SMALL SIGNAL DIODE MODEL

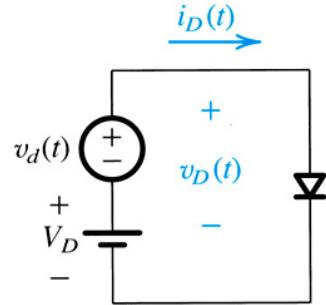

dc small-signal (ac)

$$v_D(t) = V_D + v_d(t)$$

$$i_D(t) = I_D + i_d(t)$$

The exponential diode characteristic in the forward region:

$$i_D = I_S e^{v_D/nV_T} = I_S e^{(V_D+v_d)/nV_T} = I_S e^{V_D/nV_T} e^{v_d/nV_T}$$

$$i_D = I_D e^{v_d/nV_T}$$

$$\underbrace{I_S e^{V_D/nV_T}}_{I_D}$$


Taylor series approximation:

$$e^x \cong 1+x, \text{ with } x \ll 1$$

$$\text{if } \frac{v_d}{nV_T} \ll 1 \rightarrow i_D \cong I_D \left(1 + \frac{v_d}{nV_T} \right) = I_D + \frac{I_D}{nV_T} v_d = I_D + i_d$$

$$\text{So } i_d = \frac{I_D}{nV_T} v_d$$
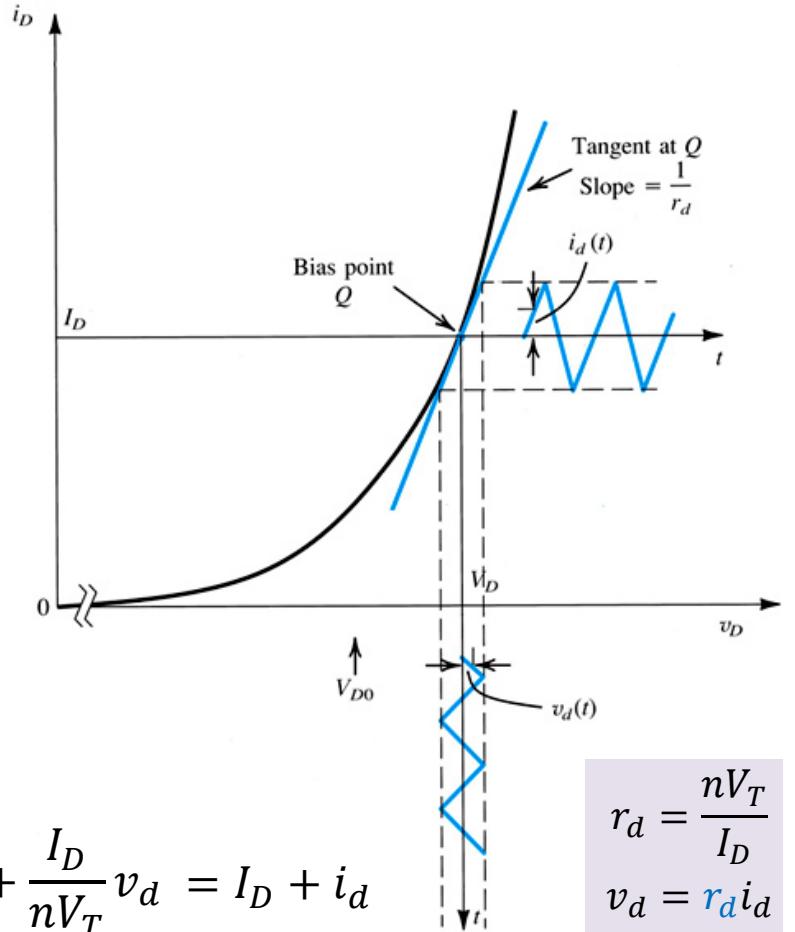
$$i_d = \frac{v_d}{r_d} \quad \text{Linear!}$$



$$r_d = \frac{nV_T}{I_D}$$

$$v_d = r_d i_d$$

\uparrow
dynamic resistance

Diode Analysis – Small Signals



MACQUARIE
University

EXAMPLE 1

Calculate the dynamic resistance of a junction diode having $n = 1$ at a temperature of 300 K for $I_{DQ} = 0.1 \text{ mA}$ 1 mA 10 mA

We know $r_d = \frac{V_T}{I_{DQ}}$

take V_T at 300K to be

$$25 \text{ mV}$$

$$\therefore \text{if } I_{DQ} = 0.1 \text{ mA}, r_d = 250 \Omega$$

$$I_{DQ} = 1 \text{ mA}, r_d = 25 \Omega$$

$$I_{DQ} = 10 \text{ mA}, r_d = 2.5 \Omega$$

Does the dynamic resistance increase or decrease as the current increases?

Increases



Decreases



Poll Everywhere

Start the presentation to see live content. Still no live content? Install the app or get help at PollEv.com/app

Answer: r_d decreases as I_{DQ} increases


Diode Analysis – Small Signals




MACQUARIE
University

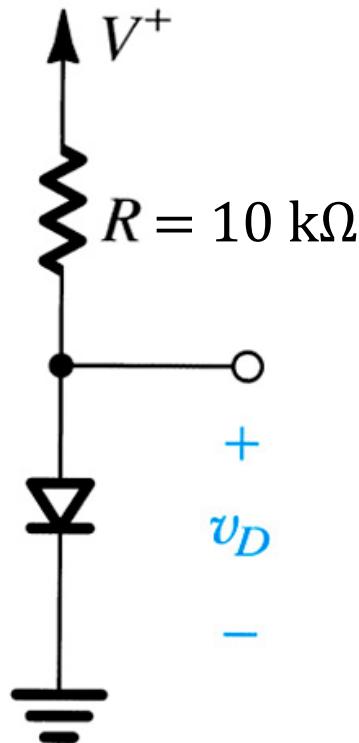EXAMPLE 2 – VOLTAGE REGULATOR

The power supply of the circuit below has a dc value of +10V and a ripple of 1V. Calculate the dc voltage of the diode and its variation caused by the power supply ripple. Assume the diode to have 0.7V drop at 1 mA current and $n = 1$.



Step 1: find the DC operating point

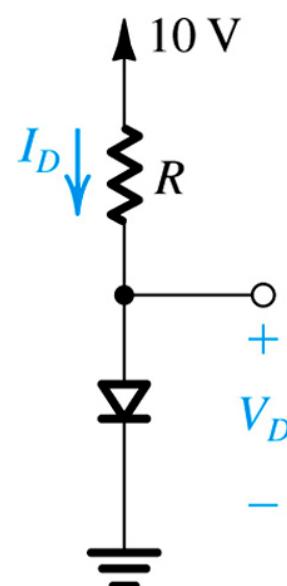

$$I_D = \frac{10 - 0.7}{10 \text{ k}\Omega}$$

$$I_D = 0.93 \text{ mA}$$

Step 2: calculate r_d

$$r_d = \frac{n \sqrt{kT}}{I_D}$$

$$r_d = 26.9 \text{ }\mu\text{A}$$


resistance around operating point

Now we just have potential dividers

$$v_d = V_s \frac{r_d}{R + r_d} = 2.68 \text{ mV}$$

Where V_s is the 1V ripple voltage (the 'small signal')

Step 3: ac equivalent circuit

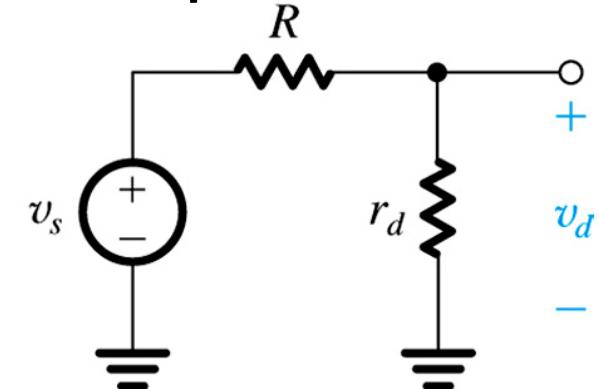

Preparation for Lab 1



LTSPICE AND ANALOG DISCOVERY 2

Preparation before the lab:

- The worksheet has been available for several days now
- Do at least the pre-lab section before coming to the timetabled support session
- Record your worksheet answers in a digital logbook and upload individual answers to the iLearn submission before 11:55pm on the day of the timetabled lab session