




MACQUARIE
University

ELEC2005

Electrical and Electronic Systems


BIPOLAR JUNCTION TRANSISTORS – PART 1

DAVID PAYNE

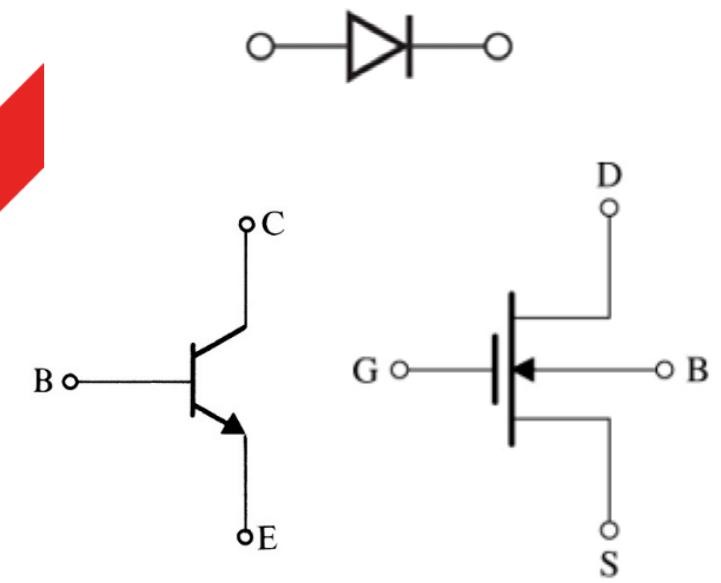

In Today's Lecture

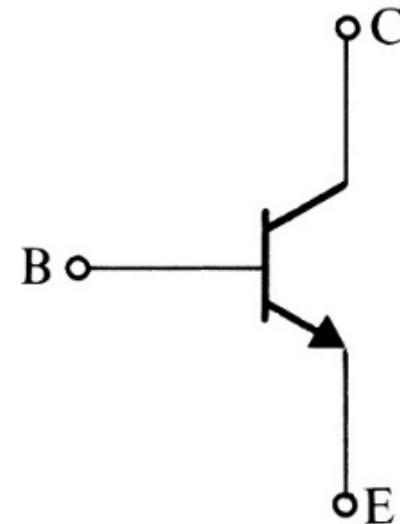
- Introduction to bipolar junction transistors (BJTs)
- BJTs in circuits
 - ❖ Device structure and circuit symbol
 - ❖ Modes of operation
 - ❖ Circuit models



Mini Quiz Review



MACQUARIE
University

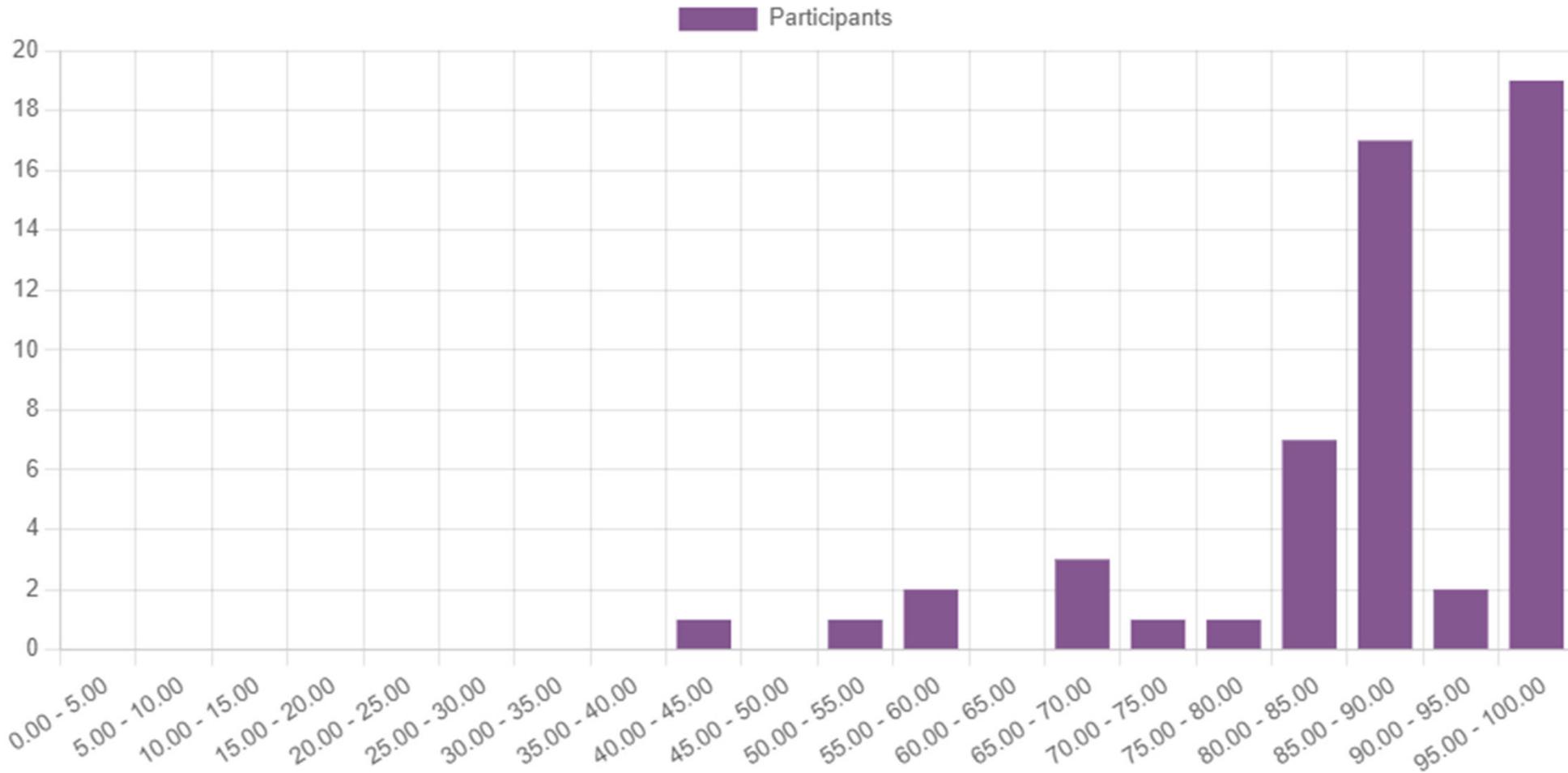



Lecture 3

- 1. BJT Device Structure**
- 2. BJT Modes of Operation**
- 3. BJT Models**

The Bipolar Junction Transistor



MACQUARIE
University

DIAGRAMS AND CIRCUIT SYMBOLS



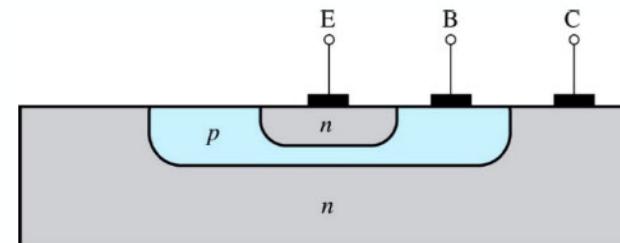


Diagram of physical npn BJT on wafer

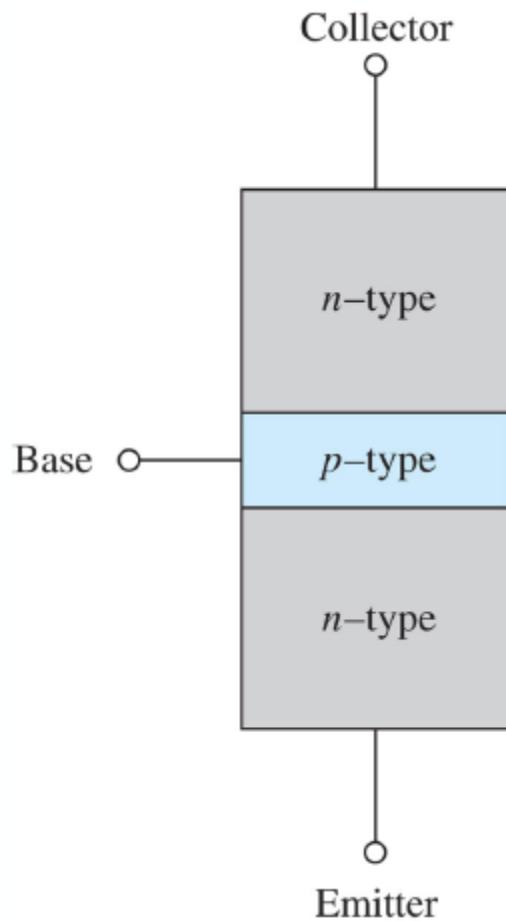


The Bipolar Junction Transistor

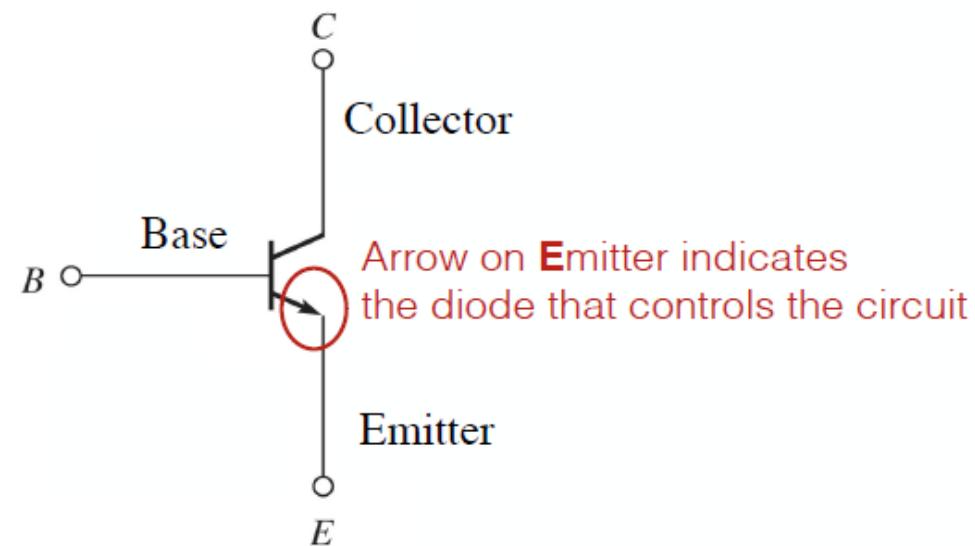

MACQUARIE
University

THE PIPE ANALOGY

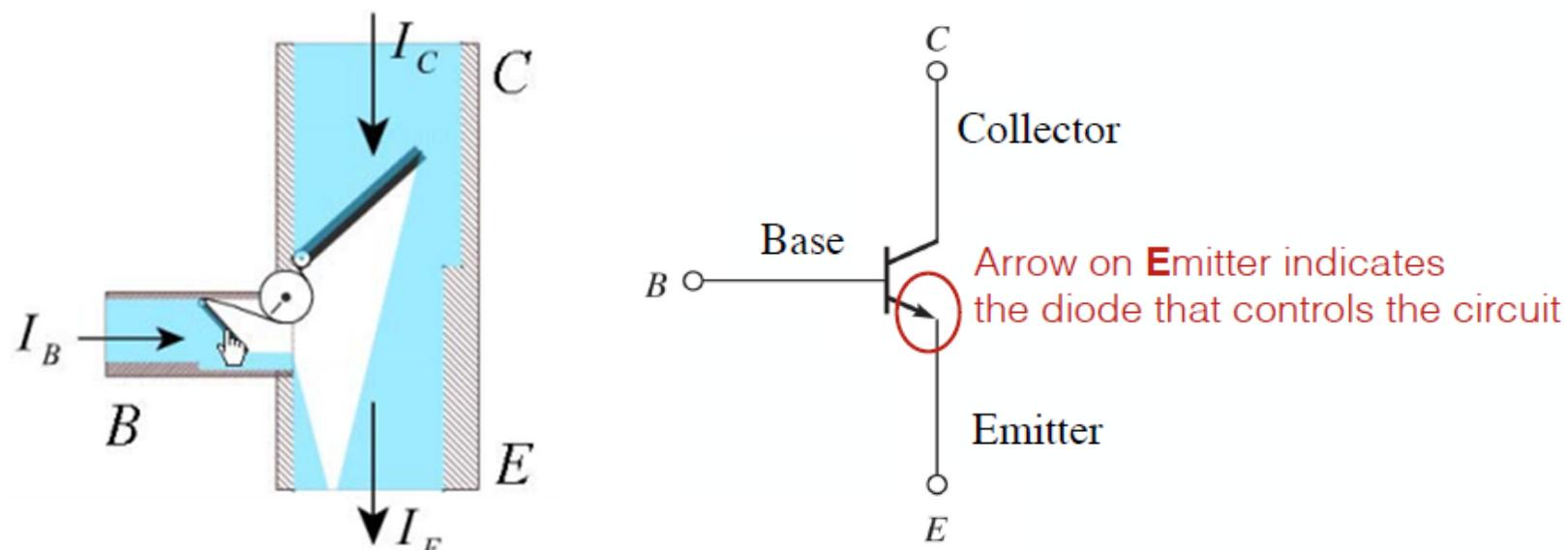- In the pipe analogy (AKA hydraulic analogy):
- Electric potential is equivalent to pressure. i.e. voltage is equivalent to the difference in pressure between two points
- A BJT is essentially a controlled valve, with the flow of water at the base pipe acting as the control. (not quite as straightforward as the ideal diode!)




The Bipolar Junction Transistor





MACQUARIE
University

DIAGRAMS AND CIRCUIT SYMBOLS: NPN / PNP

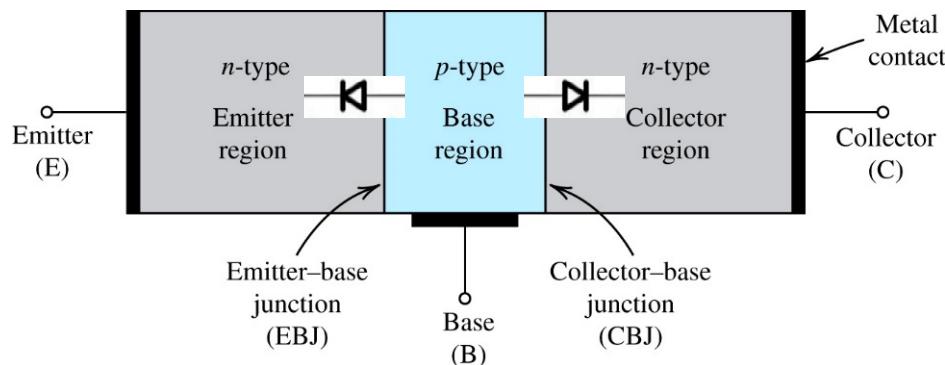- There are naturally two possible arrangements n-p-n or p-n-p



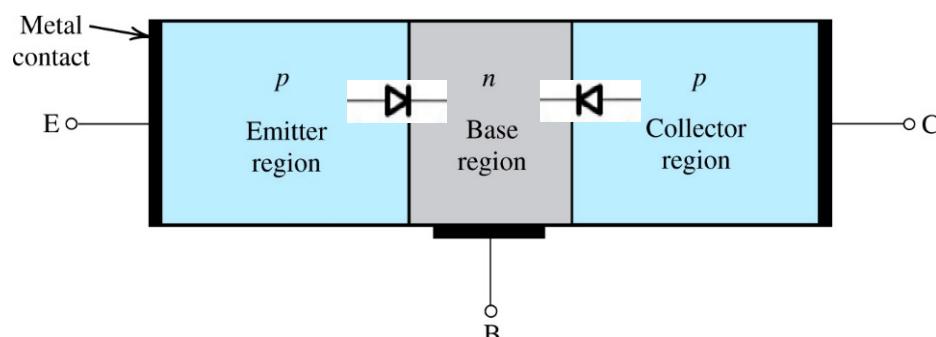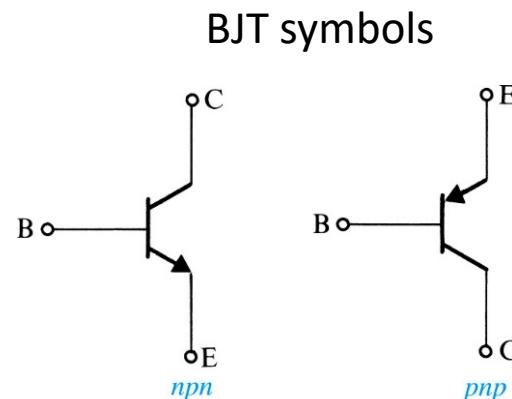A simplified structure of the **npn** transistor.



A simplified structure of the **pnp** transistor.


Arrows show the
current of controlling
pn-junction

The Bipolar Junction Transistor




DIAGRAMS AND CIRCUIT SYMBOLS: NPN / PNP

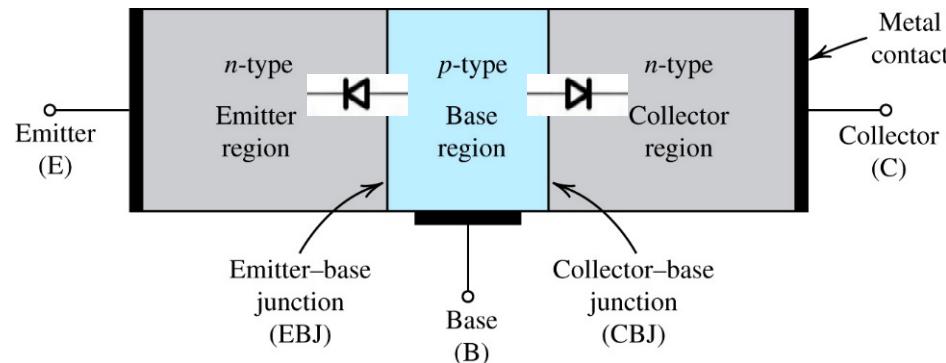- There are naturally two possible arrangements n-p-n or p-n-p




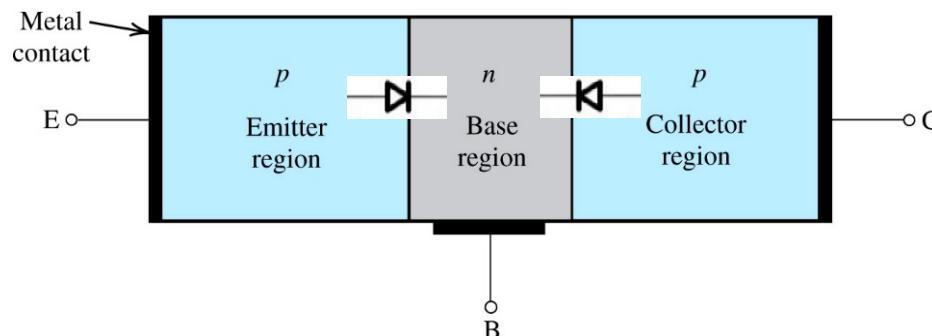A simplified structure of the **npn** transistor.



A simplified structure of the **pnp** transistor.

Which of these is a PNP transistor?

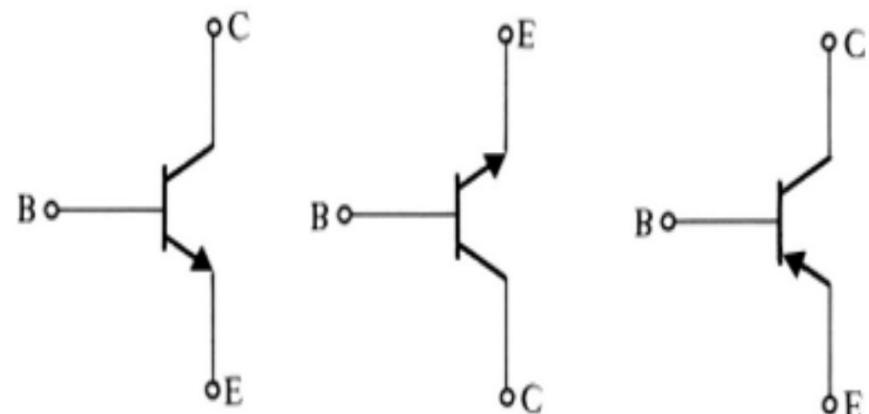


The Bipolar Junction Transistor




DIAGRAMS AND CIRCUIT SYMBOLS: NPN / PNP

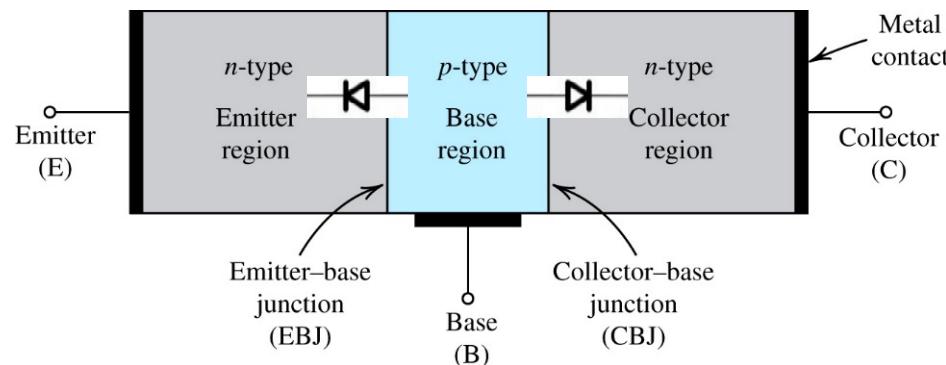- There are naturally two possible arrangements n-p-n or p-n-p




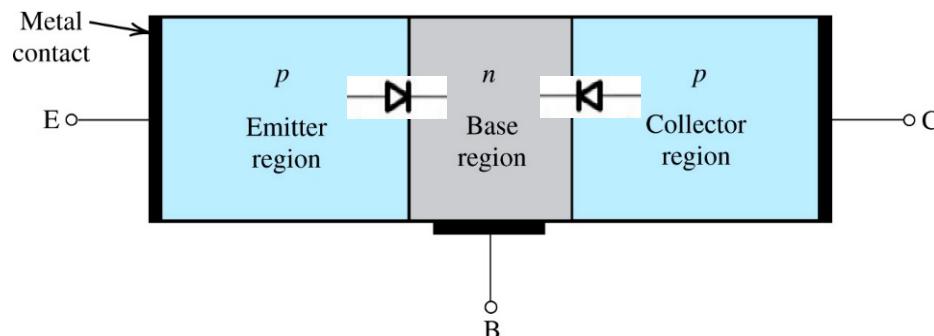A simplified structure of the **npn** transistor.



A simplified structure of the **pnp** transistor.

Which of these is a PNP transistor?

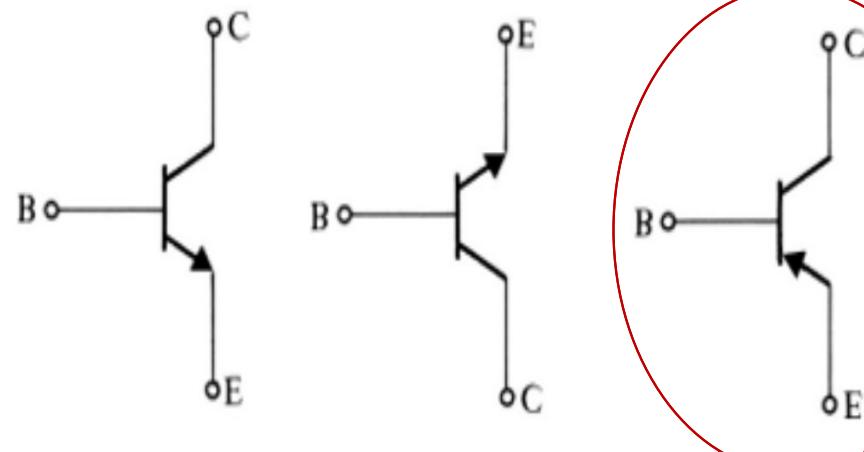



Lecture 3

1. BJT Device Structure
2. **BJT Modes of Operation**
3. BJT Models

The Bipolar Junction Transistor



MACQUARIE
University

MODES OF OPERATION


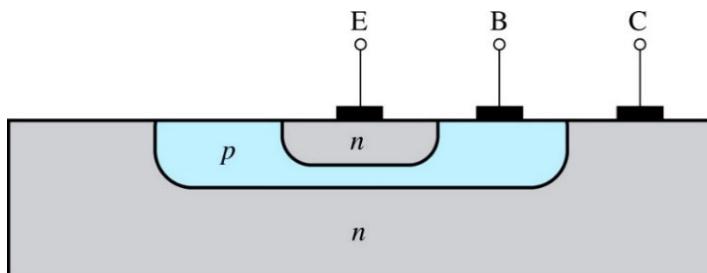
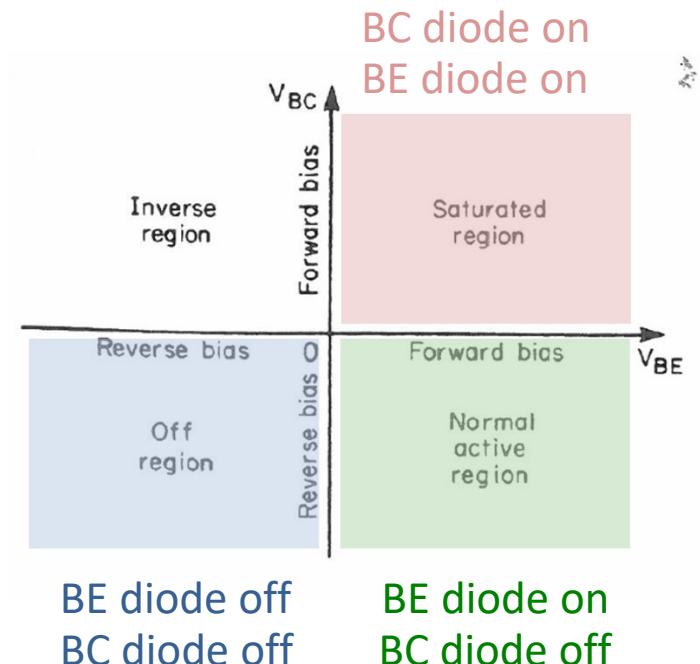


Diagram of physical npn BJT on wafer

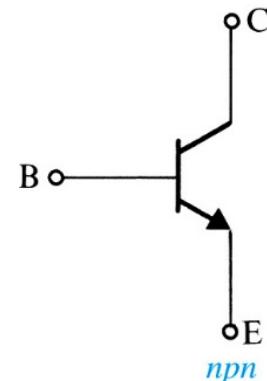

Operating mode depends on dc biasing or large signal voltages and currents:

- **active** mode – used for ac amplification
- **cutoff** and **saturation** modes – used for switching.
- BJT is not symmetrical – inverse region is not normally used

The Bipolar Junction Transistor



MACQUARIE
University

ACTIVE REGION

In Active region, BE = Forward biased, BC = Reverse biased

From Kirchoff: $i_E = i_C + i_B$

Base current is much smaller than collector current

We define:

$$i_C = \beta i_B$$

$$i_C = \alpha i_E \quad \alpha = \frac{\beta}{\beta+1}$$



Typical value: $\beta=100$ $\alpha=0.9 - 0.99$

$$i_E = \left(\frac{I_S}{\alpha} \right) \left(e^{v_{BE}/V_T} - 1 \right) \approx \left(\frac{I_S}{\alpha} \right) e^{v_{BE}/V_T}$$

Base-emitter voltage controls the collector current!

$$i_B \approx \left(\frac{I_S}{\beta} \right) e^{v_{BE}/V_T}$$

$$i_C \approx I_S e^{v_{BE}/V_T}$$

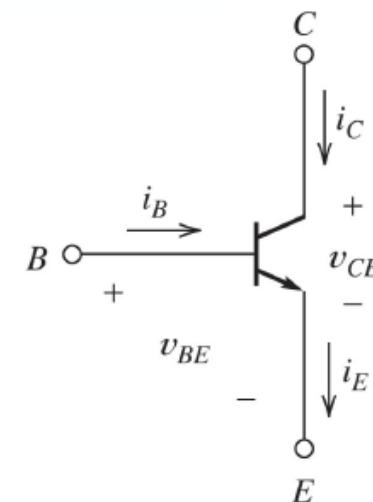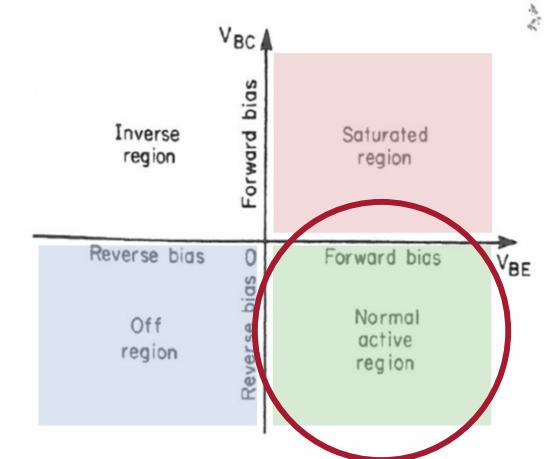

Emitter current is the total current.

$$i_E = i_B + i_C = \frac{i_C}{\alpha}$$

The Bipolar Junction Transistor



MACQUARIE
University

ACTIVE REGION

From Kirchhoff: $i_E = i_C + i_B$

Constant
(Saturation current)

Constant
(Thermal voltage)

From the diode equation:

$$i_C = I_s e^{v_{BE}/V_T}$$

Base current is much smaller
than collector current



$$i_B = \frac{i_C}{\beta} = \frac{I_s}{\beta} e^{v_{BE}/V_T}$$

common-emitter current
gain

Emitter current is the total
current.

$$i_E = i_B + i_C = \frac{i_C}{\alpha}$$

emitter injection
efficiency

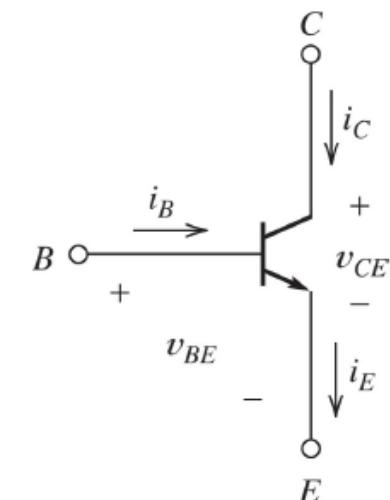
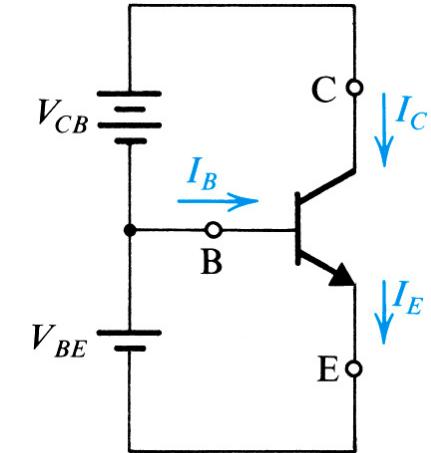


The Bipolar Junction Transistor



ACTIVE MODE – EQUIVALENT CIRCUIT

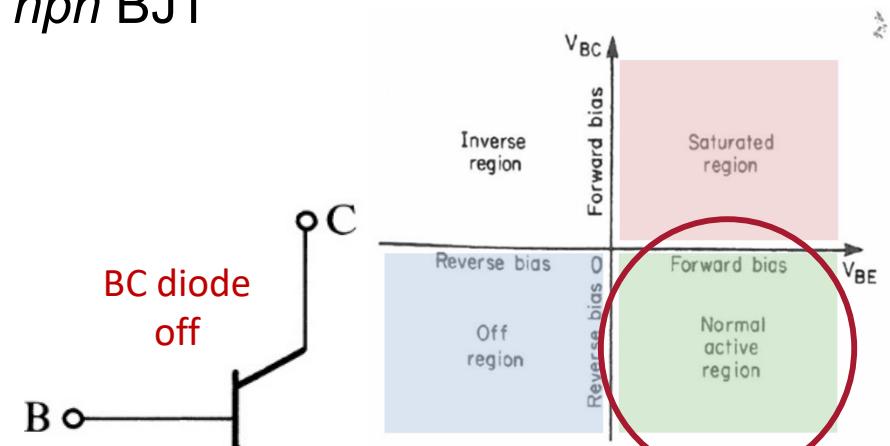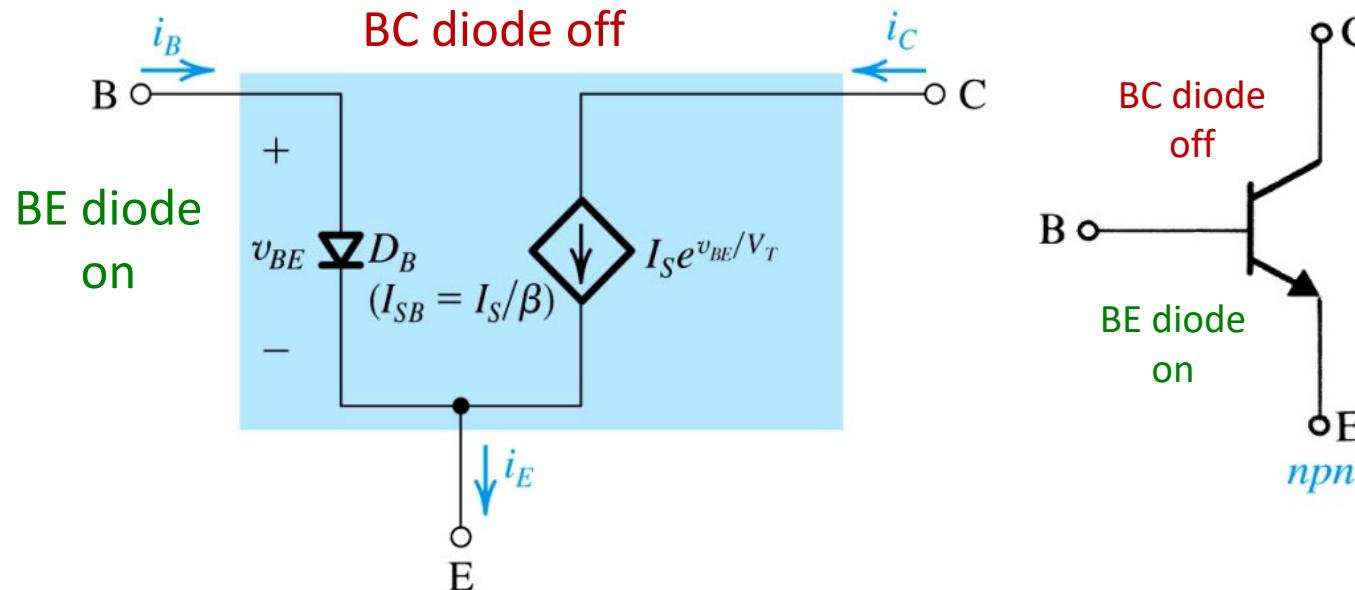Large-signal equivalent-circuit model of the *npn* BJT operating in the **forward active mode**.




The Bipolar Junction Transistor



MACQUARIE
University

ACTIVE MODE – EQUIVALENT CIRCUIT

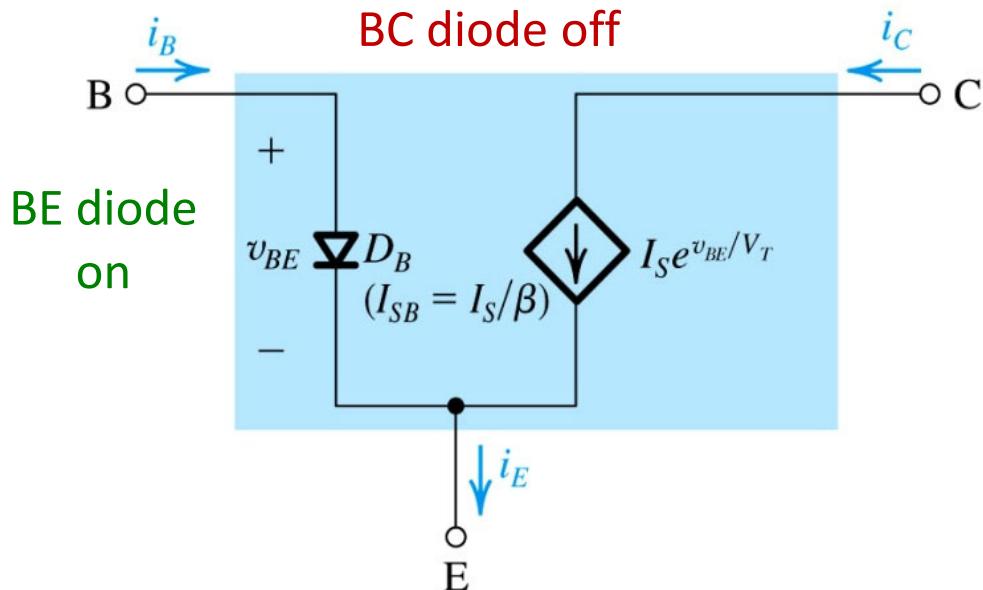Large-signal equivalent-circuit model of the *npn* BJT operating in the **forward active mode**.



Collector current is controlled by the base-emitter voltage:


$$i_C = I_S e^{v_{BE}/V_T}$$

Base current is much smaller than the collector current:

$$i_B = \frac{i_C}{\beta}$$

Emitter current is total current:

$$i_E = i_B + i_C = \frac{i_C}{\alpha}$$

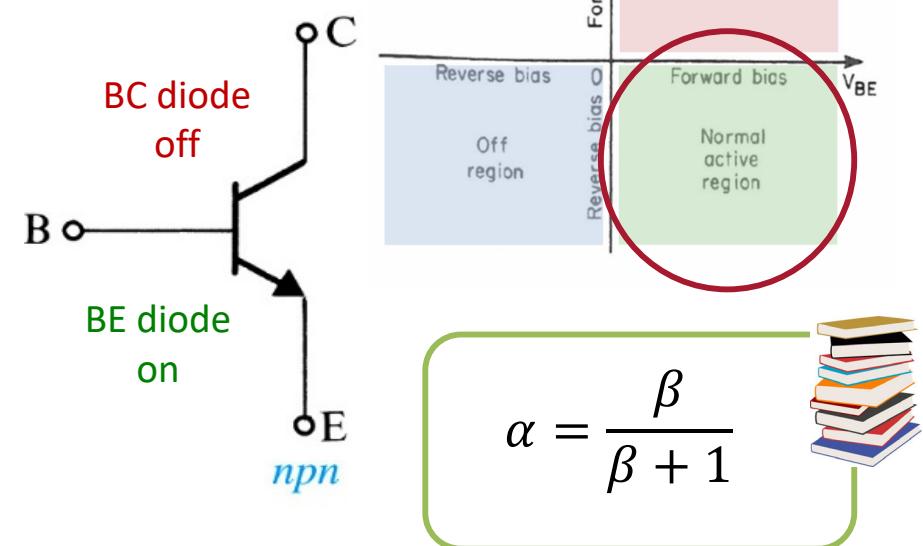




The Bipolar Junction Transistor



MACQUARIE
University

SATURATION REGION

npn BJT in saturation:

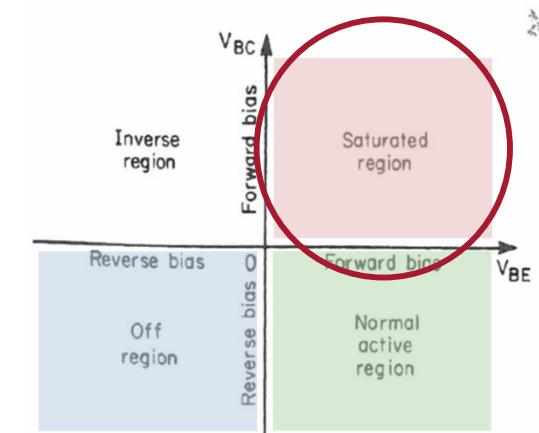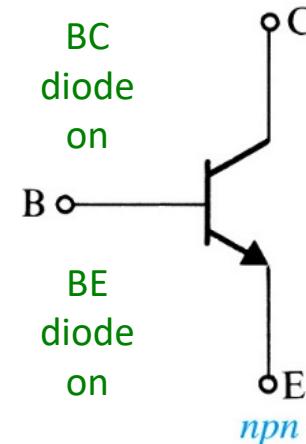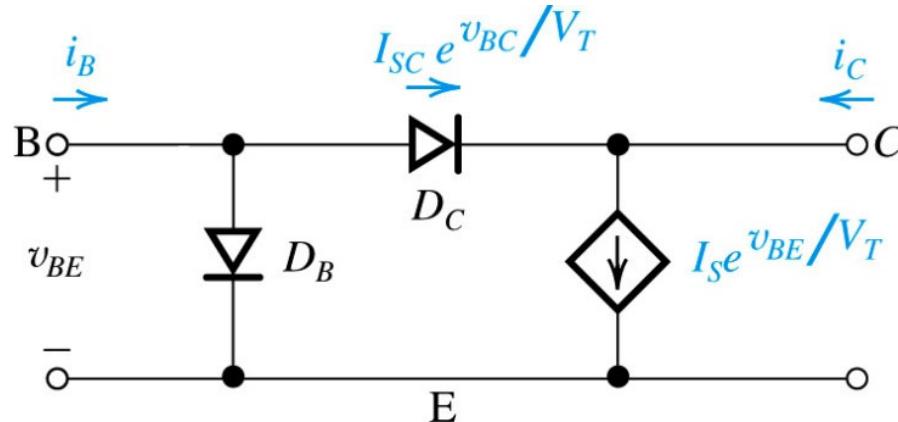




The Bipolar Junction Transistor



MACQUARIE
University

SATURATION REGION

npn BJT in saturation:

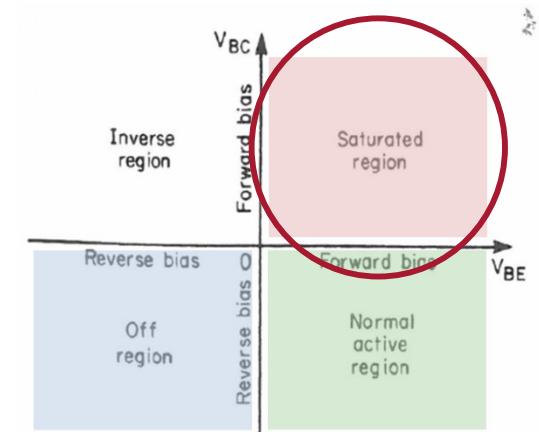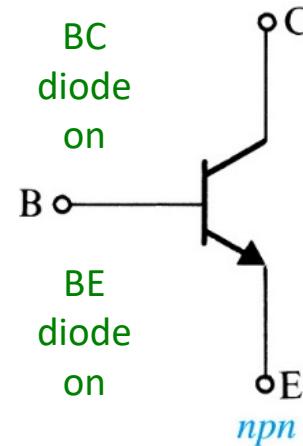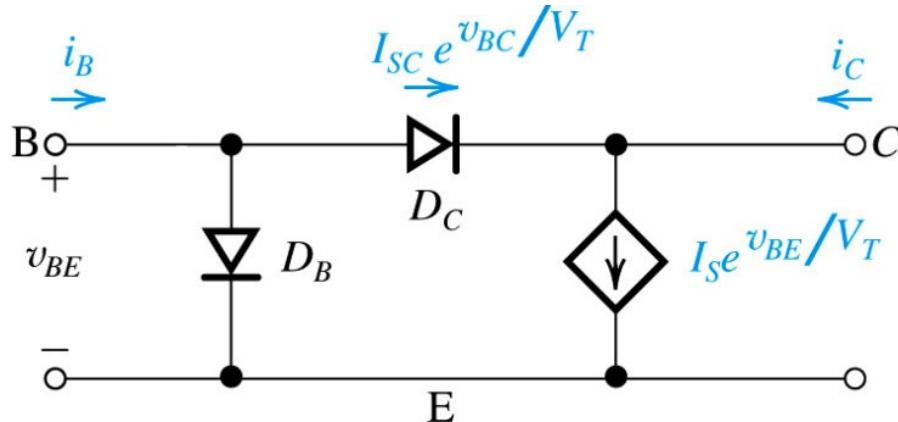

$$i_C = I_S e^{v_{BE}/V_T} - I_{SC} e^{v_{BC}/V_T}$$

$$i_B = \frac{I_S}{\beta} e^{v_{BE}/V_T} + I_{SC} e^{v_{BC}/V_T}$$


$$\beta_{forced} = \frac{i_C}{i_B} \text{ (at saturation)} \leq \beta$$

Class Exercise

Find i_B

For an npn BJT in the active mode, saturation current $I_s = 1\text{pA}$, $v_{BE} = 0.6V$, $\beta = 260$ at room temperature.

Find the base current, i_B

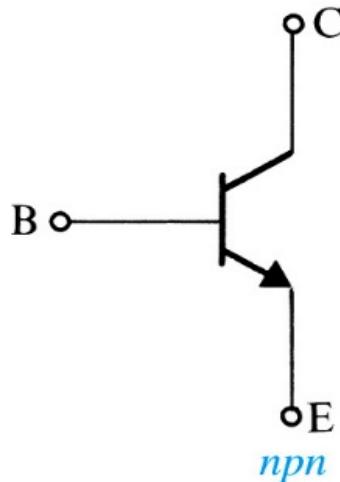

What is the value of the base current?


- 0.1 mA
- 0.5 mA
- 1 mA
- 26 mA

Class Exercise

Find i_B

For an npn BJT in the active mode, saturation current $I_s = 1\text{pA}$, $v_{BE} = 0.6V$, $\beta = 260$ at room temperature.

Find the base current, i_B

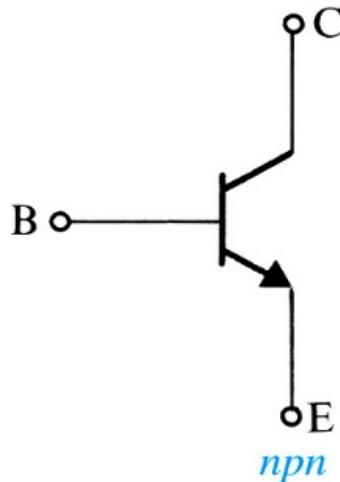

What is the value of the base current?

0.1 mA 0%

0.5 mA 0%

1 mA 0%

26 mA 0%


Start the presentation to see live content. For screen share software, share the entire screen. Get help at pollev.com/app

The Bipolar Junction Transistor




MACQUARIE
University

LOAD LINE ANALYSIS

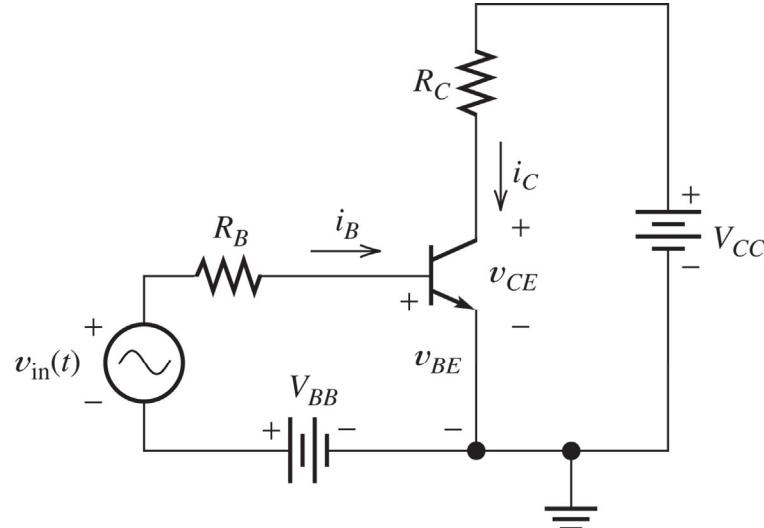


Base loop:

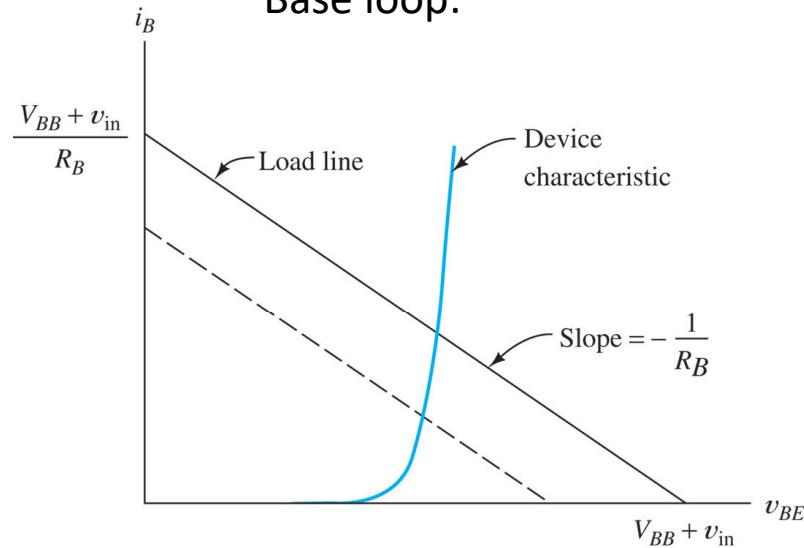

(a) Input load line (shifts to dashed line for a smaller value of v_{in})

Collector loop:

Saturation region

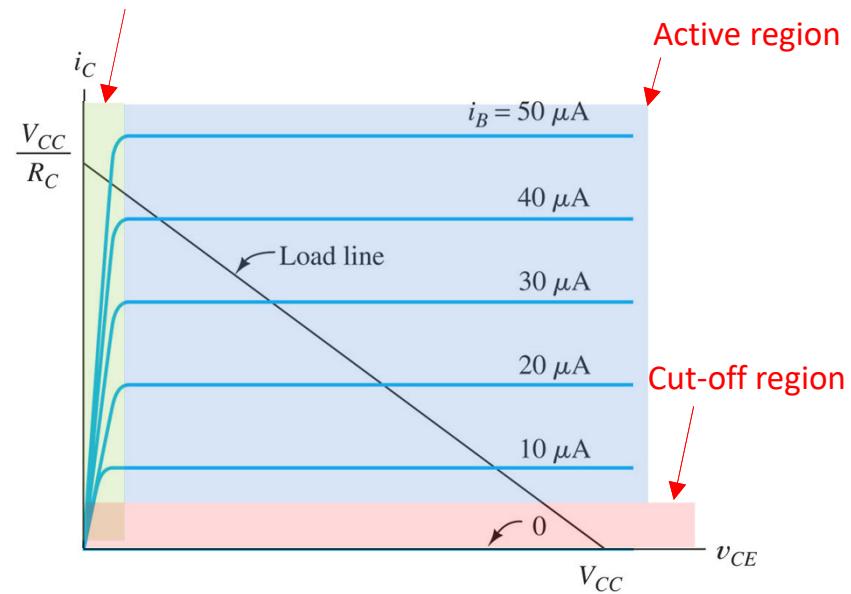


(b) Output

The Bipolar Junction Transistor




MACQUARIE
University

LOAD LINE ANALYSIS

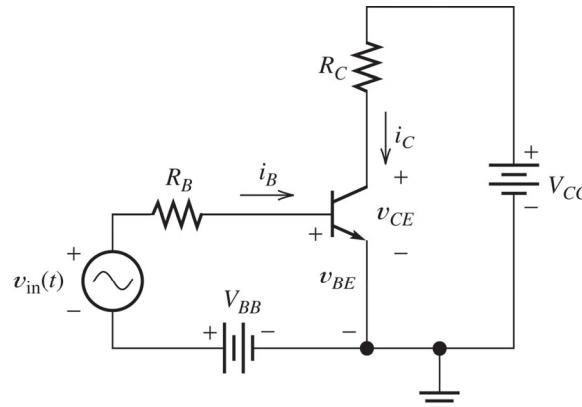


Base loop:

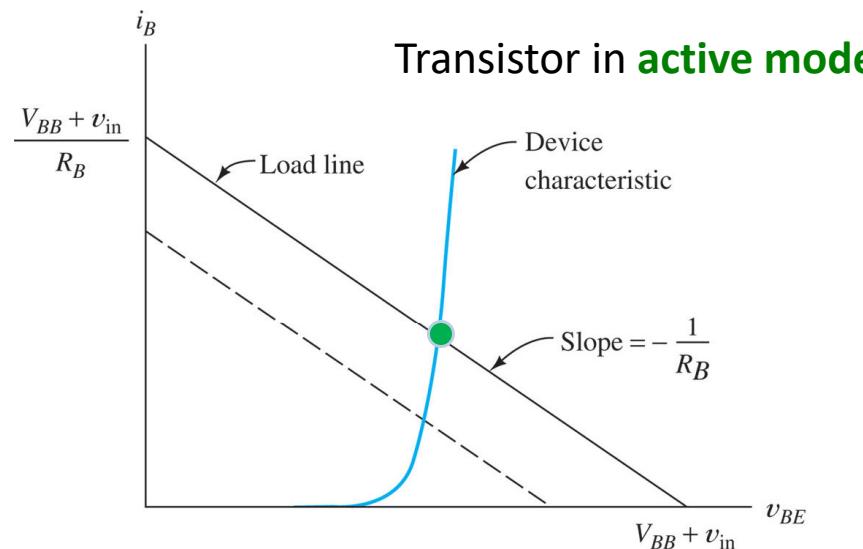

(a) Input load line (shifts to dashed line for a smaller value of v_{in})

Collector loop:

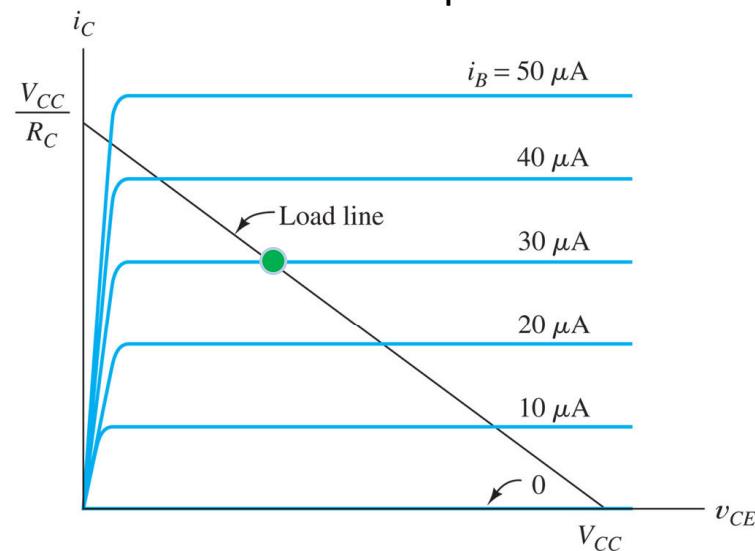

(b) Output


The Bipolar Junction Transistor




MACQUARIE
University

LOAD LINE ANALYSIS

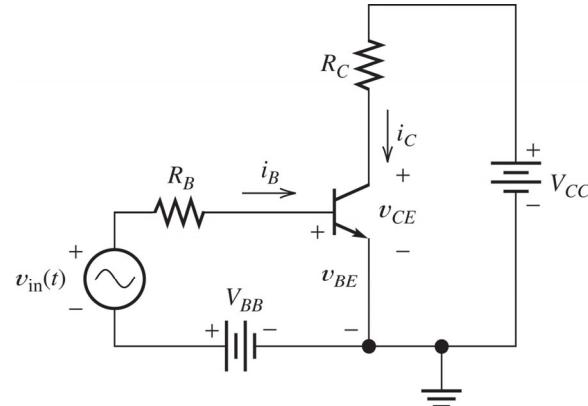If the base current is too high we reach saturation




Base loop:

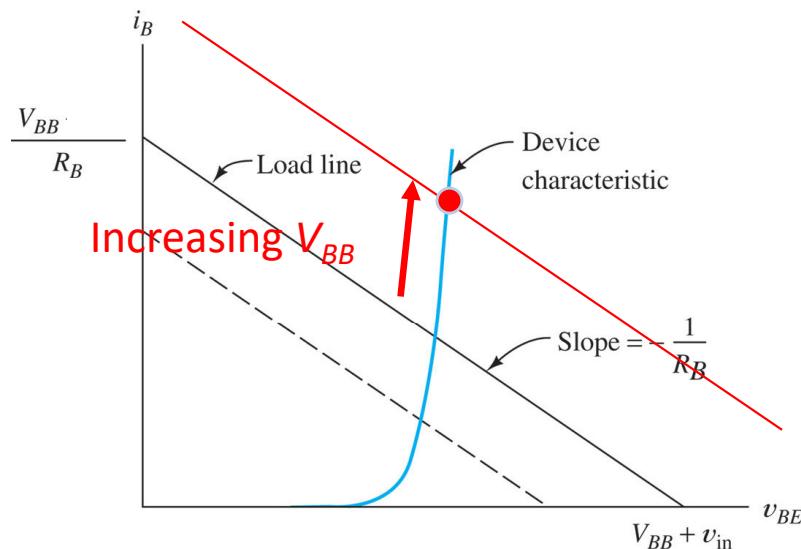

(a) Input load line (shifts to dashed line for a smaller value of v_{in})

Collector loop:

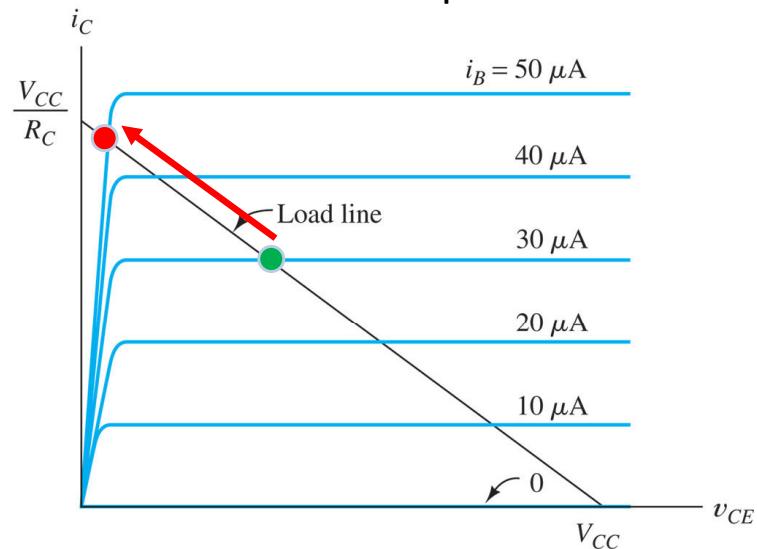

(b) Output



The Bipolar Junction Transistor



MACQUARIE
University


LOAD LINE ANALYSIS

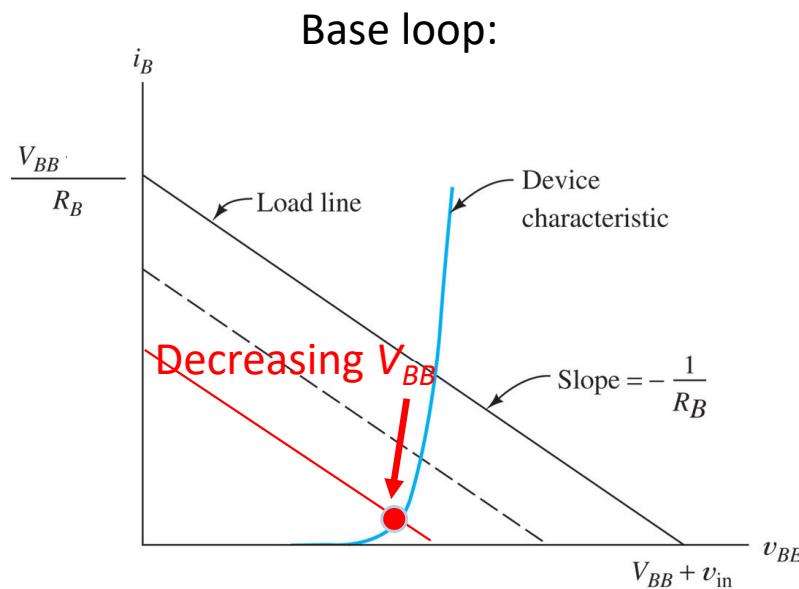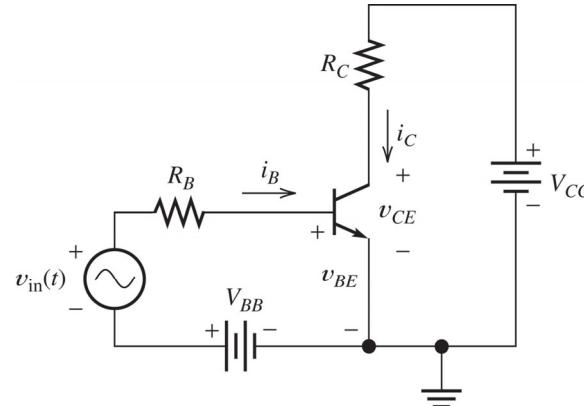If the base current is too low we reach cut-off



(a) Input load line (shifts to dashed line for a smaller value of v_{in})

Collector loop:

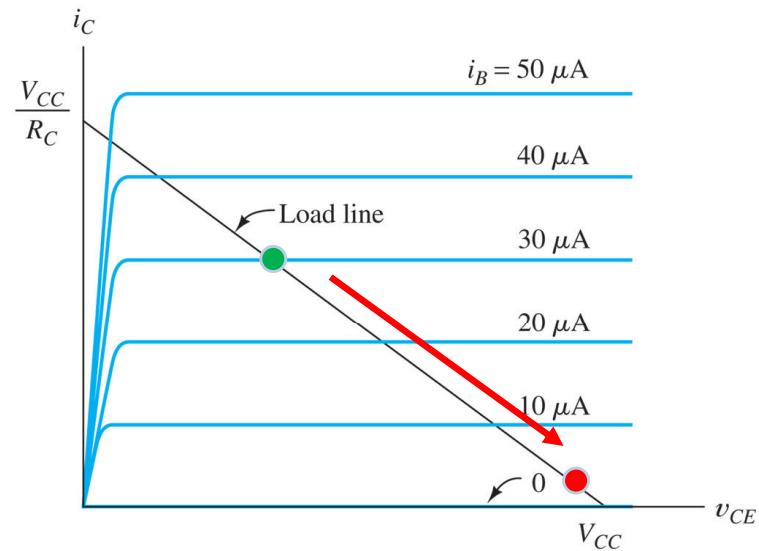

(b) Output

The Bipolar Junction Transistor



MACQUARIE
University

LARGE SIGNALS CURRENT SUMMARY

$$V_{CE} > 0 \quad V_A = \infty \quad V_T = \frac{kT}{q} \cong 25 \text{ mV at room temperature}$$

On the formula sheet!

V_{BE}	V_{BC}	$V_{CE} (> 0)$	Mode	$I_C(V_{BE}, V_{CE})$
< 0.5	< 0.4	> 0	cut-off	$I_C \cong 0$
~0.7	> 0.4	< 0.3	saturation	$V_{CE} \cong 0.2 \quad \text{or}$ $I_C = I_S e^{V_{BE}/V_T} - I_{SC} e^{V_{CE}/V_T}$
~0.7	~0.4	~0.3	edge of saturation and active	$I_C = I_S e^{V_{BE}/V_T}$
~0.7	< 0.4	> 0.3	active	$I_C = I_S e^{V_{BE}/V_T}$

For pnp BJT use the same current equations but with reversed voltage polarities



Lecture 3




1. BJT Device Structure
2. BJT Modes of Operation
3. **BJT Models**

The Bipolar Junction Transistor



MACQUARIE
University

SUMMARY OF SIMPLE BJT MODELS

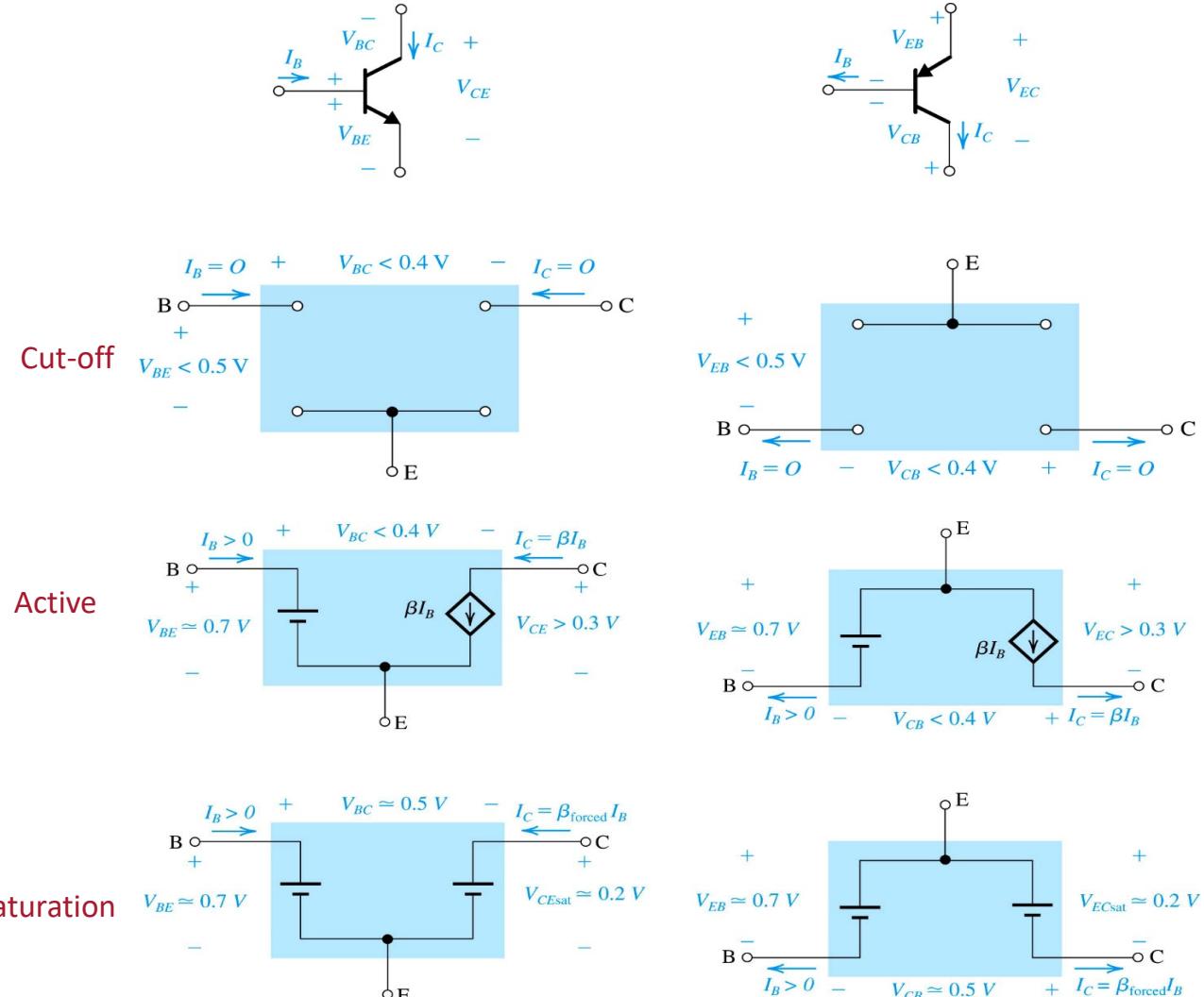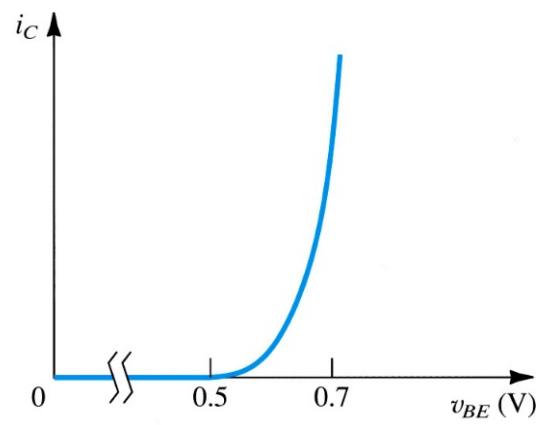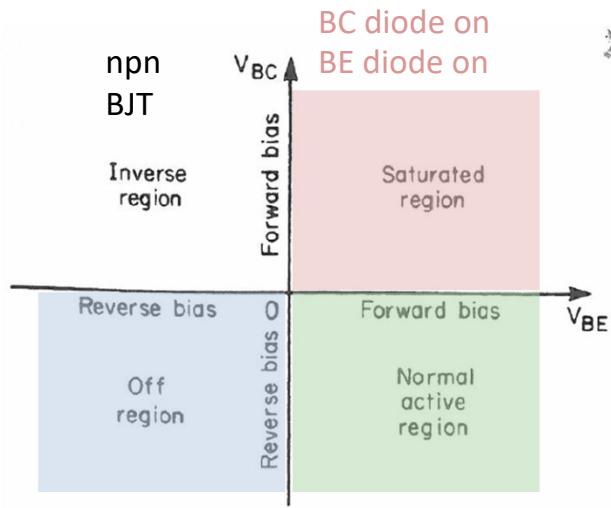

Remember these models are only approximate!




The Bipolar Junction Transistor



MACQUARIE
University

CONSTANT VOLTAGE DROP APPROXIMATION

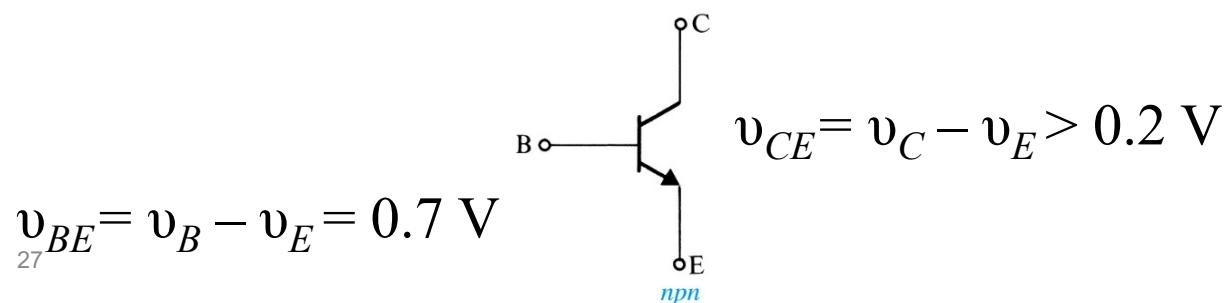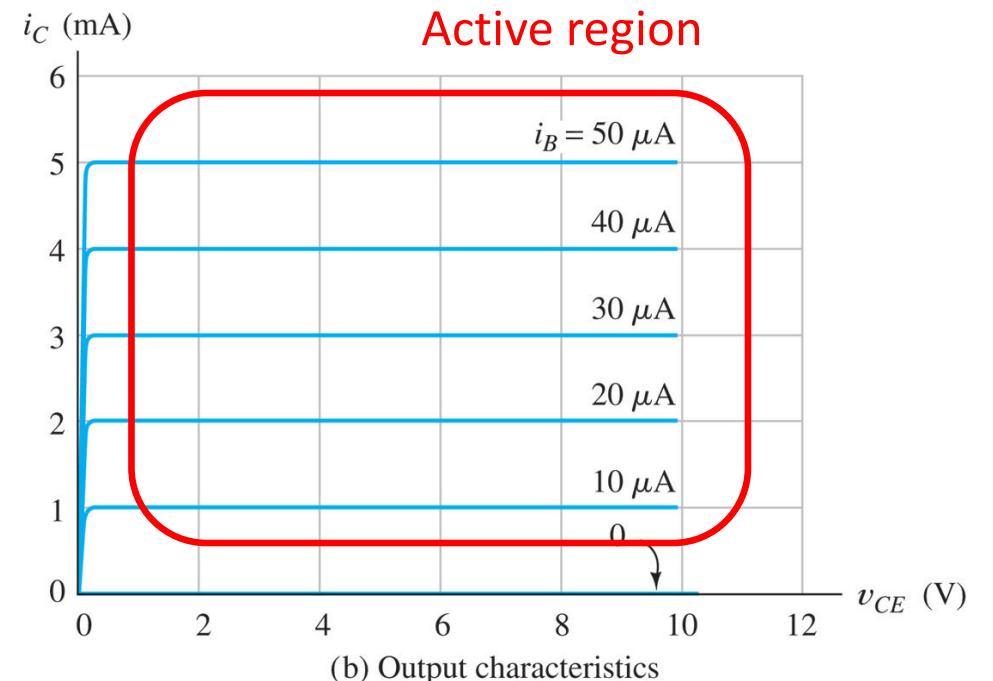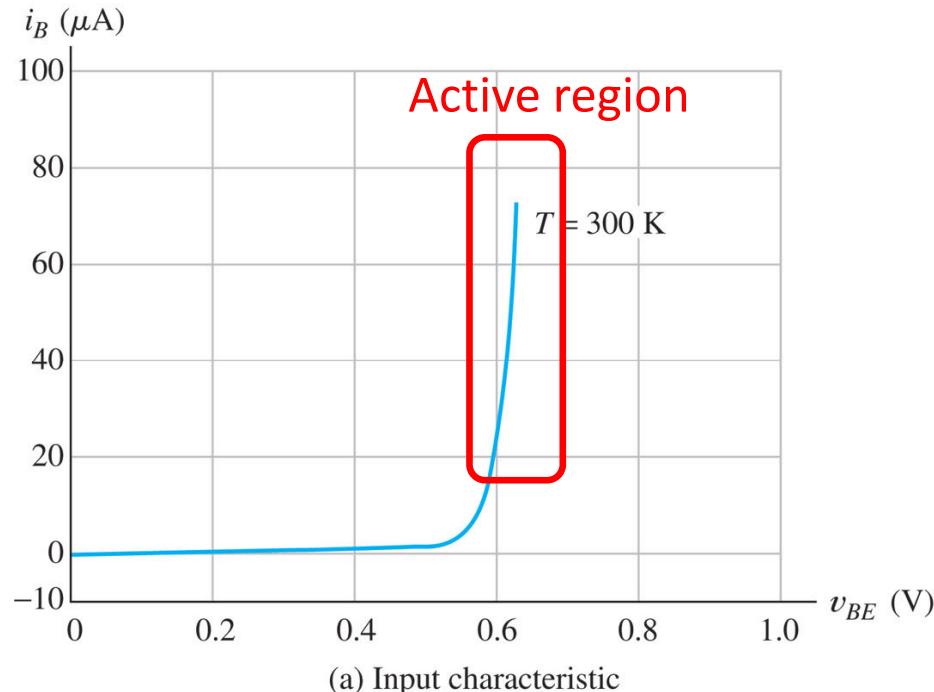In the active region we can use a constant voltage (base side) and constant current (collector side) approximation:



$$i_B = \frac{i_C}{\beta} \quad i_C = I_s e^{v_{BE}/V_T}$$
$$i_E = i_B + i_C = \frac{i_C}{\alpha}$$

The Bipolar Junction Transistor




MACQUARIE
University

EXAMPLE-1

Use the constant voltage drop model:

$V_{BE} = 0.7 \text{ V}$ when BE diode is on.

Is BE diode ON
in this circuit?

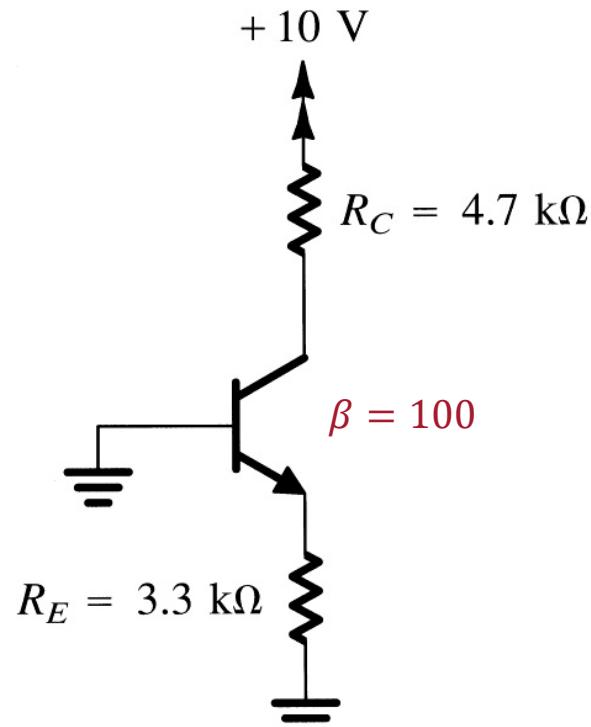

(a)

The Bipolar Junction Transistor




MACQUARIE
University

EXAMPLE-1


Use the constant voltage drop model:

$V_{BE} = 0.7 \text{ V}$ when BE diode is on

Is BE diode *ON*
in this circuit?

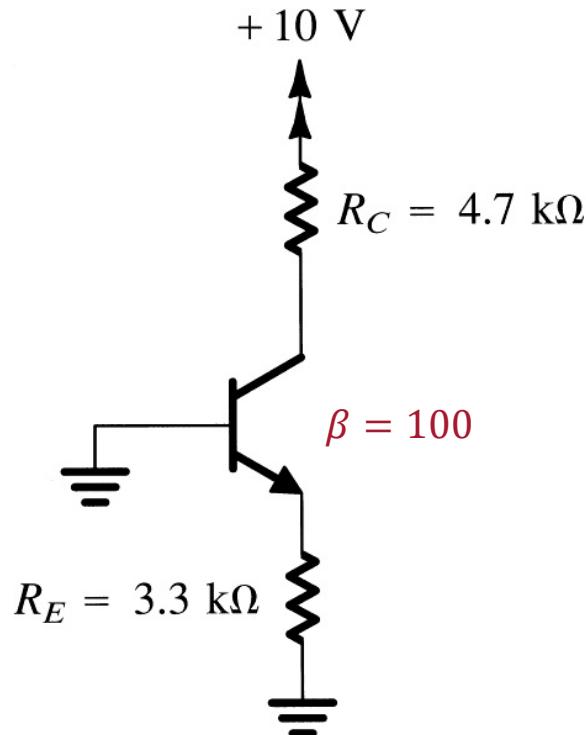

(a)

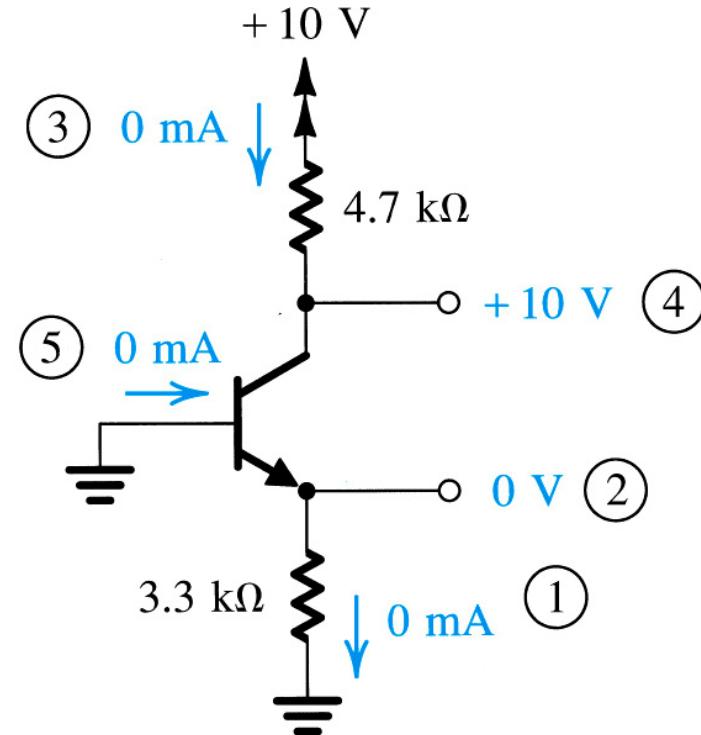

(b)

The Bipolar Junction Transistor





MACQUARIE
University

EXAMPLE-1 – CUT-OFF

That was an example of cut-off

Operating in this region:

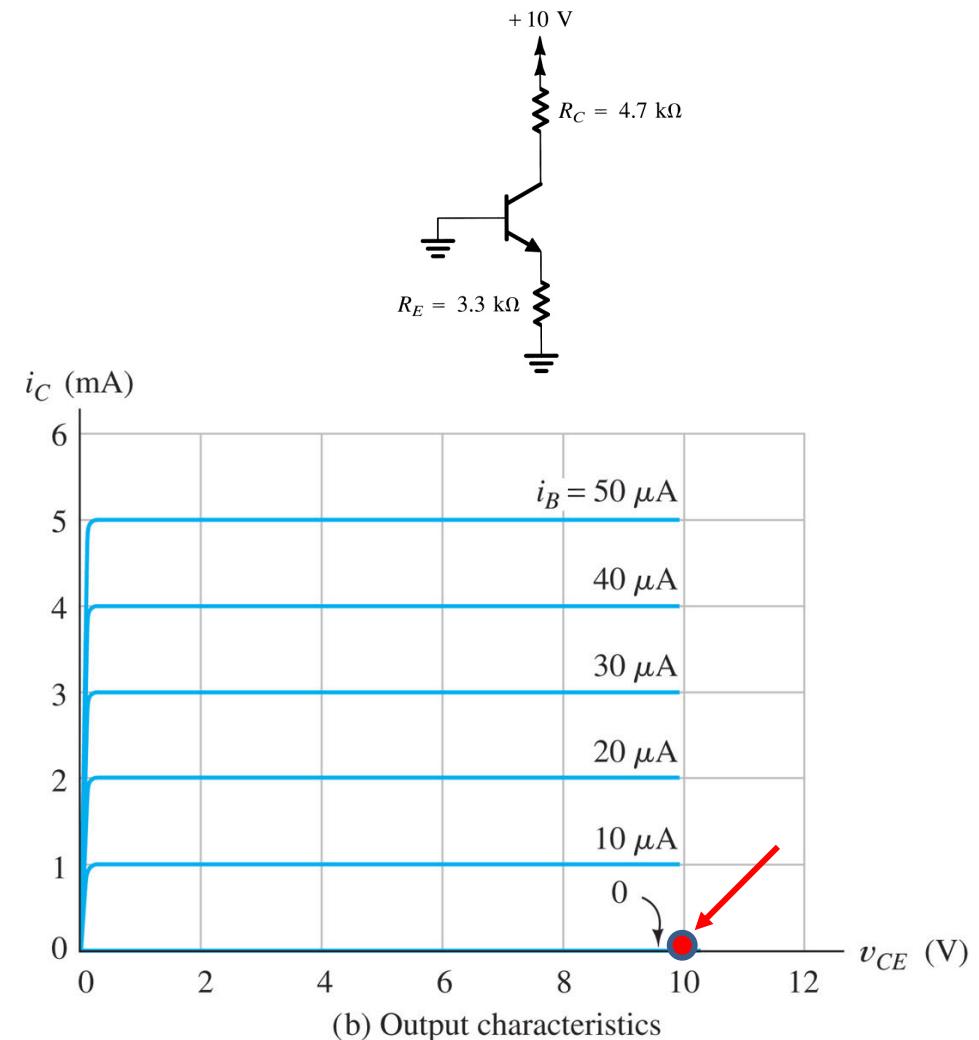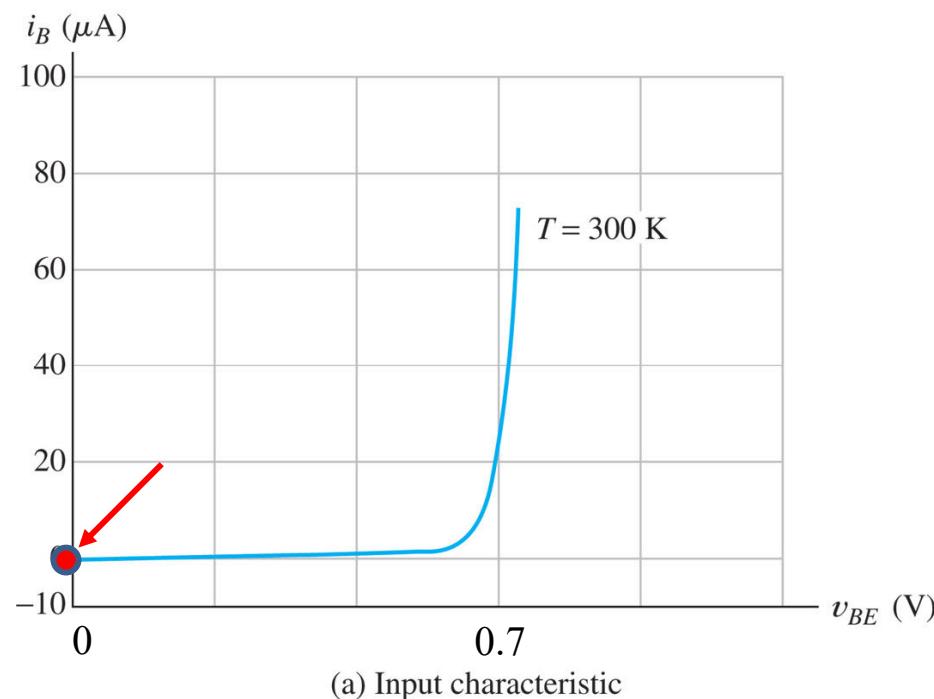

The Bipolar Junction Transistor




MACQUARIE
University

EXAMPLE-2

Use the constant voltage drop model:


$V_{BE} = 0.7 \text{ V}$ when BE diode is on

$\beta = 100$

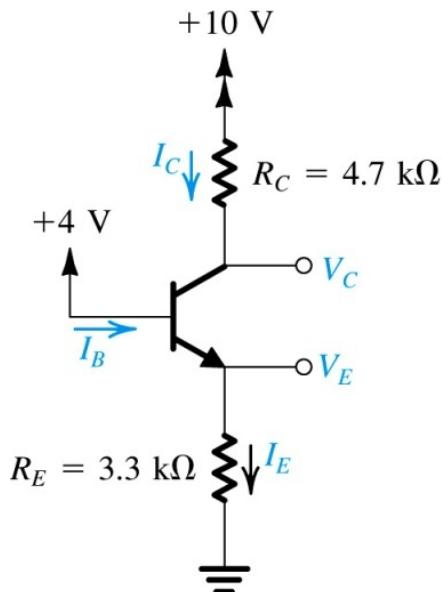

Same as the previous circuit but V_B is higher

What is the value of V_E ?

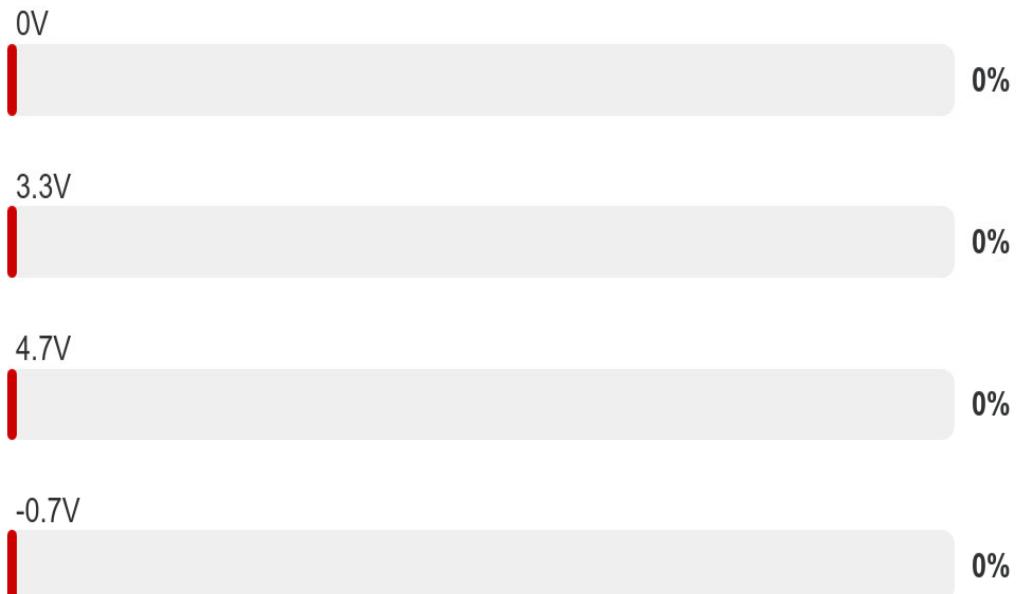

The Bipolar Junction Transistor




MACQUARIE
University

EXAMPLE-2

Use the constant voltage drop model:

$V_{BE} = 0.7 \text{ V}$ when BE diode is on

$\beta = 100$

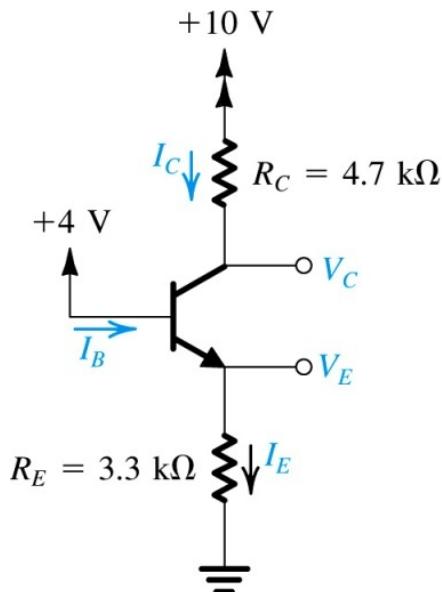

Same as the previous circuit but V_B is higher

What is the value of V_E ?



The Bipolar Junction Transistor



MACQUARIE
University



EXAMPLE-2

Use the constant voltage drop model:

$$V_{BE} = 0.7 \text{ V when BE diode is on}$$

$$\beta = 100$$

Same circuit but
 V_B is higher

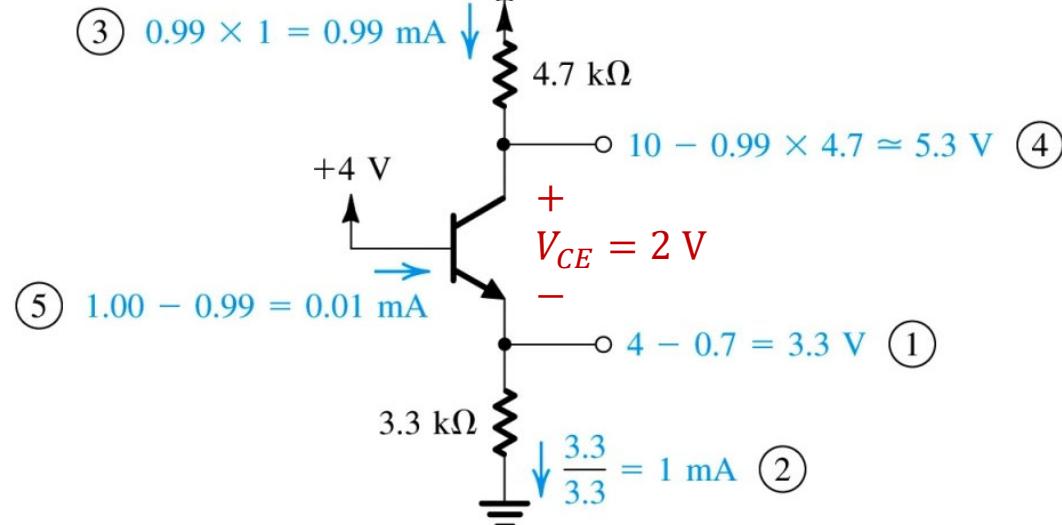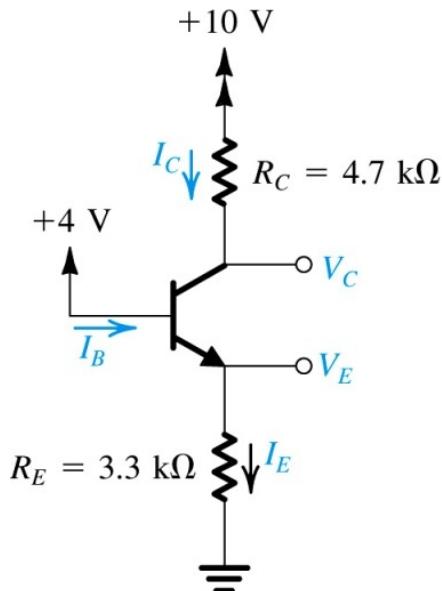

Find all the **currents** and **voltages** in the circuit

The Bipolar Junction Transistor



MACQUARIE
University

EXAMPLE-2

What operating mode is the BJT in?

0%

Cut-off


Active

Saturation

Use the constant voltage drop model:

$$V_{BE} = 0.7 \text{ V when BE diode is on} \quad \beta = 100$$

Same circuit but
 V_B is higher

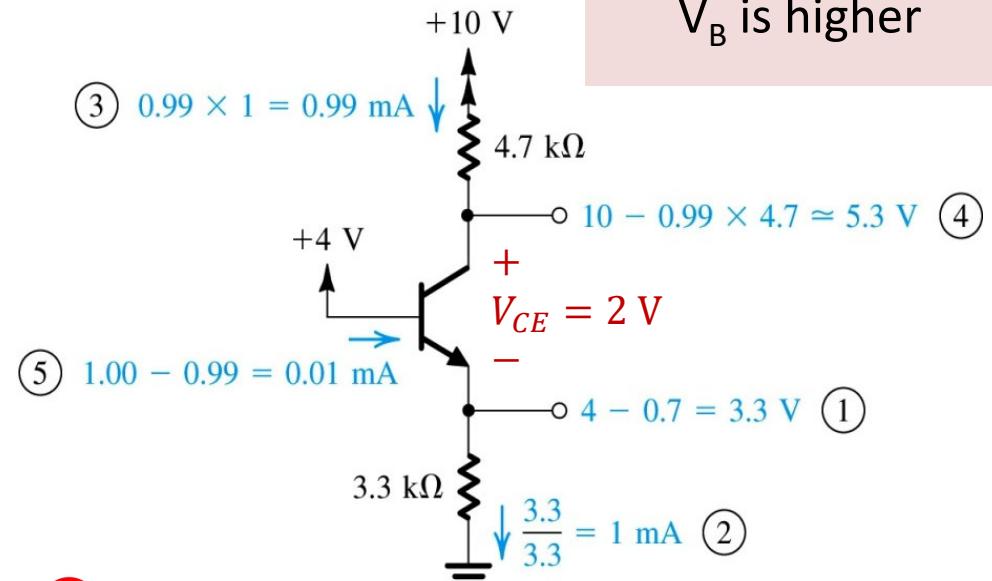

In what operating mode is this BJT?

The Bipolar Junction Transistor



MACQUARIE
University

EXAMPLE-2

What operating mode is the BJT in?

0%

Cut-off


Active

Saturation

Use the constant voltage drop model:

$$V_{BE} = 0.7 \text{ V when BE diode is on} \quad \beta = 100$$

Same circuit but
 V_B is higher

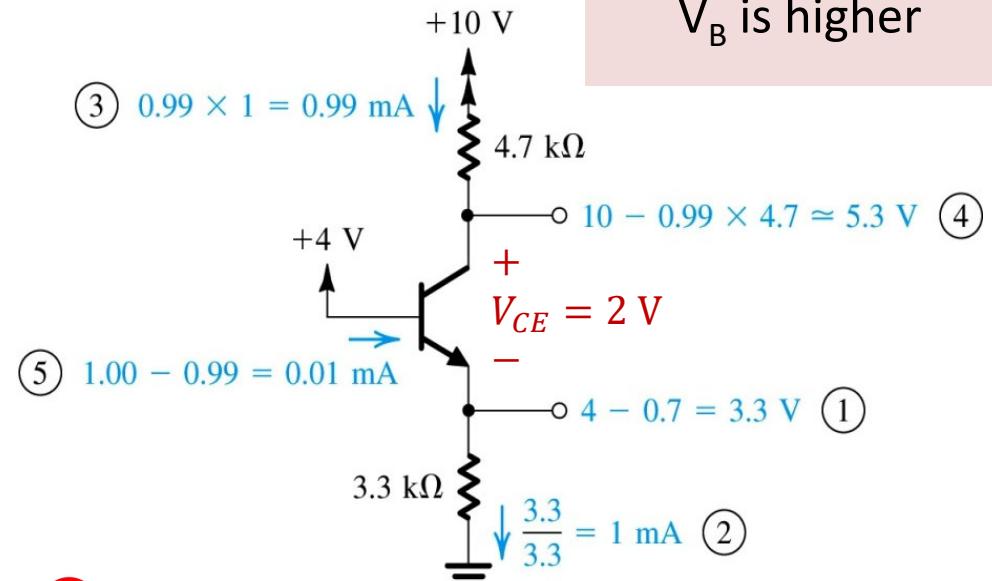

In what operating mode is this BJT?

The Bipolar Junction Transistor



MACQUARIE
University



EXAMPLE-2

Use the constant voltage drop model:

$$V_{BE} = 0.7 \text{ V when BE diode is on}$$

$$\beta = 100$$

Same circuit but
 V_B is higher

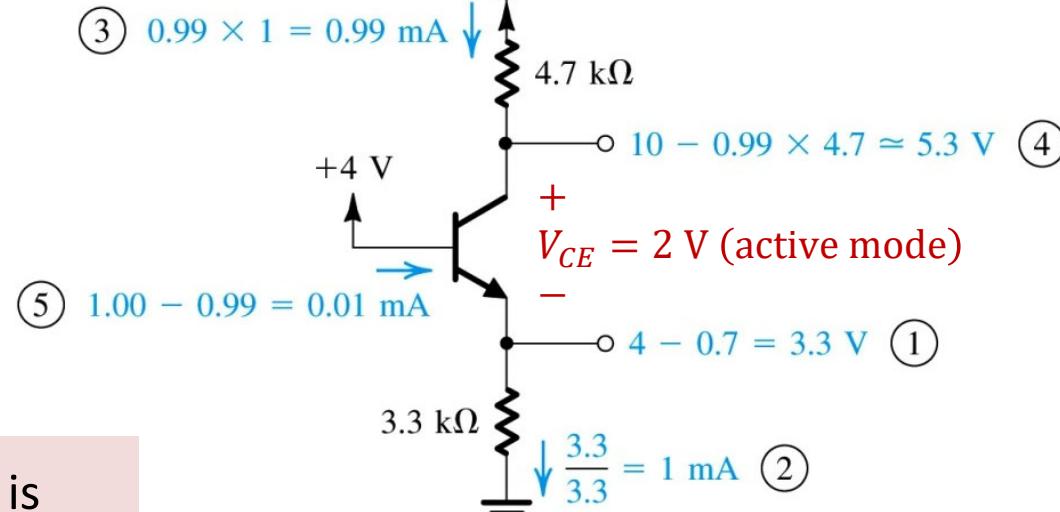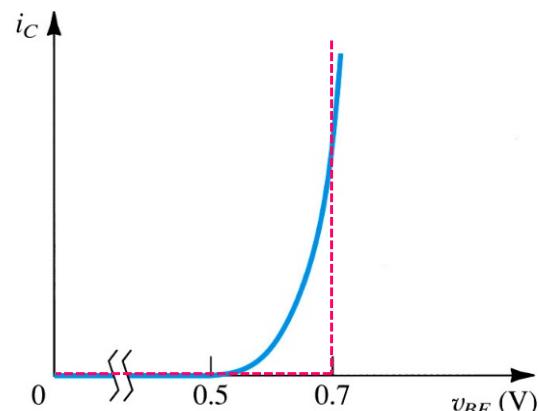

Remember, the model is
approximate, so the solution
will also be only approximate!

The Bipolar Junction Transistor






MACQUARIE
University

EXAMPLE-2 – ACTIVE

This was an example of active mode

Operating in this region:

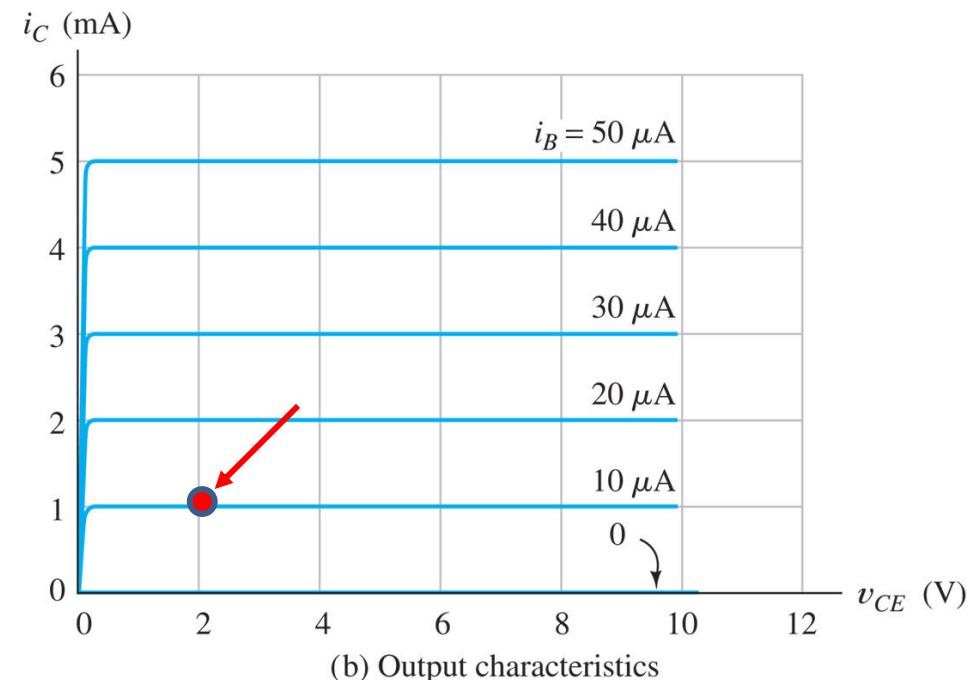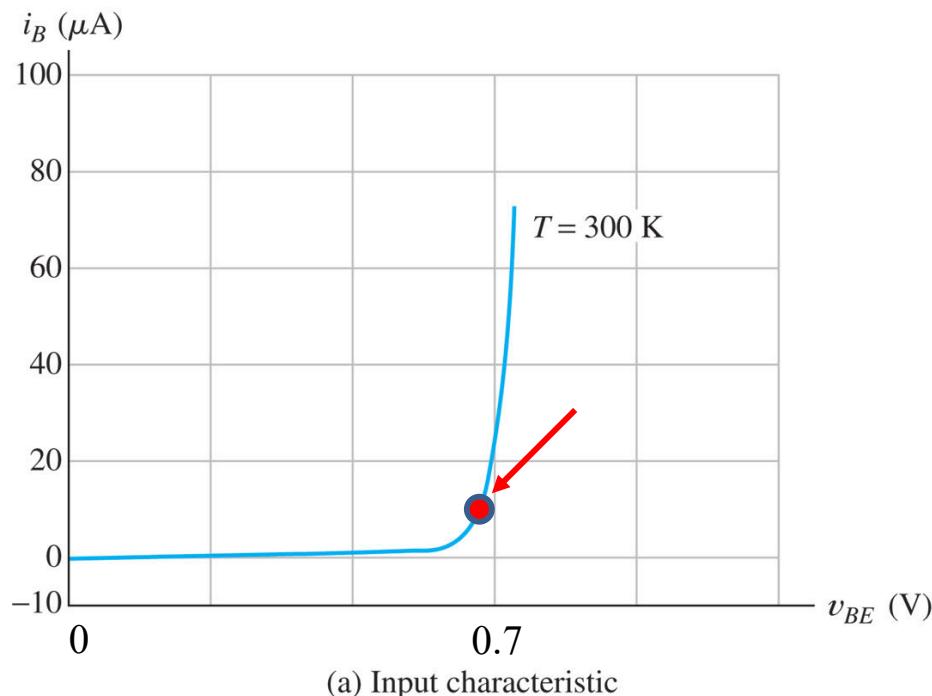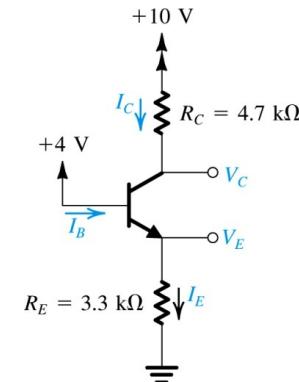

The Bipolar Junction Transistor




MACQUARIE
University

EXAMPLE-3

Use the constant voltage drop model:

$$V_{BE} = 0.7 \text{ V when BE diode is on} \quad \beta = 100$$

Same circuit but
 V_B is even higher

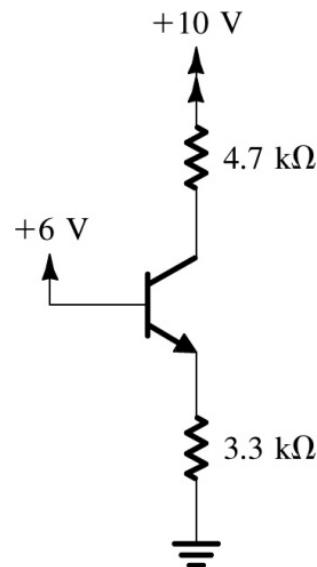

Find all the **currents** and **voltages** in the circuit

The Bipolar Junction Transistor




MACQUARIE
University

EXAMPLE-3

Use the constant voltage drop model:

$$V_{BE} = 0.7 \text{ V when BE diode is on} \quad \beta = 100$$

Same circuit but
 V_B is even higher

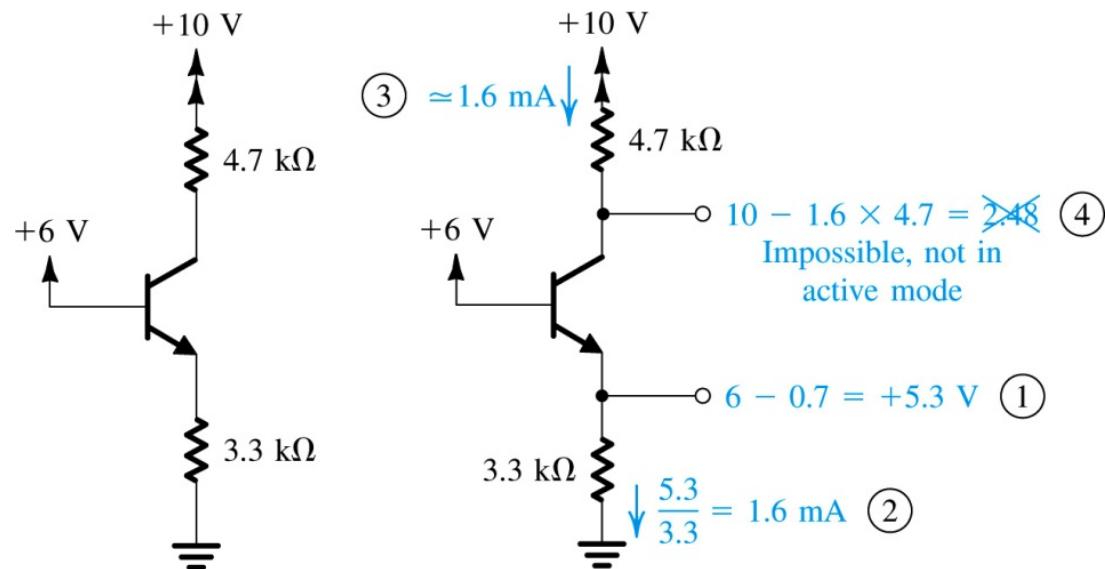

Find all the **currents** and **voltages** in the circuit

The Bipolar Junction Transistor



MACQUARIE
University




EXAMPLE-3

Use the constant voltage drop model:

$$V_{BE} = 0.7 \text{ V when BE diode is on}$$

$$\beta = 100$$

Same circuit but
 V_B is even higher

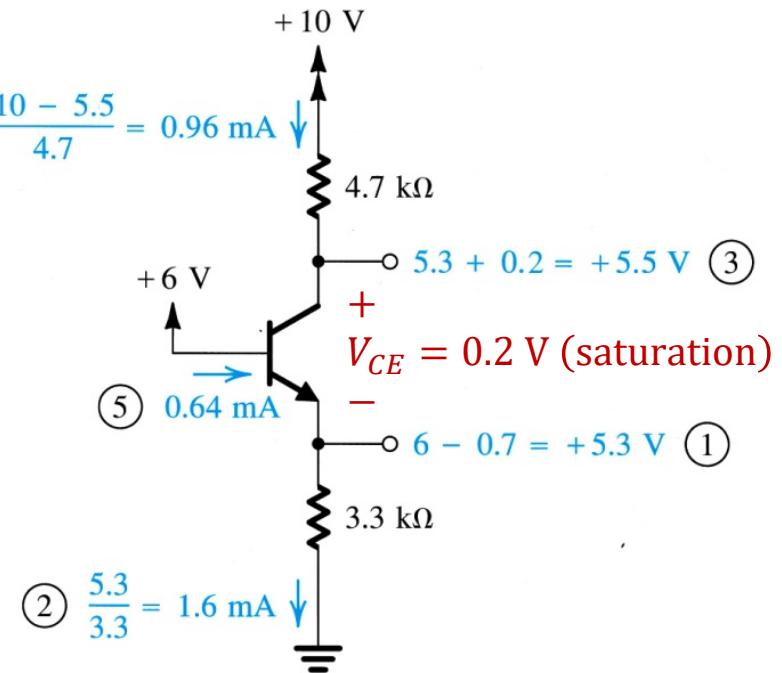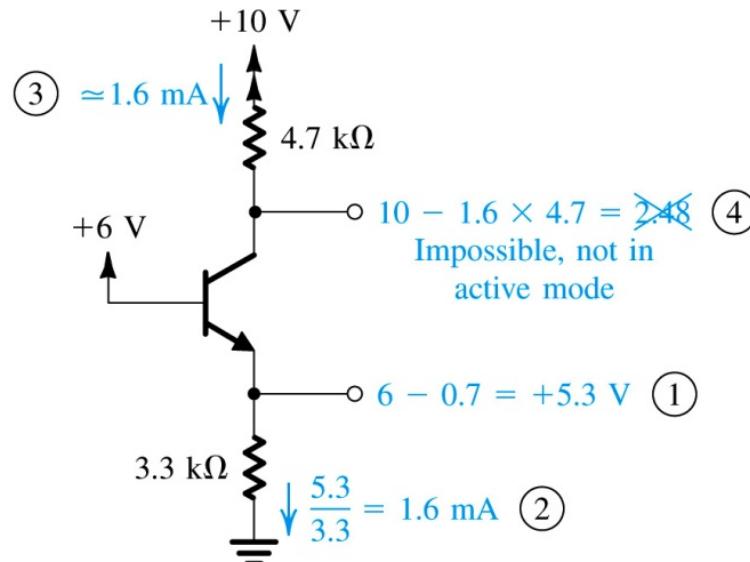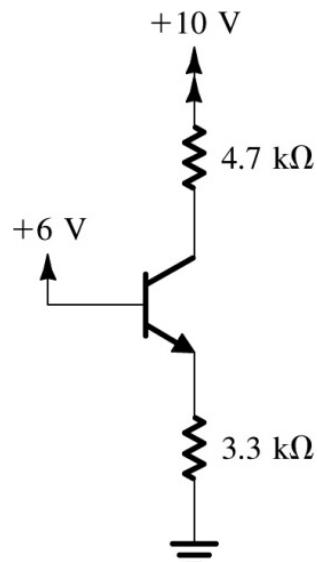

The Bipolar Junction Transistor



MACQUARIE
University


EXAMPLE-3

What is the forced Beta value in this case?

0%

Use the constant voltage drop model:
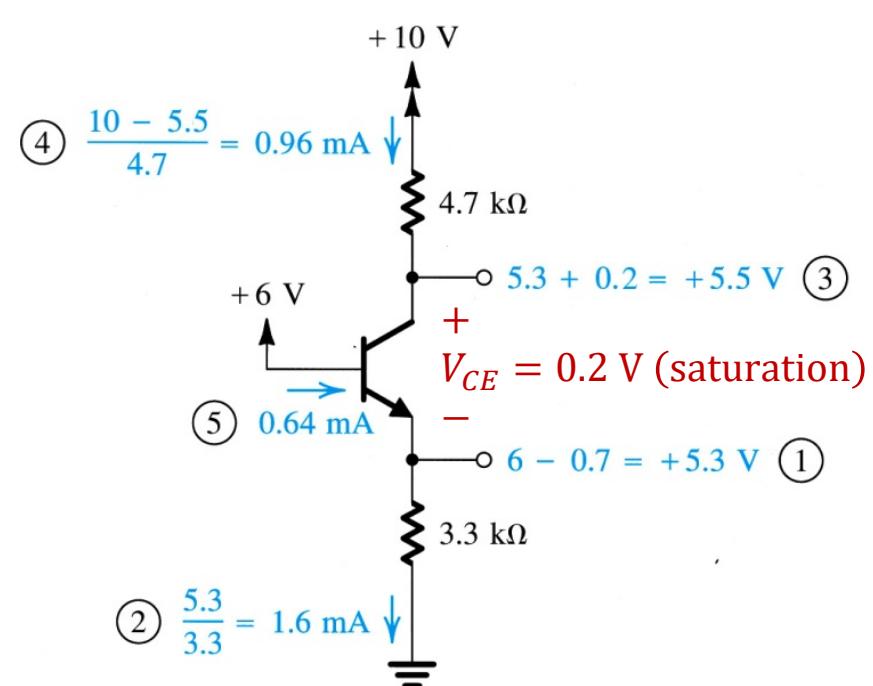
$$V_{BE} = 0.7 \text{ V when BE diode is on} \quad \beta = 100$$



Same circuit but
 V_B is even higher

The Bipolar Junction Transistor




MACQUARIE
University

EXAMPLE-3


What is the forced Beta value in this case?

0%

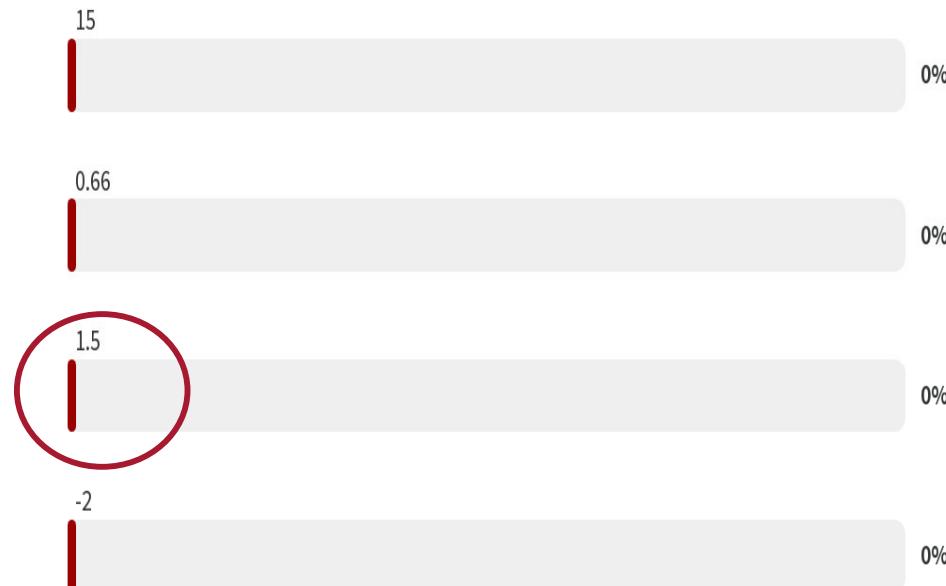

Use the constant voltage drop model:
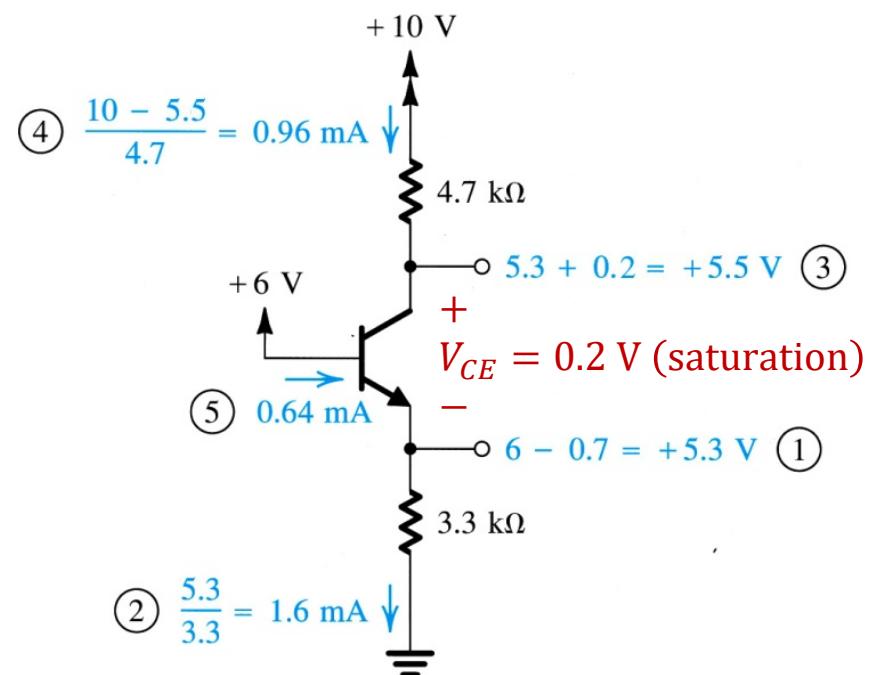
$$V_{BE} = 0.7 \text{ V when BE diode is on} \quad \beta = 100$$



Same circuit but
 V_B is even higher

The Bipolar Junction Transistor





MACQUARIE
University

EXAMPLE-3 – SATURATION

This was an example of saturation

Operating in this region:

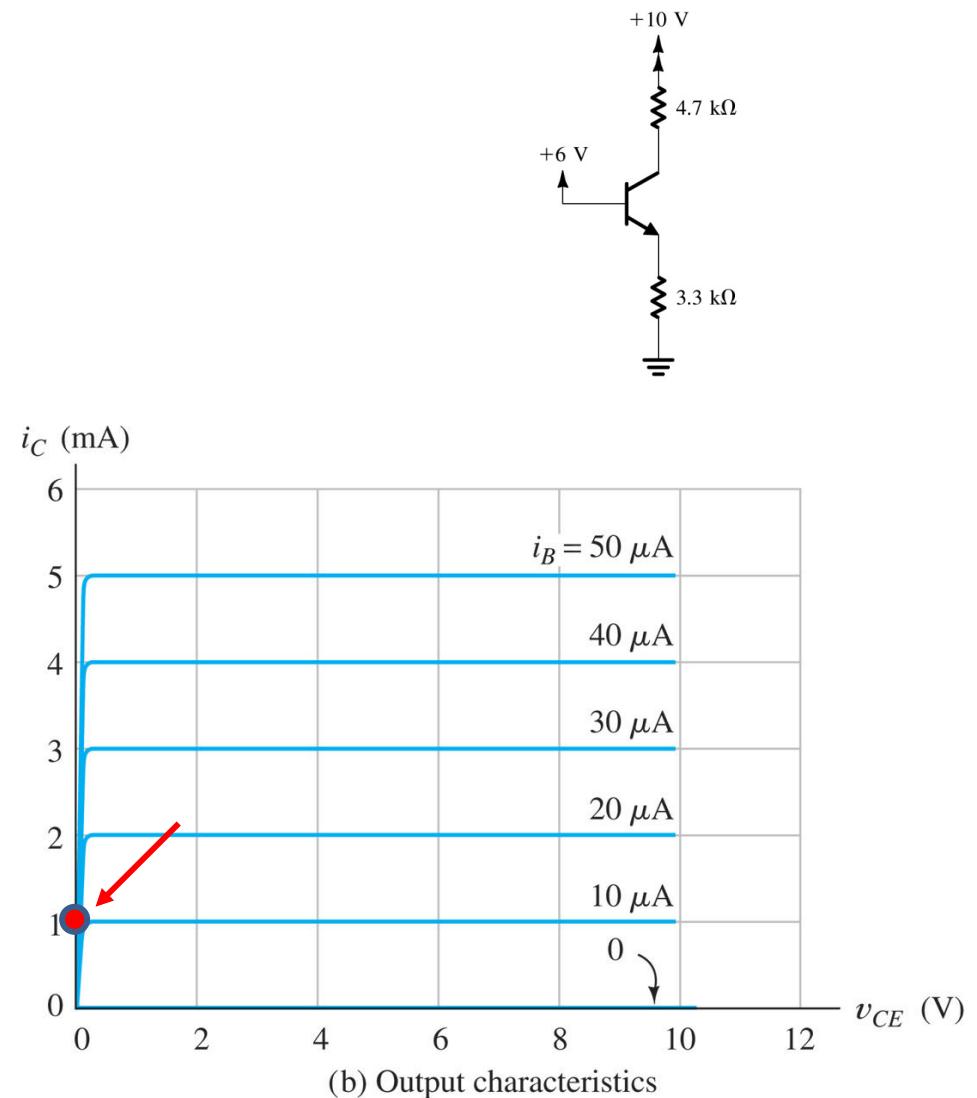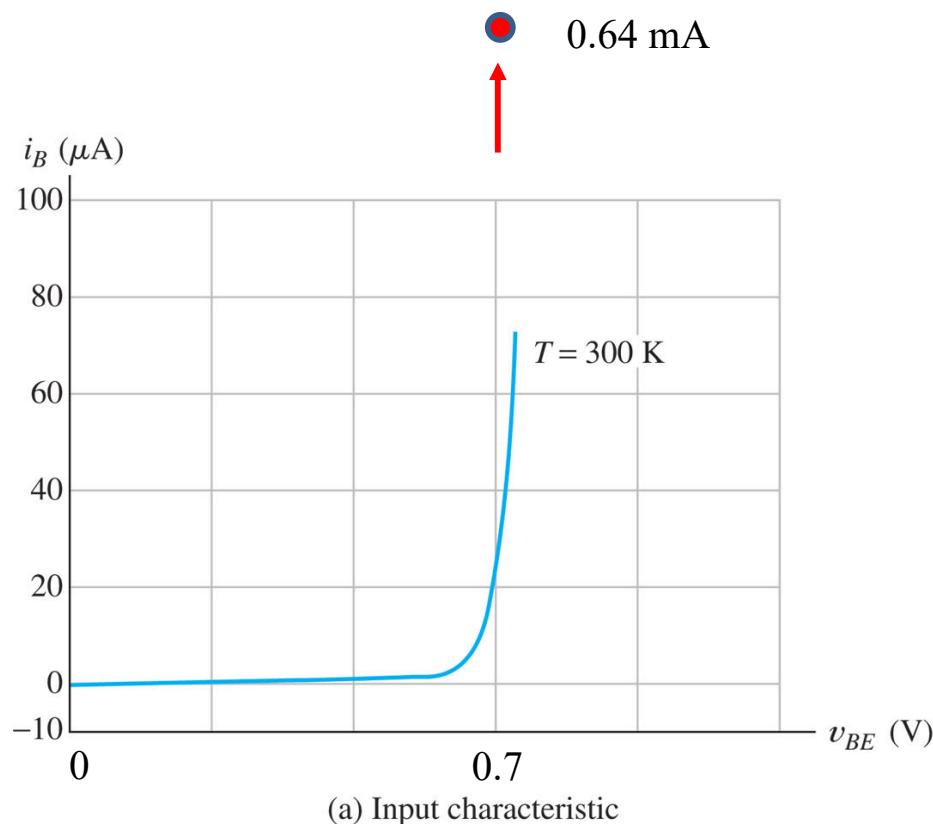

The Bipolar Junction Transistor




MACQUARIE
University

EXAMPLE-4 – PNP

What about for a PNP BJT?

$\beta = 100$

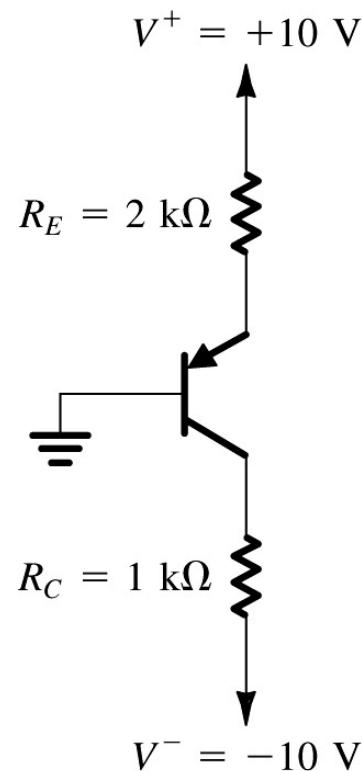

(a)

The Bipolar Junction Transistor




MACQUARIE
University


EXAMPLE-4 – PNP

What about for a PNP BJT?

$$\beta = 100$$

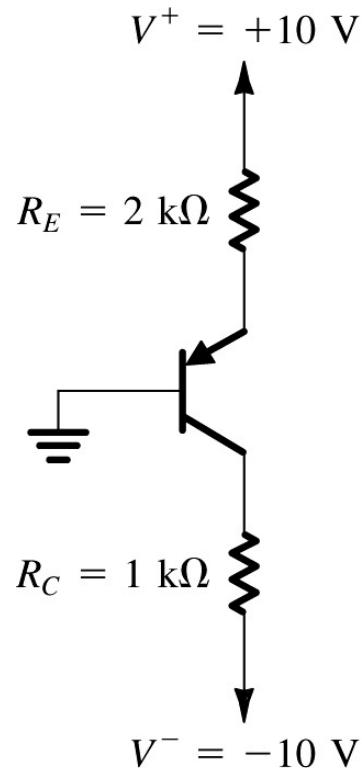

(a)

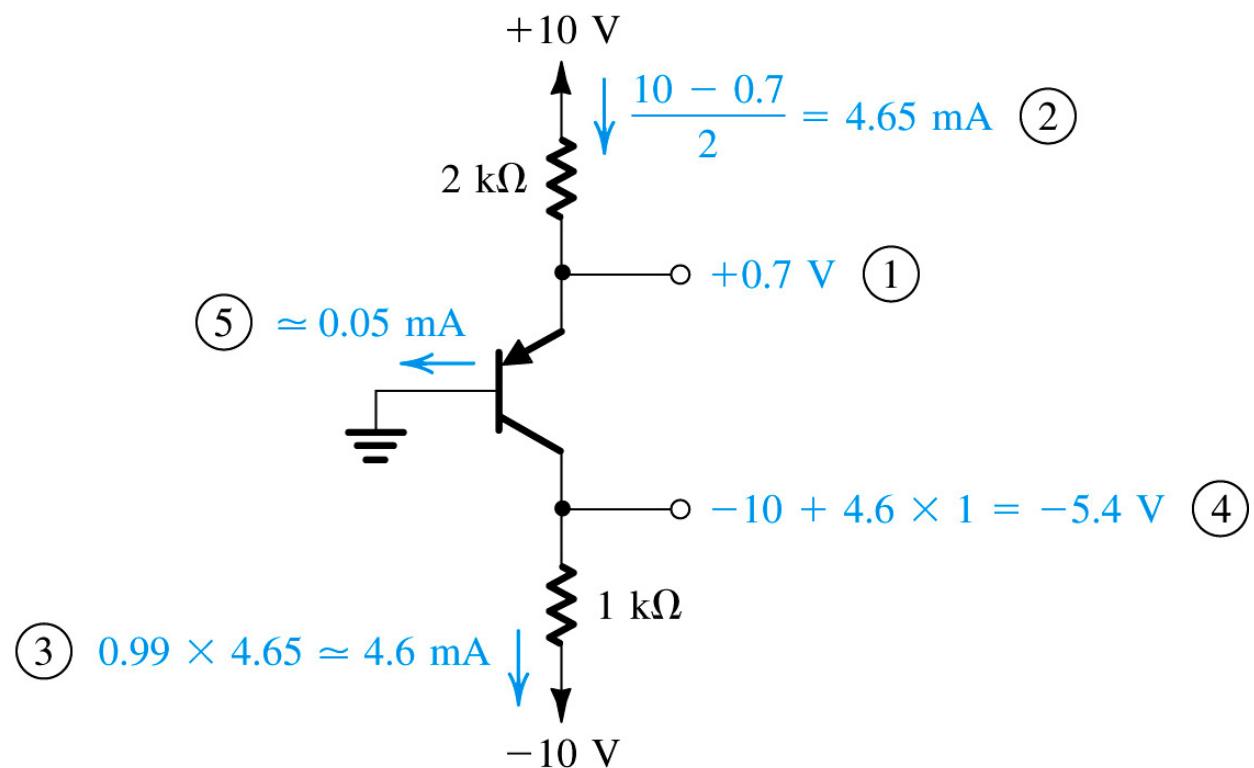

(b)


The Bipolar Junction Transistor




MACQUARIE
University

EXAMPLE-4 – PNP

Here we are in active mode:

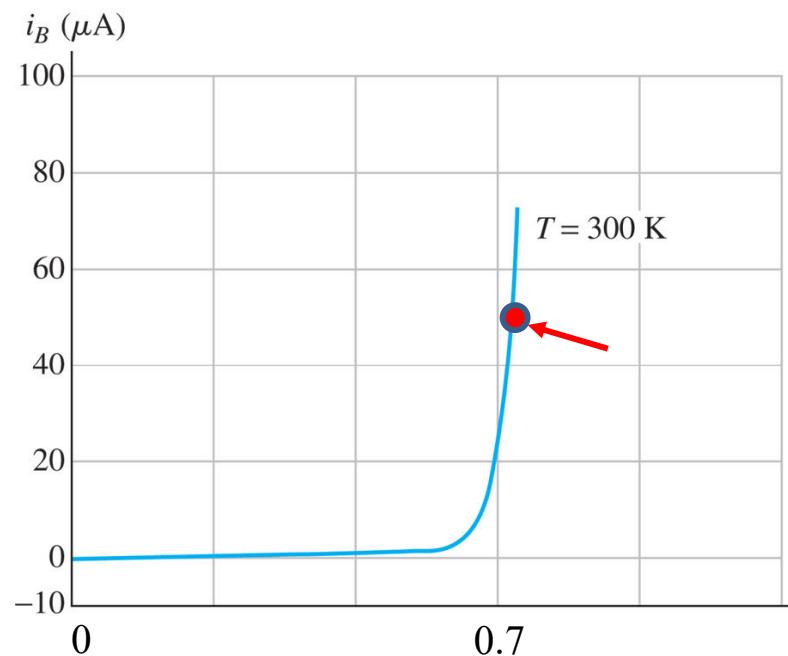

(a) Input characteristic

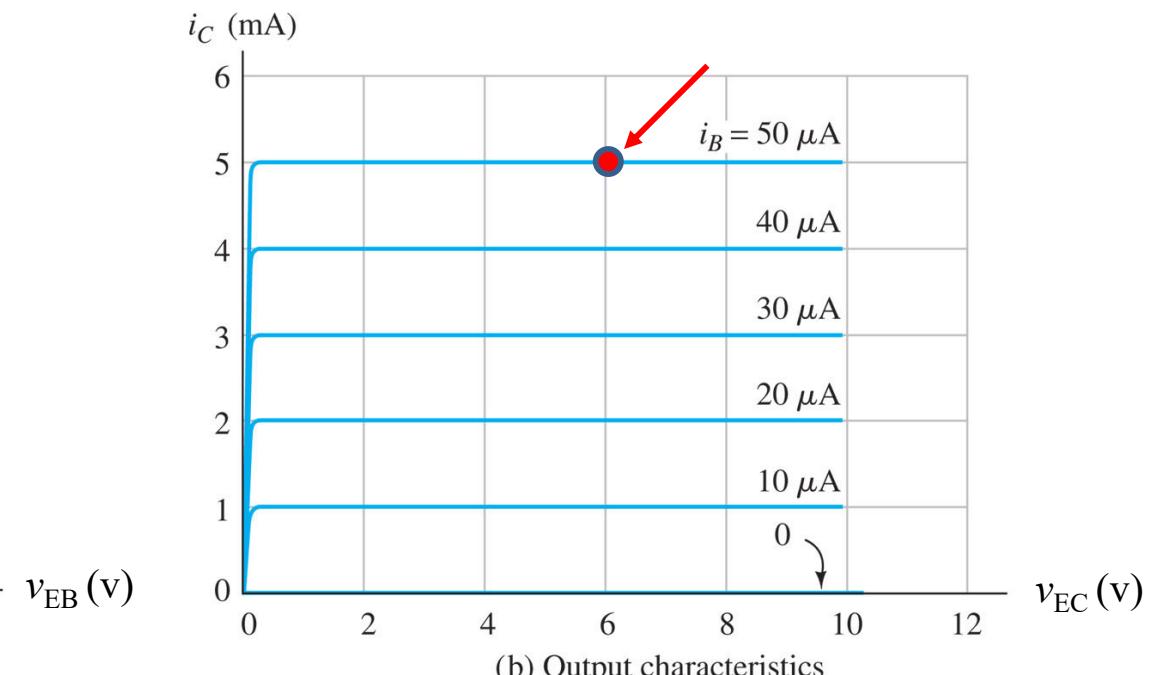

(b) Output characteristics

The Bipolar Junction Transistor




MACQUARIE
University

EXAMPLE-5

Now, with a base resistor.

$$\beta = 100$$

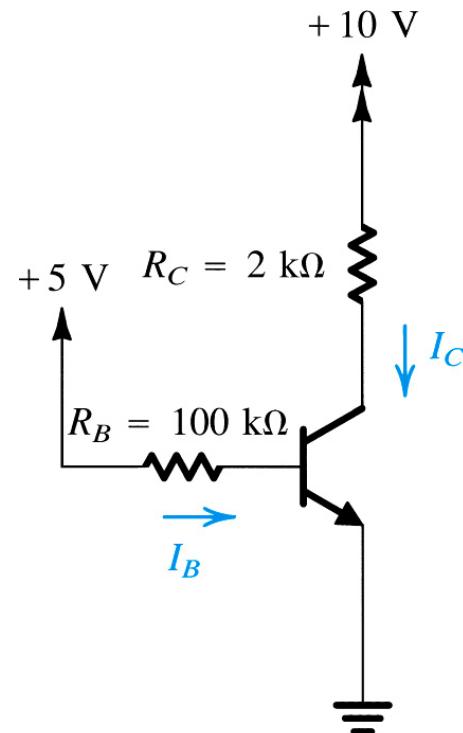

(a)


The Bipolar Junction Transistor




MACQUARIE
University

EXAMPLE-5

$$\beta = 100$$

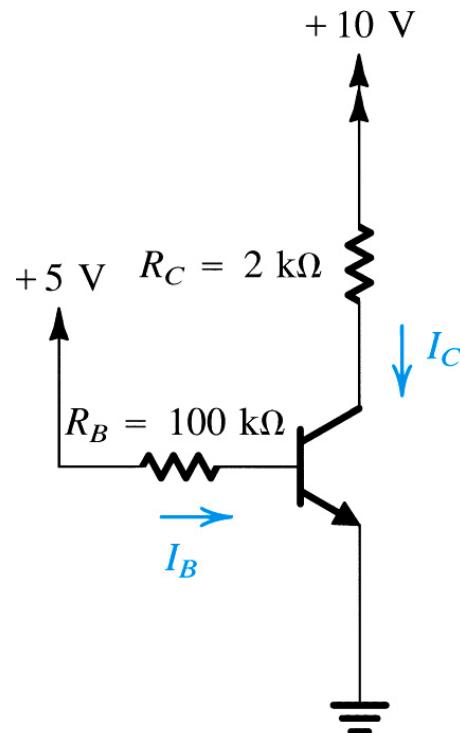

(a)

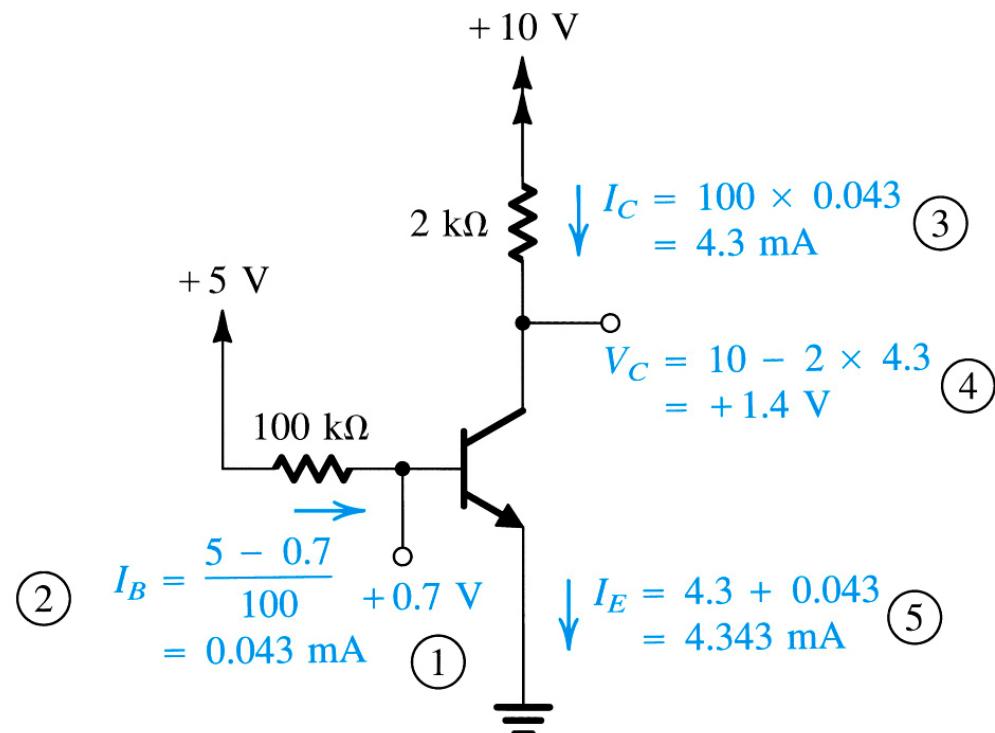

(b)



The Bipolar Junction Transistor



MACQUARIE
University

EXAMPLE-5

Here we are in active mode:

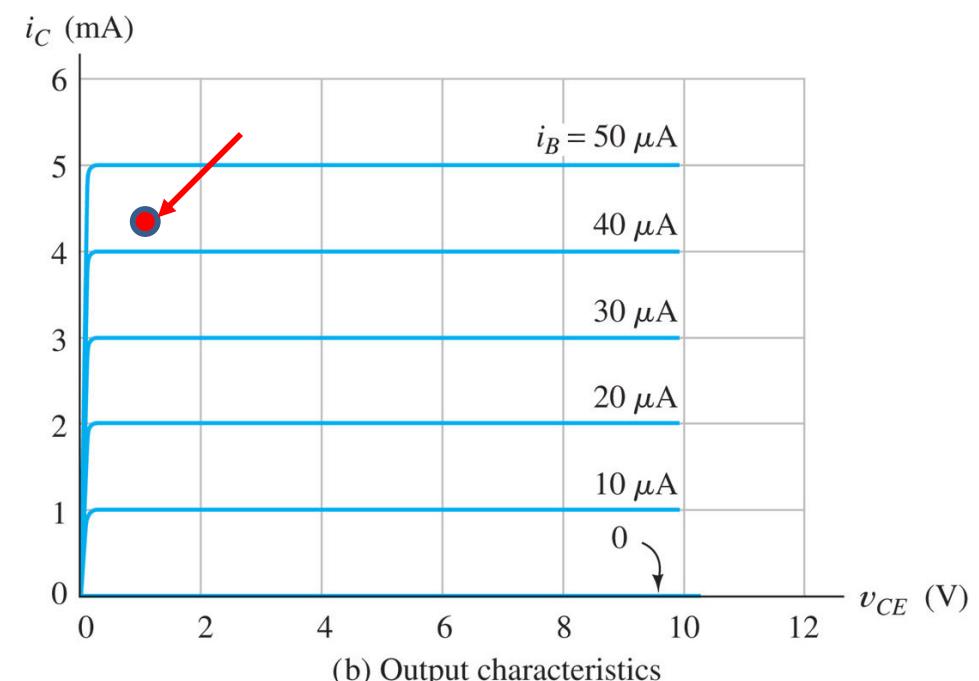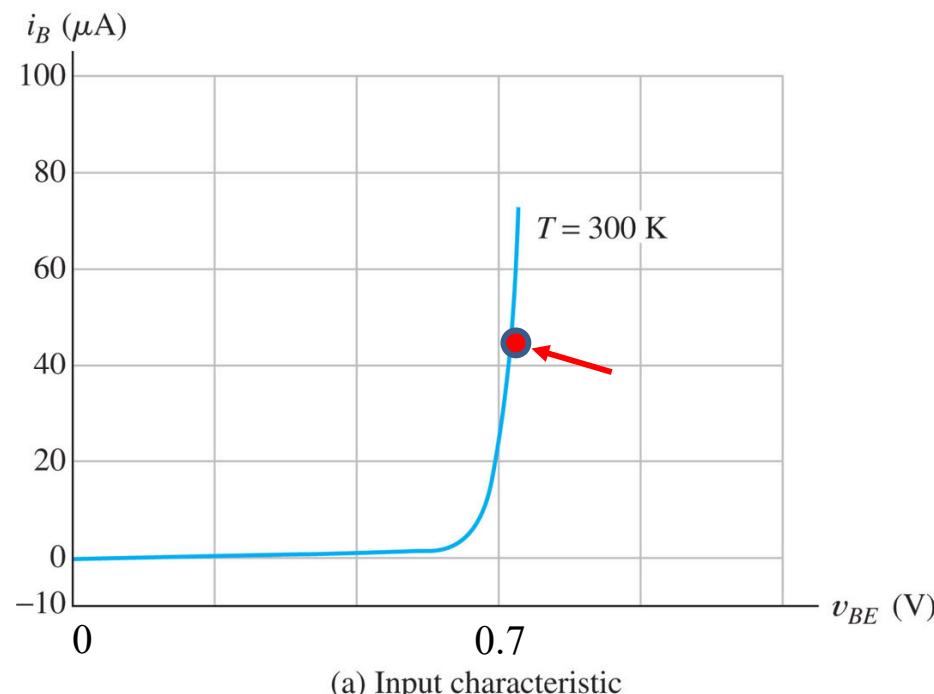


The Bipolar Junction Transistor



MACQUARIE
University

EXAMPLE-6 – NPN

$$\beta = 100$$

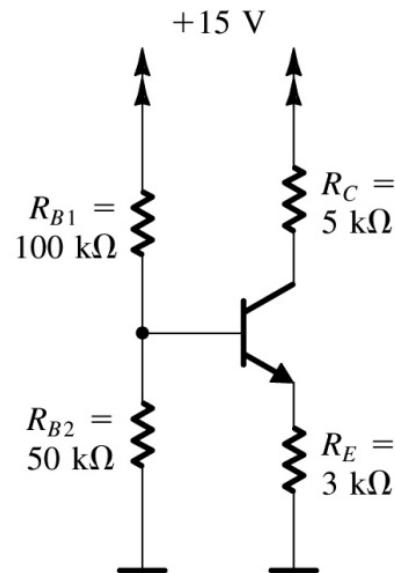

(a)


The Bipolar Junction Transistor




MACQUARIE
University

EXAMPLE-6 – NPN


$$\beta = 100$$

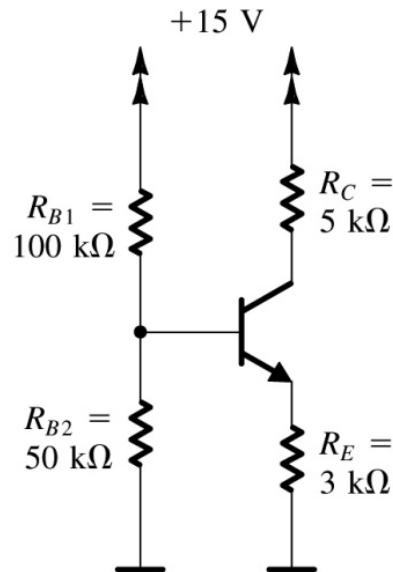


(a)

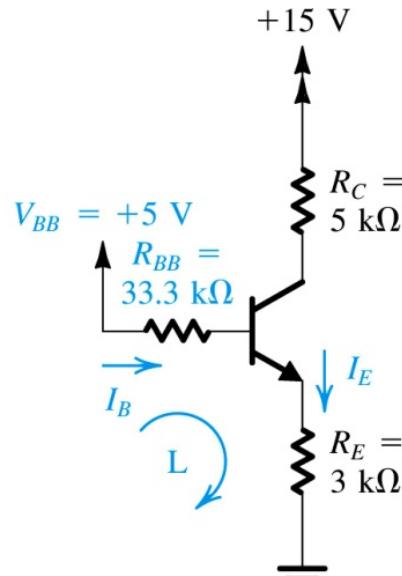

(b)

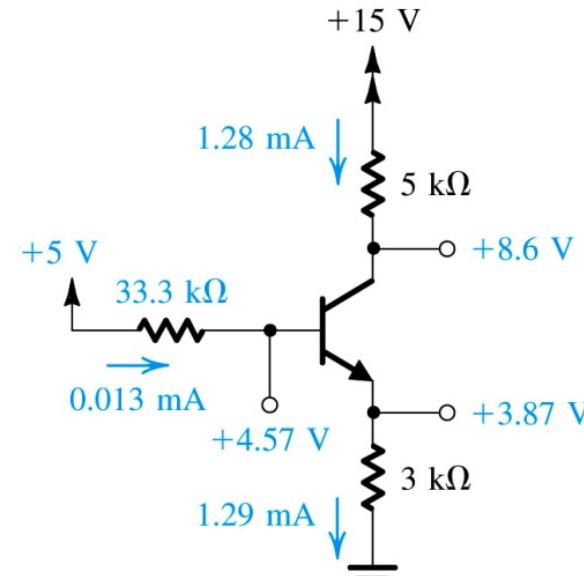

(c)

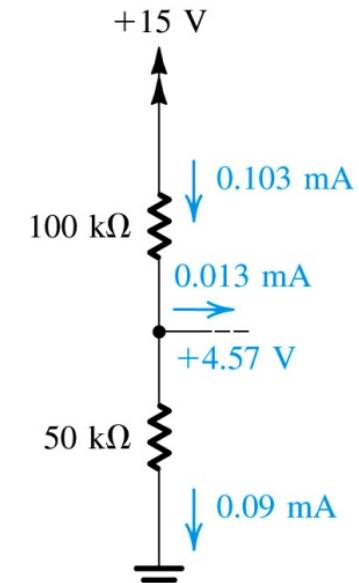

(d)

This week



DIODE CIRCUITS LAB + FIRST ASSIGNMENT

Preparation before the lab:

- The worksheet and submission quiz is available on iLearn
- Do at least the pre-lab section before coming to the timetabled support session
- Record your worksheet answers in a digital logbook and upload individual answers to the iLearn submission before 11:55pm on the day of the timetabled lab session

First Assignment!

- Your first assignment will be posted this week
- This will be an iLearn quiz on the topics of diodes and BJTs
- You will have at least 10 days to complete it (Submission due in week 5)