

# Three-phase systems

ELEC2005 Electrical and Electronic Systems - Week 9

Dr. Leonardo Callegaro

School of Engineering  
Faculty of Science and Engineering



**MACQUARIE**  
University

# Table of Contents

- 1 Balanced  $3\phi$  circuits
- 2 Power in balanced  $3\phi$  circuits
- 3 Unbalanced  $3\phi$  circuits

1 Balanced  $3\phi$  circuits

2 Power in balanced  $3\phi$  circuits

3 Unbalanced  $3\phi$  circuits

# Advantages of three-phase ( $3\phi$ ) systems

- Can transmit more power for same amount of wire (twice as much as  $1\phi$ )
  - ▶ Better infrastructure utilization
- Torque produced by  $3\phi$  machines is constant (because, **contrarily to  $1\phi$  systems, instantaneous- $3\phi$ -power is constant**)
  - ▶ No mechanical vibration
  - ▶ Longer machine lifetime
- $3\phi$  machines use less material for same power rating
  - ▶ Cost savings
- $3\phi$  machines start-up more easily than  $1\phi$  machines
  - ▶ Simple operation

# Balanced three-phase ( $3\phi$ ) circuits


- A balanced 3 phase ( $3\phi$ ) circuit has
  - ▶ 3 voltage sources with equal magnitude, but with an angle shift of  $120^\circ$
  - ▶ equal loads on each phase
  - ▶ equal impedance on the lines connecting the generators to the loads
- Bulk power systems are almost exclusively  $3\phi$ 
  - ▶ Bulk means “high-voltage” system, e.g. to transfer power between different geographical areas
- $1\phi$  is used primarily in low voltage, low power settings, such as residential and some commercial settings

$$\bar{E}_{an} = Ee^{j0}$$



$$\bar{E}_{bn} = Ee^{-j\frac{2}{3}\pi}$$

$$\bar{E}_{cn} = Ee^{j\frac{2}{3}\pi}$$


$$Z_{AN} = Z_{BN} = Z_{CN} = Z_Y$$

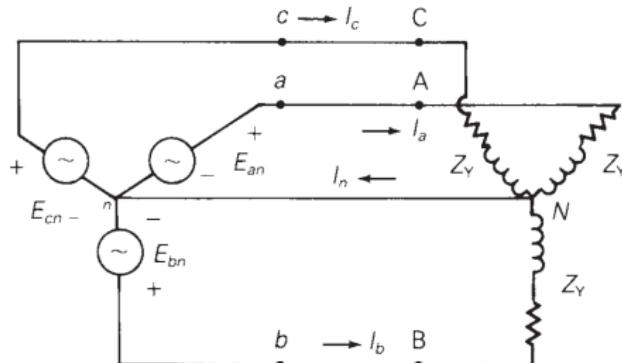
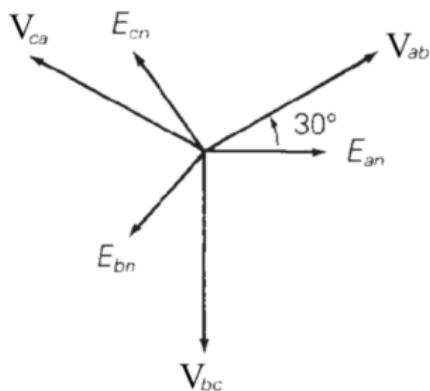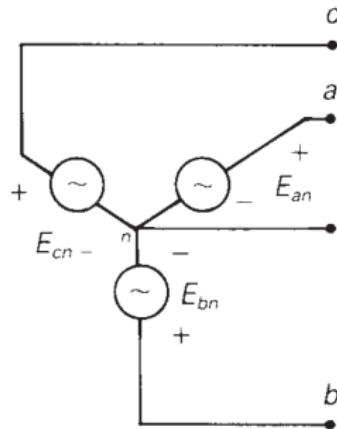
# Line to neutral and line to line voltages



(a) Phasor diagram

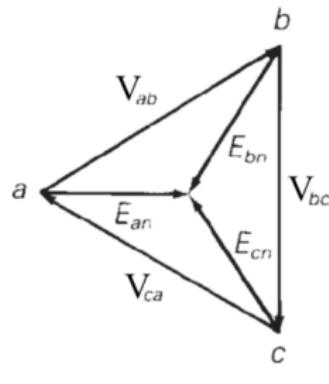

(b) Voltage triangle

Balanced line to neutral voltages

$$\bar{E}_{an} = E e^{j0}$$

$$\bar{E}_{bn} = E e^{-j\frac{2}{3}\pi} = \bar{E}_{an} e^{-j\frac{2}{3}\pi}$$

$$\bar{E}_{cn} = E e^{j\frac{2}{3}\pi}$$

Balanced line to line voltages

$$\bar{V}_{ab} = \bar{E}_{an} - \bar{E}_{bn} = \sqrt{3} \bar{E}_{an} e^{j\frac{\pi}{6}}$$

$$\bar{V}_{bc} = \bar{E}_{bn} - \bar{E}_{cn} = \sqrt{3} \bar{E}_{bn} e^{j\frac{\pi}{6}}$$

$$\bar{V}_{ca} = \bar{E}_{cn} - \bar{E}_{an} = \sqrt{3} \bar{E}_{cn} e^{j\frac{\pi}{6}}$$

Note: often the notation  $\bar{V}_{ln}$  or  $\bar{V}_{LN}$  (rather than  $\bar{E}_{ln}$ , with  $l = a, b, c$ ) is used to indicate the line to neutral voltage

$$\bar{V}_{ab} = \bar{E}_{am} - \bar{E}_{bm} = \bar{E}_{am} - \bar{E}_{am} e^{-j\frac{2}{3}\pi}$$

$$e^{j\phi} = \cos\phi + j\sin\phi$$



$$= \bar{E}_{am} \left( 1 - \left[ \cos\left(-\frac{2}{3}\pi\right) + j\sin\left(-\frac{2}{3}\pi\right) \right] \right)$$

$$= \bar{E}_{am} \left( 1 - \left[ \left(-\frac{1}{2}\right) + j\left(-\frac{\sqrt{3}}{2}\right) \right] \right)$$


$$= \bar{E}_{am} \left( 1 + \frac{1}{2} + j\frac{\sqrt{3}}{2} \right)$$

$$= \bar{E}_{am} \left( \frac{3}{2} + j\frac{\sqrt{3}}{2} \right) = \sqrt{3} \bar{E}_{am} \left( \frac{\sqrt{3}}{2} + j\frac{1}{2} \right)$$

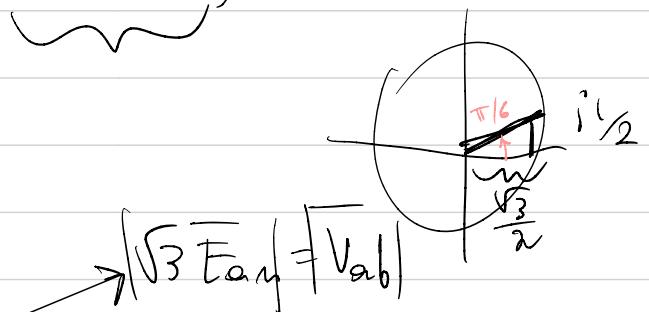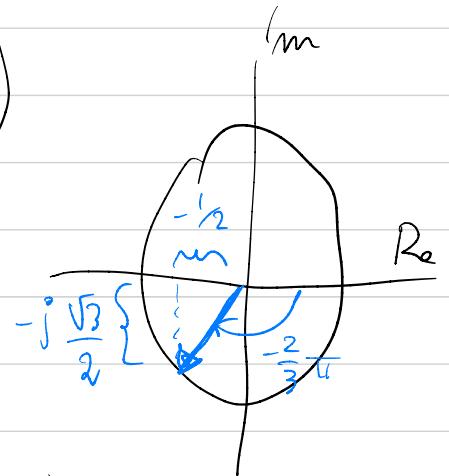
$$= \sqrt{3} \bar{E}_{am} e^{j\frac{\pi}{6}}$$



$$\rightarrow \sqrt{3} \bar{E}_{am} \left| \bar{V}_{ab} \right|$$

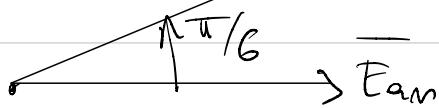



# Balanced line to neutral voltages

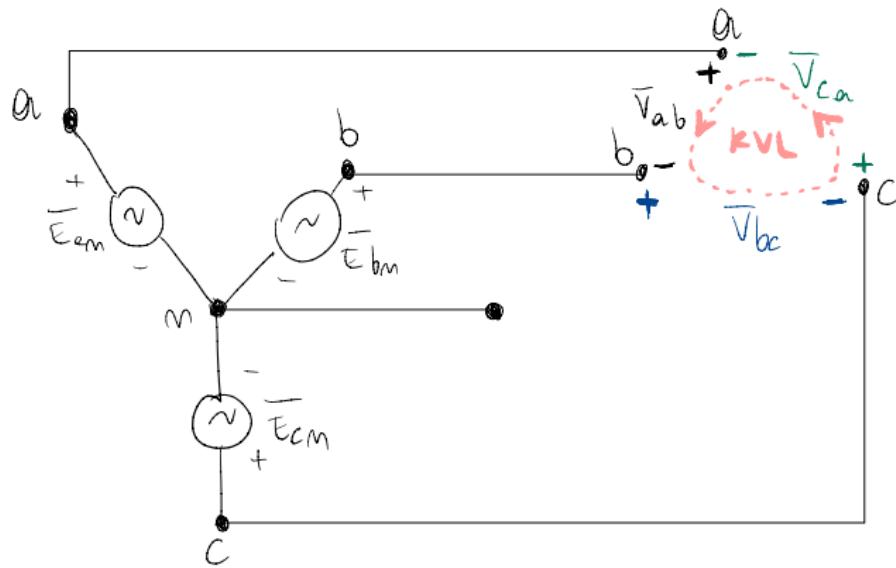


Balanced conditions:  
 $\bar{E}_{an} + \bar{E}_{bn} + \bar{E}_{cn} = 0$

KVL:  
 $\bar{V}_{ab} + \bar{V}_{bc} + \bar{V}_{ca} = 0$   
(sum of line to line voltages is always 0)

# Balanced line currents

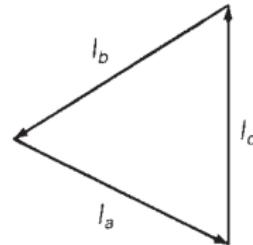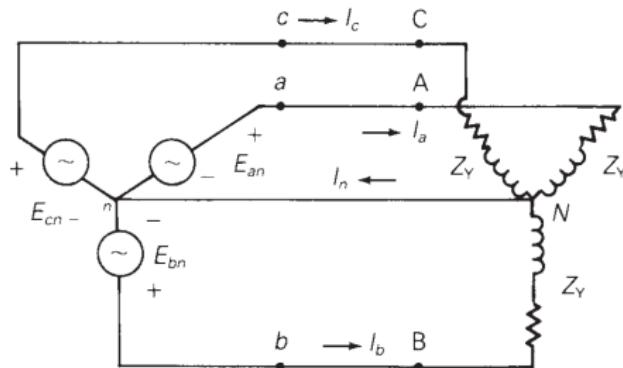
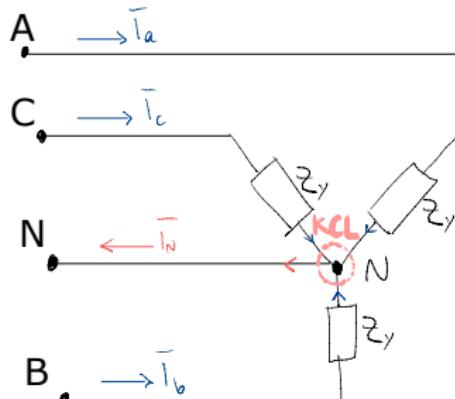
$$\bar{I}_a = \frac{\bar{E}_{an}}{Z_Y} \quad \bar{I}_b = \frac{\bar{E}_{bn}}{Z_Y} \quad \bar{I}_c = \frac{\bar{E}_{cn}}{Z_Y}$$




KCL (node N):  $\bar{I}_a + \bar{I}_b + \bar{I}_c - \bar{I}_N = 0$

Balanced conditions:  $\bar{I}_N = 0$

# Balanced- $\Delta$ loads

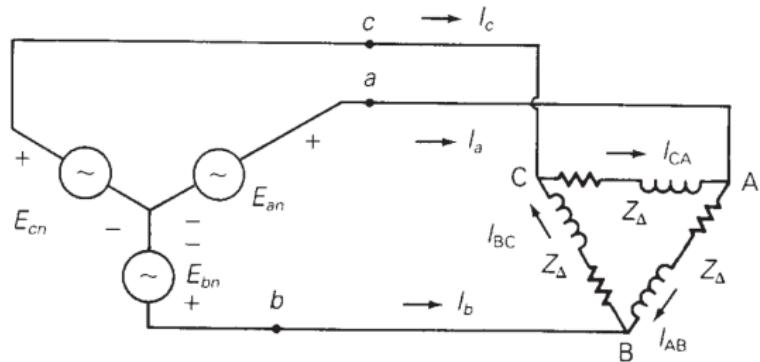**Load currents under balanced conditions:**



$$\bar{I}_{AB} = \frac{\bar{V}_{AB}}{Z_\Delta}$$

$$\bar{I}_{BC} = \frac{\bar{V}_{BC}}{Z_\Delta}$$


$$\bar{I}_{CA} = \frac{\bar{V}_{CA}}{Z_\Delta}$$

**Line current equations:**

$$\text{KCL (A): } \bar{I}_a = \bar{I}_{AB} - \bar{I}_{CA} = \sqrt{3} \bar{I}_{AB} e^{-j\frac{\pi}{6}}$$

$$\text{KCL (B): } \bar{I}_b = \bar{I}_{BC} - \bar{I}_{AB} = \sqrt{3} \bar{I}_{BC} e^{-j\frac{\pi}{6}}$$
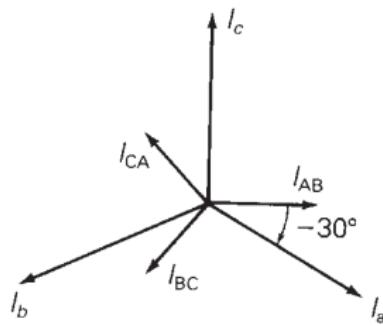
$$\text{KCL (C): } \bar{I}_c = \bar{I}_{CA} - \bar{I}_{BC} = \sqrt{3} \bar{I}_{CA} e^{-j\frac{\pi}{6}}$$





$$\bar{I}_a = \bar{I}_{AB} - \bar{I}_{CA} = \bar{I}_{AB} - \bar{I}_{AB} e^{j\frac{2}{3}\pi}$$



$$= \bar{I}_{AB} \left( 1 - \left[ \cos\left(\frac{2}{3}\pi\right) + i \sin\left(\frac{2}{3}\pi\right) \right] \right)$$

$$= \bar{I}_{AB} \left( 1 - \left( -\frac{1}{2} \right) - i \left( \frac{\sqrt{3}}{2} \right) \right)$$
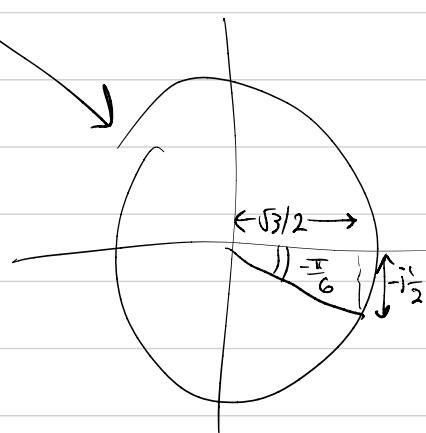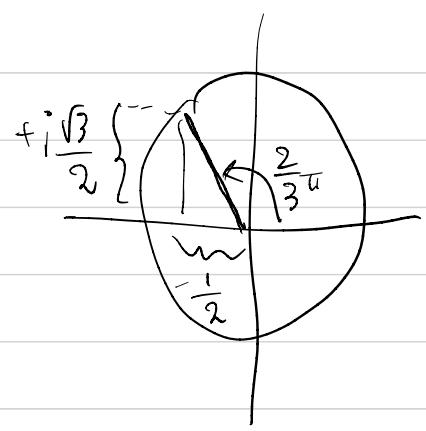
$$= \bar{I}_{AB} \left( \frac{3}{2} - j \frac{\sqrt{3}}{2} \right) = \sqrt{3} \bar{I}_{AB} \left( \frac{\sqrt{3}}{2} - j \frac{1}{2} \right) = \sqrt{3} \bar{I}_{AB} e^{-j\frac{\pi}{6}}$$


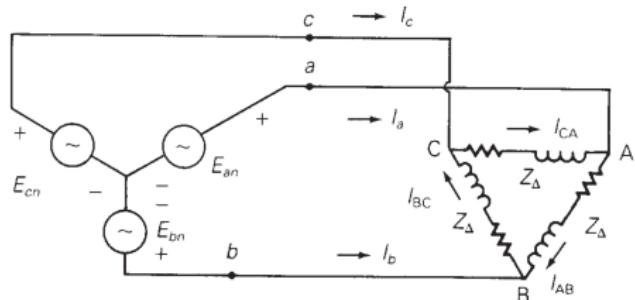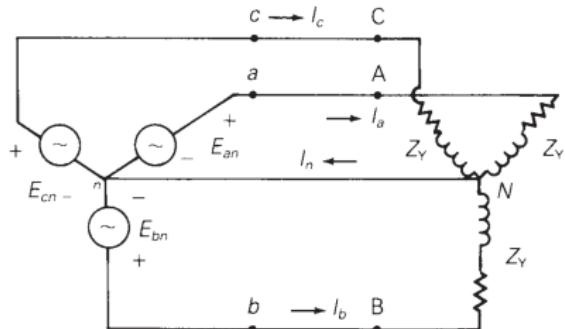
# $\Delta$ -Y conversion for balanced loads



Posing equality of **line** currents for the circuit on the left and on the right:

$$\bar{I}_a = \frac{\bar{E}_{an}}{Z_Y} = \frac{\bar{V}_{AB}}{\sqrt{3} Z_Y} e^{-j\frac{\pi}{6}}$$

$$\bar{I}_a = \sqrt{3} \bar{I}_{AB} e^{-j\frac{\pi}{6}} = \sqrt{3} \frac{\bar{V}_{AB}}{Z_\Delta} e^{-j\frac{\pi}{6}}$$


$\bar{I}_a$  is the same in both circuits if:

$$Z_Y = \frac{Z_\Delta}{3}$$
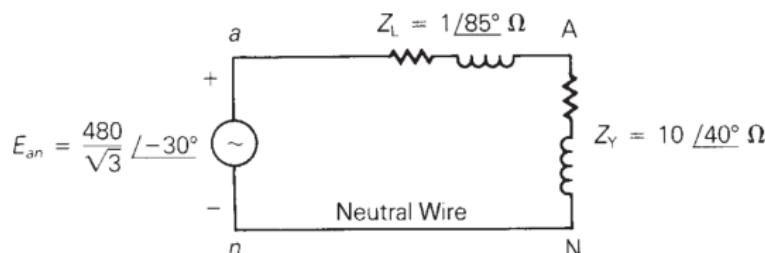
# Equivalent line-to-neutral Y diagrams

With balanced three-phase circuits, only one phase needs to be analyzed.

- $\Delta$  loads can be converted to  $Y$  loads
- all source and load neutrals connected with a zero-ohm neutral wire without changing the solution
- one phase of the circuit can be solved
  - ▶ voltage and current in remaining phases are equal in magnitude and  $\pm 120^\circ$  out of phase with those of the phase solved




1 Balanced  $3\phi$  circuits

2 Power in balanced  $3\phi$  circuits

3 Unbalanced  $3\phi$  circuits

# Instantaneous power in balanced 3 $\phi$ circuits

Instantaneous power for phase  $a$ :

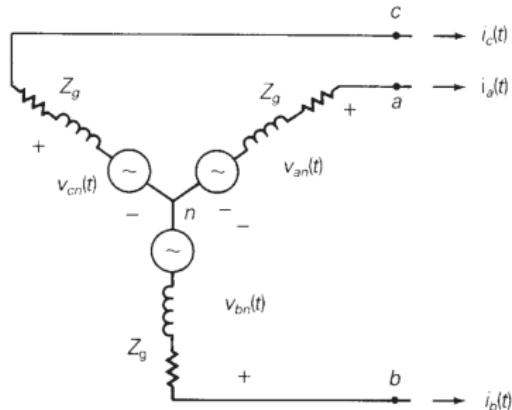

$$v_{an}(t) = \sqrt{2}V_{LN} \cos(\omega t + \delta)$$

$$i_a(t) = \sqrt{2}I \cos(\omega t + \beta)$$

$$p_a(t) = v_{an}(t) i_a(t)$$

$$= V_{LN} I \cos(\delta - \beta)$$

$$+ V_{LN} I \cos(2\omega t + \delta + \beta)$$

In the same way, the power for phase  $b$  and  $c$ , can be calculated.

The instantaneous 3 $\phi$  power is:

$\sum_L$

$$p_{3\phi}(t) = p_a(t) + p_b(t) + p_c(t) = 3V_{LN} I \cos(\underbrace{\delta - \beta}_{\phi}) = \sqrt{3}V_{LL} I \cos(\underbrace{\delta - \beta}_{\phi})$$


3 $\phi$  instant. power is not a function of time:

$$p_{3\phi}(t) = \text{constant} = P_{3\phi}$$

See: Glover (2017), pp. 63-64, for derivations (click [here](#))

# Complex power in balanced $3\phi$ circuits

Complex power for phase a:

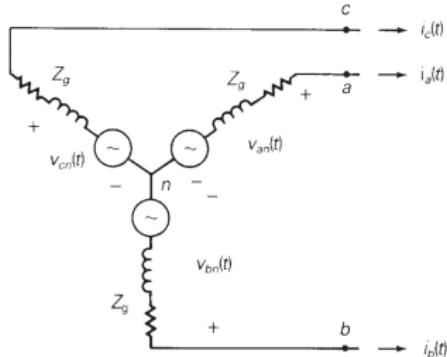

$$\bar{V}_{an} = V_{LN} e^{j\delta}$$

$$\bar{I}_a = I e^{j\beta}$$

$$\begin{aligned}\bar{S}_a &= \bar{V}_{an} \bar{I}_a^* = V_{LN} e^{j\delta} I e^{-j\beta} = V_{LN} I e^{j(\delta - \beta)} \\ &= \underbrace{V_{LN} I \cos(\delta - \beta)}_{P_a} + j \underbrace{V_{LN} I \sin(\delta - \beta)}_{Q_a}\end{aligned}$$

$$\bar{S}_{3\phi} = S_a + S_b + S_c = \underbrace{3V_{LN} I \cos(\delta - \beta)}_{P_{3\phi}} + j \underbrace{3V_{LN} I \sin(\delta - \beta)}_{Q_{3\phi}}$$


$$P_{3\phi} = \text{Re}[\bar{S}_{3\phi}] = 3V_{LN} I \cos(\delta - \beta) = \sqrt{3}V_{LL} I \cos(\delta - \beta) \text{ active power}$$

$$Q_{3\phi} = \text{Im}[\bar{S}_{3\phi}] = 3V_{LN} I \sin(\delta - \beta) = \sqrt{3}V_{LL} I \sin(\delta - \beta) \text{ reactive power}$$

$$|\bar{S}_{3\phi}| = S_{3\phi} = \sqrt{P_{3\phi}^2 + Q_{3\phi}^2} = 3V_{LN} I = \sqrt{3}V_{LL} I \quad \text{apparent power}$$
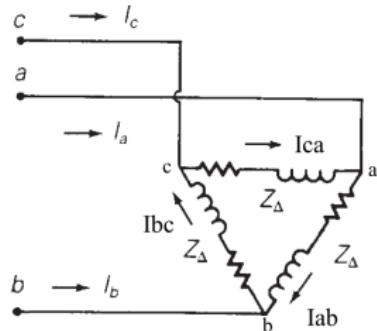
# Complex power in balanced $3\phi$ $\Delta$ -connected circuits

For the load connected between  $a$  and  $b$ :



$$\bar{V}_{ab} = V_{LL} e^{j\delta}$$

$$\bar{I}_{ab} = I_\Delta e^{j\beta}$$

$$\begin{aligned}\bar{S}_{ab} &= \bar{V}_{ab} \bar{I}_{ab}^* = V_{LL} e^{j\delta} I_\Delta e^{-j\beta} = V_{LL} I_\Delta e^{j(\delta-\beta)} \\ &= \underbrace{V_{LL} I_\Delta \cos(\delta - \beta)}_{P_{ab}} + j \underbrace{V_{LL} I_\Delta \sin(\delta - \beta)}_{Q_{ab}}\end{aligned}$$

For the entire load:

$$\bar{S}_{3\phi} = \bar{S}_{ab} + \bar{S}_{bc} + \bar{S}_{ca} = 3\bar{S}_{ab} = 3V_{LL} I_\Delta e^{j(\delta-\beta)}$$

$$P_{3\phi} = \text{Re}[\bar{S}_{3\phi}] = 3V_{LL} I_\Delta \cos(\delta - \beta) = \sqrt{3}V_{LL} I \cos(\delta - \beta) \text{ active power}$$

$$Q_{3\phi} = \text{Im}[\bar{S}_{3\phi}] = 3V_{LL} I_\Delta \sin(\delta - \beta) = \sqrt{3}V_{LL} I \sin(\delta - \beta) \text{ reactive power}$$

$$|\bar{S}_{3\phi}| = S_{3\phi} = \sqrt{{P_{3\phi}}^2 + {Q_{3\phi}}^2} = 3V_{LL} I_\Delta = \sqrt{3}V_{LL} I \quad \text{apparent power}$$

1 Balanced  $3\phi$  circuits


2 Power in balanced  $3\phi$  circuits

3 Unbalanced  $3\phi$  circuits


# Unbalanced 3 $\phi$ circuits

An unbalanced system is due to unbalanced voltage sources or an unbalanced load. Example:

Balanced 3 $\phi$  voltage set

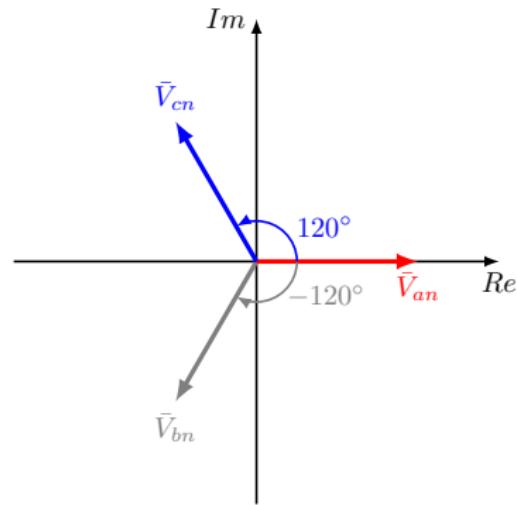


Unbalanced 3 $\phi$  voltage set

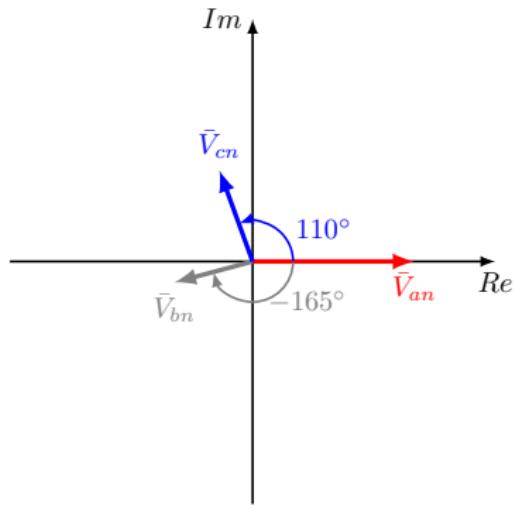

*Symmetrical Components (Fortescue, 1909):* any 3 $\phi$  voltage/current set can be resolved into three sets of sequence components: zero (0), positive (+) and negative (-)

# Exemple 2.4 (p.61)

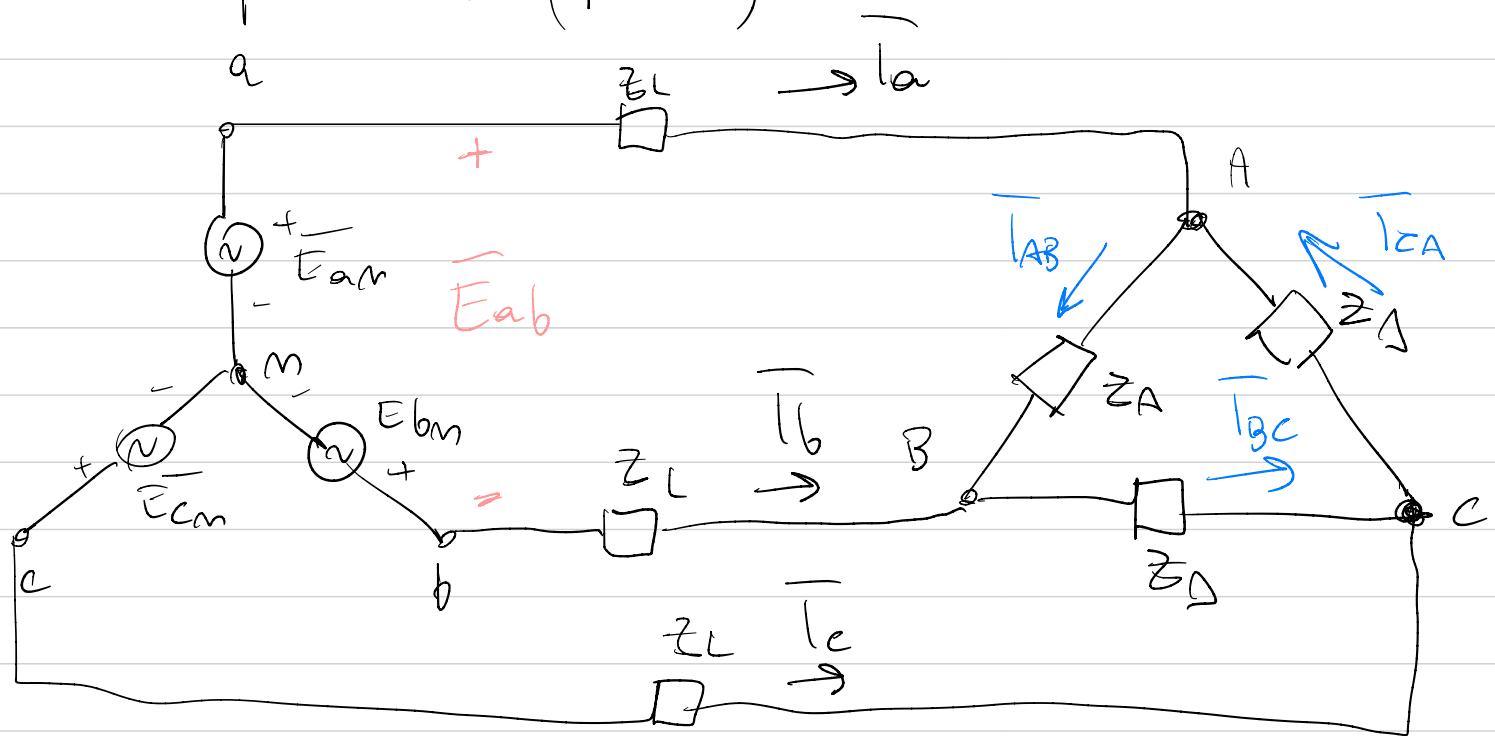

$$Z_A = 30 \angle 40^\circ \Omega \quad Z_L = 1 \angle 85^\circ \Omega$$

$$\bar{E}_{ab} = 480 \angle 0^\circ V \quad (\text{line to line})$$


- $\bar{I}_a, \bar{I}_b, \bar{I}_c = ?$
- $\bar{V}_{AB}, \bar{V}_{BC}, \bar{V}_{CA} = ?$
- $\bar{I}_{AB}, \bar{I}_{BC}, \bar{I}_{CA} = ?$

(1) Transform the  $\Delta$  load into  $\gamma$  load




$$Z_\gamma = \frac{Z_\Delta}{3} = \frac{30 \angle 40^\circ}{3} = 10 \angle 40^\circ \Omega$$

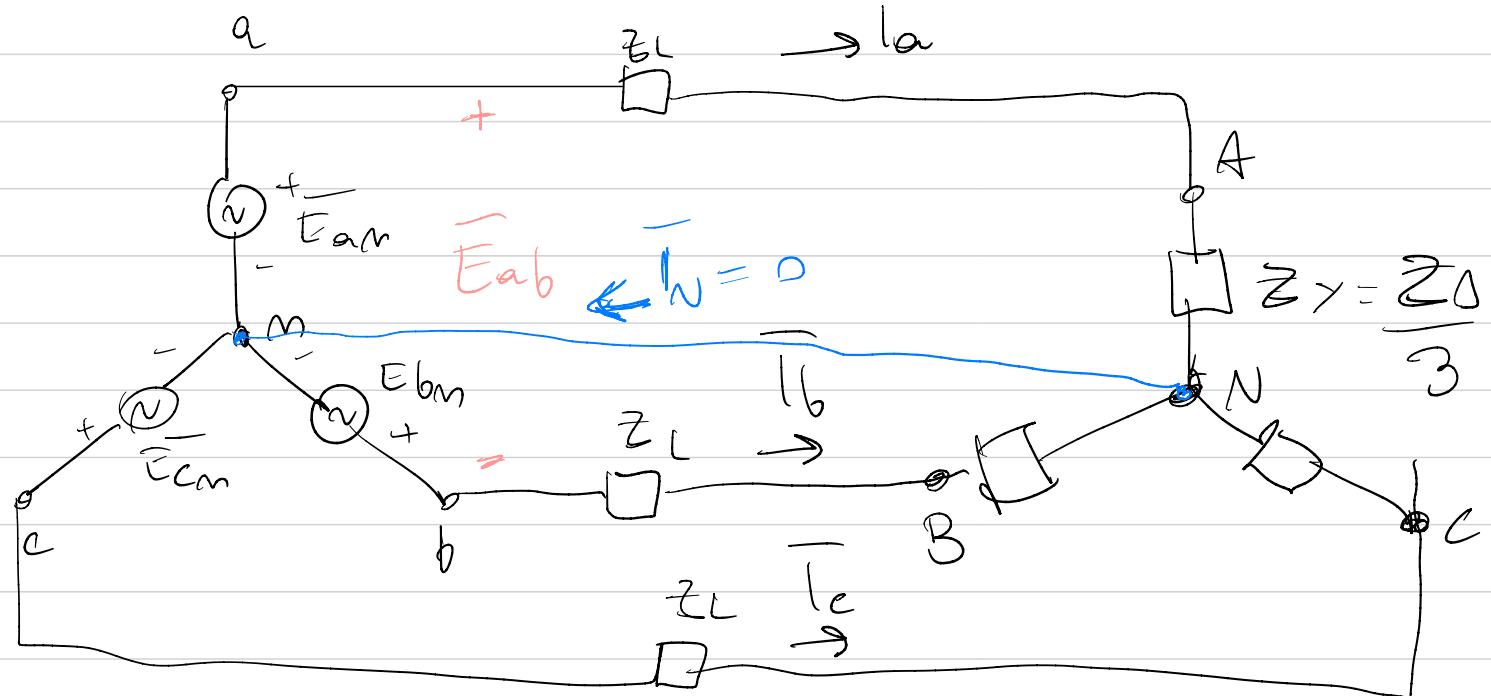(2) Study simple phase ( $\gamma$ ) equivalent



Study simple phase equivalent (phase a)

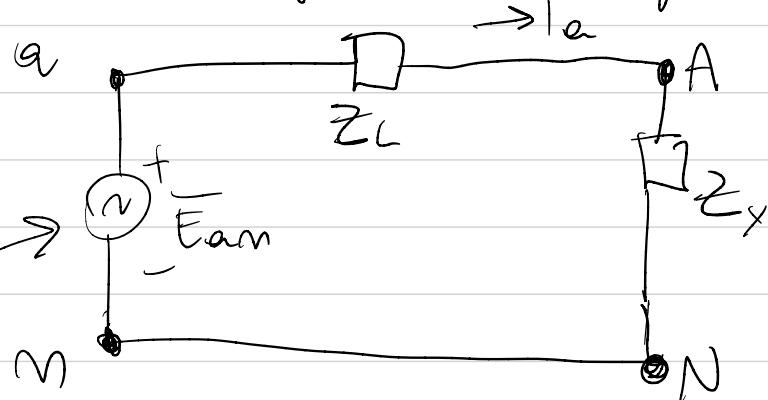


$$\bar{E}_{am} = ?$$

$$\bar{E}_{ab} = \sqrt{3} \bar{E}_{am} e^{+j\frac{\pi}{6}}$$

$$\bar{E}_{am} = \frac{h80 [0^\circ - 30^\circ]}{\sqrt{3}} = \frac{h80 [-30^\circ]}{\sqrt{3}} V$$

$$h80 [0^\circ] = \bar{E}_{ab}$$

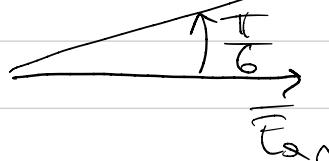

$$\bar{E}_{am} = \frac{\bar{E}_{ab}}{\sqrt{3}} e^{-j\pi/6}$$

$$\bar{I}_a = \frac{\bar{E}_{an}}{Z_L + Z_y} = \left( \frac{480}{\sqrt{3}} \right) \angle -30^\circ = 25.83 \angle -73.8^\circ A$$

$$\bar{I}_b = 25.83 \angle -73.8^\circ - 120^\circ = 25.83 \angle 167^\circ$$

$$\bar{I}_c = 25.83 \angle -73.8^\circ + 120^\circ = 25.83 \angle 16.2^\circ$$

Currents on the  $\Delta$ -load?

$$\bar{I}_{AB} = \frac{\bar{I}_a}{\sqrt{3}} e^{j\frac{\pi}{6}} = \frac{\bar{I}_a}{\sqrt{3}} \angle -73.8^\circ + 30^\circ = 1h.91 \angle -43.8^\circ A$$

$$\bar{I}_{BC} = 1h.91 \angle -43.8^\circ - 120^\circ = 1h.91 \angle -163.8^\circ A$$

$$\bar{I}_{CA} = 1h.91 \angle -43.8^\circ + 120^\circ = 1h.91 \angle +76.2^\circ A$$

load voltages

$$\bar{V}_{AB} = \bar{I}_{AB} \cdot Z_\Delta = 1h7.33 \angle -3.78^\circ V$$


$$\bar{V}_{BC} = 1h7.3 \angle -123.78^\circ V$$

$$\bar{V}_{CA} = 1h7.3 \angle 116.22^\circ V$$

# Symmetrical components method


Represent any  $3\phi$  vector set as the superposition of 3 balanced,  $3\phi$  sets:

$$V_{a0} \quad V_{b0} \quad V_{c0}$$

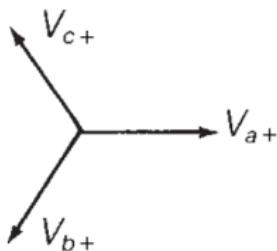



(a) Zero-sequence components

(b) Positive-sequence components

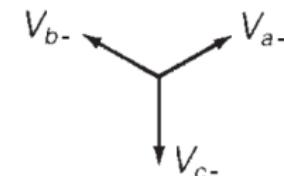

(c) Negative-sequence components


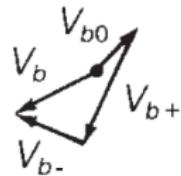
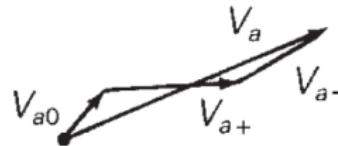
Example of a three-phase unbalanced set  $\bar{V}_a, \bar{V}_b, \bar{V}_c$ , where each voltage phasor is built using sequence components:



## Symmetrical components method (cont'd)



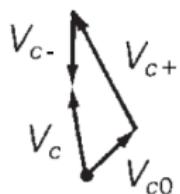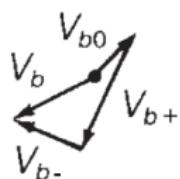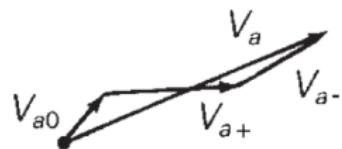Example of a three-phase unbalanced set  $\bar{V}_a, \bar{V}_b, \bar{V}_c$ , where each voltage phasor is built using sequence components:





$$\overbrace{\bar{V}_a = \bar{V}_{a0} + \bar{V}_{a+} + \bar{V}_{a-}}$$

$$\overbrace{\bar{V}_b = \bar{V}_{b0} + \bar{V}_{b+} + \bar{V}_{b-}}$$

$$\overbrace{\bar{V}_c = \bar{V}_{c0} + \bar{V}_{c+} + \bar{V}_{c-}}$$

$$V_{a0} \quad V_{b0} \quad V_{c0}$$

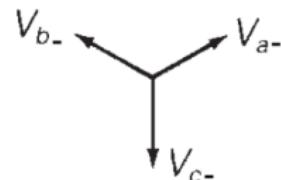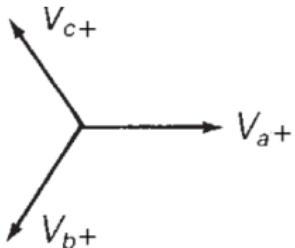

(a) Zero-sequence components

$$\bar{V}_{a0}$$

$$\bar{V}_{b0} = \bar{V}_{a0}$$

$$\bar{V}_{c0} = \bar{V}_{a0}$$

(b) Positive-sequence components

$$\bar{V}_{a+}$$

$$\bar{V}_{b+} = (\bar{V}_{a+})e^{-j\frac{2\pi}{3}}$$

$$\bar{V}_{c+} = (\bar{V}_{a+})e^{j\frac{2\pi}{3}}$$

(c) Negative-sequence components

$$\bar{V}_{a-}$$

$$\bar{V}_{b-} = (\bar{V}_{a-})e^{j\frac{2\pi}{3}}$$

$$\bar{V}_{c-} = (\bar{V}_{a-})e^{-j\frac{2\pi}{3}}$$

$$\begin{bmatrix} \bar{V}_a \\ \bar{V}_b \\ \bar{V}_c \end{bmatrix} = \begin{bmatrix} 1 & 1 & 1 \\ 1 & \alpha^2 & \alpha \\ 1 & \alpha & \alpha^2 \end{bmatrix} \begin{bmatrix} \bar{V}_{a0} \\ \bar{V}_{a+} \\ \bar{V}_{a-} \end{bmatrix}$$

$$\begin{bmatrix} \bar{V}_{a0} \\ \bar{V}_{a+} \\ \bar{V}_{a-} \end{bmatrix} = \frac{1}{3} \begin{bmatrix} 1 & 1 & 1 \\ 1 & \alpha & \alpha^2 \\ 1 & \alpha^2 & \alpha \end{bmatrix} \begin{bmatrix} \bar{V}_a \\ \bar{V}_b \\ \bar{V}_c \end{bmatrix}$$


where  $\alpha = e^{j\frac{2\pi}{3}}$ ,  $\alpha^2 = e^{-j\frac{2\pi}{3}}$  and  $\bar{V}_a, \bar{V}_b, \bar{V}_c$  the  $3\phi$  unbalanced phasor set
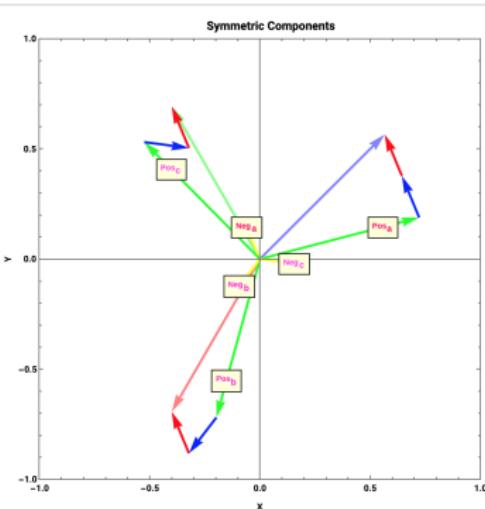
# Symmetrical components method (continued)

Balanced  $3\phi$  voltage set




Unbalanced  $3\phi$  voltage set  
(phase a angle is not zero)



Figures from:


<https://demonstrations.wolfram.com/FortescuesTheoremForAThreePhaseUnbalancedSystem>
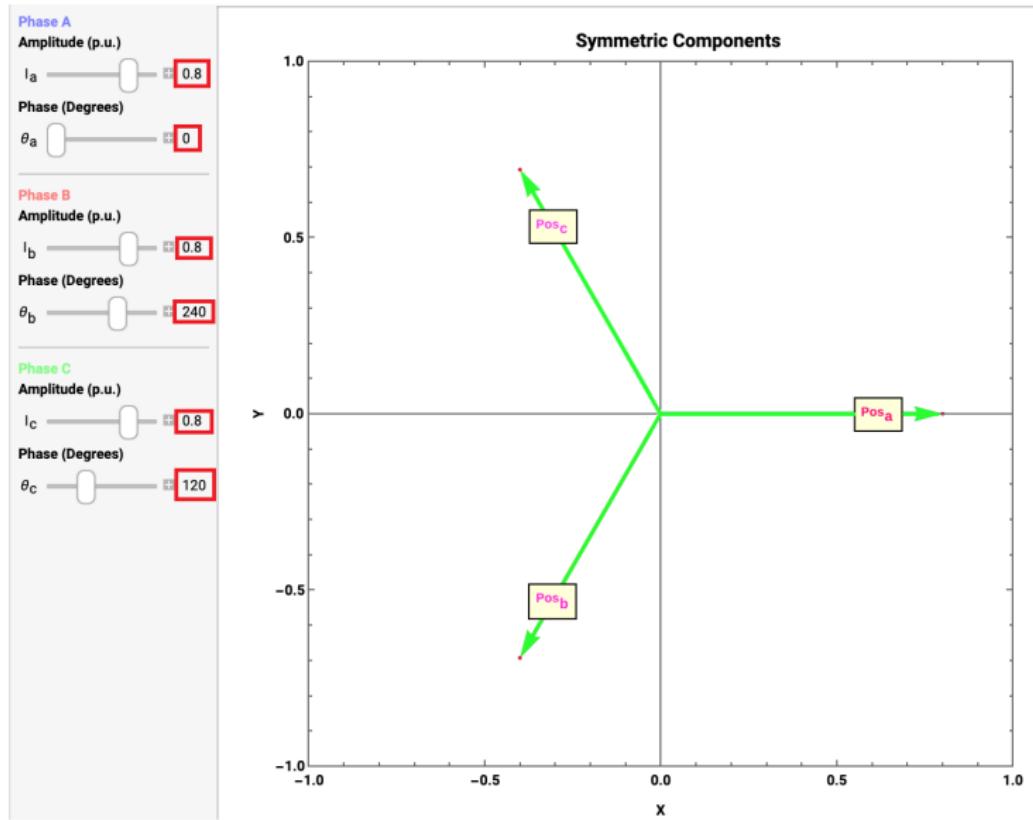
## Balanced $3\phi$ voltage set: has only positive-sequence components



Unbalanced  $3\phi$  voltage set: has positive, negative and zero-sequence components  
 (in this example the unbalance is due *Phase A* angle not being  $0^\circ$  (but  $45^\circ$ )
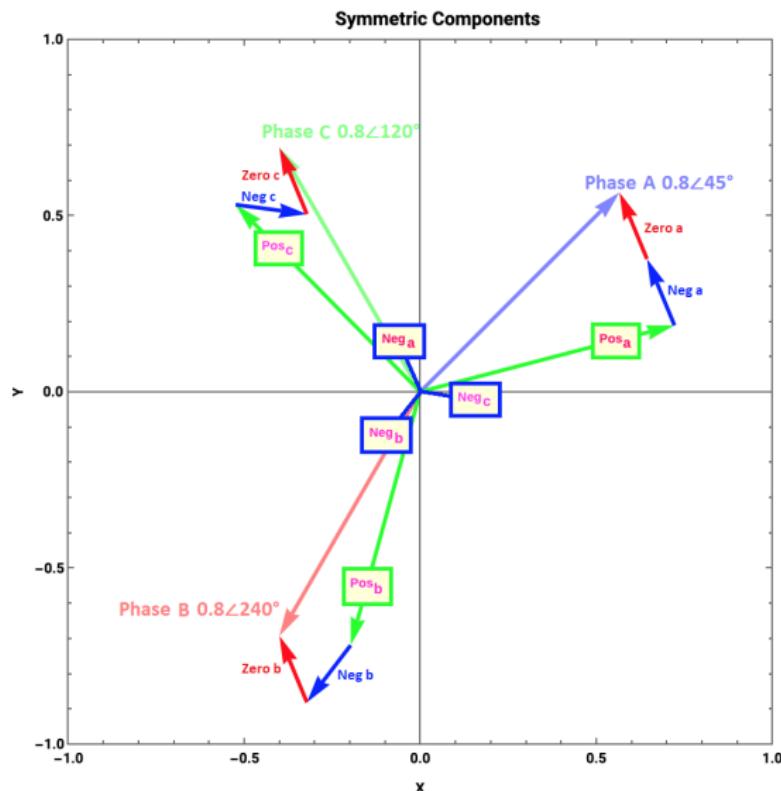
<b>Phase A</b>
Amplitude (p.u.)
$I_a$ 0.8
Phase (Degrees)
$\theta_a$ 45
<b>Phase B</b>
Amplitude (p.u.)
$I_b$ 0.8
Phase (Degrees)
$\theta_b$ 240
<b>Phase C</b>
Amplitude (p.u.)
$I_c$ 0.8
Phase (Degrees)
$\theta_c$ 120



# Readings

From *Glover (2017), Power System Analysis and Design*

- Chapter 2: Fundamentals (MQ library [link](#))
  - ▶ 2.5: Balanced Three-Phase Circuits
    - ★ Example 2.4: Balanced- $\Delta$  and Y-Loads
  - ▶ 2.6: Power in Balanced Three-Phase Circuits
    - ★ Example 2.5: Power in a balanced three-phase system
  - ▶ 2.7: Advantages of Balanced Three-Phase versus Single-Phase Systems

## References

- Glover, J. D., Overbye, T. J., & Sarma, M. S. (2017). Chapter 2 in *Power system analysis & design* (Sixth edition). Boston, MA, USA: Cengage Learning