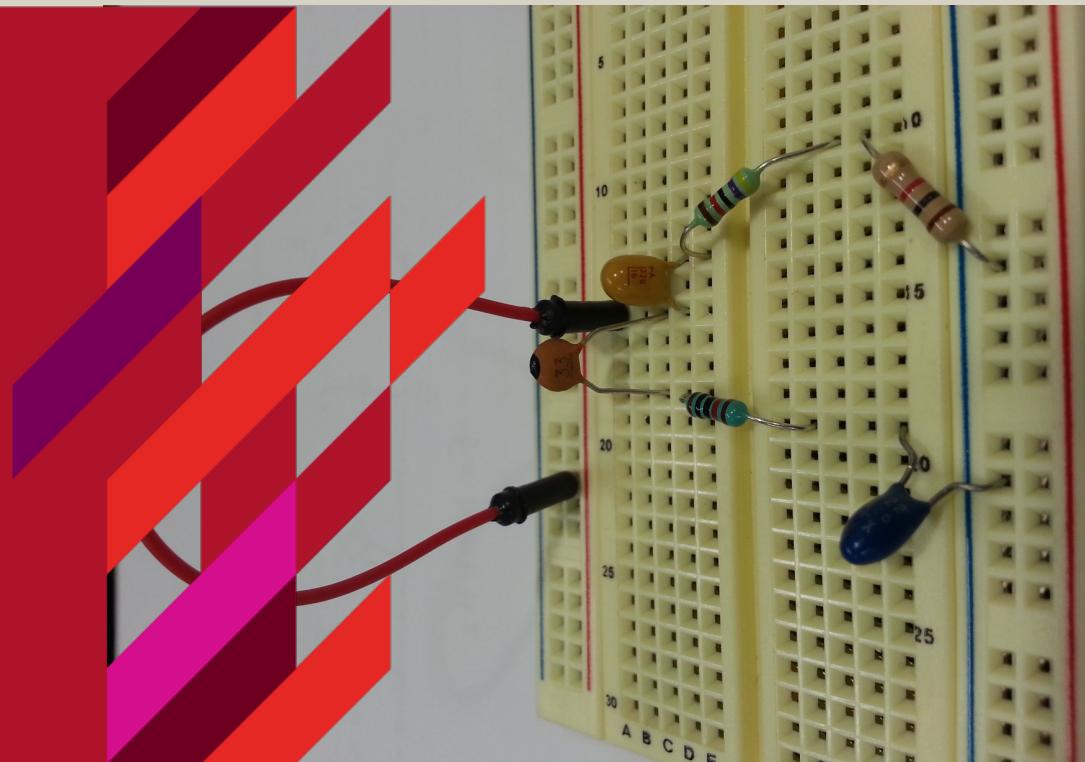




# ELEC2070 Circuits and Devices

Week 2: Power transfer + Energy storage elements (capacitors + inductors)


Stuart Jackson





MACQUARIE  
University

# Maximum power transfer

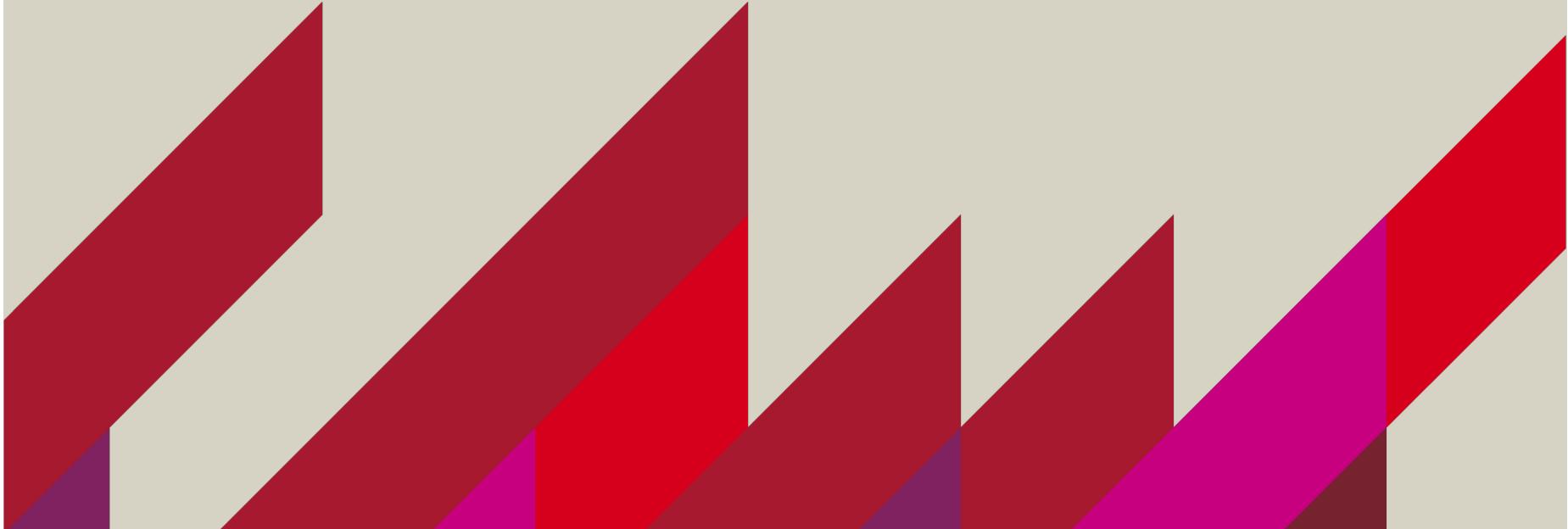


# Instantaneous Power




The definition is correct for any circuit element

## Instantaneous power

$$p(t) = v(t) \cdot i(t) \text{ W}$$

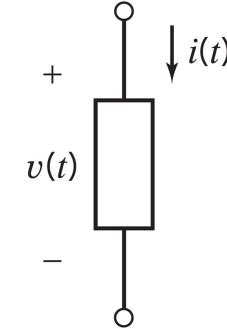


Example 10.6-3 voltage and current

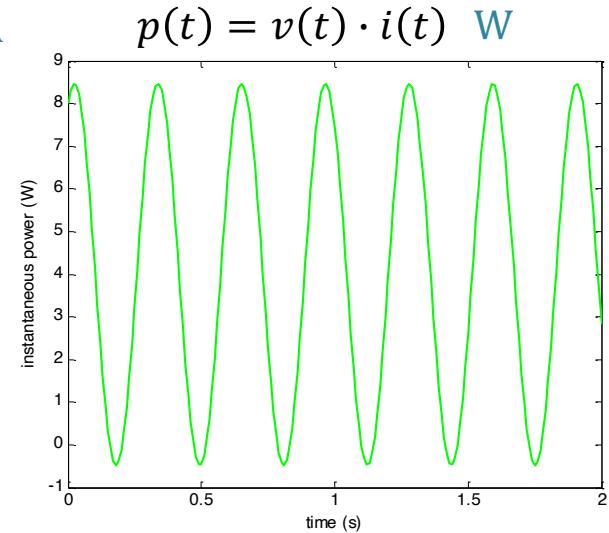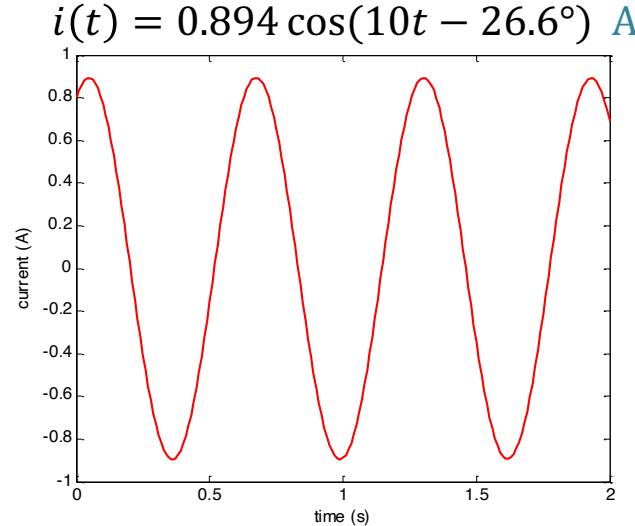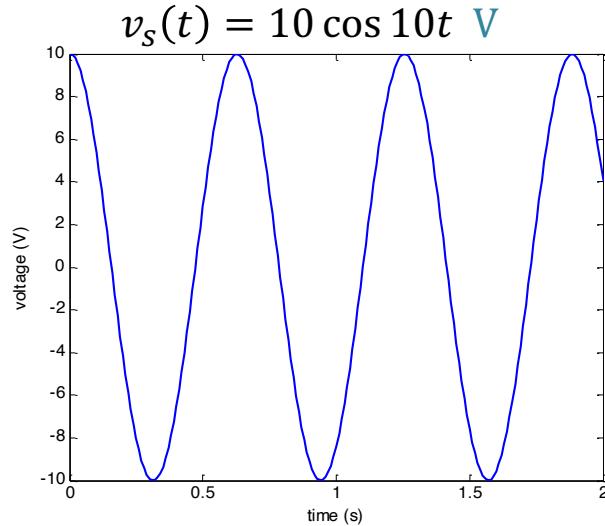

# Power has direction

Because current has direction (relative to voltage)

---

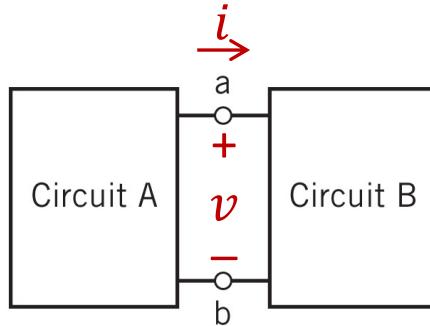

$$p(t) = v(t) \cdot i(t) \text{ W}$$

In this example power is transferred from left to right (assuming voltage and current are positive in the direction shown).


Circuit A is supplying it and Circuit B is receiving it.

Instantaneous power is also conserved. Total power (in a closed circuit) is zero.

$p(t) > 0$  power received

$p(t) < 0$  power supplied

# Power transfer

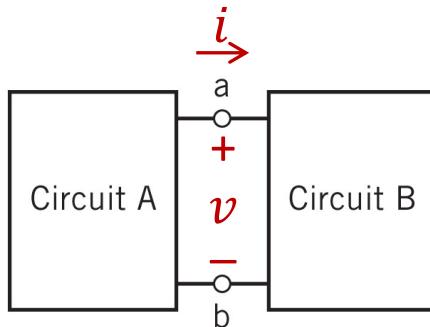

$$p(t) = v(t) \cdot i(t) \text{ W}$$



Circuit A and Circuit B are arbitrary.


(They can also be the two parts of the same circuit.)

**We can calculate power transferred from any part to any other part if we know the voltage and the current at the intersection between the 2 circuits.**

# Employing our equivalent circuits

Is a simpler circuit with the same terminal voltage and current

---

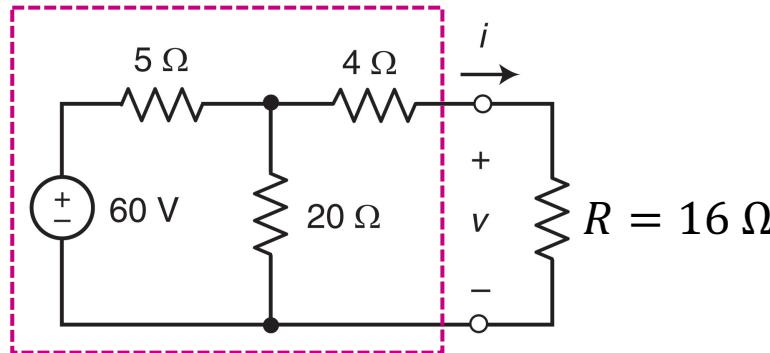

$$p(t) = v(t) \cdot i(t) \text{ W}$$


To find the power received by  $R$  we need to know its voltage and current but **not the other voltages and currents in the circuit.**

We can use an equivalent circuit for the rest of the circuit as long as we don't change the voltage across  $R$  and the current through  $R$ .


If there are current or voltage sources in the rest of the circuit, we can use Thevenin or Norton equivalent circuits.

# Transferred power - example

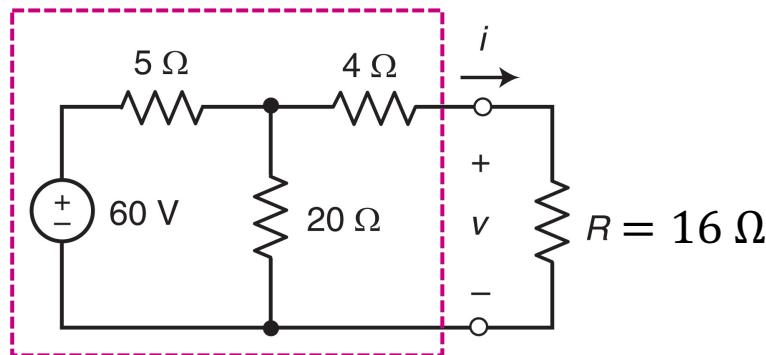Question: Find the power transferred to  $R$  ( $= 16 \Omega$ ) (we will use  $p = v \times i$ )



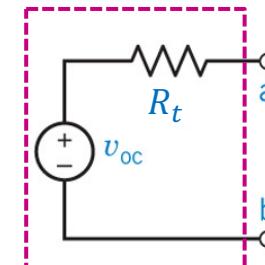1. First find the Thévenin equiv. of LHS:



$$v_{oc} = 48 \text{ V}$$

$$R_t = 8 \Omega$$

2. Now connect the equivalent circuit to  $R$

Use voltage divider rule:  $v = \frac{R}{R+R_t} v_{oc} = 32 \text{ V}$

Next use Ohm's Law to find current:  $i = \frac{v_{oc}}{R+R_t} = 2 \text{ A}$


Therefore the transferred power is:  $p = 64 \text{ W}$



# Maximum power transfer

---


Circuit A

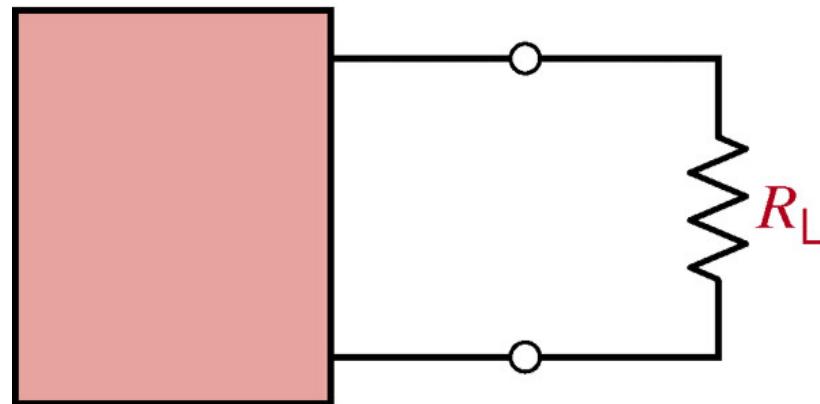

We can calculate the maximum power available to  $R_L$ , without knowing the value of  $R_L$ .



# Replace circuit A with Thévenin

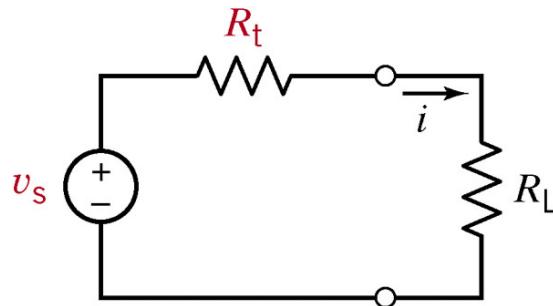

Want to find the value of  $R_L$  that results in the maximum power delivered to it.

Now, the power dissipated by  $R_L$  is  $p = i^2R_L$

But the current is  $i = v_s / (R_t + R_L)$  therefore the power in  $R_L$  is:  $p = (\frac{v_s}{R_t + R_L})^2 R_L$

Assuming  $v_s$  and  $R_t$  are constant:

Then the change in power (in  $R_L$ ) with the change in  $R_L$  or  $\frac{dp}{dR_L} = v_s^2 \frac{(R_t + R_L)^2 - 2(R_t + R_L)R_L}{(R_t + R_L)^4}$

Now the maximum power is when  $\frac{dp}{dR_L} = 0$  or  $(R_t + R_L)^2 - 2(R_t + R_L)R_L = 0$

or  $R_t + R_L - 2R_L = 0$  or

$$R_L = R_t$$


This says: a resistor connected to a circuit A will receive the maximum power from A when its resistance is equal to the Thévenin resistance of A.


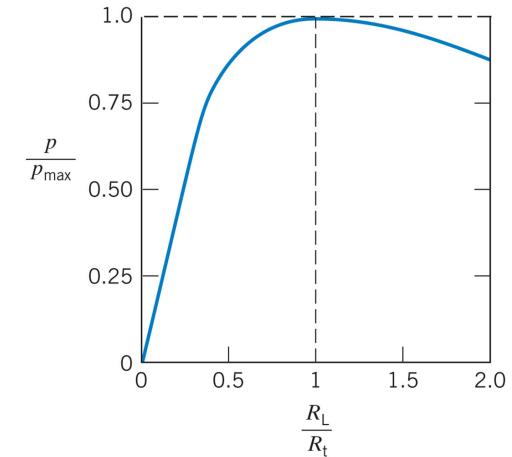
# Maximum power transfer

Since the power is given by:  $p = \left(\frac{v_s}{R_t + R_L}\right)^2 R_L$

Substituting  $R_L = R_t$  we get the maximum power  $p_{max} = \frac{v_s^2}{4R_t}$



Using:  $R_L = R_t$  and  $R_t = \frac{v_{oc}}{i_{sc}}$

You can calculate all the following (and more) using this condition:

$$p_{max} = \left(\frac{v_{oc}}{2}\right)^2 \frac{1}{R_t}$$


$$p_{max} = \left(\frac{i_{sc}}{2}\right)^2 R_t$$

$$p_{max} = \frac{v_{oc} i_{sc}}{4}$$

**Homework: Check if formulas are correct!**



# Maximum available power


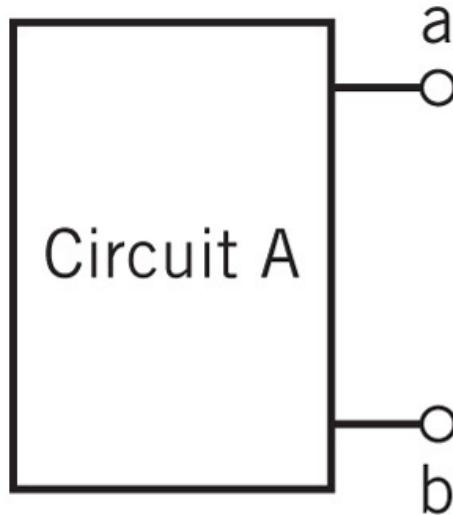


Maximum available power from any circuit (with sources) is the power that could be delivered by that circuit when it is terminated by a resistance that is equal to its Thévenin resistance.

**“Maximum available power” may also be called “available power”**



# Previous example problem

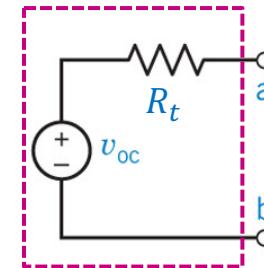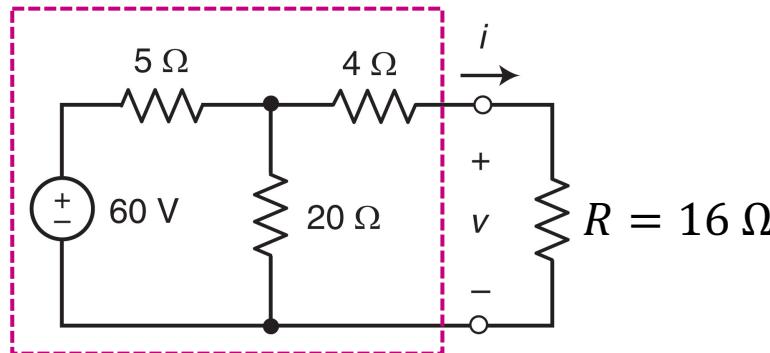

$$v_{oc} = 48 \text{ V}$$

$$R_{th} = 8 \Omega$$

The maximum available power can only be transferred if:  $R = R_t = 8 \Omega$

So calculating the max. power transfer: ( $= v \times i$ )

$$\text{The voltage across } R: v = \frac{R}{R + R_t} v_{oc} = \frac{8}{8 + 8} \times 48 = 24 \text{ V}$$

$$\text{The current through } R: i = \frac{v_{oc}}{R + R_t} = 3 \text{ A}$$

Max. power transferred:

$$p_{max} = 72 \text{ W}$$

Compared to 64 W  
when  $R = 16 \Omega$





# Example problem 1

Find the resistance  $R_L$  that will result in the maximum power delivered.

Find Thévenin equivalent circuit of LHS

$v_{oc}$  can be found by voltage divider rule:  $v_{oc} = 180 \times (150/180) = 150 \text{ V}$

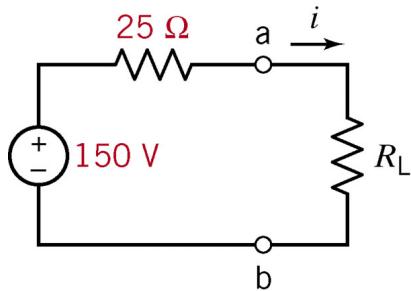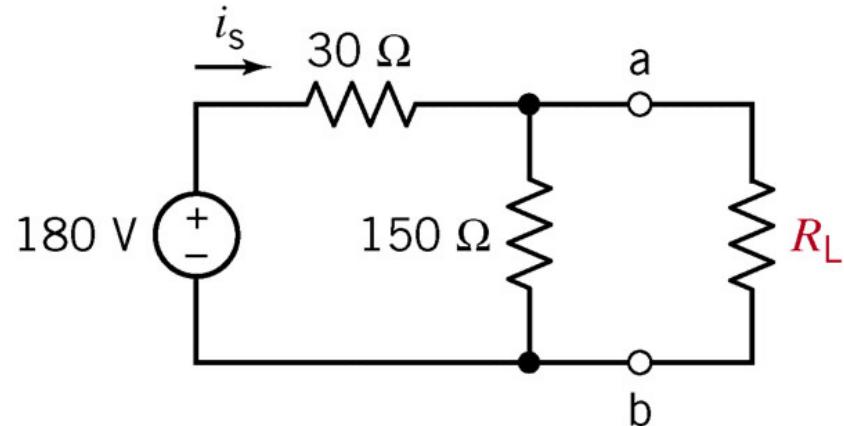$R_t$  can be found by switching off the 180 V source,  $R_t = 30 \times 150 / 180 = 25 \Omega$



Max. power when  $R_L = 25 \Omega$

$$\text{Power} = v_{ab} \times i = 75 \times (150/50) = 225 \text{ W}$$

$$\text{Check: } p_{max} = \frac{v_{oc}^2}{4R_t} = \frac{150^2}{4 \times 25} = 225 \text{ W}$$



# Example problem 2

Find  $R_L$  in circuit (a) that allows maximum power transfer and find that power.

(Need to find Thévenin equiv. of LHS)

Use fig. (b) to find  $v_{oc}$ :

Using KVL we have:

$$-6 + (6+4)i - 2v_{ab} = 0$$

But using Ohm's Law:  $v_{ab} = 4i$

Therefore:  $-6 + 10i - 8i = 0$

Or:  $i = 3 \text{ A}$


Hence:  $v_{oc} = v_{ab} = 12 \text{ V}$

Use fig. (c) to find  $i_{sc}$  (note  $v_{ab} = 0$ )


KVL around loop:  $-6 + 6i_{sc} = 0$

Hence:  $i_{sc} = 1 \text{ A}$ .


Therefore  $R_t = 12/1 = 12 \Omega$

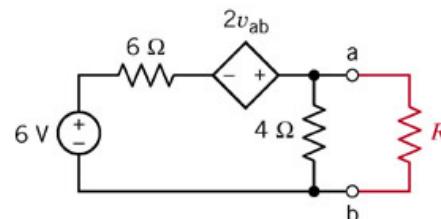


(a)

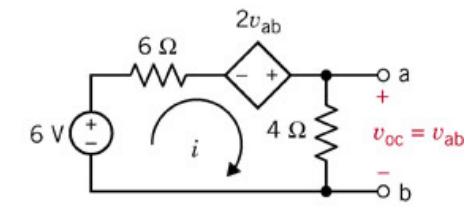

(b)

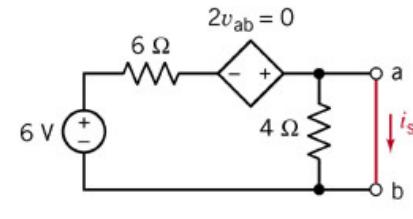

(c)

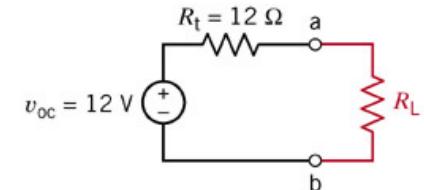

(d)

$$R_L = R_t = 12 \Omega$$

$$\text{Max. power delivered} = v_{oc}^2 / 4R_t$$

$$= (12)^2 / 4 \times 12 = 3 \text{ W}$$



MACQUARIE  
University

# ENERGY STORAGE ELEMENTS





# The “Big Ideas” in Chap. 7

---

- **Capacitors and inductors** store energy (as opposed to resistors, which dissipate energy) – they are **PASSIVE** elements
- While they are classed as linear elements, the current-voltage relationships are a function of time
- Their general behaviour in a circuit is represented by differential equations (as opposed to resistors, which are simply related by Ohm’s Law).
- A set of series/parallel capacitors (or inductors) can be reduced to an equivalent capacitor (or inductor). The formulas for inductors are similar to those for resistances. The formulas for capacitors are similar to those of conductances.
- In a DC circuit (or in any circuit when currents and voltages do not change with time), **capacitors act like open circuits**, and **inductors act like short circuits**.
- Signals can be integrated or differentiated using circuits that contain capacitors or inductors.




# Capacitors

Pass current ONLY when the voltage is changing




# Capacitor basics

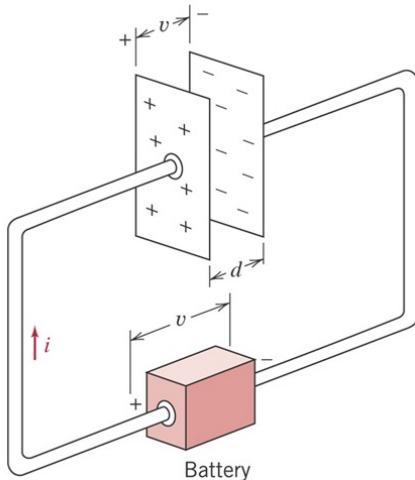

A capacitor is a two terminal element which can be modelled as two parallel conducting plates separated by a non-conducting material, called a *dielectric*. Electric charge is stored on the plates.

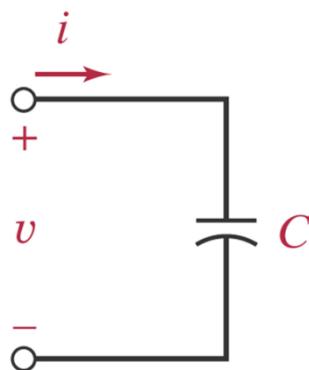The **capacitance** ( $C$ ) is directly proportional to the area ( $A$ ) of the dielectric and inversely proportional to the spacing ( $d$ ) between the plates



$$C = \frac{k\epsilon_0 A}{d}$$


Where     $C$  = the capacitance in **farads** (F)  
 $k$  = is the relative permittivity (dielectric constant)  
 $\epsilon_0$  = permittivity of free space  
 $d$  = distance between the plates

$$\epsilon = \epsilon_0 = 8.854 \text{ pF/m.}$$

# Energy is stored in the electric field between the plates




MACQUARIE  
University

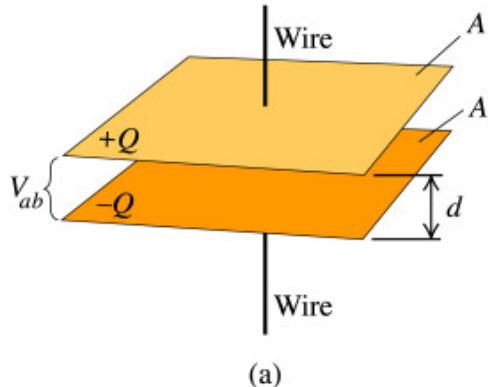

$$E = \frac{V}{d}$$

Electric field

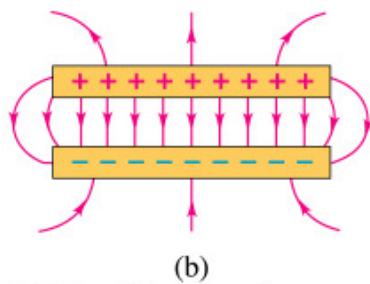

$$C = \frac{Q}{V}$$

Electric charge  
Voltage

*Coulombs per volt*  
1 Farad=1 C per V

Copyright © Addison Wesley Longman, Inc.

<http://www.physics.sjsu.edu/becker/physics51/capacitors.htm>

**Self study:**


**Learn what a “displacement current” is**


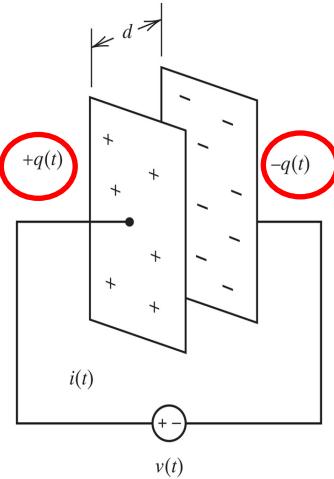
# The important equations

---

The charge stored by a capacitor:  $q(t) = Cv(t)$



The capacitor current is given by:  $i(t) = \frac{d}{dt} q(t)$

Hence capacitor current is:

$$i(t) = C \frac{d}{dt} v(t)$$

The capacitor voltage is given by:

$$v(t) = \frac{1}{C} \int_{-\infty}^t i(\tau) d\tau$$

# Types of capacitors

## Integrated circuit capacitors:

Practical capacitance values on CMOS wafers range from 0.5 pF to a few tens of picofarads.


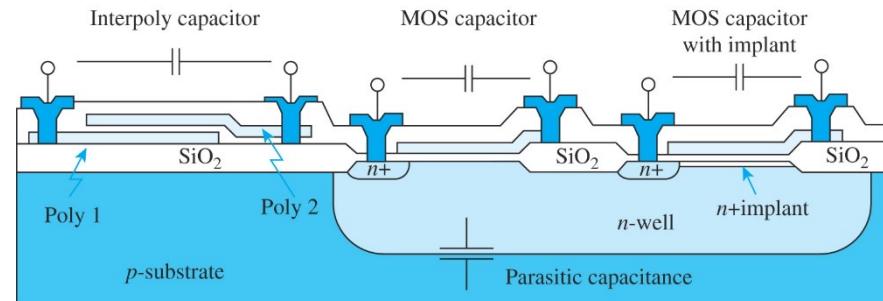
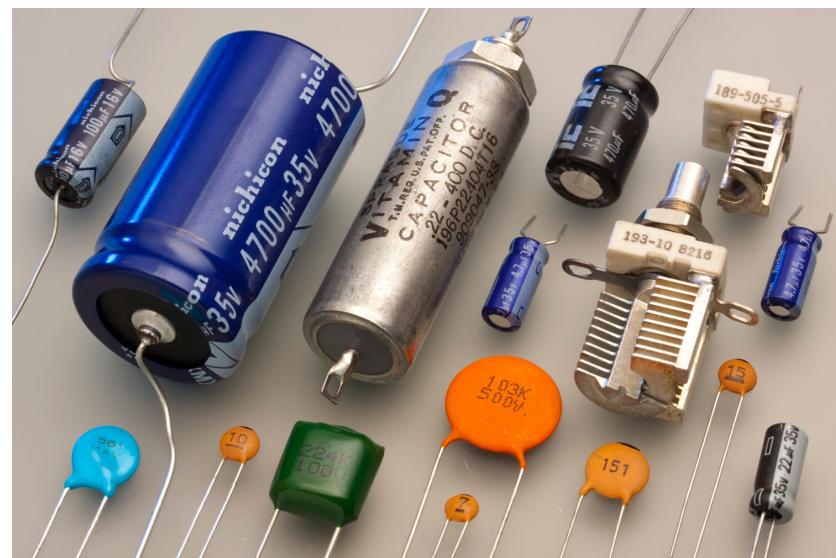


Figure A.8 Interpoly and MOS capacitors in an *n*-well CMOS process.

SEDRA/SMITH "Microelectronic Circuits" 6<sup>th</sup> Edition, Oxford University Press
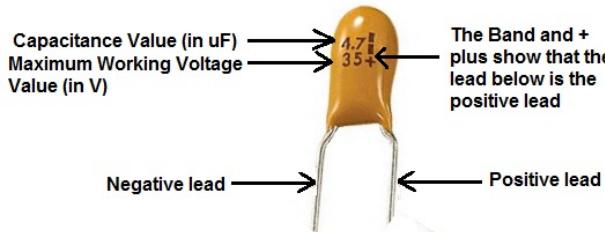
## Discrete capacitors:


<http://www.learningaboutelectronics.com/images/How-to-read-a-tantalum-capacitor.png>





# “Real” capacitors

---

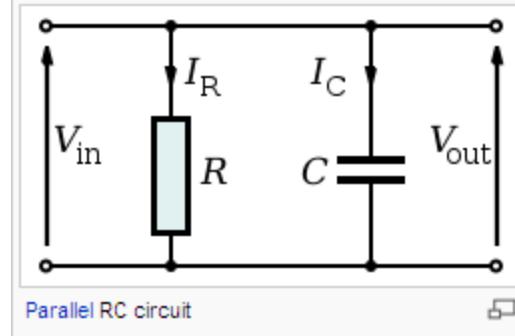

Physical capacitors may be modelled by a resistance in parallel with the capacitor. The dielectric material between the plates is not a perfect insulator. The effect of the dielectric material is modelled as a high value resistor. Because the value of this resistance is quite large, the resistance is often ignored in circuit analysis.

# Points to note

---

Any two conducting surfaces not in direct contact with each other may be characterised by a nonzero (usually very small) capacitance.

A capacitance of several hundred microfarads ( $\mu\text{F}$  is considered “large”)




# Implications of the equations

---

Since current is proportional to the time rate of change of voltage, a CONSTANT voltage applied across a capacitor will result in NO current flow. This means capacitors are “open circuit to DC”
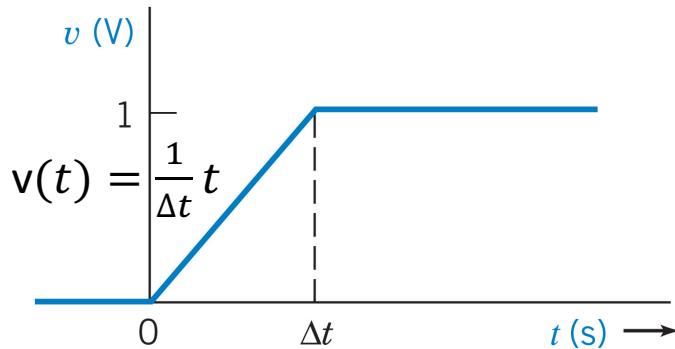
# Can we have an instantaneous voltage across a capacitor?



A voltage ramp will cause a constant current.

A constant current will cause a voltage ramp across the capacitor

Using  $i(t) = C \frac{d}{dt} v(t)$  we have:

$$i(t) = \begin{cases} 0 & t < 0 \\ \frac{C}{\Delta t} & 0 < t < \Delta t \\ 0 & t > \Delta t \end{cases}$$


Instantaneous voltage means  $\Delta t=0$  which implies  $i(t) = \frac{C}{\Delta t} = \infty$

→ **Voltage across a capacitor cannot change instantaneously**



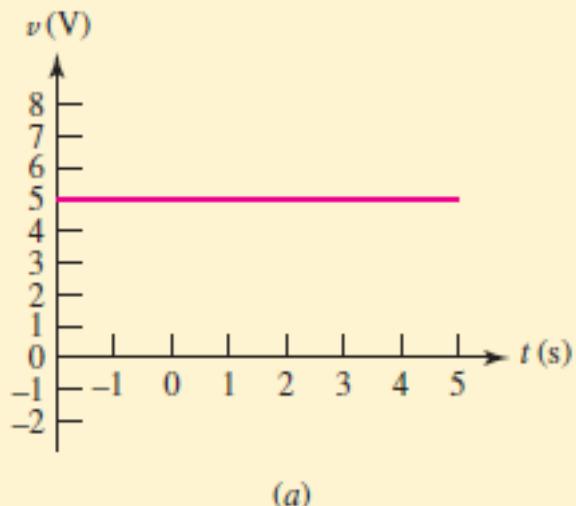
# Example problem

Determine the current  $i$  flowing through the capacitor of Fig. 7.1 for the two voltage waveforms of Fig. 7.3 if  $C = 2 \text{ F}$ .




(a)

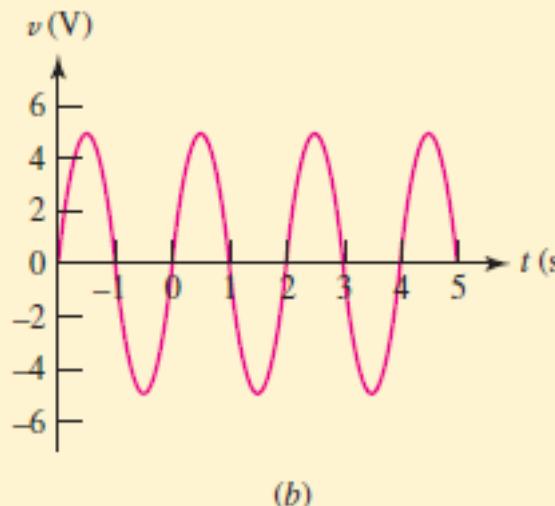

(b)

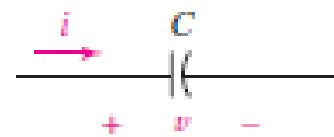■ **FIGURE 7.3** (a) A dc voltage applied to the terminals of the capacitor. (b) A sinusoidal voltage waveform applied to the capacitor terminals.



■ **FIGURE 7.1** Electrical symbol and current-voltage conventions for a capacitor.




# Solution


The current  $i$  is related to the voltage  $v$  across the capacitor by Eq. [1]:

$$i = C \frac{dv}{dt}$$

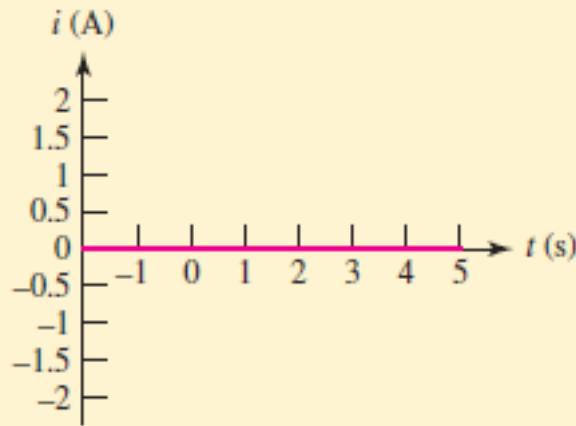For the voltage waveform depicted in Fig. 7.3a,  $dv/dt = 0$ , so  $i = 0$ ; the result is plotted in Fig. 7.4a. For the case of the sinusoidal waveform of Fig. 7.3b, we expect a cosine current waveform to flow in response, having the same frequency and twice the magnitude (since  $C = 2 \text{ F}$ ). The result is plotted in Fig. 7.4b.



(a)

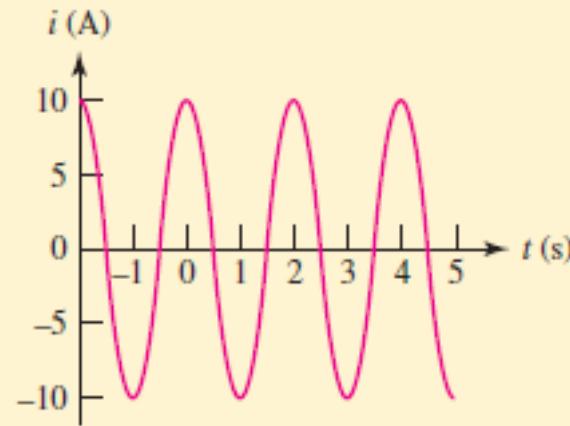

(b)

**FIGURE 7.4** (a)  $i = 0$  as the voltage applied is dc. (b) The current has a cosine form in response to a sine wave voltage.



# Initial conditions for voltage

---

The voltage can be found from :  $v(t) = \frac{1}{C} \int_{-\infty}^t i(\tau) d\tau$

Not that practical!!

Separate the time frames:  $v(t) = \frac{1}{C} \int_{-\infty}^{t_0} i(\tau) d\tau + \frac{1}{C} \int_{t_0}^t i(\tau) d\tau$



We get:  $v(t) = v(t_0) + \frac{1}{C} \int_{t_0}^t i(\tau) d\tau$

The initial voltage condition: the voltage across the capacitor at time =  $t_0$


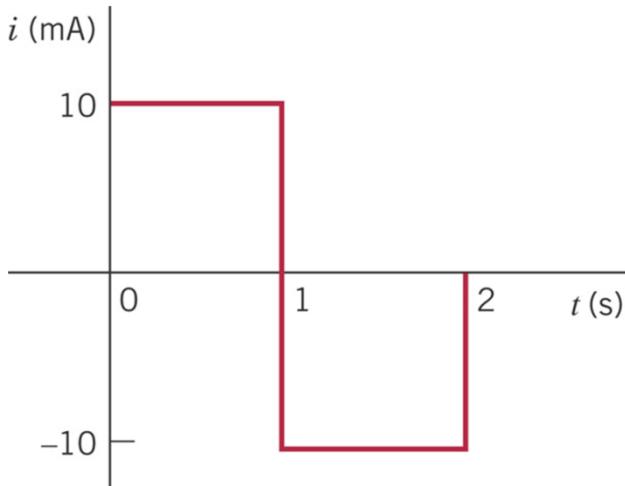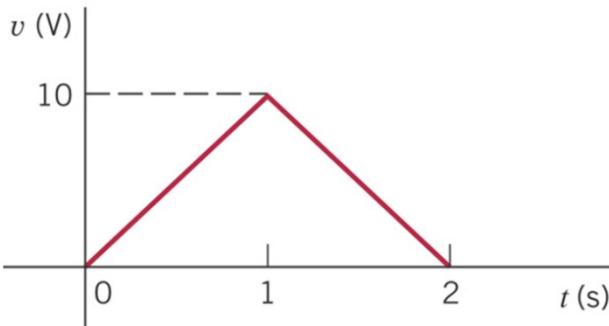
# Example problem

Find the current through the capacitor,  $C = 1 \text{ mF}$ , when the voltage across the capacitor is given by,



## Solution

$$v(t) = \begin{cases} 0, & t \leq 0, \\ 10t, & 0 < t \leq 1, \\ 20 - 10t, & 1 < t \leq 2, \\ 0, & t > 2. \end{cases}$$

$$i = C \frac{dv}{dt} = 10^{-3} \frac{dv}{dt}$$



$$= \begin{cases} 0, & t \leq 0, \\ 10^{-2}, & 0 < t < 1, \\ -10^{-2}, & 1 < t < 2, \\ 0, & t > 2. \end{cases}$$

Note that  $v$  is a continuous function of  $t$  and that  $i$  has discontinuities.


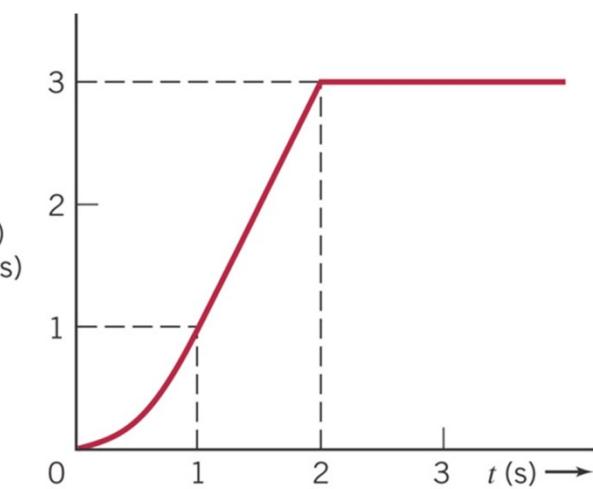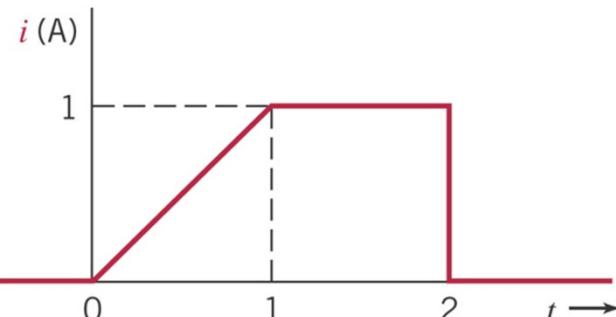
# Example problem

Find the voltage across the capacitor,  $C = \frac{1}{2}$  F, when the current through the capacitor is given by,



## Solution

$$i = \begin{cases} 0, & t < 0 \\ t, & 0 < t < 1, \\ 1, & t > 1. \end{cases}$$

For  $t < 0$ ,  $v = 0$

For  $t > 0$ ,



$$v = \frac{1}{C} \int_0^t id\tau = \begin{cases} \frac{1}{C} \int_0^t \tau d\tau = \frac{t^2}{2C}, & t < 1, \\ \frac{1}{C} \int_0^1 \tau d\tau + \frac{1}{C} \int_1^t 1 d\tau = v(1) + \frac{t-1}{C} = \frac{1}{2C} + \frac{t-1}{C}, & 1 \leq t < 2 \\ v(2) + \frac{1}{C} \int_2^t 0 d\tau = v(2) = \frac{3}{2C}, & 2 \leq t. \end{cases}$$

$$v = \begin{cases} 0, & t < 0 \\ t^2, & 0 \leq t < 1, \\ 2t - 1, & 1 \leq t < 2, \\ 3, & t \geq 2 \end{cases}$$

Putting in the value for  $C$



# Capacitor circuits with a switch

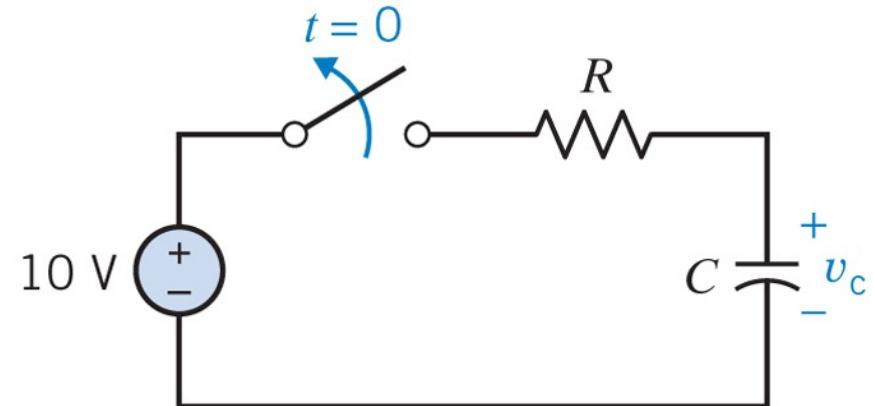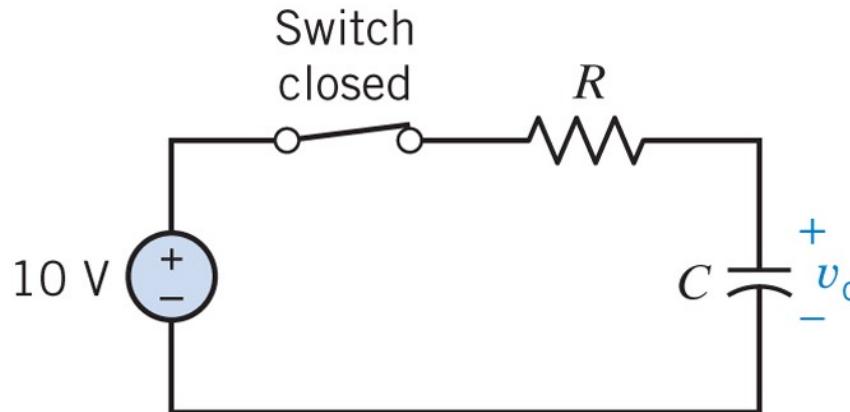

Voltage of a capacitor cannot change instantaneously:

Therefore the voltage across the capacitor in the above circuit:  $v_c(0^-) = v_c(0^+) = 10 \text{ V}$

$$v_c(t_0^-) = v_c(t_0^+)$$

The voltage across a capacitor just before  $t_0$  is the SAME as just after  $t_0$




MACQUARIE  
University

# Energy storage in a capacitor





# Energy storage in a capacitor

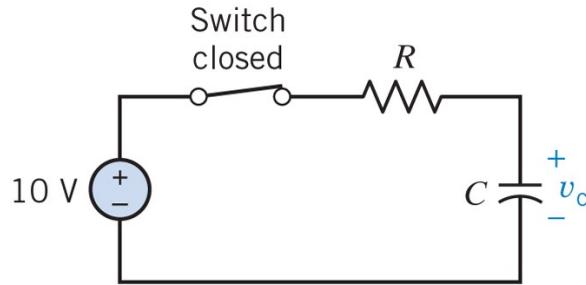

The definition of energy is given by:

$$w(t) = \int_{-\infty}^t p(\tau) d\tau$$

When we insert the definition of power we get:  $w_c(t) = \int_{-\infty}^t v_c(\tau)i(\tau)d\tau$

But for a capacitor:  $i(t) = C \frac{d}{dt} v_c(t)$

$$w_c(t) = \int_{-\infty}^t C v_c \frac{dv_c}{dt} d\tau = C \int_{v_c(-\infty)}^{v_c(t)} v_c dv_c = \frac{1}{2} C v_c^2 \Big|_{v_c(-\infty)}^{v_c(t)} = \frac{1}{2} C v_c^2(t) \text{ Joules}$$

$$w_c(t) = \frac{1}{2} C v_c^2(t)$$

Energy stored in the capacitor at time  $t$




# Energy is stored!

We have:  $w_c(t) = \frac{1}{2} C v^2(t)$  J

Or knowing  $C=q/v$ , then:
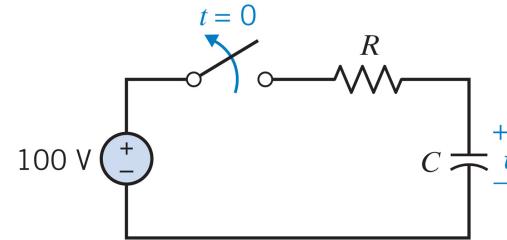
$$w_c(t) = \frac{1}{2C} q^2(t) \text{ J}$$




*Example:*

$$C = 10 \text{ mF}$$





$$v_c(0^-) = v_c(0^+) = 100 \text{ V}$$
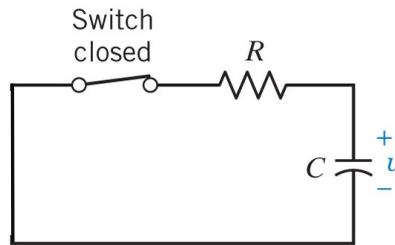
$$w_c(t) = \frac{1}{2} 10^{-2} 100^2 = 50 \text{ J}$$



If we later remove the voltage source and close the switch, all this energy will be dissipated in the resistor.

# Example problem

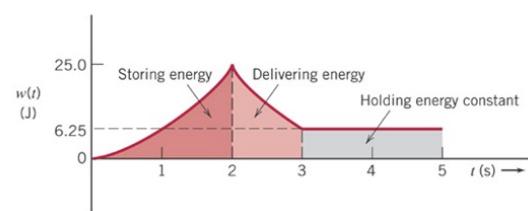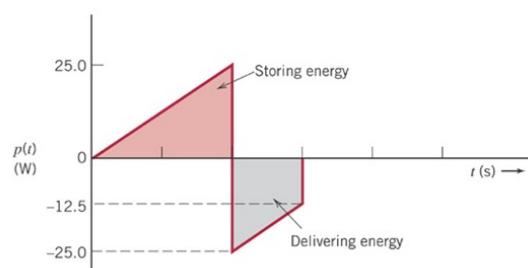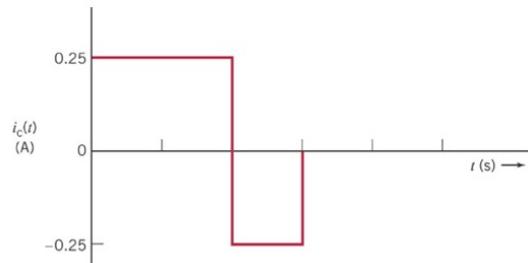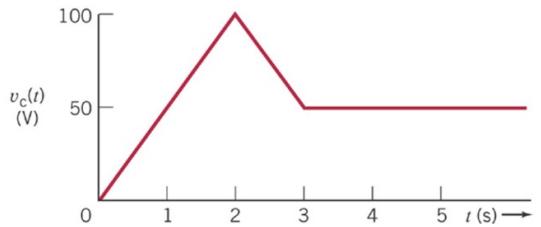

The voltage across a 5 mF capacitor varies as a function of time as shown. Determine and plot the capacitor current, power, and energy.

## Solution

$$i = C \frac{dv_c(t)}{dt}$$




$$P = v_c i = Cv_c \frac{dv_c(t)}{dt}$$

$$w_c = \int_0^t P(\tau) d\tau = \int_0^t Cv_c \frac{dv_c(t)}{dt} d\tau$$

(Note that  $w_c$  is the energy under the  $P$  curve.)

(c)

# Solution

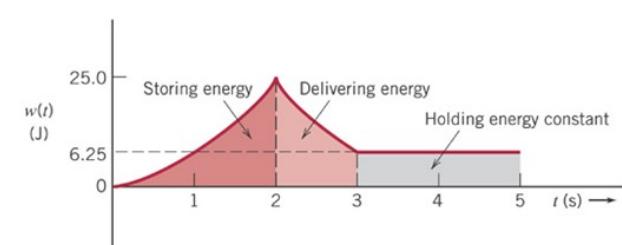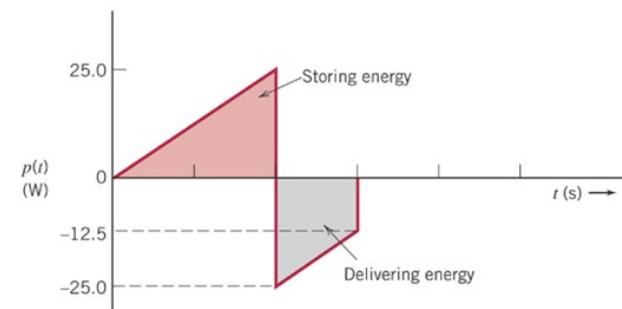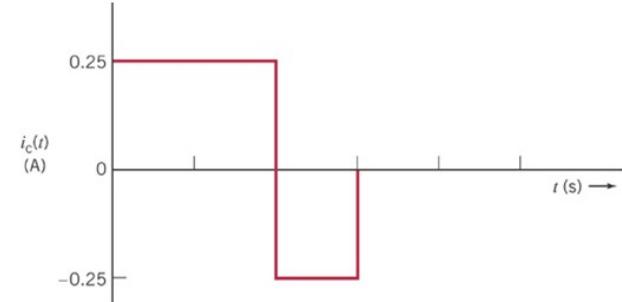

$$v = \begin{cases} 0, & t < 0, \\ 50t, & 0 \leq t < 2, \\ 200 - 50t, & 2 \leq t \leq 3, \\ 0, & t > 3 \end{cases}$$

$$i = C \frac{dv}{dt} = \begin{cases} 0, & t < 0, \\ 0.25, & 0 \leq t < 2, \\ -0.25, & 2 \leq t \leq 3, \\ 0, & t > 3 \end{cases}$$

$$p = vi = \begin{cases} 0, & t < 0, \\ 12.5t, & 0 \leq t < 2, \\ 12.5t - 50, & 2 \leq t \leq 3, \\ 0, & t > 3 \end{cases}$$

$$w_c = \int_0^t pd\tau = \begin{cases} 0, & t < 0, \\ 6.25t^2, & 0 \leq t < 2, \\ 25 + \int_2^t (200 - 50\tau)(-0.25)d\tau = 6.25t^2 - 50t + 100, & 2 \leq t \leq 3, \\ \int_0^3 pd\tau = 6.25 & t > 3 \end{cases}$$

$$C = 0.005 \text{ F}$$



MACQUARIE  
University


# Series and parallel combinations

Capacitors






# Parallel capacitors

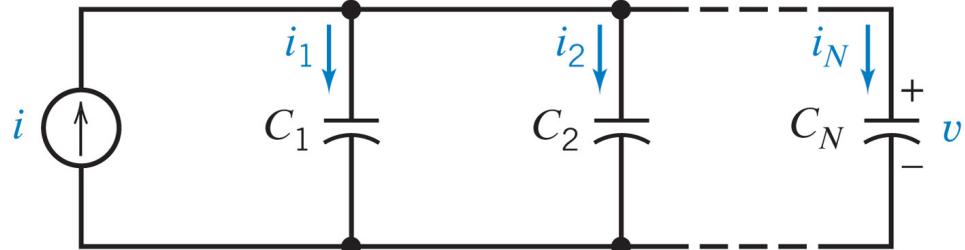

KCL:

$$i = i_1 + i_2 + \dots + i_N$$

$$i_n = C_n \frac{dv}{dt}$$

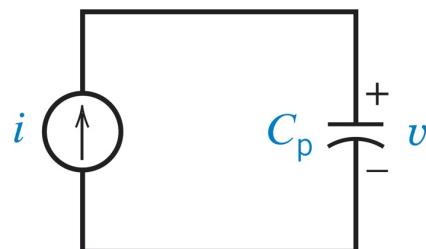

$$i = C_1 \frac{dv}{dt} + C_2 \frac{dv}{dt} + \dots + C_N \frac{dv}{dt}$$

$$i = (C_1 + C_2 + \dots + C_N) \frac{dv}{dt}$$


The capacitors all have the same initial condition  $[v(0)]$

$$C_p = (C_1 + C_2 + \dots + C_N)$$

Remember conductance?




# Series capacitors

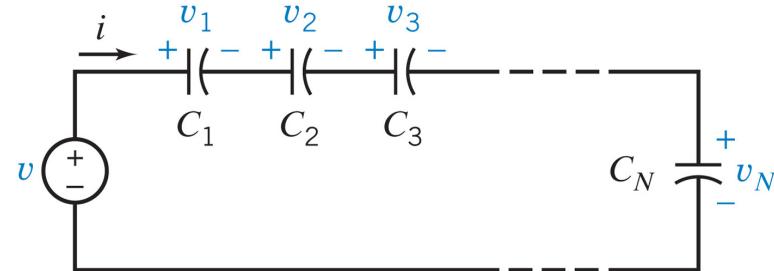

KVL:

$$v = v_1 + v_2 + \cdots + v_N$$

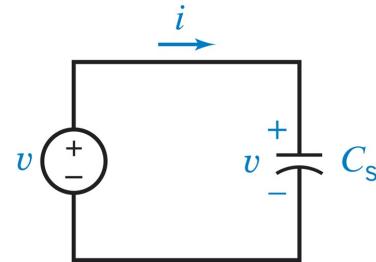

$$v = v_1(t_0) + v_2(t_0) + \cdots + v_N(t_0) + \left( \frac{1}{C_1} + \frac{1}{C_2} + \cdots + \frac{1}{C_N} \right) \int_{t_0}^t i(\tau) d\tau$$

$$v(t_0) = v_1(t_0) + v_2(t_0) + \cdots + v_N(t_0)$$

$$\frac{1}{C_s} = \left( \frac{1}{C_1} + \frac{1}{C_2} + \cdots + \frac{1}{C_N} \right)$$


Voltage:

$$v = \left( \sum_{n=1}^N \frac{1}{C_n} \right) \int_{t_0}^t i d\tau + v(t_0)$$

For 2 series capacitors:

$$C_s = \frac{C_1 C_2}{C_1 + C_2}$$


# Example problem

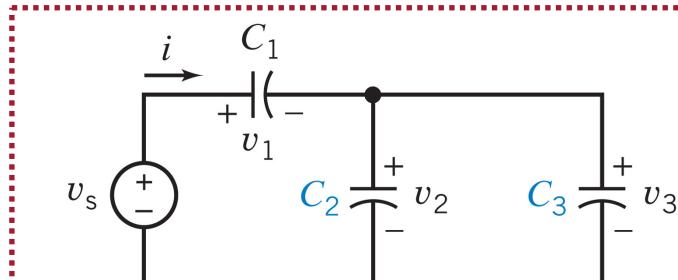


$$C_1 = C_2 = C_3 = 2 \text{ mF}$$

$$v_1(0) = 10 \text{ V}$$

$$v_2(0) = v_3(0) = 20 \text{ V}$$

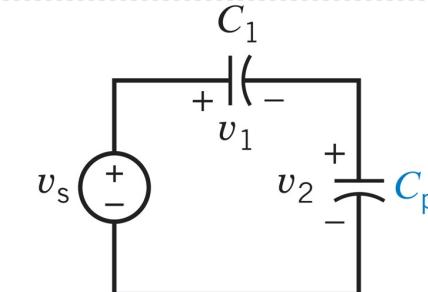

$$C_p = C_2 + C_3 = 4 \text{ mF}$$

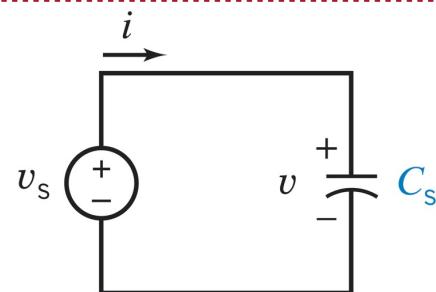

$$C_s = \frac{C_1 C_p}{C_1 + C_p} = \frac{2 \times 10^{-3} \times 4 \times 10^{-3}}{2 \times 10^{-3} + 4 \times 10^{-3}} = \frac{8}{6} \text{ mF}$$

$$v_s(0) = v_1(0) + v_2(0) = 30 \text{ V}$$



# Summary

---

## Important Characteristics of an Ideal Capacitor

1. There is no current through a capacitor if the voltage across it is not changing with time. A capacitor is therefore an *open circuit to dc*.
2. A finite amount of energy can be stored in a capacitor even if the current through the capacitor is zero, such as when the voltage across it is constant.
3. It is impossible to change the voltage across a capacitor by a finite amount in zero time, as this requires an infinite current through the capacitor. (A capacitor resists an abrupt change in the voltage across it in a manner analogous to the way a spring resists an abrupt change in its displacement.)
4. A capacitor never dissipates energy, but only stores it. Although this is true for the *mathematical model*, it is not true for a *physical* capacitor due to finite resistances associated with the dielectric as well as the packaging.




# Inductors

Maintain a voltage ONLY when the current is changing




# The inductor circuit element

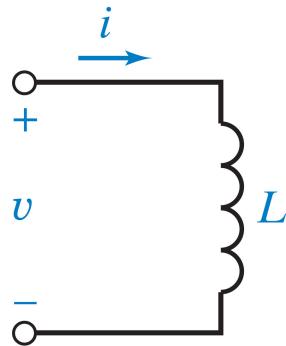

The inductor equations:

$$v(t) = L \frac{di}{dt}$$

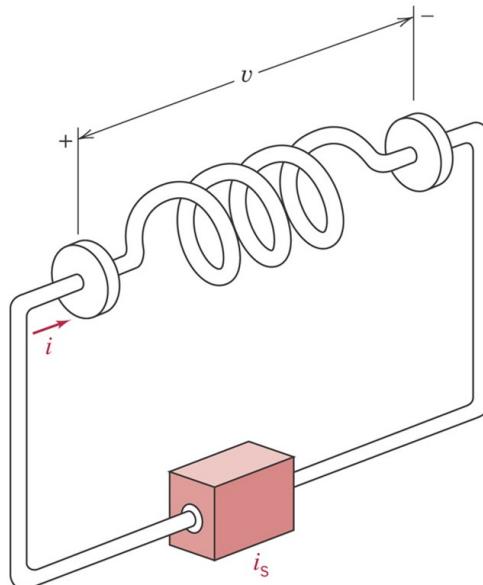
A constant current produces no voltage.  
A time-varying current produces an induced voltage.




**Current through an inductor cannot change instantaneously (but its voltage can)**

$$i(t) = \frac{1}{L} \int_{-\infty}^t v(\tau) d\tau$$

# Inductors

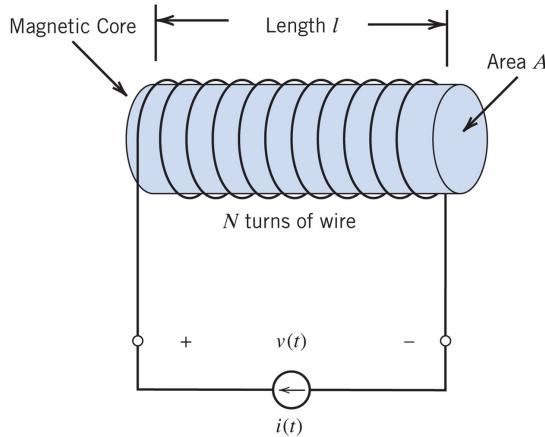

Solenoid  
(single layer  
coil)

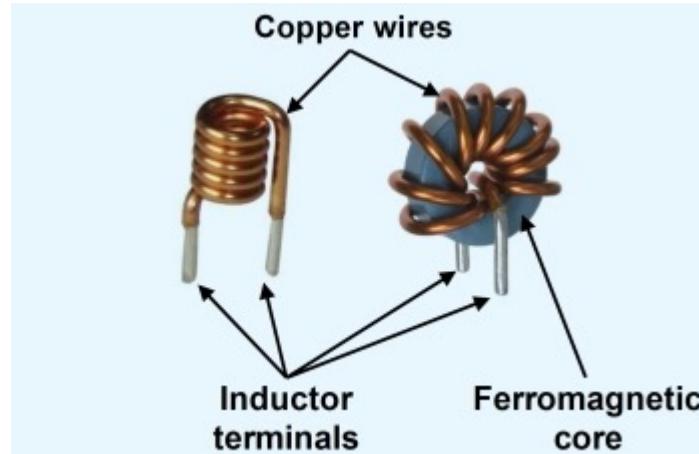

<http://www.hobbytronica.eu/electrical-resistance-capacitance-and-inductance/>

For inductors wound  
into a coil:

$$L = \frac{\mu N^2 A}{l}$$

Annotations for the formula:

- Magnetic constant (permeability) ( $\text{H/m}$ ) points to  $\mu$
- Cross-sectional area of core ( $\text{m}^2$ ) points to  $A$
- Inductance (Henry) points to  $L$
- Length of core (m) points to  $l$


**Inductance is a measure of the ability of a device to store energy in the form of a magnetic field**



# Inductors are expensive to make

Because magnetic materials are expensive

$$L = \frac{\mu N^2 A}{l}$$

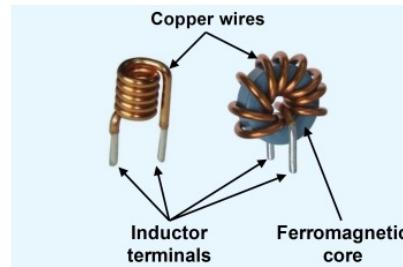

$$\mu = \mu_r \cdot \mu_0$$


Permeability of air

$$\mu_0 = 4\pi \times 10^{-7} \text{ H/m}$$

Relative permeability of iron

$$\mu_r = \text{varies}$$

How a multilayer chip inductor is made

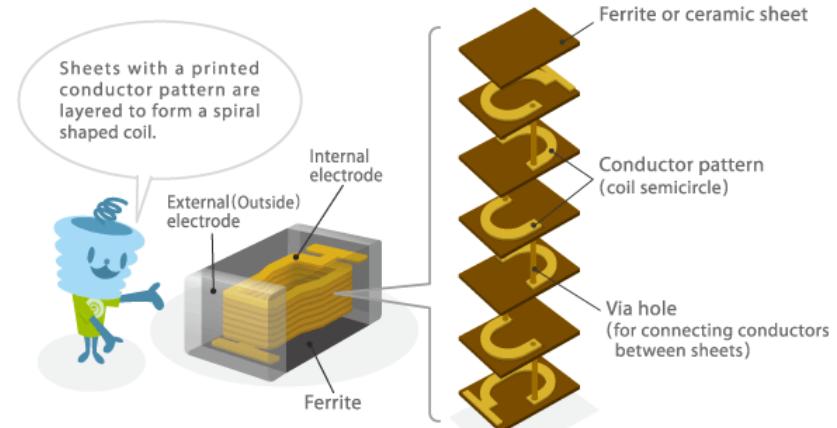

(Illustration shows a simplified version of sheet type multilayer construction.  
Other types using printed thick-film as multilayer material also exist.)

<http://www.global.tdk.com/techmag/inductive/vol3/index.htm>


Some representative relative permeabilities:

magnetic iron .....	200
nickel .....	100
permalloy..... (78.5% nickel, 21.5% iron)	8,000
mumetal..... (75% nickel, 2% chromium, 5% copper, 18% iron)	20,000



# The magnetic field

$$L = \frac{\mu N^2 A}{l}$$

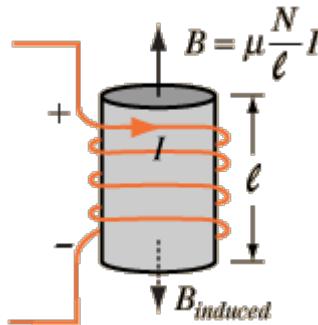


<http://hyperphysics.phy-astr.gsu.edu/hbase/electric/indeng.html>

Iron cores have a higher permeability than air and CONCENTRATE the magnetic field – the inductance is therefore increased.

$$B = \mu \frac{N}{l} I$$

Magnetic field  
Current

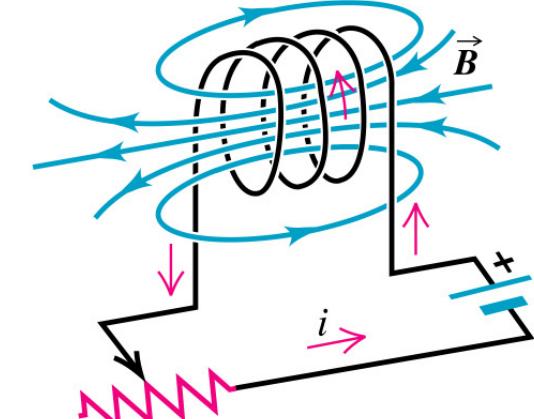


Copyright © Addison Wesley Longman, Inc.

<http://www.physics.sjsu.edu/becker/physics51/induction.htm>

# Example problem

Given the waveform of the current in a 3 H inductor as shown in Fig. 7.12a, determine the inductor voltage and sketch it.

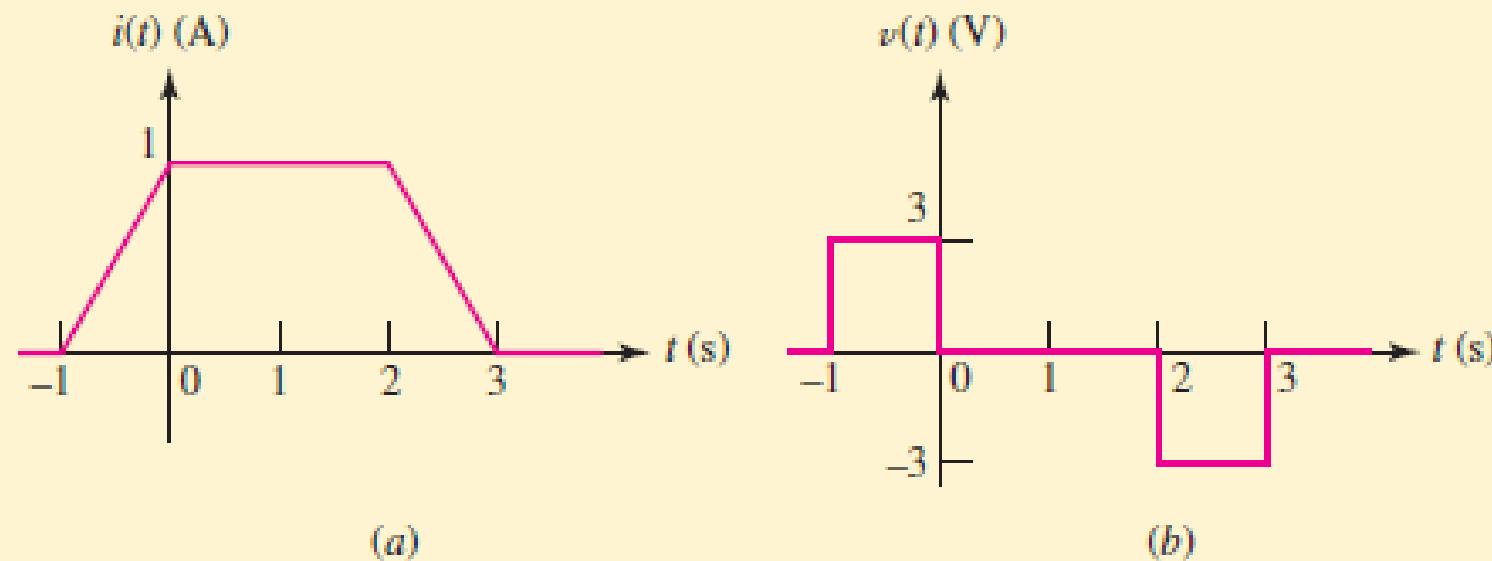

**FIGURE 7.12** (a) The current waveform in a 3 H inductor. (b) The corresponding voltage waveform,  $v = 3 di/dt$ .



# Solution

Defining the voltage  $v$  and the current  $i$  to satisfy the passive sign convention, we may obtain  $v$  from Fig. 7.12a using Eq. [5]:

$$v = 3 \frac{di}{dt}$$

Since the current is zero for  $t < -1$  s, the voltage is zero in this interval. The current then begins to increase at the linear rate of 1 A/s, and thus a constant voltage of  $L di/dt = 3$  V is produced. During the following 2 s interval, the current is constant and the voltage is therefore zero. The final decrease of the current results in  $di/dt = -1$  A/s, yielding  $v = -3$  V. For  $t > 3$  s,  $i(t)$  is a constant (zero), so that  $v(t) = 0$  for that interval. The complete voltage waveform is sketched in Fig. 7.12b.




# Initial current condition

The current in an inductor:


$$i(t) = \frac{1}{L} \int_{-\infty}^t v(\tau) d\tau$$

This can be separated into 2 parts:

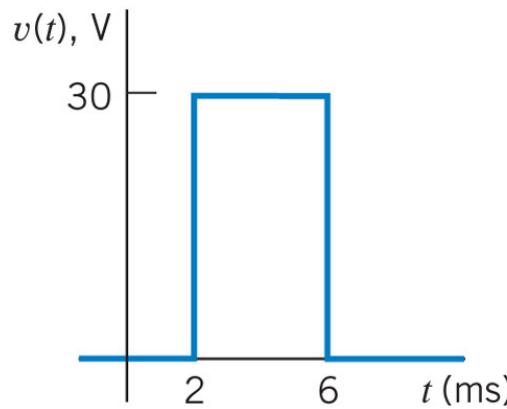
$$i(t) = \frac{1}{L} \int_{-\infty}^{t_0} v(\tau) d\tau + \frac{1}{L} \int_{t_0}^t v(\tau) d\tau = i(t_0) + \frac{1}{L} \int_{t_0}^t v(\tau) d\tau$$



VOLTAGE

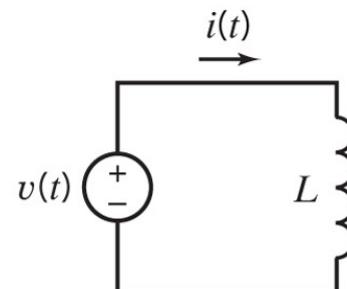


CIRCUIT

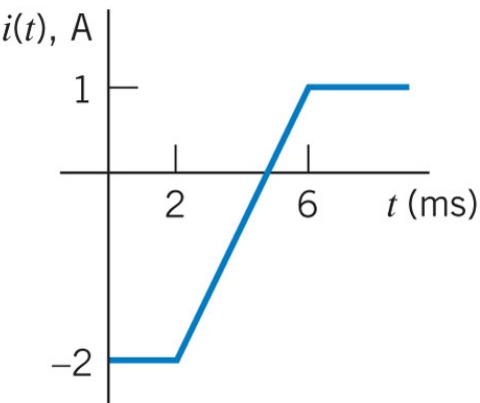

CURRENT



# Example problem 1

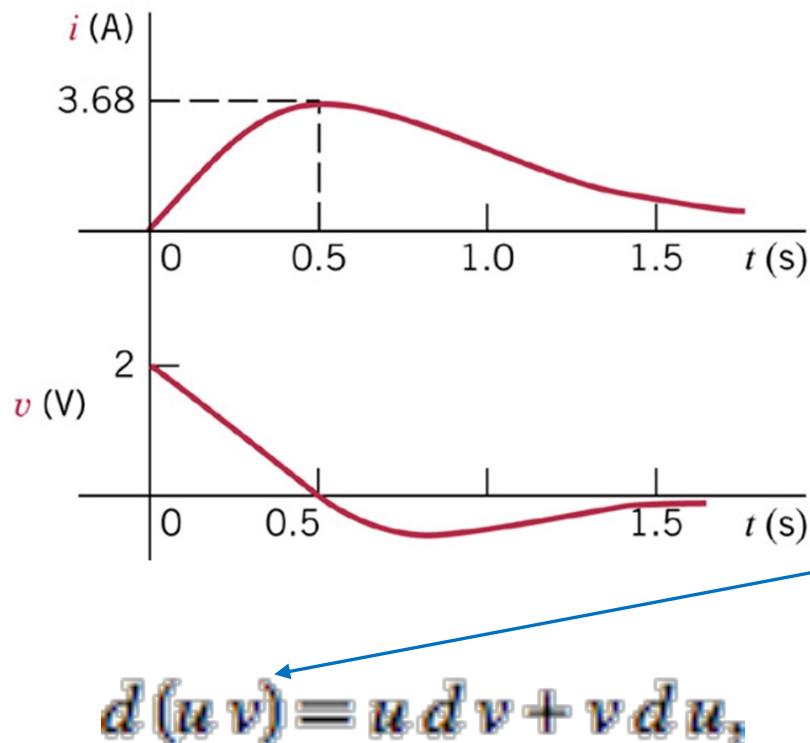

Find the voltage across an  $L = 0.1$  H inductor when the current in the inductor is,  $i = 20te^{-2t}$  A, for  $t \geq 0$  and  $i(0) = 0$ .


## Solution

$$\begin{aligned} v &= L \frac{di}{dt} = (0.1) \frac{d}{dt} (20te^{-2t}) \\ &= 2 \frac{d}{dt} (te^{-2t}) \\ &= 2[t(-2)e^{-2t} + e^{-2t}] \\ &= 2[1 - 2t]e^{-2t} \quad v \end{aligned}$$

Recall: differentiation of a product of two functions ( $u$  and  $v$ )



# Example problem 2

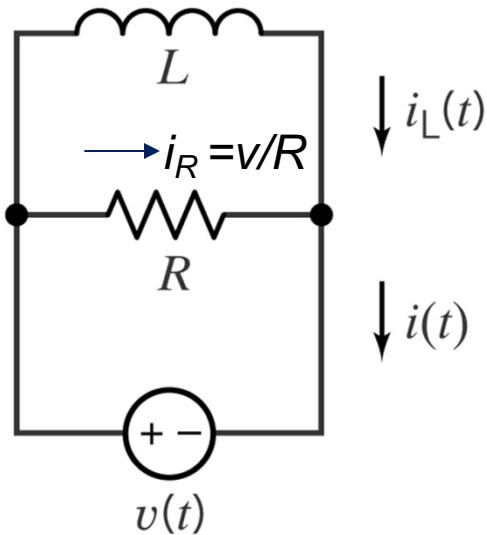

The input to the circuit is,  $v(t) = 4e^{-20t}$  V for  $t > 0$ ,

The output current is,  $i(t) = -1.2e^{-20t} - 1.5$  A for  $t > 0$ .

The initial conductor current is,  $i(0) = -3.5$  A

Determine the inductance,  $L$ , and the resistance,  $R$ .

## Solution

Apply the KCL,  $i(t) - i_L(t) - \frac{V}{R} = 0$


$$i(t) = i_L(t) + \frac{V}{R}$$

$$= \left[ \frac{1}{L} \int_0^t v(\tau) d\tau + i_L(0) \right] + \frac{V(t)}{R}$$

$$-1.2e^{-20t} - 1.5 = \left[ \frac{1}{L} \int_0^t 4e^{-20\tau} d\tau - 3.5 \right] + \frac{4e^{-20t}}{R}$$



# Solution

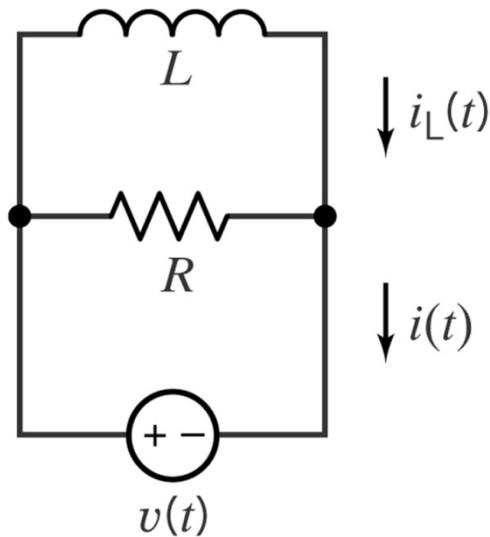

$$\begin{aligned}-1.2e^{-20t} - 1.5 &= \left[ \frac{1}{L} \int_0^t 4e^{-20\tau} d\tau - 3.5 \right] + \frac{4e^{-20t}}{R} \\-1.2e^{-20t} - 1.5 &= \frac{4}{L(-20)} e^{-20\tau} \Big|_0^t - 3.5 + \frac{4e^{-20t}}{R} \\-1.2e^{-20t} - 1.5 &= \frac{1}{(-5L)} [e^{-20t} - 1] - 3.5 + \left( \frac{4}{R} \right) e^{-20t}\end{aligned}$$

Therefore,  $-1.5 = \frac{1}{(5L)} - 3.5$ , and  $L = 0.1 \text{ H}$

and,  $-1.2e^{-20t} = \frac{1}{(-5L)} e^{-20t} + \left( \frac{4}{R} \right) e^{-20t}$


$$-1.2 = \frac{1}{(-5L)} + \left( \frac{4}{R} \right), \quad -1.2 = -2 + \frac{4}{R}$$

$$R = \frac{4}{.8} = 5 \Omega$$



MACQUARIE  
University

# Energy storage in an inductor

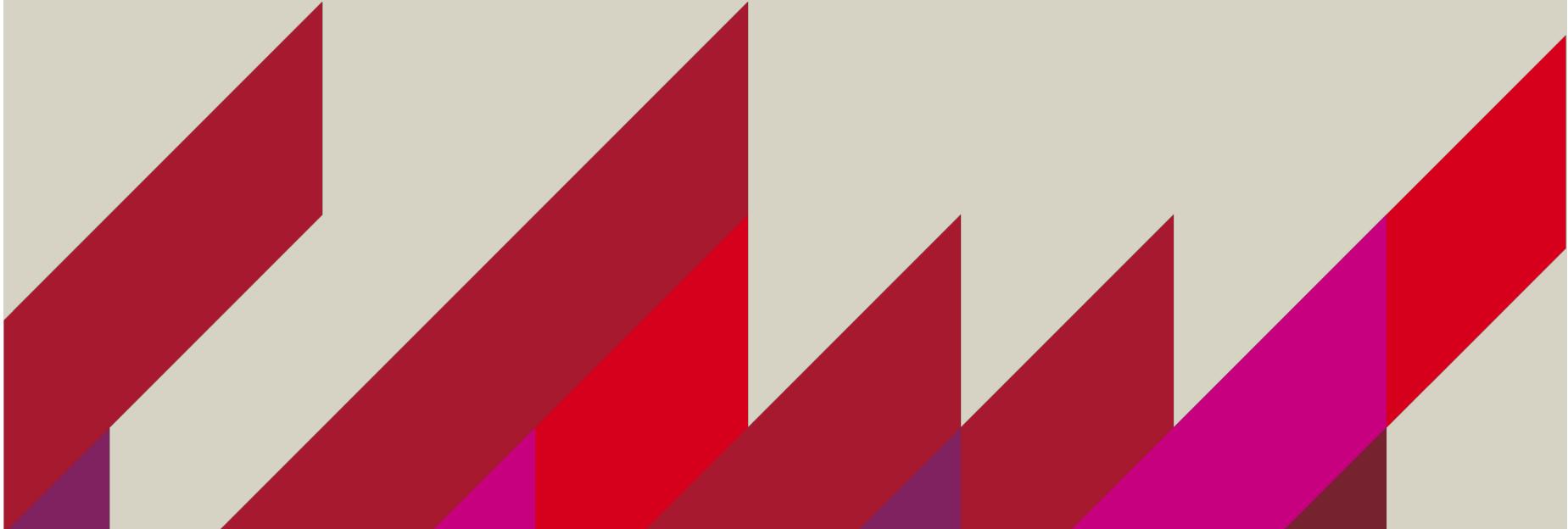



# Energy storage

---

The energy:  $w(t) = \int_{-\infty}^t p(\tau)d\tau$

Which is:  $w(t) = \int_{-\infty}^t v(\tau)i(\tau)d\tau$       Noting that:  $v(t) = L \frac{di(t)}{dt}$

We get:  $w(t) = \int_{-\infty}^t iL \frac{di}{dt} d\tau = L \int_{i(-\infty)}^{i(t)} idi = \frac{1}{2} Li^2 \Big|_{i(-\infty)}^{i(t)} = \frac{1}{2} Li^2(t)$  **J**

Remember:

An inductor does not generate or dissipate energy

Inductors and capacitors are both passive elements



MACQUARIE  
University


# Series and parallel combinations

INDUCTORS





# Parallel inductors

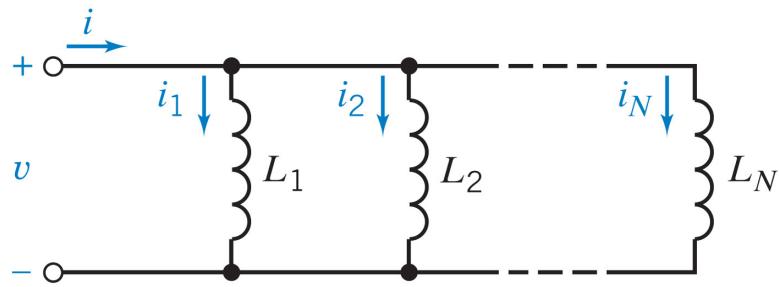

Applying KCL:  $i = i_1 + i_2 + \cdots + i_N$


But:  $i_n(t) = i_n(t_0) + \frac{1}{L_n} \int_{t_0}^t v(\tau) d\tau$

Hence:  $i = i_1(t_0) + i_2(t_0) + \cdots + i_N(t_0) + \left( \frac{1}{L_1} + \frac{1}{L_2} + \cdots + \frac{1}{L_N} \right) \int_{t_0}^t v(\tau) d\tau$

Therefore:


$$\frac{1}{L_p} = \left( \frac{1}{L_1} + \frac{1}{L_2} + \cdots + \frac{1}{L_N} \right)$$

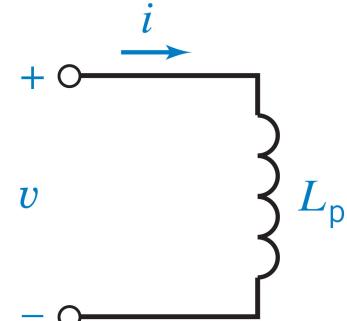With the initial current:  $i(t_0) = i_1(t_0) + i_2(t_0) + \cdots + i_N(t_0)$





# Series inductors

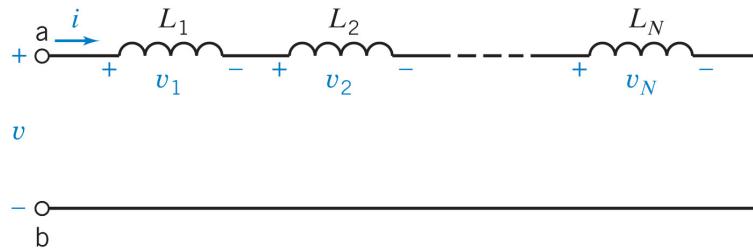


Use KVL:  $v = v_1 + v_2 + \cdots + v_N$

But:  $v_n = L_n \frac{di}{dt}$

Therefore:  $v = L_1 \frac{di}{dt} + L_2 \frac{di}{dt} + \cdots + L_N \frac{di}{dt}$


$$v = (L_1 + L_2 + \cdots + L_N) \frac{di}{dt}$$

$$L_s = (L_1 + L_2 + \cdots + L_N)$$

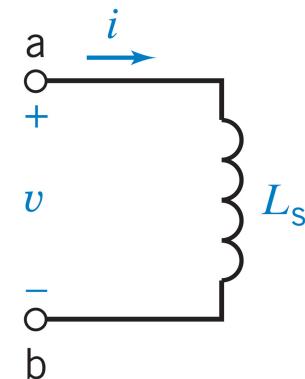



# Example problem

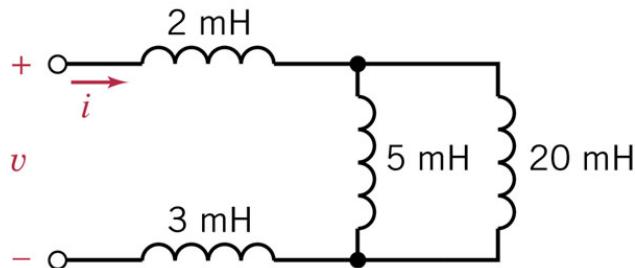

Find the equivalent inductance of the circuit. All the inductor circuits are zero at  $t_0$ .

## Solution

The equivalent inductance of the 5 mH and 20 mH inductances in parallel,  $L_p$  is,

$$L_p = \frac{1}{\frac{1}{20 \times 10^{-3}} + \frac{1}{5 \times 10^{-3}}} = 4 \times 10^{-3}$$

$$\begin{aligned} L_{eq} &= 2 \times 10^{-3} + 4 \times 10^{-3} + 3 \times 10^{-3} = 9 \times 10^{-3} \\ &= 9 \text{ mH} \end{aligned}$$



# Summary

---

## Important Characteristics of an Ideal Inductor

1. There is no voltage across an inductor if the current through it is not changing with time. An inductor is therefore a *short circuit to dc*.
2. A finite amount of energy can be stored in an inductor even if the voltage across the inductor is zero, such as when the current through it is constant.
3. It is impossible to change the current through an inductor by a finite amount in zero time, for this requires an infinite voltage across the inductor. (An inductor resists an abrupt change in the current through it in a manner analogous to the way a mass resists an abrupt change in its velocity.)
4. The inductor never dissipates energy, but only stores it. Although this is true for the *mathematical model*, it is not true for a *physical* inductor due to series resistances.



MACQUARIE  
University

# Initial conditions of switched circuits





# Circuit analysis with switches

1. Analyse the circuit before the switch changes position at  $t = t_0$  (steady-state)
2. Recognise that capacitor voltages and inductor currents cannot change instantaneously
$$v_C(t_0^-) = v_C(t_0^+)$$
$$i_L(t_0^-) = i_L(t_0^+)$$
3. Analyse the circuit (differential equations) for  $t > t_0$

Initial conditions

# Steady state DC circuits with capacitors and inductors

---



1. Voltage across an inductor with DC current is zero

$$v(t) = L \frac{di(t)}{dt} = 0$$

2. Replace inductors with short circuits


3. Current through a capacitor with DC voltage is zero

$$i(t) = C \frac{dv(t)}{dt} = 0$$

4. Replace capacitors with open circuits



# Example problem

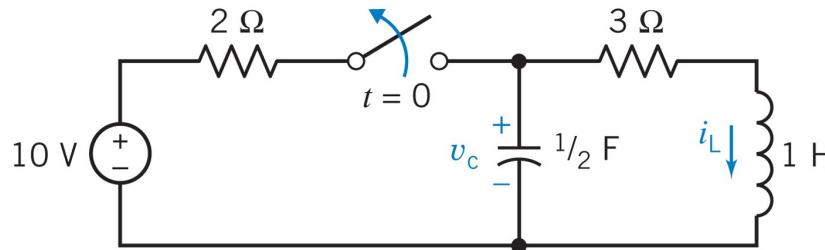


Switch OPENS at  $t=0$

$$v_c(0^+) = ?$$

$$i_L(0^+) = ?$$

$t < 0$ :

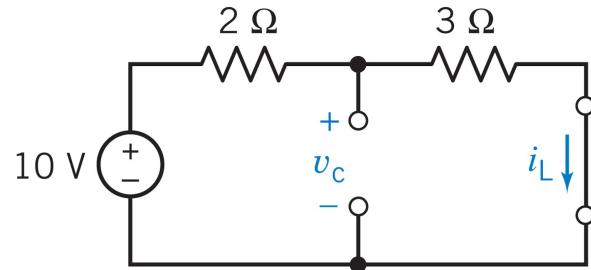

$$i_L(0^-) = \frac{10}{5} = 2 \text{ A}$$

$$i_L(0^+) = i_L(0^-) = 2 \text{ A}$$

$$v_c(0^-) = 10 \times \frac{3}{5} = 6 \text{ V}$$

$$v_c(0^+) = v_c(0^-) = 6 \text{ V}$$




# Summary of temporal response

## VARIABLE

## INDUCTORS

## CAPACITORS

Passive sign convention

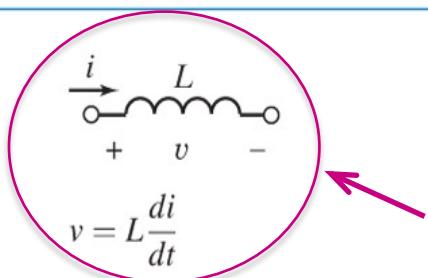

$$v = L \frac{di}{dt}$$

$$i = \frac{1}{L} \int_0^t v d\tau + i(0)$$

$$p = Li \frac{di}{dt}$$


Voltage

$$w = \frac{1}{2} Li^2$$

Current

Current

Power

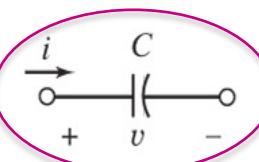

$$v = \frac{1}{C} \int_0^t id\tau + v(0)$$

$$i = C \frac{dv}{dt}$$

$$p = Cv \frac{dv}{dt}$$

Energy

$$w = \frac{1}{2} Cv^2$$

An instantaneous change is not permitted for the element's

You must remember these!

None of these formulas will be provided in the exam !!!

Will permit an instantaneous change in the element's

Voltage

Voltage

This element acts as a (see note below)

Short circuit to a constant current into its terminals









Open circuit to a constant voltage across its terminals

These are good to remember too but you can infer them from the equations.

Note: Assumes that the element is in a circuit with steady-state condition.

# Summary of series and parallel circuits

Table 7.13-2 Parallel and Series Capacitors and Inductors

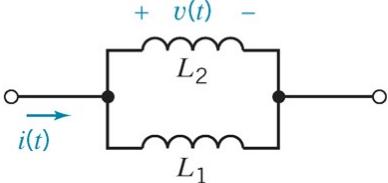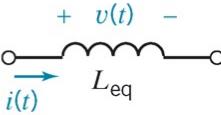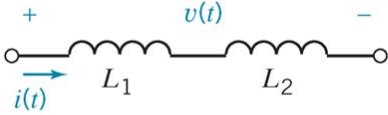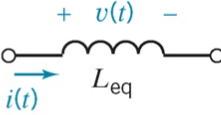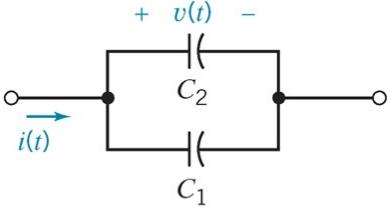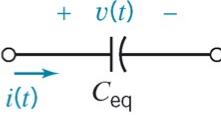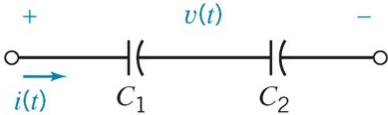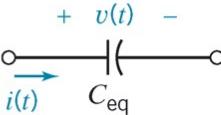SERIES OR PARALLEL CIRCUIT	EQUIVALENT CIRCUIT	EQUATION
		$L_{\text{eq}} = \frac{1}{\frac{1}{L_1} + \frac{1}{L_2}}$
		$L_{\text{eq}} = L_1 + L_2$
		$C_{\text{eq}} = C_1 + C_2$
		$C_{\text{eq}} = \frac{1}{\frac{1}{C_1} + \frac{1}{C_2}}$



These formulas will NOT be provided in the exam.

Cf.  
Resistance

Cf.  
Conductance



# Problem 7.2-22

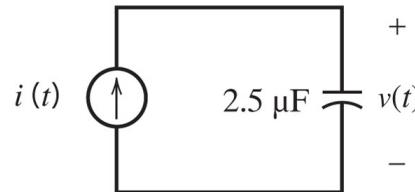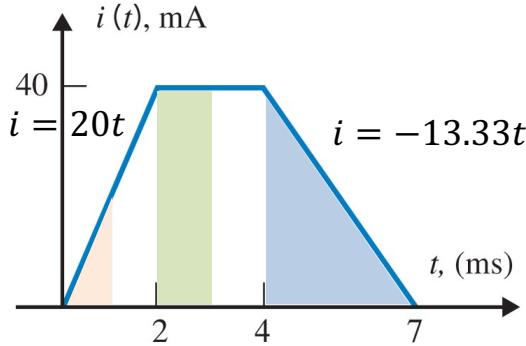

$$v(0) = -20 \text{ V}$$

$$v(1 \text{ ms}) = ?$$

$$v(3 \text{ ms}) = ?$$

$$v(7 \text{ ms}) = ?$$

$$v(t) = v(0) + \frac{1}{C} \int_0^t i(\tau) d\tau \quad \rightarrow \quad v(t) = -20 + \frac{1}{2.5 \times 10^{-6}} X \text{ "area under curve"}$$

$$v(1 \text{ ms}) = -20 + \frac{1}{2.5 \times 10^{-6}} \left( \frac{1 \times 10^{-3} \times 20 \times 10^{-3}}{2} \right) = -20 + 4 = -16 \text{ V}$$


$$v(2 \text{ ms}) = -20 + \frac{1}{2.5 \times 10^{-6}} \left( \frac{2 \times 10^{-3} \times 40 \times 10^{-3}}{2} \right) = -20 + 16 = -4 \text{ V}$$

$$v(3 \text{ ms}) = v(2 \text{ ms}) + \frac{1}{2.5 \times 10^{-6}} (1 \times 10^{-3} \times 40 \times 10^{-3}) = -4 + 16 = 12 \text{ V}$$

$$v(4 \text{ ms}) = v(3 \text{ ms}) + 16 = 28 \text{ V}$$


$$v(7 \text{ ms}) = v(4 \text{ ms}) + \frac{1}{2.5 \times 10^{-6}} \left( \frac{3 \times 10^{-3} \times 40 \times 10^{-3}}{2} \right) = 52 \text{ V}$$

# Problem 7.8-6

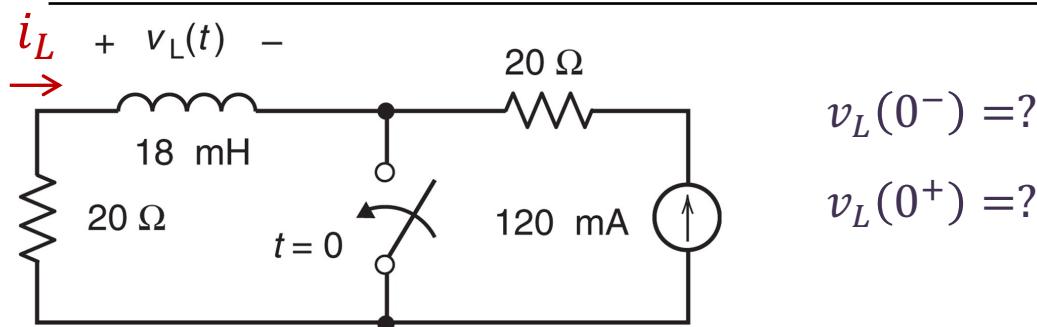

Also write the differential equation for  $i_L$

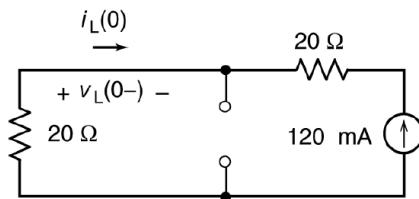
$t < 0$        $v_L(0^-) = 0$  (when DC inductors act like short circuits)



$i_L(0^-) = -120 \text{ mA}$  (note polarity!)

$i_L(0^+) = -120 \text{ mA}$  (inductor currents do not change rapidly)

$t > 0$

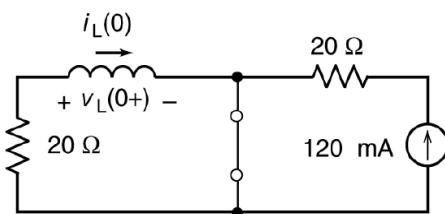


$$v_L(t) = L \frac{di_L(t)}{dt}$$

KVL (LH mesh):  $v_L(t) + 20i_L(t) = 0 \rightarrow v_L(0^+) + 20i_L(0^+) = 0$

$$v_L(0^+) = 2.4 \text{ V}$$



# Problem 7.8-6

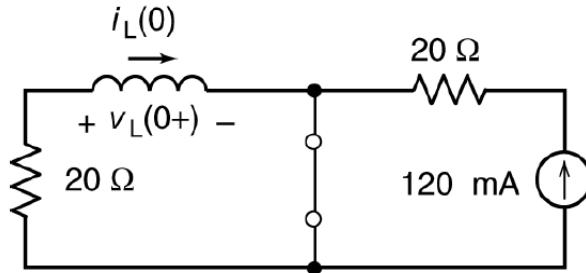

Differential equation:

$$\text{We use: } v_L(t) = L \frac{di_L(t)}{dt}$$

For  $t > 0$

$$\text{KVL of LH mesh : } v_L(t) + 20 i_L(t) = 0$$

$$18 \times 10^{-3} \frac{di_L}{dt} + 20 i_L = 0$$

Differential  
equation of  $i_L$

$$\frac{di_L}{dt} + \frac{20}{18 \times 10^{-3}} i_L = 0$$

This part is the inverse  
of "time constant"

$$\frac{di_L}{dt} + \frac{1}{\tau} i_L = f(t)$$

General form of first order  
differential equation